

# Microelectronic Circuit Design

## Third Edition - Part III

## Solutions to Exercises - Partial

---

### CHAPTER 10

---

#### Page 509

$$V_o = \sqrt{2P_o R_L} = \sqrt{2(20W)(16\Omega)} = 25.3 V \quad A_v = \frac{V_o}{V_i} = \frac{25.3V}{0.005V} = 5.06 \times 10^3$$

$$I_o = \frac{V_o}{R_L} = \frac{25.3V}{16\Omega} = 1.58 A \quad I_i = \frac{V_i}{R_S + R_{in}} = \frac{0.005V}{10k\Omega + 20k\Omega} = 0.167 \mu A \quad A_i = \frac{I_o}{I_i} = \frac{1.58A}{0.167\mu A} = 9.48 \times 10^6$$

$$A_P = \frac{P_o}{P_S} = \frac{25.3V(1.58A)}{0.005V(0.167\mu A)} = 4.79 \times 10^{10} \quad \text{Checking: } A_p = (5.06 \times 10^3)(9.48 \times 10^6) = 4.80 \times 10^{10}$$

---

#### Page 510

$$(i) A_{v dB} = 20 \log(5060) = 74.1 dB \quad A_{i dB} = 20 \log(9.48 \times 10^6) = 140 dB \quad A_{P dB} = 10 \log(4.80 \times 10^{10}) = 107 dB$$
$$(ii) A_{v dB} = 20 \log(4 \times 10^4) = 92.0 dB \quad A_{i dB} = 20 \log(2.75 \times 10^8) = 169 dB \quad A_{P dB} = 10 \log(1.10 \times 10^{13}) = 130 dB$$

---

#### Page 511

(i) The constant slope region spanning a maximum input range is between  $0.4 \leq v_i \leq 0.65$ ,

and the bias voltage  $V_I$  should be centered in this range:  $V_I = \frac{0.4 + 0.65}{2}V = 0.525 V$ .

$v_i \leq 0.65 - 0.525 = 0.125 V$  and  $v_i \leq 0.525 - 0.40 = 0.125 V$ . For  $v_I = 0.8V$ , the slope is 0.  $A_v = 0$ .

(ii)  $v_O = V_O + v_o$  For  $v_i = 0$ ,  $v_I = V_I = 0.6$ ,  $V_O = 14V$  and  $A_v = +40$ .  $V_o = A_v V_i = 40(0.01V) = 4V$

$$v_O = (14.0 + 4.00 \sin 1000\pi t) \text{ volts} \quad V_O = 14 V$$

---

**Page 519**

$$g_{11} = \frac{1}{20k\Omega + 76(50k\Omega)} = 0.262 \text{ } \mu S \quad g_{21} = 0.262\mu S(76)(50k\Omega) = 0.995$$

$$g_{22} = \frac{1}{50k\Omega} + \frac{1}{20k\Omega} + \frac{75}{20k\Omega} = 3.82 \text{ } mS \quad g_{12} = -\frac{1}{g_{22}(20k\Omega)} = -\frac{1}{3.82mS(20k\Omega)} = -0.0131$$

$$R_{in} = \frac{1}{g_{11}} = 3.82 \text{ } M\Omega \quad A = g_{21} = 0.995 \quad R_{out} = \frac{1}{g_{22}} = 262 \text{ } \Omega$$

---

**Page 520**

$$(i) P = A_v A_i = A_v^2 \frac{R_s + R_{in}}{R_L}$$

$$(ii) V_o = \sqrt{2(100W)(8\Omega)} = 40 \text{ V} \quad 40 = 0.001 \left( \frac{50k\Omega}{5k\Omega + 50k\Omega} \right) A \left( \frac{8\Omega}{0.5\Omega + 8\Omega} \right) \rightarrow A = 46,800$$

$$P = \frac{I_o^2 R_L}{2} = \frac{0.5\Omega}{2} \left( \frac{40V}{8\Omega} \right)^2 = 6.25 \text{ W} \quad A_i = \left( \frac{40V}{8\Omega} \right) \left( \frac{5k\Omega + 50k\Omega}{0.001V} \right) = 2.75 \times 10^8$$

$$(iii) 40 = 0.001 \left( \frac{5k\Omega}{5k\Omega + 5k\Omega} \right) A \left( \frac{8\Omega}{8\Omega + 8\Omega} \right) \rightarrow A = 160,000$$

$$P = \frac{I_o^2 R_L}{2} = \frac{8\Omega}{2} \left( \frac{40V}{8\Omega} \right)^2 = 100 \text{ W!} \quad A_i = \left( \frac{40V}{8\Omega} \right) \left( \frac{5k\Omega + 5k\Omega}{0.001V} \right) = 5.00 \times 10^7$$


---

**Page 521**

$$A_v(s) = \frac{300s}{(s+5000)(s+100)} \quad \text{Zeros at } s=0 \text{ and } s=\infty; \text{ Poles at } s=-5000 \text{ and } s=-100.$$


---

**Page 523**

$$A_v(s) = -\frac{2\pi x 10^6}{s+5000\pi} = \frac{-400}{1 + \frac{s}{5000\pi}} \rightarrow A_{mid} = -400 \quad f_H = \frac{5000\pi}{2\pi} = 2.50 \text{ kHz}$$

$$BW = f_H - f_L = 2.50 \text{ kHz} - 0 = 2.50 \text{ kHz} \quad GBW = (400)(2.50 \text{ kHz}) = 1.00 \text{ MHz}$$


---

**Page 524**

$$(i) |A_v(j5)| = 50 \frac{|5^2 - 4|}{\sqrt{(5^2 - 2)^2 + 4(5^2)}} = 41.87 \quad 20 \log(41.87) = 32.4 \text{ dB}$$

$$\angle A_v(j5) = \angle(5^2 - 4) - \tan^{-1} \left[ \frac{-2(5)}{5^2 - 2} \right] = 0 - (-23.5^\circ) = 23.5^\circ$$

$$|A_v(j1)| = 50 \frac{|1^2 - 4|}{\sqrt{(1^2 - 2)^2 + 4(1^2)}} = 67.08 \quad 20 \log(41.87) = 36.5 \text{ dB}$$

$$\angle A_v(j1) = \angle(1^2 - 4) - \tan^{-1} \left[ \frac{-2(1)}{1^2 - 2} \right] = 180^\circ - (-63.43^\circ) = 243^\circ = -117^\circ$$

**Page 524**

$$(ii) A_v(j\omega) = \frac{20}{1 + j\frac{0.1\omega}{1 - \omega^2}}$$

$$|A_v(j0.95)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(0.95^2)}{(1 - 0.95^2)^2}}} = 14.3 \quad \angle A_v(j0.95) = \angle 20 - \tan^{-1} \left[ \frac{0.1(0.95)}{1 - 0.95^2} \right] = 0 - (44.3^\circ) = -44.3^\circ$$

$$|A_v(j1)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(1^2)}{(1 - 1^2)^2}}} = 0 \quad \angle A_v(j1) = \angle 20 - \tan^{-1} \left[ \frac{0.1(1)}{1 - 1^2} \right] = 0 - (90^\circ) = -90.0^\circ$$

$$|A_v(j1.1)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(1.1^2)}{(1 - 1.1^2)^2}}} = 17.7 \quad \angle A_v(j1.1) = \angle 20 - \tan^{-1} \left[ \frac{0.1(1.1)}{1 - 1.1^2} \right] = 0 - (-27.6^\circ) = 27.6^\circ$$


---

**Page 526**

$$f_H = \frac{1}{2\pi} \frac{1}{(1k\Omega \parallel 100k\Omega)(200pF)} = 804 \text{ kHz}$$


---

**Page 527**

$$A_v(s) = \frac{250}{1 + \frac{250\pi}{s}} \quad A_o = 250 \quad f_L = \frac{250\pi}{2\pi} = 125 \text{ Hz} \quad f_H = \infty \quad BW = \infty - 125 = \infty$$


---

**Page 528**

$$f_L = \frac{1}{2\pi} \frac{1}{(1k\Omega \parallel 100k\Omega)(0.1\mu F)} = 15.8 \text{ Hz}$$


---

**Page 529**

$$(i) \ A_v(s) = \frac{-400}{\left(1 + \frac{100}{s}\right)\left(1 + \frac{s}{50000}\right)} \quad A_o = 400 \text{ or } 52 \text{ dB}$$

$$f_L = \frac{100}{2\pi} = 15.9 \text{ Hz} \quad f_H = \frac{50000}{2\pi} = 7.96 \text{ kHz} \quad BW = 7960 - 15.9 = 7.94 \text{ kHz}$$

$$(ii) \angle A_v(j0) = -90 - 0 - 0 = -90^\circ$$

$$\angle A_v(j100) = -90^\circ - \tan^{-1}\left(\frac{100}{100}\right) - \tan^{-1}\left(\frac{100}{50000}\right) = -90 - 45 - 0.57 = -136^\circ$$

$$\angle A_v(j50000) = -90^\circ - \tan^{-1}\left(\frac{50000}{100}\right) - \tan^{-1}\left(\frac{50000}{50000}\right) = -90 - 89.9 - 45 = -225^\circ$$

$$\angle A_v(j\infty) = -90 - 90 - 90 = -270^\circ$$


---

**Page 531**

The numerator coefficient should be  $6 \times 10^6$ .

$$A_v(s) = 30 \frac{2 \times 10^5 s}{s^2 + 2 \times 10^5 s + 10^{14}} \quad A_o = 30$$

$$f_o = \frac{1}{2\pi} \sqrt{10^{14}} = 1.59 \text{ MHz} \quad Q = \frac{10^7}{2 \times 10^5} = 50 \quad BW = \frac{1.59 \text{ MHz}}{50} = 31.8 \text{ kHz}$$


---

**Page 533**

The transfer function should be  $A_v(s) = \frac{6.4 \times 10^{12} \pi^2 s}{(s + 200\pi)(s + 80000\pi)}$ .

$$A_v(s) = \frac{1000}{\left(1 + \frac{200\pi}{s}\right)\left(1 + \frac{s}{80000\pi}\right)^2} \quad A_o = 1000 \text{ or } 60 \text{ dB}$$

$$f_L = \frac{200\pi}{2\pi} = 100 \text{ Hz} \quad f_H = 0.644 \left( \frac{80000\pi}{2\pi} \right) = 25.8 \text{ kHz} \quad BW = 25800 - 100 = 25.7 \text{ kHz}$$


---