

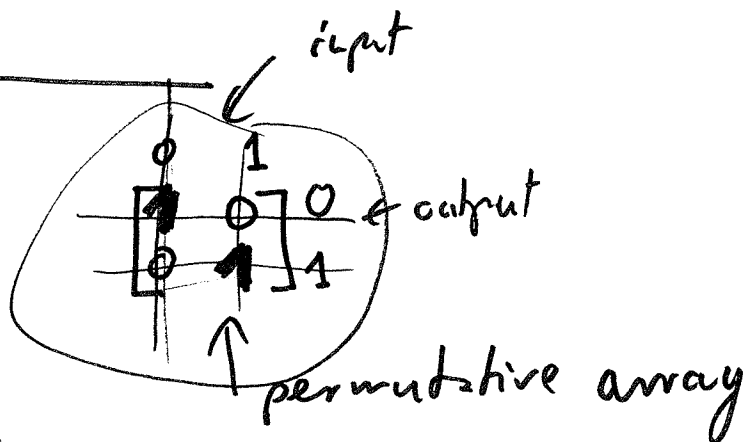


# Reversible gates (Lecture 3) ①




1) wire

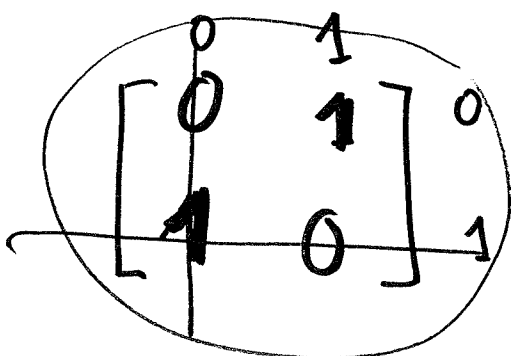



2) inverter

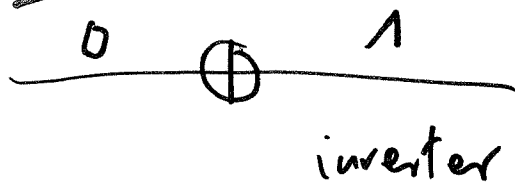

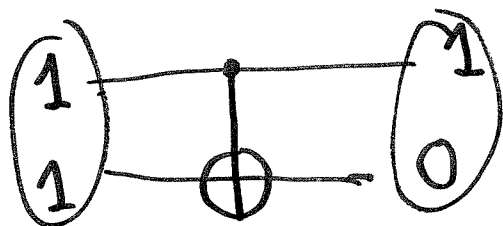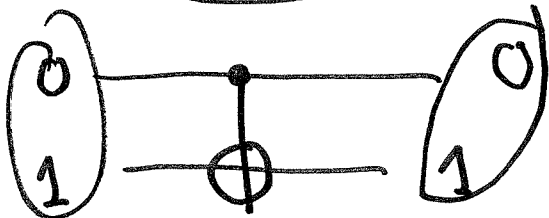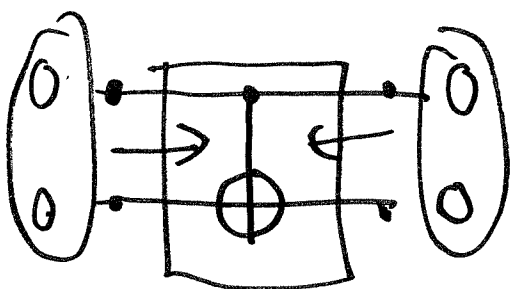
reversible gates are represented by permutative matrices



3) Feynman gate

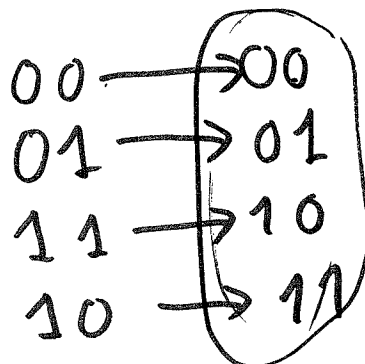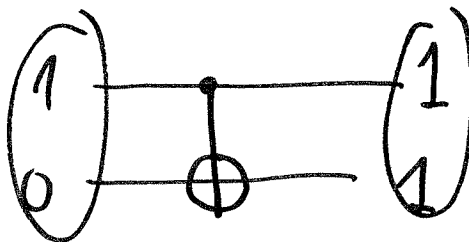

# 4) Unitary matrix for Feynman ②


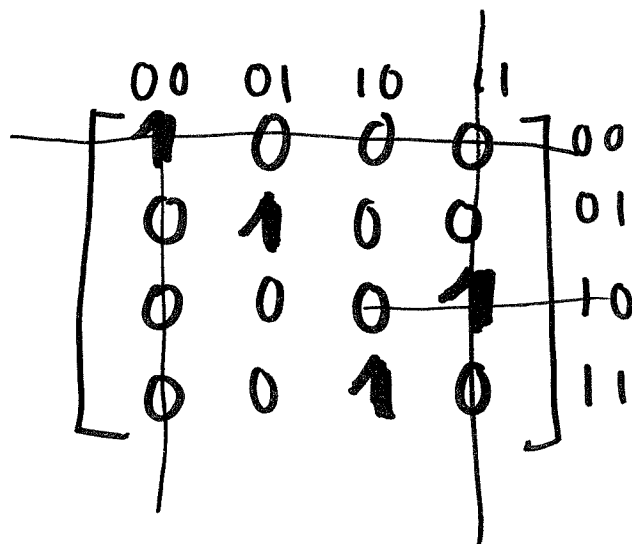


this is quantum gate.

If inputs only binary, then reversible.

It is also permutative!


Variant of Feynman

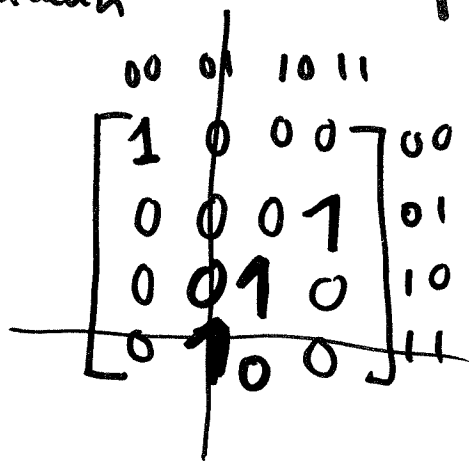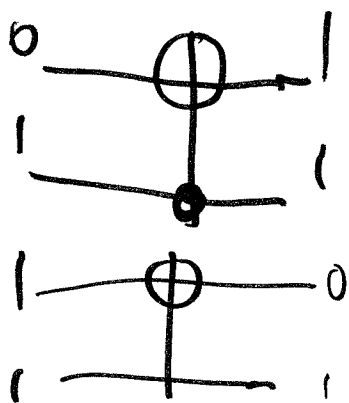

error up Feynman has also permutative matrix!

# 5) Toffoli Gate

③

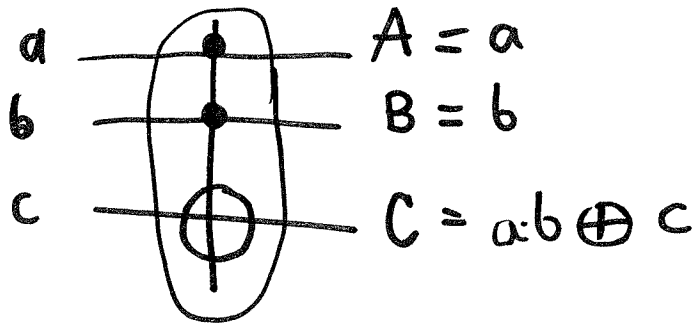


$$ab \oplus 1 = \overline{ab} = \bar{a} + \bar{b}$$

abc


| 000 | 001 | 010 | 011 | 100 | 101 | 110 | 111 |
|-----|-----|-----|-----|-----|-----|-----|-----|
| 1   | 0   | 0   | 0   |     |     |     |     |
| 0   | 1   | 0   | 0   |     |     |     |     |
| 0   | 0   | 1   | 0   |     |     |     |     |
| 0   | 0   | 0   | 1   |     |     |     |     |
|     |     |     |     | 1   | 0   |     |     |
|     |     |     |     | 0   | 1   |     |     |
|     |     |     |     |     |     | 0   | 1   |
|     |     |     |     |     |     | 1   | 0   |

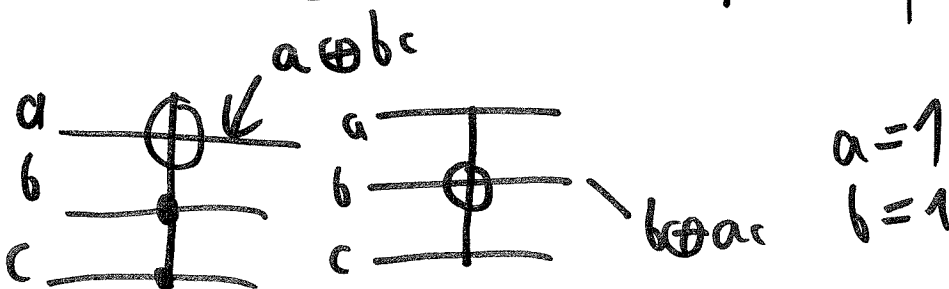$a=b=1$   
 $a \oplus bc$   
 $b \oplus ac$




All Toffoli gates, for any # of inputs, are described by permutative matrices

# 6) Fredkin

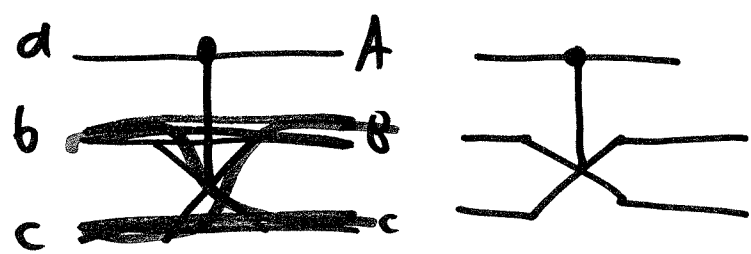


multiplexer

Find the matrix - do it!

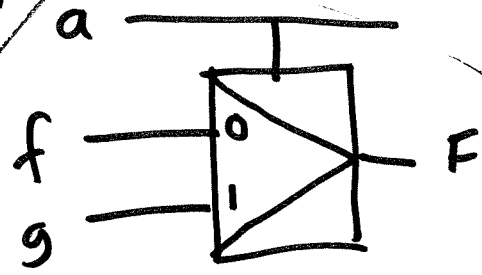

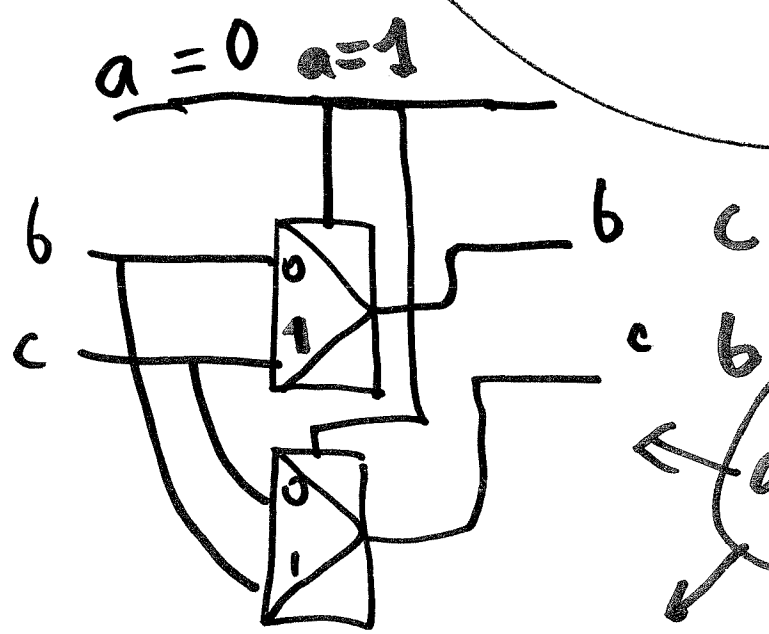
$$F = \begin{cases} f & \text{when } a = 0 \\ g & \text{when } a = 1 \end{cases}$$





Fredkin is Controlled-swap. gate

a = 0  
b  
c

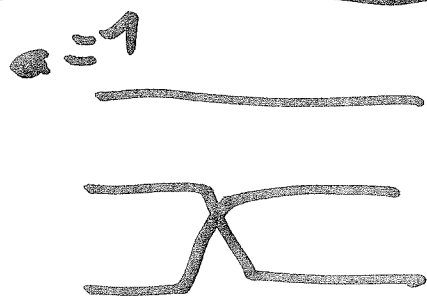


controlled-swap

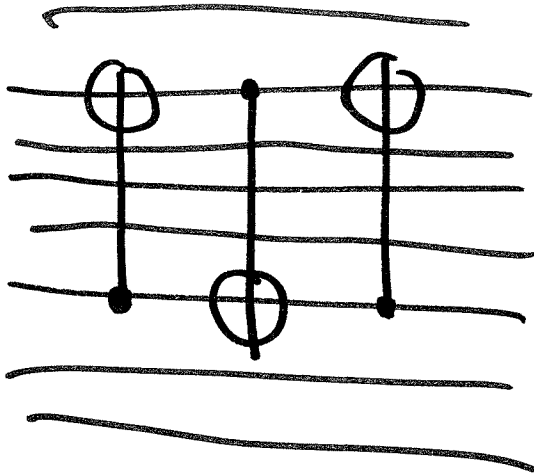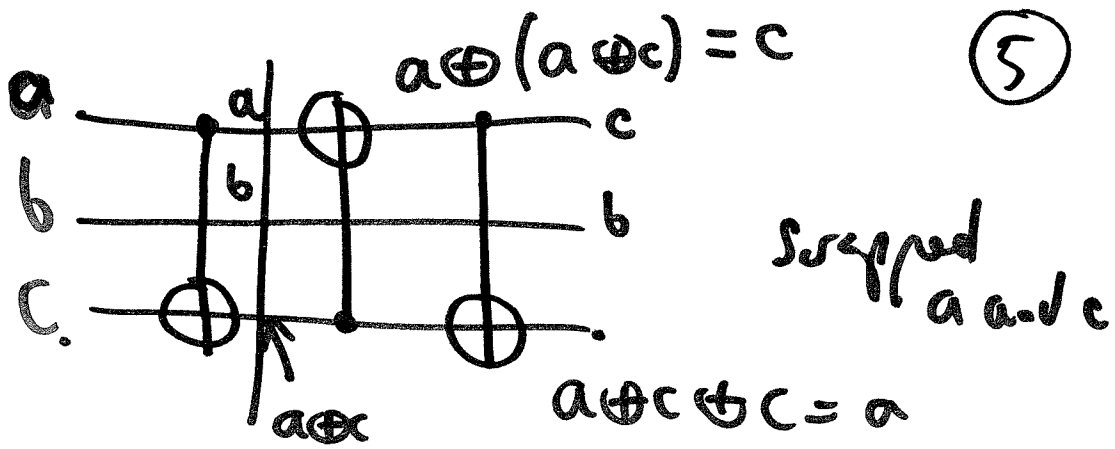

analyze

SWAP GATE  
FROM Feynman  
gates

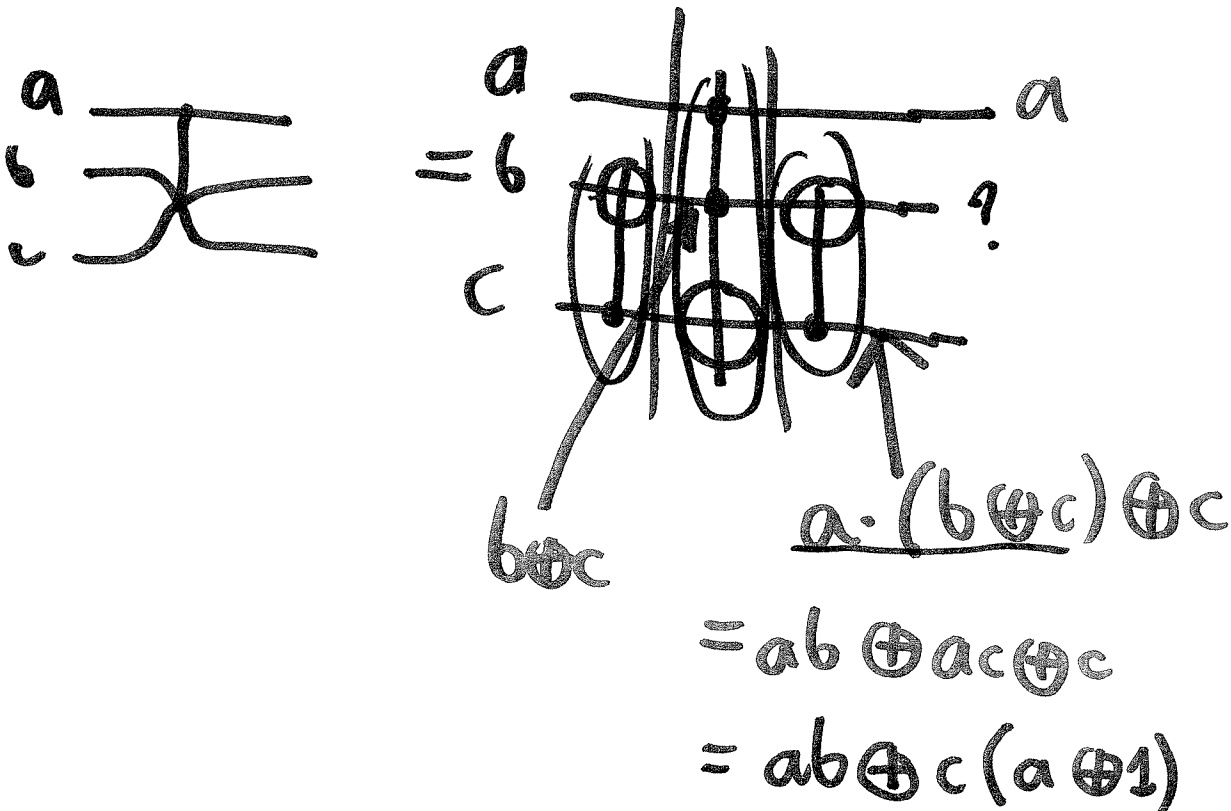How to realize Fredkin from  
Diffoli and Feynman?




$$= ab \oplus c(a \oplus 1)$$

⑥


$$= ab \oplus c \bar{a}$$

$$= ab + \bar{a}c$$

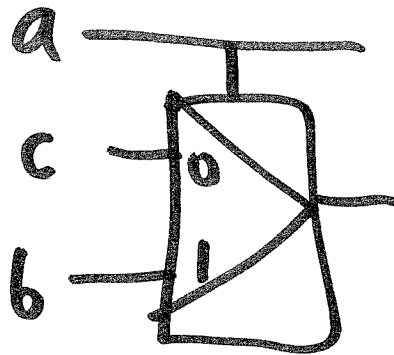
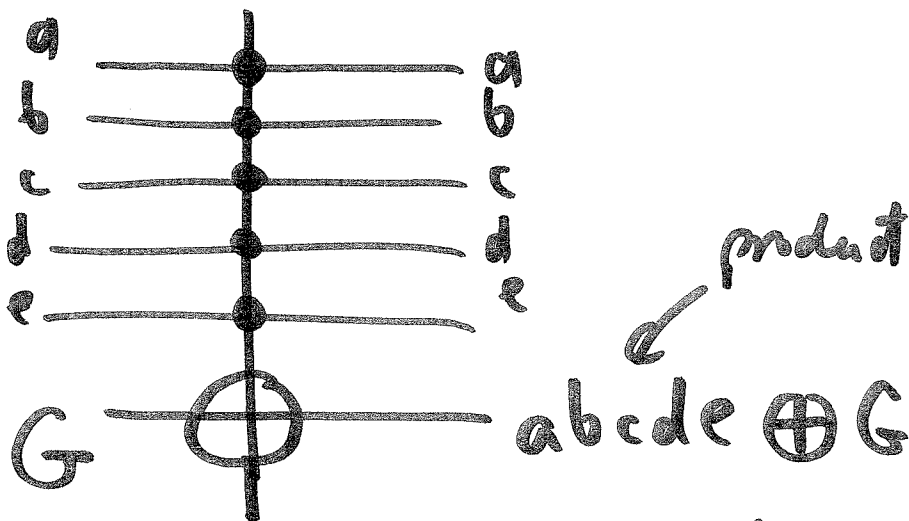
### Conclusion

We will use gates  
NOT, Feynman, Toffoli  
and Fredkin



Toffoli with many  
inputs

The diagram shows a quantum circuit with three horizontal lines representing qubits. The top line is labeled 'a', the middle line is labeled 'b', and the bottom line is labeled '0' (representing an ancilla bit). The circuit consists of three CNOT gates. The first CNOT has its control on qubit 'a' and target on qubit '0'. The second CNOT has its control on qubit 'b' and target on qubit '0'. The third CNOT has its control on qubit 'a' and target on qubit '0'. To the right of the circuit, the expression  $a \oplus b \oplus ab = a + b$  is written, with a line pointing from the ancilla bit line to the expression. Below this, the text 'ancilla bit' is written.

reductio of  $R$  is explicit.

— expensive

- lead to circuits with many ancilla bits

# Realization of ESOP as reversible circuit


⑧

## Theorem

Every ESOP is realised using NOT, Fe, Toffoli with one ancilla bit.

All inputs go through.
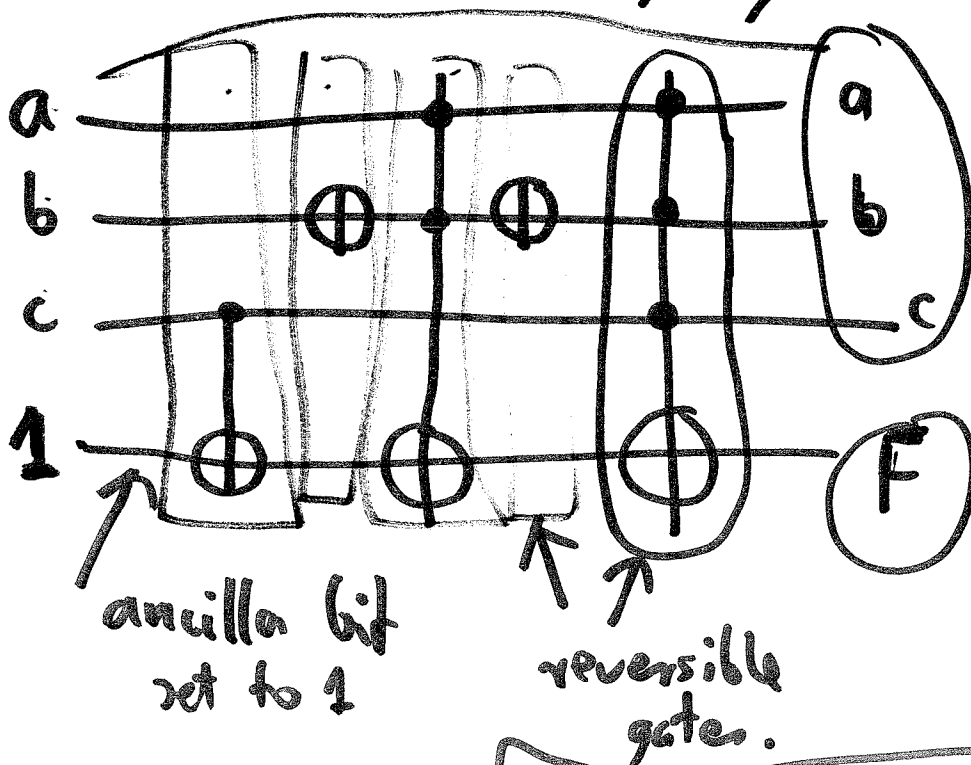
$$F = a\bar{b} \oplus abc \oplus c \oplus 1$$




ESOP is composition of reversible gates



$$\underline{f = ab}$$

(8A)

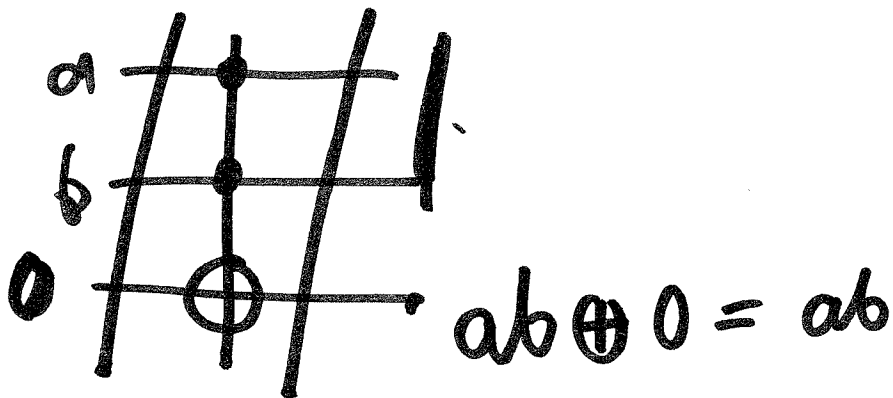

### Remark 1

Our method automatically converts functions from non-reversible to reversible.


### Remark 2

Single product requires one ancilla bit set to 0 as shown above

$$F(a,b,c) = \cancel{a} \oplus \cancel{b} \oplus (\bar{c} \oplus 1) \quad \textcircled{9}$$

$$G(a,b,c) = ab \oplus \bar{a}bc$$

$$H(a,b,c) = abc$$

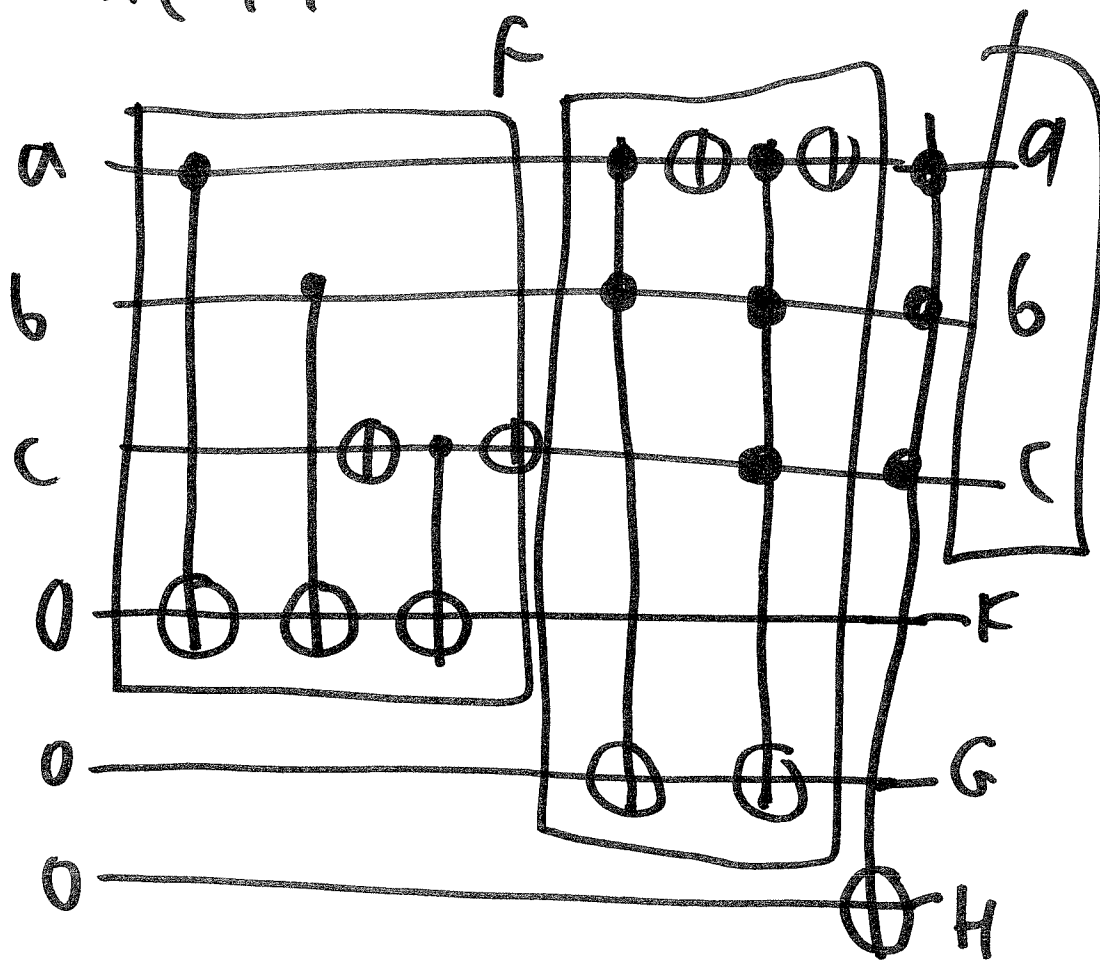

quantum  
array

Here we realized 3-output  
function (F, G, H) with  
3 ancilla bits set to 0

(16)

## Analysis of reversible circuits.

If two gates are connected in parallel, to calculate their permutative matrix we do a Kronecker product of matrices of these gates.


Kronecker product  
= tensor product  
= tensor multiplication.

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix} \otimes \begin{bmatrix} x & y \\ z & v \end{bmatrix}$$

(11)

$$= \begin{bmatrix} a \begin{bmatrix} x & y \\ z & v \end{bmatrix} & b \begin{bmatrix} x & y \\ z & v \end{bmatrix} \\ c \begin{bmatrix} x & y \\ z & v \end{bmatrix} & d \begin{bmatrix} x & y \\ z & v \end{bmatrix} \end{bmatrix} = \begin{bmatrix} ax & ay & bx & by \\ az & av & bz & bv \\ cx & cy & dx & dy \\ cz & cv & dz & dv \end{bmatrix}$$

Kronecker Product

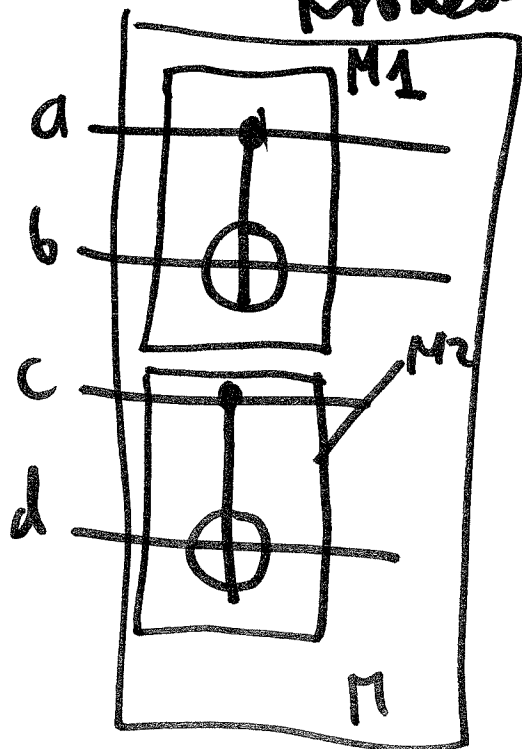

$$M = M_1 \otimes M_2$$

at

(12)

00 01 10 11

M1 M2


$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$

$$M_1 \otimes M_2 \begin{bmatrix} 1 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} \\ 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 1 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} \\ 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 1 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} \\ 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 0 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} 1 \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} \end{bmatrix}$$

$M_1 \otimes M_2$


(13)

|                                                               |                                                       |                                                       |                                                       |
|---------------------------------------------------------------|-------------------------------------------------------|-------------------------------------------------------|-------------------------------------------------------|
| $\begin{matrix} 1 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 0 \end{matrix}$ | 0                                                     | 0                                                     | 0                                                     |
| 0                                                             | $\begin{matrix} 1 & 1 \\ 0 & 1 \\ 1 & 0 \end{matrix}$ | 0                                                     | 0                                                     |
| 0                                                             | 0                                                     | 0                                                     | $\begin{matrix} 1 & 1 \\ 0 & 1 \\ 1 & 0 \end{matrix}$ |
| 0                                                             | 0                                                     | $\begin{matrix} 1 & 1 \\ 0 & 1 \\ 1 & 0 \end{matrix}$ | 0                                                     |

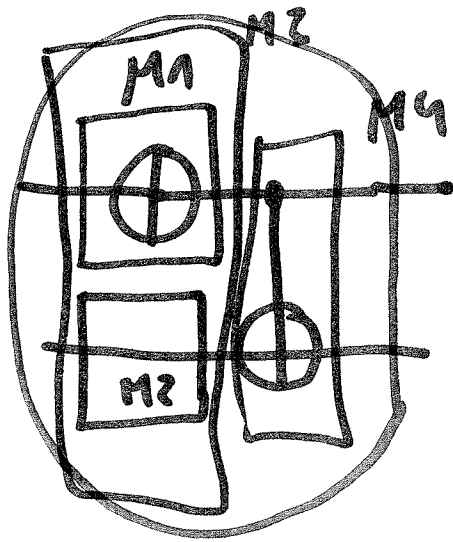

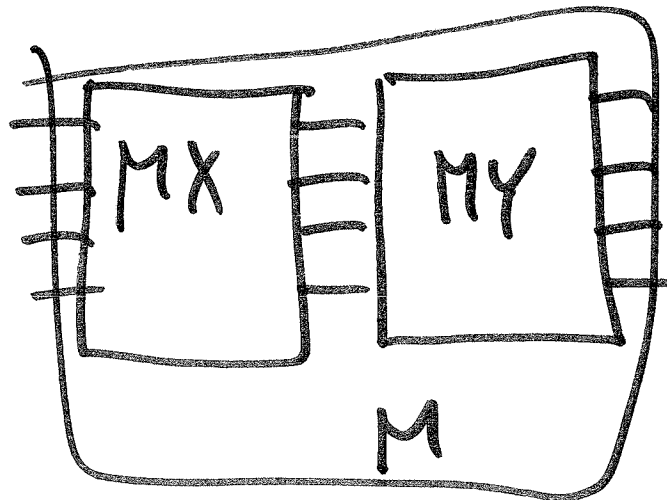(14)

The permutive matrix of  
 serial connection of gates  
 with matrices  $MX$  and  $MY$   
 is  $MY * MX$



$$M = MY * MX$$

Please pay attention to reverse  
 order of matrices.

Prove why it is so?

$$M_1 = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \leftarrow \text{investor}$$

14A

$$M_2 = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \leftarrow \text{wire}$$

$$M_1 \otimes M_2 = \begin{bmatrix} 0 \cdot \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} & 1 \cdot \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \\ 1 \cdot \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} & 0 \cdot \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \end{bmatrix}$$

Properties of Kronecker product

$$a \otimes (b \otimes c) = (a \otimes b) \otimes c$$

~~$$a \times b = b + a$$~~



example continued

15

$$M_1 \otimes M_2$$

=

$$\begin{bmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \end{bmatrix}$$

$$M_4 =$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$

~~$M = M_1 \otimes M_2$~~

$$M = M_4 * (M_1 \otimes M_2)$$


$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} * \begin{bmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 \\ \vdots & \vdots & \vdots & \vdots \\ 0 & 1 & 0 & 0 \end{bmatrix}$$

## HOMEWORK 2

### PART 1

Given is the following circuit.

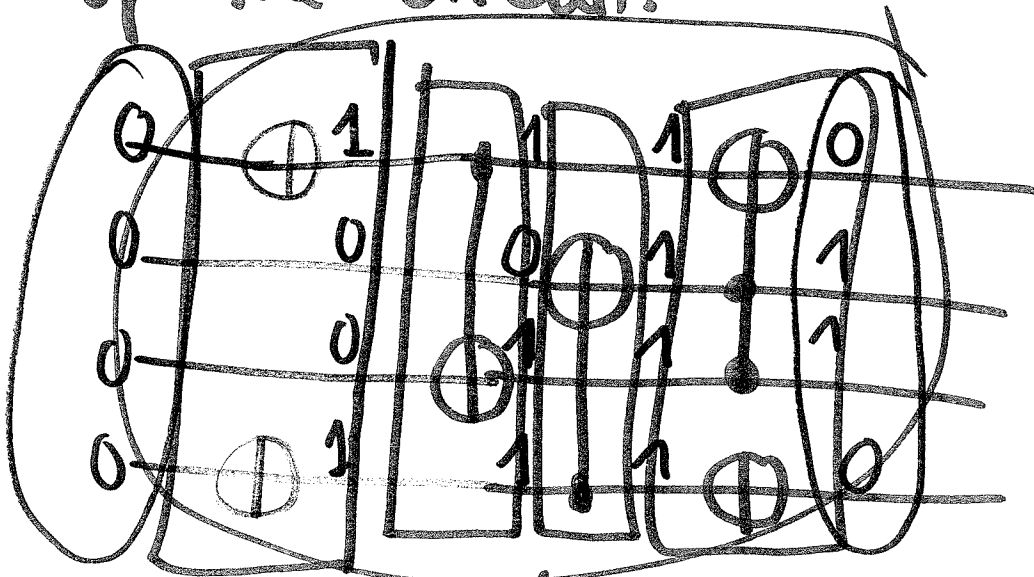1. Use Matlab to calculate all intermediate Matrices and the final matrix of the circuit.  $M$



suggestion - use swap  
gate

2. Given matrix  $M$  calculate  
the output state for  
the input state  $0000$

$$10 \rangle \quad \begin{matrix} 0000 = 0 \begin{bmatrix} 1 \\ 0 \end{bmatrix} \text{---} \\ 0 \begin{bmatrix} 1 \\ 0 \end{bmatrix} \text{---} \\ 0 \begin{bmatrix} 1 \\ 0 \end{bmatrix} \text{---} \\ 0 \begin{bmatrix} 1 \\ 0 \end{bmatrix} \text{---} \end{matrix}$$

$$0 \otimes 0 \otimes 0 \otimes 0 = \left[ \begin{bmatrix} 1 \\ 0 \end{bmatrix} \otimes \begin{bmatrix} 1 \\ 0 \end{bmatrix} \right] \otimes \begin{bmatrix} 1 \\ 0 \end{bmatrix} \otimes \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \left[ \begin{matrix} 1 \\ 0 \\ 0 \\ \vdots \\ 0 \end{matrix} \right] \Bigg\}^{16}$$

$$\downarrow$$

$$\left[ \begin{matrix} 1 \begin{bmatrix} 1 \\ 0 \end{bmatrix} \\ 0 \begin{bmatrix} 1 \\ 0 \end{bmatrix} \end{matrix} \right] = \begin{matrix} 000 \\ \left[ \begin{matrix} 1 & 00 \\ 0 & 01 \\ 0 & 10 \\ 0 & 11 \end{matrix} \right] \end{matrix}, \quad \left[ \begin{matrix} 1 \\ 0 \\ \vdots \\ 0 \end{matrix} \right]$$

$$16 \left[ \begin{matrix} 1 \\ 0 \\ \vdots \\ 0 \end{matrix} \right]$$


$$0 = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$1 = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$\begin{bmatrix} \langle \text{placeholder for signal zero} \rangle \\ \langle \text{placeholder for signal one} \rangle \end{bmatrix}$$

$$\begin{matrix} 0 & & 1 \\ & \oplus & \\ \begin{bmatrix} 1 \\ 0 \end{bmatrix} & & \end{matrix}$$
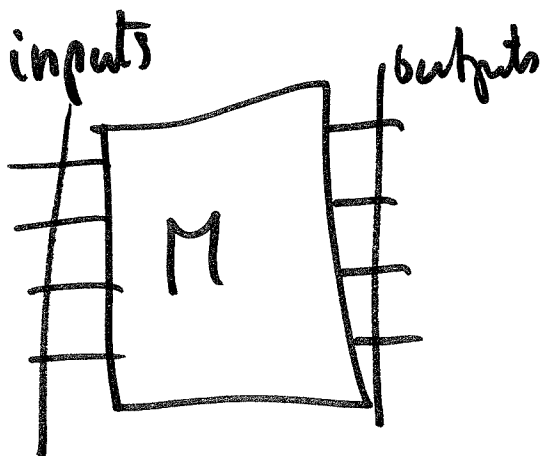
$$\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \times \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 0+0 \\ 1+0 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$



$$\begin{bmatrix} 16 \times 16 \end{bmatrix} \begin{bmatrix} 16 \\ \times 1 \end{bmatrix}$$

$$\text{outputs} = M \times \text{inputs}$$

$$M = M1 \otimes M2$$

①9

$$\gg M = \text{kron}(M1, M2)$$

↑  
in Matlab

$$M1 = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$$

$$\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$$

$\gg$

$$M1 * M2$$

All these are easy  
in Matlab

# Positive Polarity Reed Muller (20)

We start from DSOP

DSOP<sub>1</sub>

| ab \ cd | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 0  | 0  | 0  | 0  |
| 01      | 0  | 0  | 1  | 0  |
| 11      | 0  | 1  | 1  | 1  |
| 10      | 0  | 1  | 1  | 1  |

Annotations for DSOP<sub>1</sub>:

- $bcd$  (points to the row where  $b=1, c=1, d=0$ )
- $acd$  (points to the column where  $a=1, c=1, d=0$ )
- $a\bar{c}d$  (points to the cell at  $a=1, c=0, d=1$ )
- $\bar{a}bcd$  (points to the cell at  $a=0, b=1, c=1, d=0$ )

$$DSOP = bcd \oplus acd \oplus a\bar{c}d \oplus \bar{a}bcd$$

$$= bcd \oplus acd \oplus 1 \oplus a(\bar{c} \oplus 1)d \oplus a(b \oplus 1)cd$$

$$= bcd \oplus acd \oplus (ac) \oplus \bar{a}cd$$

DSOP<sub>2</sub>

|  |   |   |   |   |
|--|---|---|---|---|
|  |   |   |   |   |
|  |   |   | 1 |   |
|  | 1 | 1 |   | 1 |
|  |   |   |   |   |

Annotations for DSOP<sub>2</sub>:

- $\bar{a}bcd$  (points to the cell at  $a=0, b=1, c=1, d=0$ )
- $acd$  (points to the cell at  $a=1, c=1, d=0$ )
- $ad$  (points to the cell at  $a=1, d=1$ )

$$f = ad \oplus ac(1 \oplus d) \oplus (1 \oplus a)bcd$$

$$= (ad) \oplus (ac) \oplus (acd) \oplus bcd \oplus (abcd)$$

I calculated PPRM form  
from  $DSVP_1$  and  $DSVP_2$ .

(21)

Because function was the  
same in both cases I

obtained the same  
PPRM form in both cases

equal

$$\underline{abcd} \oplus \underline{acd} \oplus \underline{ad} \oplus \underline{ac} \oplus \underline{bcd}$$

positive polarity.

Part 3 of homework

a) Given is function G

| ab \ c | 0 | 1 |
|--------|---|---|
| 00     | 0 | 1 |
| 01     | 0 | 1 |
| 11     | 1 | 0 |
| 10     | 0 | 1 |

Find the  
PPRM  
of this  
function.

b) Find all FPRMs of this function.

(22)

end of homework for today

we will continue on Wed.

PPRM

$$f = \underline{a} \oplus \underline{b} \oplus \underline{cde} \oplus \underline{ac}$$

$$\begin{array}{ccccc} a & b & c & d & e \\ 1 & 1 & 1 & 1 & 1 \end{array}$$

$$f = \bar{a} \oplus b \oplus \bar{a}b \oplus \bar{a}\bar{c} \oplus b\bar{c}$$

abc

010  $\Leftarrow$  polarity.



$$\overline{a}\overline{c}$$

polarity 00

(23)

10  
Pm

$$= (1 \oplus a) \overline{c} = \underline{\overline{c} \oplus a\overline{c}}$$

$$= (1 \oplus a)(1 \oplus c) \quad \text{Pola} \quad (11)$$

$$= \underline{1 \oplus a \oplus c \oplus ac}$$

FOR FUNCTION OF  
n variables

there is  $2^n$  various  
polarities.

there is  $2^n$  FPRM forms.

We select the best form,  
with minimum cost.