

LECTURE 4 Wednesday ①

① Kronecker Multiplication

can be applied to any
size and shape of matrices.

here are examples

$$\begin{bmatrix} a \\ b \end{bmatrix} \otimes \begin{bmatrix} c \\ d \end{bmatrix} = \begin{bmatrix} a \begin{bmatrix} c \\ d \end{bmatrix} \\ b \begin{bmatrix} c \\ d \end{bmatrix} \end{bmatrix} = \begin{bmatrix} ac \\ ad \\ bc \\ bd \end{bmatrix}$$

$$|0\rangle = 0 = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$|1\rangle = 1 = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$|0\rangle \otimes |1\rangle = \begin{bmatrix} 1 \\ 0 \end{bmatrix} \otimes \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 \begin{bmatrix} 0 \\ 1 \end{bmatrix} \\ 0 \begin{bmatrix} 0 \\ 1 \end{bmatrix} \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} \begin{matrix} 00 \\ 01 \\ 10 \\ 11 \end{matrix}$$

$$\begin{aligned} [a \ b] \otimes [c \ d] &= [a [c \ d] \quad b [c \ d]] \\ &= [ac \ ad \ bc \ bd] \end{aligned}$$

$$[a \ b] \otimes \begin{bmatrix} c \\ d \end{bmatrix} = [a \begin{bmatrix} c \\ d \end{bmatrix} \ b \begin{bmatrix} c \\ d \end{bmatrix}] \quad (2)$$

$$= \begin{bmatrix} ac & bc \\ ad & bd \end{bmatrix}$$

$$\begin{bmatrix} a \\ b \end{bmatrix} \otimes [c \ d] = \begin{bmatrix} a[c \ d] \\ b[c \ d] \end{bmatrix} = \begin{bmatrix} ac & ad \\ bc & bd \end{bmatrix}$$

$$\begin{matrix} & * \\ \begin{bmatrix} a & b \\ c & d \end{bmatrix} & * \begin{bmatrix} x & y \\ z & v \end{bmatrix} = \begin{bmatrix} ax+bz & ay+bv \\ cx+dz & cy+dv \end{bmatrix} \end{matrix}$$

② convolution operator on vectors



$$[a \ b] \text{ conv } [c \ d]$$

$$(ax+b) \cdot (cx+d) = acx^2 + axd + bcx + bd$$

$$= (ac)x^2 + (ad+bc)x + bd$$

$$[ac \ ; \ ad+bc \ ; \ bd]$$

③ CARTESIAN PRODUCT OF SETS ③

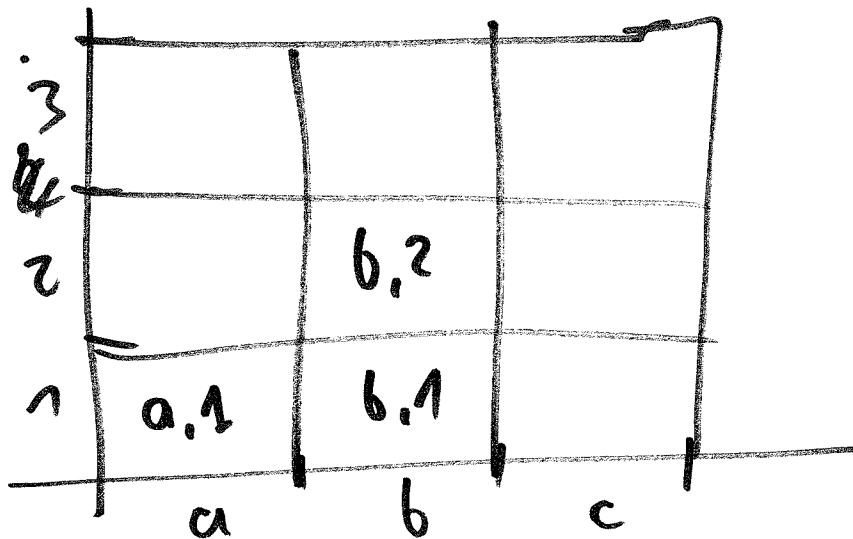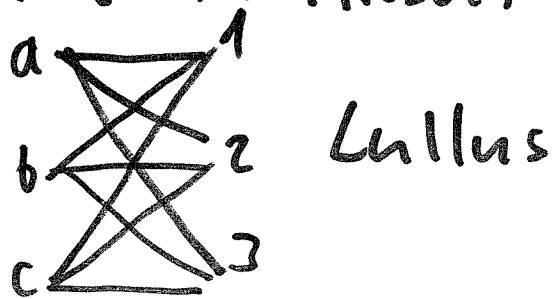

CARTESIAN PRODUCT.

$$\begin{bmatrix} a \\ b \\ c \end{bmatrix} \text{ CART } \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} ax & ay & az & bx & by & bz & cx & cy & cz \end{bmatrix}$$

④ Reed-Muller forms of Boolean functions a, b, c - 3 variables

1 a b c
 ab ac bc
 abc

these are standard trivial (or basis) functions

1	a	b	c	ab	ac	bc	abc
---	---	---	---	----	----	----	-----

↑ order of coeffic

f_1

1	0	1	1	0	1	0	0
---	---	---	---	---	---	---	---

this vector represents PPR1

f_2

1	1	1	0	1	1	0	1
---	---	---	---	---	---	---	---

$f_1 \oplus f_2$

exoring binary vectors creates other functions as vectors

0	1	0	1	1	1	0	1
---	---	---	---	---	---	---	---

another order for PPRM

(5)

$$\left(\begin{bmatrix} 1 \\ a \end{bmatrix} \otimes \begin{bmatrix} 1 \\ b \end{bmatrix} \right) \otimes \begin{bmatrix} 1 \\ c \end{bmatrix}$$

$$\downarrow$$

$$\begin{bmatrix} 1 \begin{bmatrix} 1 \\ b \end{bmatrix} \\ a \begin{bmatrix} 1 \\ b \end{bmatrix} \end{bmatrix} = \begin{bmatrix} 1 \\ b \\ a \\ ab \end{bmatrix}$$






$$\begin{bmatrix} 1 \\ b \\ a \\ ab \end{bmatrix} \otimes \begin{bmatrix} 1 \\ c \end{bmatrix} = \begin{bmatrix} 1 \begin{bmatrix} 1 \\ c \end{bmatrix} \\ b \begin{bmatrix} 1 \\ c \end{bmatrix} \\ a \begin{bmatrix} 1 \\ c \end{bmatrix} \\ ab \begin{bmatrix} 1 \\ c \end{bmatrix} \end{bmatrix} = \begin{bmatrix} 1 \\ c \\ b \\ bc \\ a \\ ac \\ ab \\ abc \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 1 \\ 0 \\ 0 \\ 1 \end{bmatrix}$$

We use Kronecker product
of vectors to find order
of basis functions

$$f = ac \oplus abc$$


⑤ Butterflies, kernels, and matrices

⑥

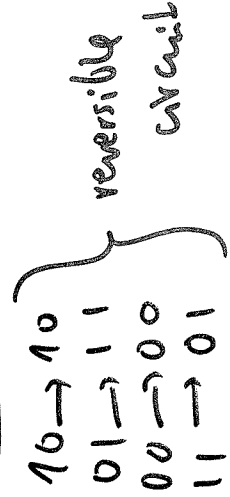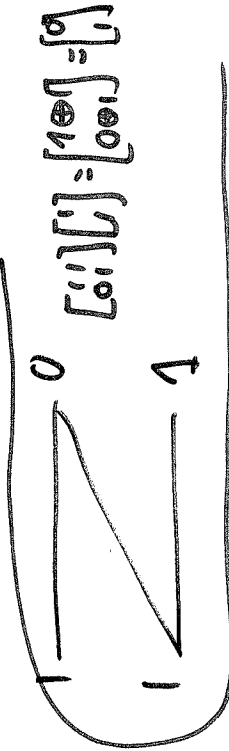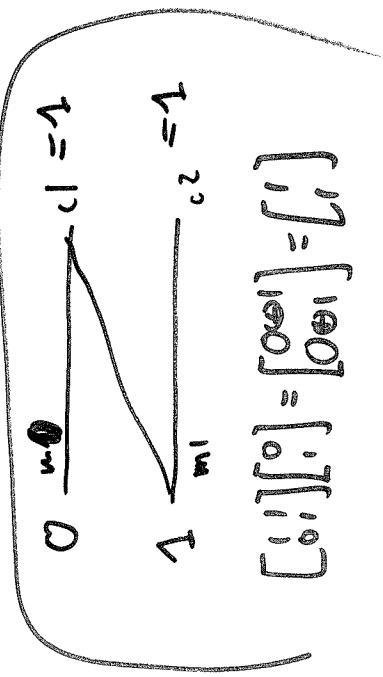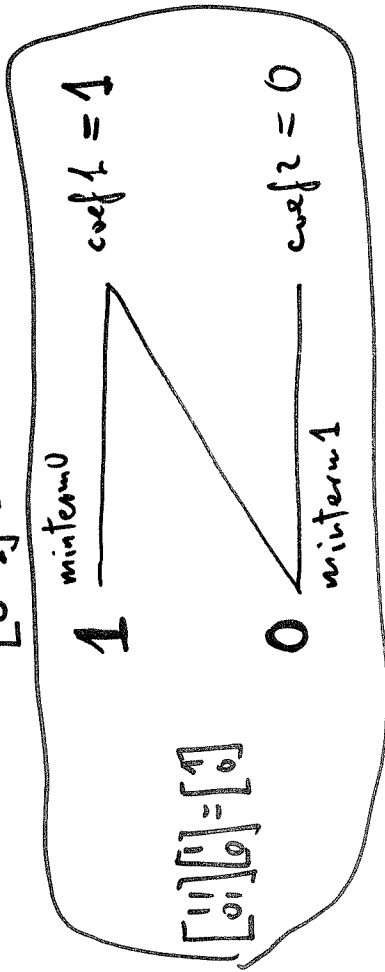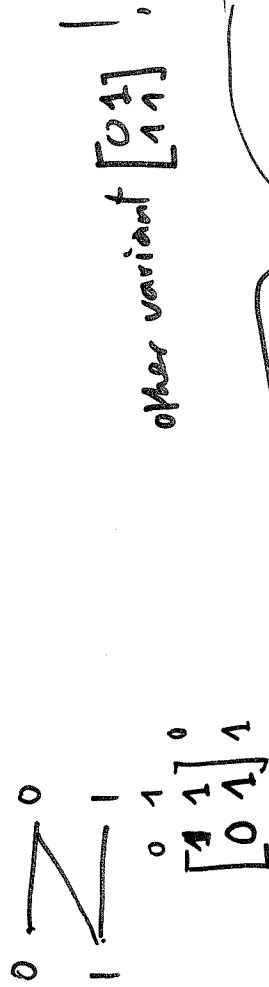


7

7

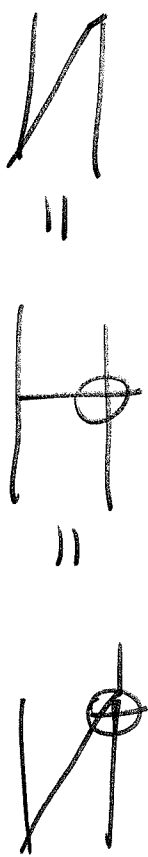

$\begin{bmatrix} 1 & 1 \\ 1 & 0 \end{bmatrix}$ $\begin{bmatrix} 1 & 0 \\ 1 & 1 \end{bmatrix}$ ← other variant

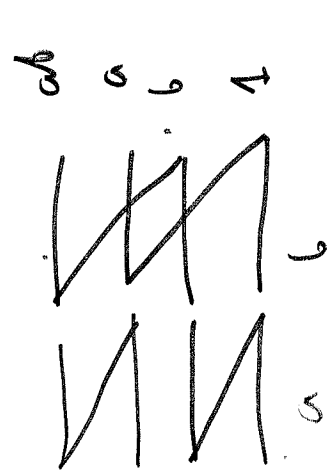the variants affect only order of coefficients, not their set




butterfly circuit

for 2 variables will require $2 \times 2 = 4$ rows and 4 columns

4×4 matrix


remember, this is a reversible circuit

$2^4 \times 2^4$ matrix
 16×16

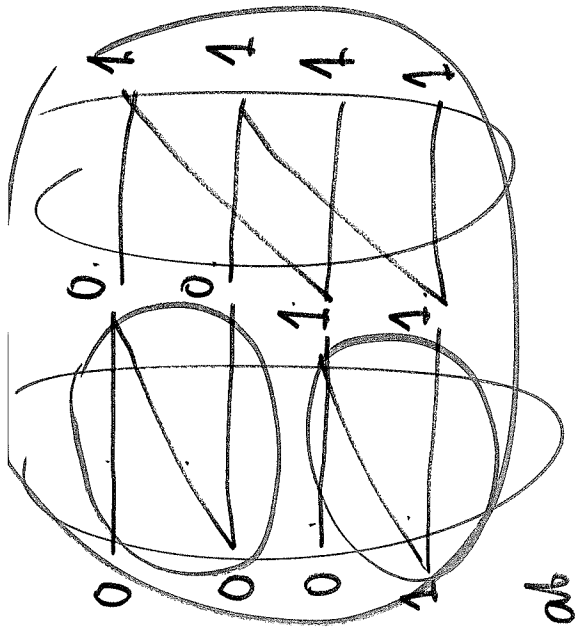

$$\bar{a}\bar{b} \oplus a\bar{b} \oplus \bar{a}b \oplus ab \quad \textcircled{x}$$

$$= ab$$

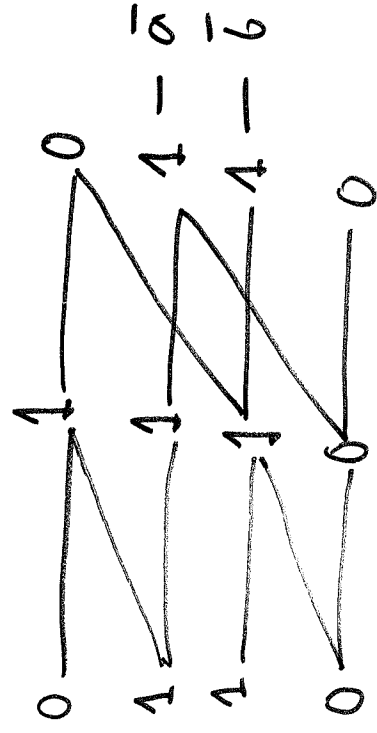

$$\bar{a}\bar{b} = a \oplus b =$$

$$\bar{a}b + a\bar{b}$$



we propagate values
from left to right
through the network
(butterfly)

9

NPRM transform for two variables, a, b.

$$\begin{array}{c|cc|cc} \bar{a}\bar{b} & \bar{a}b & a\bar{b} & ab \\ \hline 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 \end{array} \rightarrow \begin{bmatrix} \bar{a}\bar{b} \\ \bar{a}b \\ a\bar{b} \\ ab \\ 1 \end{bmatrix}$$
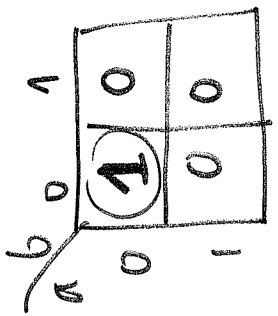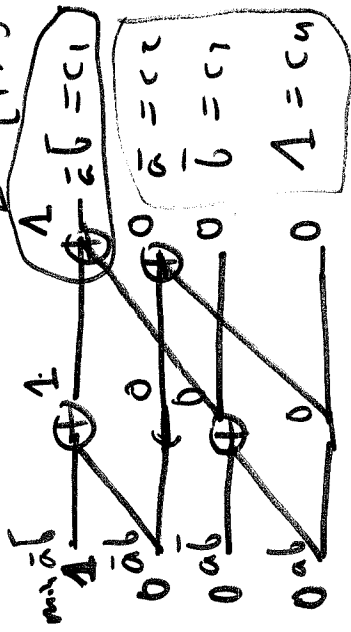
$$\begin{bmatrix} \bar{a} \\ 1 \end{bmatrix} \times \begin{bmatrix} \bar{b} \\ 1 \end{bmatrix} = \begin{bmatrix} \bar{a} & \bar{b} \\ 1 & 1 \end{bmatrix} = \begin{bmatrix} \bar{a} & \bar{b} \\ 1 & 1 \end{bmatrix}$$



$$\bar{a}\bar{b} = \text{bubbled function}$$


$$\bar{a}\bar{b} = \text{NPRM if its negative polarity function}$$

negative polarity.

Remember.
Matrices, Butterflies and circuits are equivalent

You can use small matrices of transform (with exor'ing) or large matrices of reversible gates to get the same results, but using small matrices is faster!

(10)

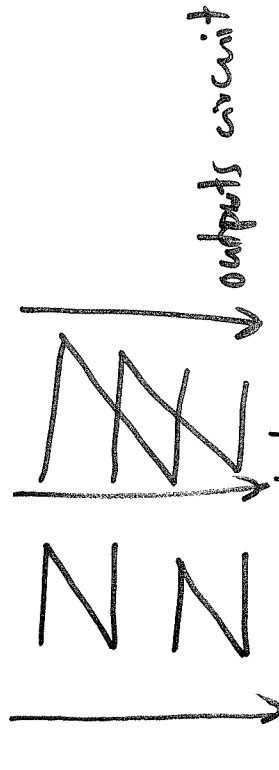

coefficients

$\bar{a}\bar{b}$ $\bar{a}b$ $a\bar{b}$ ab
00 01 10 11

$$= \begin{bmatrix} 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

← calculation of matrix of whole RM transform using Kronecker product

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \bar{a}$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \stackrel{\bar{a}}{\leftarrow} \bar{a} \stackrel{b}{\leftarrow} 1$$

$$\begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 \cdot 1 \oplus 1 \cdot 1 \\ 0 \cdot 1 \oplus 1 \cdot 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \stackrel{\bar{a}}{\leftarrow} \bar{a}$$

1, $\bar{a}$

NPRM

You (as me) may have trouble with order of coefficients. But you can always check!!

How to expand our butterfly

for more variables


var a var b var c

1

2

4

dist

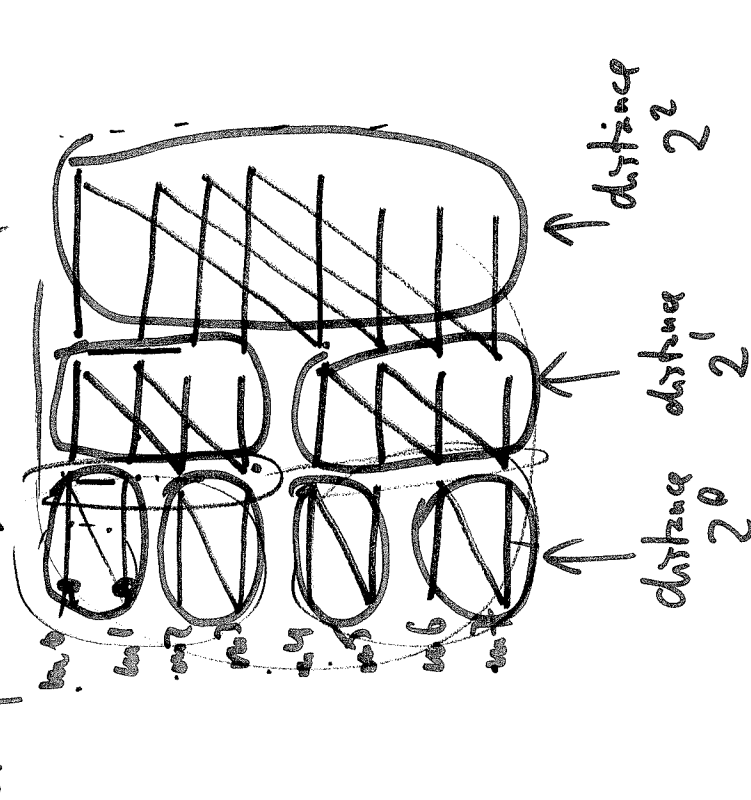

(11)


We showed a regular method of expand butterflies to any number of variables.

Similar methods are used for Walsh, Hadamard, Haar, Fourier and other transforms.

This is much used in DSP and image processing circuits and systems

⑫

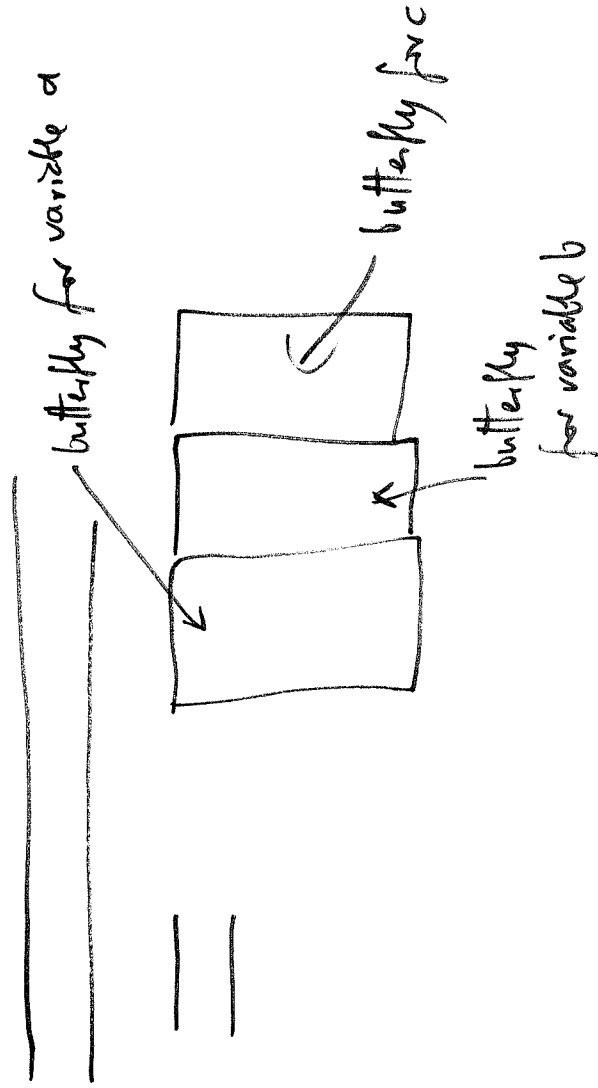Observation
Every possible FPRM form
can be calculated by
a combination of stages
of butterfly diagram
for $\bar{a}$ a





Idea Switch butterfly columns from
positive to negative polarity
in all possible ways $\rightarrow 2^n$

Universal
FPRM
circuit




(6)

for $a=0$

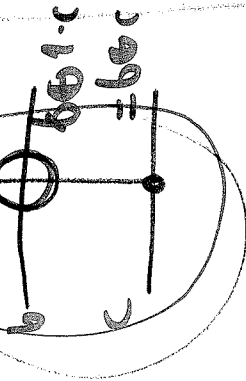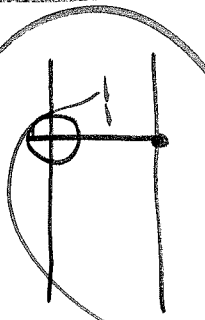


$$b \oplus 1 \cdot c = b \oplus c$$

for $a=1$

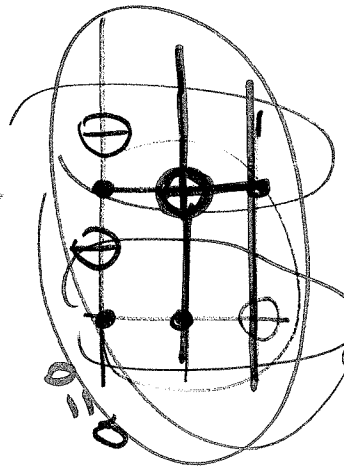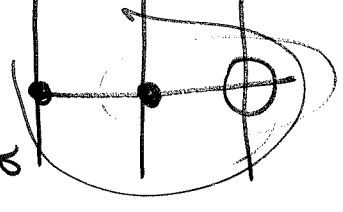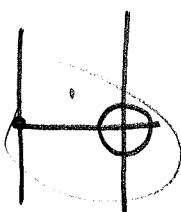

$$a \oplus 0 = a$$

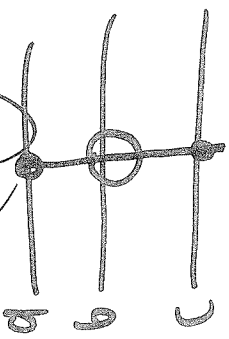

$$a \cdot c \oplus b$$

$$a=0 \rightarrow b$$

$$a=1 \rightarrow c \oplus b$$



$$b \oplus 0 \cdot c = b$$

$$Z \oplus Z$$

Synthesis of (13)


circuit that
is controlled to
execute both polarity
expansions for
each column

controls

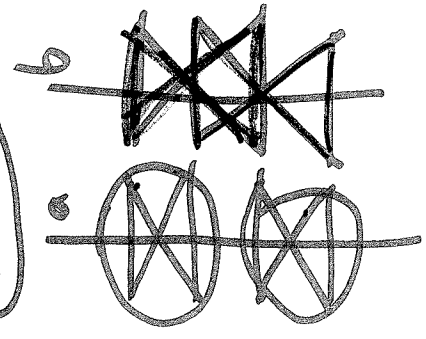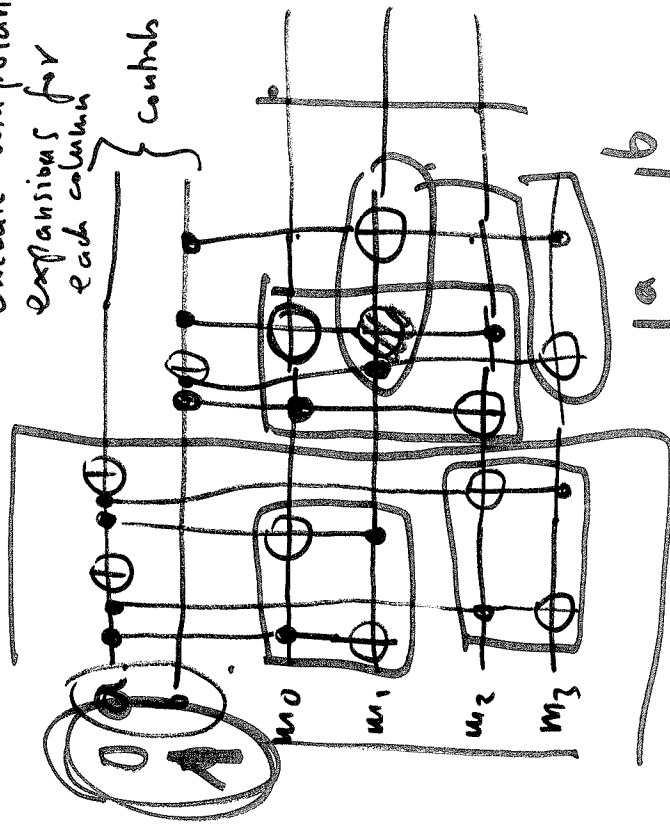

Please analyse this circuit carefully!

(14)

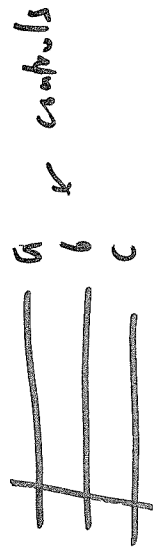


000 $\rightarrow$ 3 wires $\rightarrow 2^3$ states

$2^3 = 8$

Last part of homework 3



Design a complete circuit for all FPRMs of 3 variables that finds the FPRM (one out of $2^3 = 8$) polarity with the minimum number of coefficients = 1

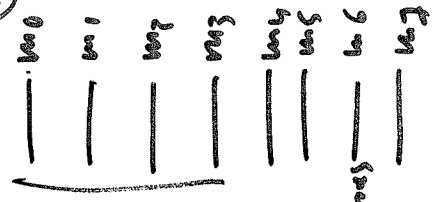$\rightarrow$ you will have to calculate for each polarity how many coefficients on output are equal to 1!



⑧ Part of your homework /
 You will have to design
 the circuit that is called
 "number of ones".

⑨

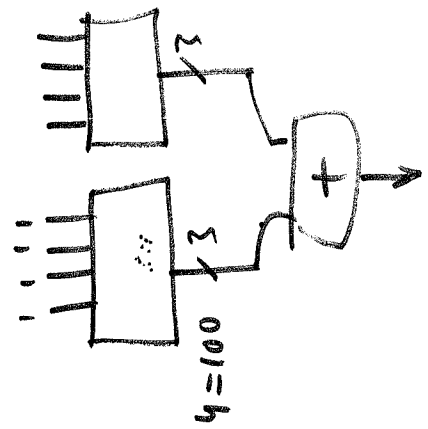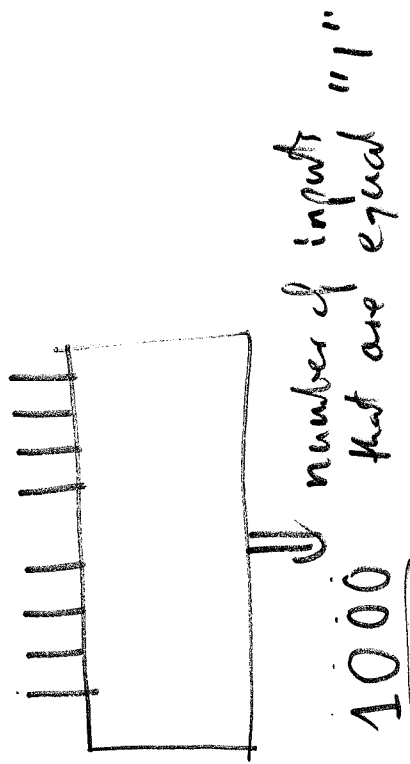

Circuit for detection of "number of ones" in 4 bits

cd \ ab	00	01	11	10
00	0	1	2	1
01	1	2	3	2
11	2	3	4	3
10	1	2	3	2

of ones for every cell

I have to "subtract 1" in this zero

cd \ ab	00	01	11	10
00	000	001	010	001
01	001	010	011	010
11	010	011	100	011
10	001	010	011	010

This is a good example of a symmetric function

(16)

$$\underline{bd+cd} + \underline{bc} + \underline{ac} + \underline{ad} + \underline{ab}$$

$$b(d+c+a) + d(c+a+b)$$

cd \ ab	00	01	11	10
00	0	1	1	0
01	0	1	1	1
11	1	1	1	1
10	0	1	1	1

cd \ ab	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	0	1	0	1
10	1	0	1	0


cd \ ab	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	1	0
10	0	0	0	0

$$x = abcd$$

$$z = a \oplus b \oplus c \oplus d$$

⑦

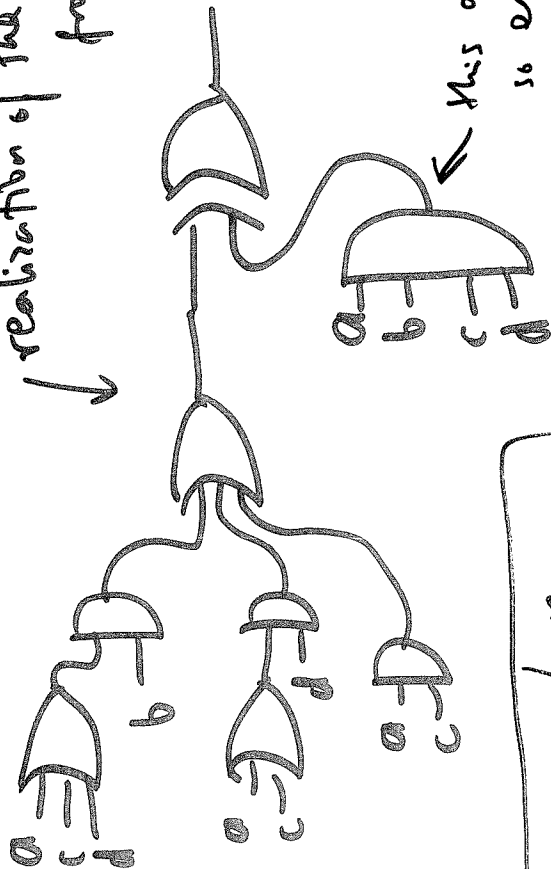
realization of the circuit
from page 16
using exoring



← this group is included
so exoring is the
same as sharpening

sharpen
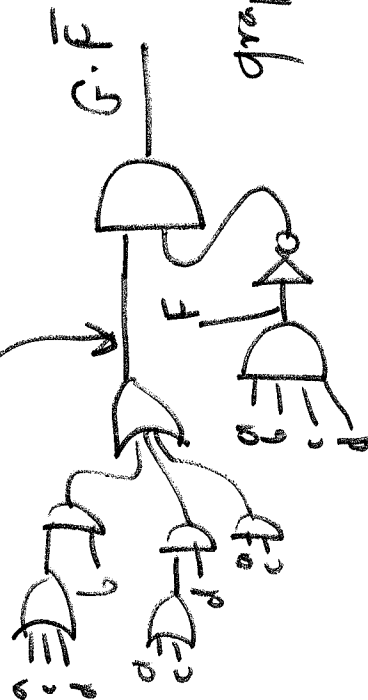
$$G \# F = G \cdot \bar{F} \quad \text{General inhibition method.}$$




graphical subtraction



Graphical synthesis, in software uses sharp

9 The method of inhibiting or subtracting

I subtract for only

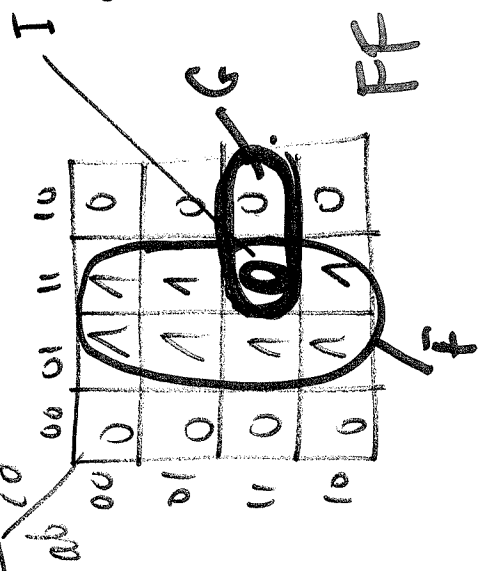

$$F \# G = F \cdot \overline{G}$$

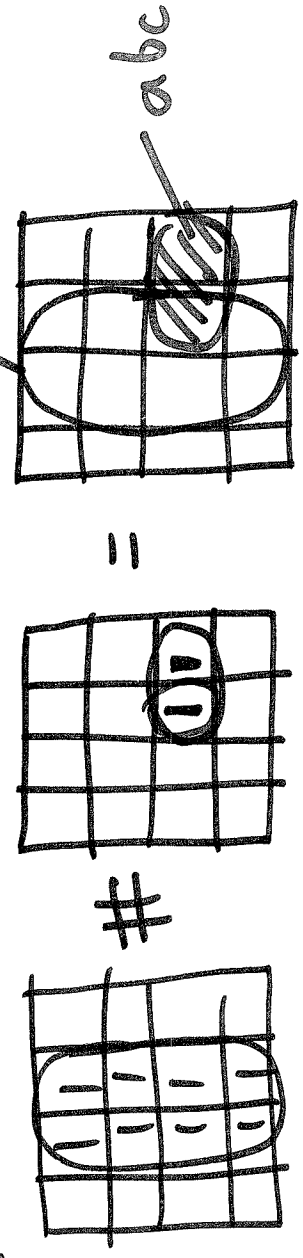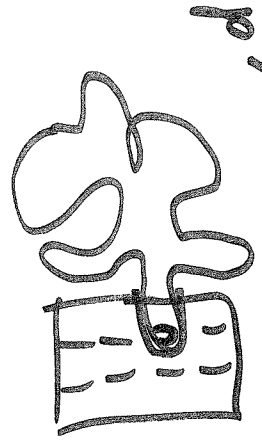

$$F \# G = F \cdot \overline{G}$$

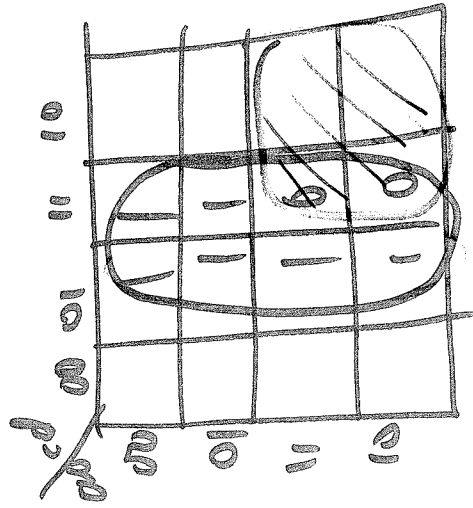


Illustration of
graphical subtraction



$$\overline{d \cdot ac}$$

$$= d \cdot (\overline{a} \cdot \overline{c})$$


$d \# ac$

↑ sharp, cube calculus
operation

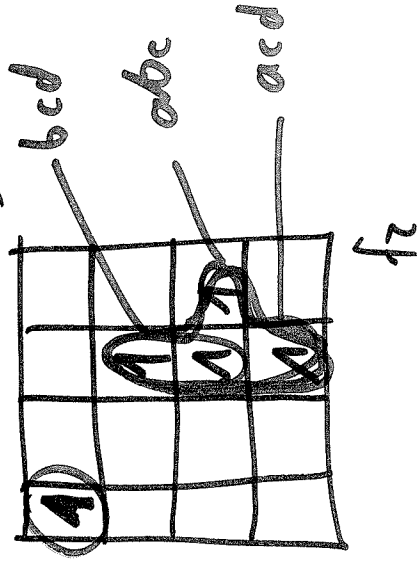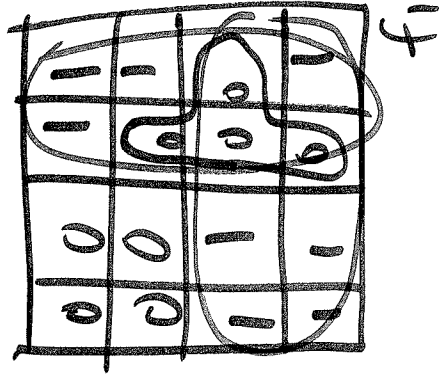
Example of multi-output design using inhibition



$$ac(b+d) + bcd$$

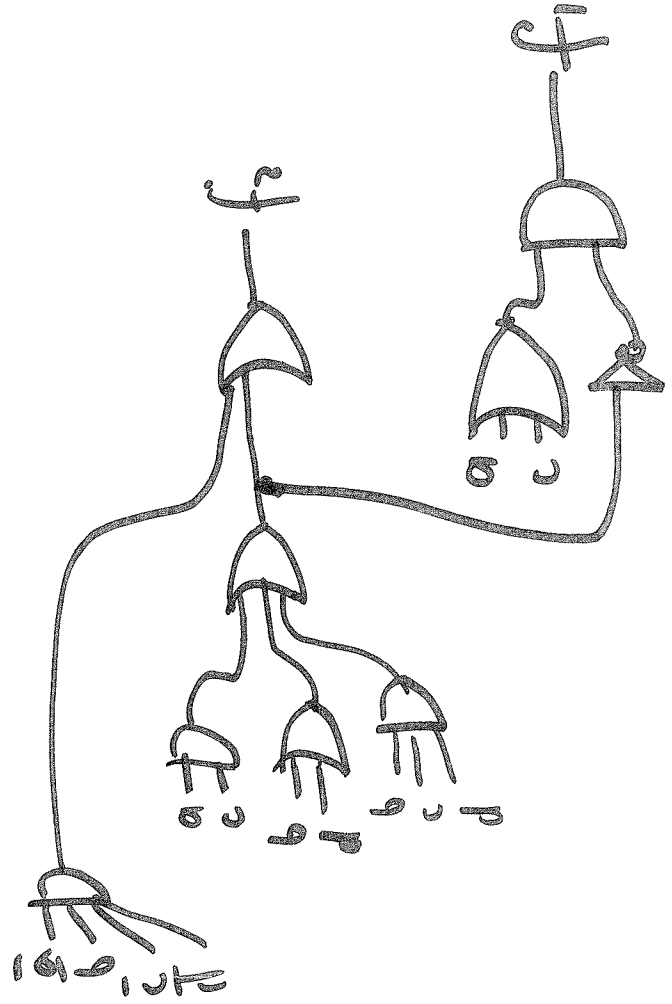



10) Using multiplexers in synthesis

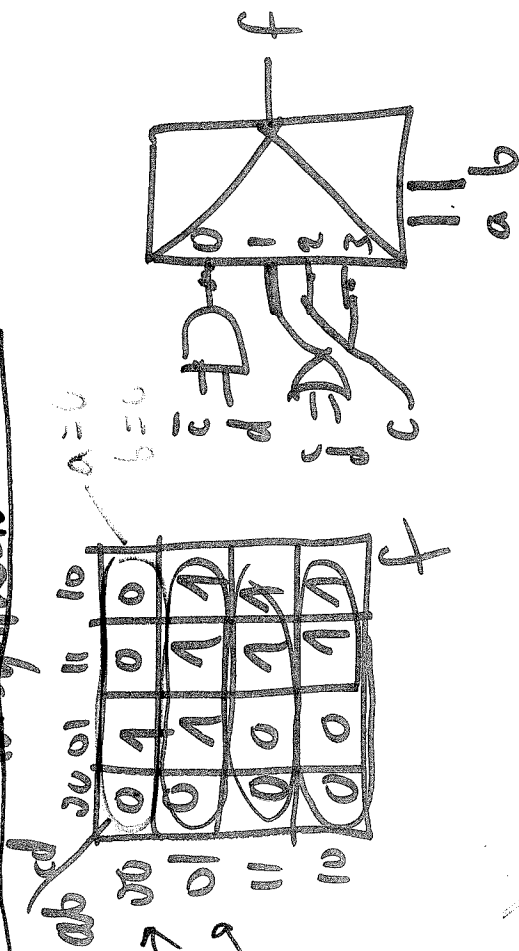



$$a=0 \quad b=1$$

$$a=1 \quad b=0$$

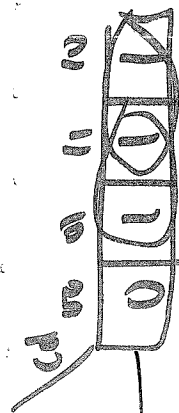

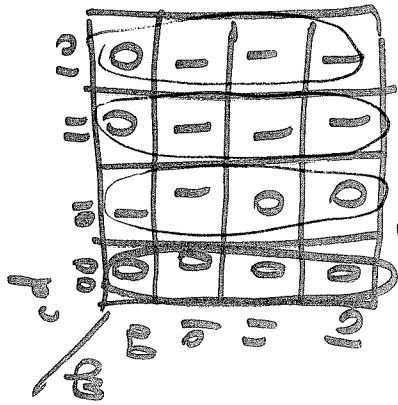

shapes of cofactors for c, d in address

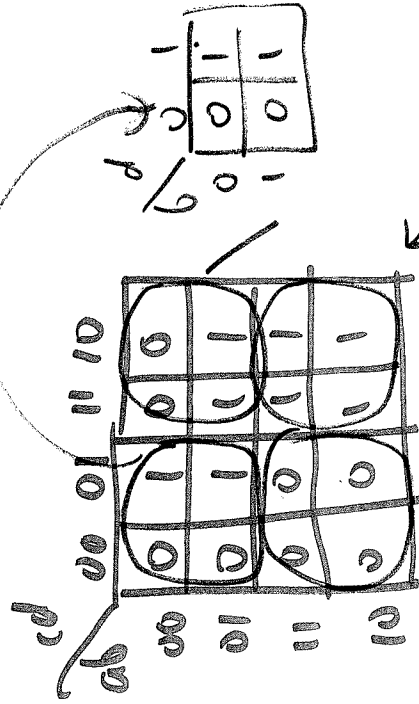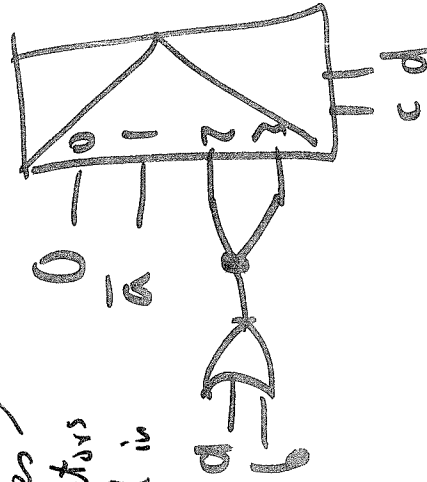

shapes of cofactors for variables a, c

