

Asynchronous Circuits Design

Marc Renaudin

TIMA

Marc.Renaudin@imag.fr

<http://tima.imag.fr>

<http://tima.imag.fr/cis/>



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

1

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
- Design experiments
- Conclusion and prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

2

CIS group of TIMA laboratory

TIMA (<http://tima.imag.fr>)

About 130 people

Six research groups

- MNS : Micro and Nano Systems
- RMS : Reliable Mixed Signal Systems
- SLS : System Level Synthesis
- VDS : Verification and modeling of Digital Systems
- QLF : QuaLiFication of circuits
- CIS : Concurrent Integrated Systems



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

3

CIS group of TIMA laboratory

“CIS” Group (<http://tima.imag.fr/cis>)

About 25 people

Research topics

- *Asynchronous circuits design and prototyping*
- *CAD Tools for Asynchronous circuits and systems*
- *Formal verification of asynchronous designs (Coll. with VDS D. Borrione)*
- *Hardware-software design for low power low noise*
- *Secure circuit design*
- *SoCs and NoCs design*
- *Signal driven sampling and processing*



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"




Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

4

CIS group of TIMA laboratory

Main results (<http://timam.imag.fr/cis>)

   - Asynchronous Processors
 - ASPRO (16 bit RISC)
 - MICA (8 bit CISC)
- Contactless Smart Card
- Secure chip design (DES, AES)
- A-ADC & non-uniformly sampled signal processing
- High dynamic range CMOS image sensors
- TAST framework (modeling, synthesis, validation)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

5

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
- Design experiments
- Conclusion and prospects




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

6

Asynchronous circuit design principles

 

- Unified asynchronous interface
 - Control and data are encoded (together or not)
 - Two basic rules :
 - the emitter issues a request when a data is valid
 - the receiver issues an acknowledge when the data is processed
- **Several hardware implementation of the handshake protocol**
- **Delay insensitivity**



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

7

Asynchronous circuit design principles

Features of a basic asynchronous cell

 

- Bit level
- Arithmetic function
- Complex function

- Maximum speed : minimum forward latency
 - Maximum throughput : minimum cycle time
 - Respect the handshake protocol
- **design issues solved locally => cells are easy to reuse**



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

8

Asynchronous circuit design principles

Design of a FIR filter

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"



Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

9

Asynchronous circuit design principles

The C-Element or Muller gate


Symbol

  

Truth
table

$$Z = XY + Z(X+Y)$$

X	Y	Z
0	0	0
0	1	Z^{-1}
1	0	Z^{-1}
1	1	1

 

- State holding
- Reset



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

10

Asynchronous circuit design principles

 - Protocol
 - Two phases
 - Four phases
- Signaling
 - Data encoding / Request
 - Three states
 - Four states
 - Acknowledge



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

11

Asynchronous circuit design principles

Two Phase Protocol

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

12

Asynchronous circuit design principles

Four Phase Protocol

 

=> Several derivatives exist



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

13

Asynchronous circuit design principles

Data Valid/Invalid Signaling

- Three state coding
- Four state coding

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex




CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

14

Asynchronous circuit design principles

Data encoding : Three states (dual rail)

   

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex




CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

15

Asynchronous circuit design principles

Data encoding : Four states (dual rail)

   

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

16

Asynchronous circuit design principles

Completion Signal Generation

 - Internal clock
- Use of a delay model
- Current sensing
- Use the data encoding



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

17

Asynchronous circuit design principles

Completion Signal Generation

- Internal clock

 

(First Data Flow Computer DDM1, 1978)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

18

Asynchronous circuit design principles

Completion Signal Generation

- Use of a delay model

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

19

Asynchronous circuit design principles

Completion Signal Generation

- Current sensing

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

20

Asynchronous circuit design principles

Completion Signal Generation


- Using data encoding (dual rail)

 

Asynchronous circuit design principles

Completion Signal Generation

- Using data encoding

 

Asynchronous circuit design principles

- Conclusion

- Asynchronous circuit communicate using an handshaking protocol

- Data/Request have to be encoded

- A completion signal is required

- The implementation may be delay insensitive

- Hazard free logic is required

- Hardware overhead ?



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

23

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties
- Design experiments and products
- Conclusion and prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

24

Asynchronous circuit classes

- Hazard free logic
- QDI / Speed Independent Circuits
 - Data path : a dual-rail OR Gate
 - Sequencing : the Q-Element
- Bounded delay circuits
 - Huffman circuits / Burst mode circuits
 - Sequencing : the Q-Element
- Micropipeline circuits




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 25

Asynchronous circuit classes

- Synchronous circuits

 

– Time is discrete

→ combinatorial logic is simple
(hazards ignored)

→ trivial communication mechanism

→ worst case approach

Global clock
=>
Global timing assumption



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 26

Asynchronous circuit classes

- Asynchronous circuits

 No global clock = no global timing assumption
Sequencing is based on Handshaking
=> Hazard free logic is required



- Delay insensitive circuits
- Quasi delay insensitive circuits
- Speed independent circuits
- Huffman / Burst-mode circuits
- Micropipeline

Robustness & Complexity
are decreasing :
more timing assumptions



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

27

Hazards

 - Static hazards
- Dynamic hazards
- Combinatorial hazards
- Functional hazards
- Sequential hazards



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"



Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

28

Hazards : introduction

- Hazard = spurious signal change
- Hazards appear during processing
 - it is then related to signal dynamics and component delays (wires and gates)
- Avoiding hazard implies :
 - to characterize the interaction between the circuit and its environment (define assumptions)
 - to characterize wire and gate delays (define assumptions)

  - Static hazard 0
- Static hazard 1
- Dynamic hazard 0
- Dynamic hazard 1



No hazard

With hazard



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


29

Hazards : Single Input Change (SIC)


Kmap to circuit with hazard

a \ bc	00	01
00	0	0
01	0	1
11	1	1
10	1	0

$$S = ac + /ab$$

 

Static hazard 1

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


30

Hazards : Single Input Change (SIC)

Solution

a bc	0	1
00	0	0
01	0	1
11	1	1
10	1	0

$$S = ac + /ab + bc$$

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

31

Hazards : Single Input Change (SIC)

Result

It has been proven that no hazard are generated during 0 to 0, 0 to 1 and 1 to 0 transitions in an AndOr circuit.

Dynamic hazard cannot be generated with AndOr circuits under the SIC condition

It is then only required to suppress 1 to 1 static hazards !

=> The solution is to cover 1 to 1 transitions in the Karnaugh Map



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

32

Hazards : Multiple Input Change (MIC)

Functional, Static and Dynamic hazards can be generated in this case !

Functional hazard : inherent to the specification. There is no possible hazard free implementation (with no timing assumption). The specification must be free of functional hazard.

ab	00	01	11	10
cd	00	1	1	1
	01	0	1	1
	11	0	1	1
	10	1	1	0

0010 to 0111 transition.

If b changes after d
there is a static 0
hazard at the output !



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

33


Hazards : Multiple Input Change (MIC)

Logic hazard : static 1

$$S = /c/d + /a/d + bd$$

ab	00	01	11	10
cd	00	1	1	1
	01	0	1	1
	11	0	1	1
	10	1	1	0

0100 to 0111 transition.

 

Solution : add $/ab$

No static 0 hazard in AndOr circuit under the MIC condition !



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

34


Hazards : Multiple Input Change (MIC)

Dynamic hazard : dynamic 0

$$S = /c/d + /a/d + bd + /ab$$

0111 to 1110 transition. No functional hazard.

ab	00	01	11	10
cd	00	1	1	
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	1	1	0	0

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

35


Hazards : Multiple Input Change (MIC)

Dynamic hazard : dynamic 0

Solution : strengthen /a/d

$$\rightarrow S = /c/d + /a/d/b + bd + /ab$$

ab	00	01	11	10
cd	00	1	1	1
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	1	1	0	0

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

36

Hazards : conclusion

Avoiding hazard is a Karnaugh Map covering problem !

1 to 1 : the transition must be covered

1 to 0 and 0 to 1 : avoid activation and deactivation of a minterm

0 to 0 : no hazard in an AndOr circuit.

The covering problem may not have a solution if there are several MIC transitions. Therefore a delay insensitive implementation may no exist !



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

37

Asynchronous circuit classes

- Asynchronous circuits

 No global clock = no global timing assumption
Sequencing is based on Handshaking
=> Hazard free logic is required



- Delay insensitive circuits
- Quasi delay insensitive circuits
- Speed independent circuits
- Huffman / Burst-mode circuits
- Micropipeline

Robustness & Complexity
are decreasing :
more timing assumptions



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

38

Asynchronous circuit classes

- Hazard free logic
- QDI / Speed Independent Circuits
 - Data path : a dual-rail OR Gate
 - Sequencing : the Q-Element
- Bounded delay circuits
 - Huffman circuits / Burst mode circuits
 - Sequencing : the Q-Element
- Micropipeline circuits



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 39

Asynchronous circuit classes

QDI Asynchronous circuits

 - Functionally correct without any assumption on the wire and gate delays (unbounded delay model) except...
- "Isochronic fork" timing assumption



→ High level of robustness (with respect to delay variations)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 40

Asynchronous circuit classes

Speed Independent Asynchronous circuits

- Functionally correct whatever the delays in the gates
(unbounded delay model)
 - The wires are assumed to be zero delay
 - => all wires are required to respect the isochronic fork property
- Less accurate than the QDI model



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

41

QDI/SI asynchronous circuits

 - Quasi Delay Insensitive & Speed Independent :
=> hazard free control logic & hazard free data-paths



- time is no longer discrete
- hazard free combinatorial logic
- handshake based communications
- mean time approach

→ **No timing assumption**



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

42


QDI/SI asynchronous circuits

- Implementing delay insensitivity : examples
 - Choice of a communication protocol (request - acknowledge)
 - 1 bit Channel
 - Data encoding

Data	ai0	ai1
0	1	0
1	0	1
Invalid	0	0

 

– 4 phase protocol

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex



CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

43

QDI/SI asynchronous circuits

- An example : dual-rail OR Gate

  

Implement both the function and the protocol



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

44

QDI/SI Asynchronous circuits

- An example : the Q-Element

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

45

Asynchronous circuit classes

- Hazard free logic
- QDI / Speed Independent Circuits
 - Data path : a simple OR Gate
 - Sequencing : the Q-Element
- Bounded delay circuits
 - Huffman circuits / Burst mode circuits
 - Sequencing : the Q-Element
- Micropipeline circuits



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

46

Huffman/Burst-mode asynchronous circuits

 - The correctness depends on the gate/wire delays
- Based on the "bounded delay" model
- "Fundamental mode" assumption for the environment



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex



CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

47

Huffman/Burst-mode asynchronous circuits

- An example : The Q-Element

  


TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

48

Timing assumptions

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

49

Asynchronous circuit classes

- Hazard free logic
- QDI / Speed Independent Circuits
 - Data path : a simple OR Gate
 - Sequencing : the Q-Element
- Bounded delay circuits
 - Huffman circuits / Burst mode circuits
 - Sequencing : the Q-Element
- Micropipeline circuits



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

50

Micropipeline asynchronous circuits

- Micropipeline

 

- time is discrete
- combinatorial logic is simple
- communication channels
(handshake based)
- worst case approach locally

→ Local timing assumptions



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

51

Micropipeline asynchronous circuits

 - An example : function F
hazard free control logic + standard data path



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

52

Asynchronous circuit classes

- Conclusion
 - QDI / Speed Independent circuits are the most robust with respect to delays (isochronic fork for some/all wires)
 - Huffman & Burst-Mode circuits use the bounded delay model and require fundamental mode
- **QDI : Data-paths & Controllers**
- **Speed Independent / Burst-Mode : Controllers**
(burst-mode controllers are difficult to compose)
- **Micropipeline : Standard data-path + QDI/SI Controllers**



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

53

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties
- Design experiments and products
- Conclusion and prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

54

Design Methodologies and Tools

- Graph based (Petri-Nets)
 - Signal Transition Graphs
 - Burst-mode specification
- Language based (CSP based)
 - Tangram
 - CHP




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

55

 



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

56

Synthesis example : graph based

  


TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

57

Synthesis example : graph based

 

State graph

 


TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

58

Synthesis example : graph based

 

Synthesis example : graph based

 

Synthesis example : graph based

	A_{req}	A_{acq}		
B_{req}	00	01	11	10
B_{req}	00	0	0	-
B_{req}	01	0	0	0
B_{req}	11	-	1*	1
B_{req}	10	-	1	1

$/A_{req}, B_{acq}$

$A_{req}, /B_{acq}$



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

61

Synthesis example : graph based

	A_{req}	A_{acq}		
A_{acq}	00	01	11	10
B_{req}	00	0	1*	-
B_{req}	01	0	1*	-
B_{req}	11	-	1	1
B_{req}	10	-	1	0*

$not(B_{req})$

B_{req}



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

62

Synthesis example : graph based

Breq
Areq . Bacq => 1* => Breq ?
Areq . $\overline{\text{Bacq}}$ => 0* => Breq ?

 Aacq
 $\overline{\text{Breq}}$ => 1* => Aacq ?
 $\text{Breq} \Rightarrow 0^*$ => Aacq ?



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

63

Design Methodologies and Tools

- Graph based : Signal Transition Graphs

Tools :

- Petrify (Barcelona)
- Atacs (Utah) (VHDL entry)
- SIS (Berkeley)
- ASSASSIN (Imec)
- ...



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

64


Design Methodologies and Tools

- Graph based : Burst-Mode specification

 


Limitations :

- a) maximal set property

 

Ambiguous when X+

- b) Unique entry point

 

2 different input/output values
when entering state 6



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

65

Design Methodologies and Tools

- Graph based : Burst-Mode specification

 

Fundamental mode required



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex



CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

66

Design Methodologies and Tools

- Graph based : Burst-Mode
(Q-Element)

  

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

67

Design Methodologies and Tools

- Graph based : Burst-Mode Specification

Tools :

- Minimalist (Colombia University)
- 3D (USC San Diego)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

68

Design Methodologies and Tools

- Language based
 - CSP based (Communicating Sequential Processes)
 - CHP language (Caltech)
 - Synthesis is difficult => circuit designed can be very fast
 - Tangram language (Philips)
 - Tool suite (Synth., Sim., Test => circuit designed are slow)
 - Balsa language (Univ. of Manchester)
 - TAST (Tima)
 - HDLs : modeling/synthesis are not mature yet




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

69

Design Methodologies and Tools

 


TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

70

TAST*: TIMA ASYNCHRONOUS SYNTHESIS TOOLS

 


Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
- Design experiments
- Conclusion and prospects



Asynchronous Circuit Properties

 

- Data flow behavior/delay insensitivity :
=> distributed control
 - minimum execution time and power consumption
 - activity and power consumption are spread in time
 - modularity and composition : reusability, IP exchange



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

73

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
 - Systems design requirements
 - Modularity and locality
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Noise
 - Security
 - Automatic performance regulation
 - Dynamic voltage scaling
- Design experiments
- Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

74

Systems design requirements

 - Assemble / Reuse new and existing modules
- Modules with very different architectures
- Modules activity may be very different
- Modules with different speed/power trade-offs
- Flexible on-chip communication mechanisms
- Low power
- Mix digital and Analog modules



- Modularity and locality => reusability
 - Get rid of global constraints (like a unique global clock)
 - Avoid inheritance of constraints from block to block (like clock, noise, communication and synchronization mechanisms...)
 - Do not consume when not in use



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

75

Systems design requirements

- Modularity, Locality ...
- Need to Adopt
 - the right Hardware model and
 - the right Specification model

 Asynchronous Logic
and
Communicating Concurrent Processes



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

76

Asynchronous circuit properties

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
 - Systems design requirements
 - **Modularity and locality**
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Noise
 - Security
 - Automatic performance regulation
 - Dynamic voltage scaling
- Design experiments
- Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

77

Modularity and Locality

- Communication through channels (no clock)
 - Protocols are in charge of interfacing modules
=> the design of different modules is not inter-dependent
 - Design problems are solved locally inside each module
(architecture, speed, power, back-end issues...)
 - Building a complex architecture using modules implementing hands shake communication protocols is easy
 - Stand-by mode is free
 - Channels are used to trigger modules processing
 - Go from zero to maximum activity immediately, on request



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

78

Modularity and Locality

 - Speed and functionality issues are solved separately
 - Within a module
 - For inter-module communications



- Pipelining is preserving functional correctness in an asynchronous circuit
- => Performance optimization do not change the functionality



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

79

Modularity and Locality

- Circuit architecture

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

80

Modularity and Locality

- Thanks to asynchronous circuits
 - Provide a complete framework for jointly implementing communication channels and functions (hardware communicating processes)
 - Systems design is then easier :
 - Distributed control (protocol implementation)
 - Delay insensitive communications between modules
 - Modules are independent from each other in terms of :
 - Functionality (global state not known)
 - Speed (maximum speed)
 - Activity (power)
 - Noise (uncorrelated current consumption)
 - Scalability

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

81

Asynchronous circuit properties

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
 - Systems design requirements
 - Modularity and locality
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Noise
 - Security
 - Automatic performance regulation
 - Dynamic voltage scaling
- Design experiments
- Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

82

On-chip Communication Systems

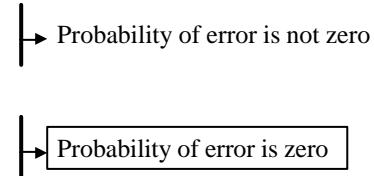- Multiple Clock Domains
 - Multiple Independent Clocks
=> Metastability may occur at clock domain boundaries
- Existing solutions
 - Control the Mean Time Between Failure (MTBF)
 - Non adaptive synchronization
 - Adaptive synchronization
 - Wait for metastability to resolve
 - Stretchable/stoppable clocks
 - Fully asynchronous (GALA)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

83

Metastability

- Phenomenon and related problems
 - Any system attempting to solve one of the following problems is of limited reliability (called a synchronizer) :
 - given an input signal and a time reference, decide whether the input signal makes a transition before or after the reference,
 - given an input signal and a voltage reference decide whether the input signal voltage is higher or lower than the reference.

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"



Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

84

Metastability

First case :

  - Asynchronous signal sampling : Synch
 - D and C are asynchronous
 - Set up and hold times may be violated
 - So what's the behavior ?
- Ordering events : ME
 - a and b are asynchronous signals
 - which signal is coming first ?
 - Sa and Sb are mutually exclusive



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex



CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 85

Metastability

Second case :

  - Signal comparison : Synch
 - “a” is an analog signal
 - is “a” below the threshold ?
 - how long does it take to decide ?
- Ordering signals : ME
 - “a” and “b” are analog signals
 - which signal is below the other ?
 - “Sa” and “Sb” are mutually exclusive



$$\begin{aligned} a > b \Rightarrow & Sa = 1, Sb = 0 \\ a < b \Rightarrow & Sa = 0, Sb = 1 \end{aligned}$$



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 86

Metastability

Where do these problems occur ?

- Analog circuits
 - Comparators
 - Analog to digital converters
 - Serial links
 - CDR (clock data recovery)
- Digital circuits
 - Processing asynchronous signals : interrupt signal
 - Communications between clock domains



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"




Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

87

Metastability

Metastability phenomenon

   - When I1 is opening and I2 is closing, we might have $A=B=V_m$ (set up and hold times violation)
- Inner loop levels are consistent and the system may stay in this state for an infinite time in theory !
- In practice, there are perturbations which force the system to go back to one of the stable states.



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"




Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

88

Metastability

Metastability phenomenon

   - When set up and hold times are satisfied $t_{DQ} = tp_{DQ}$ bounded !
- When set up and hold times are violated t_{DQ} increases !
- In practice t_{DQ} is finite but not bounded !!



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

89

Metastability

- Phenomenon model and characteristics

– Probability that the metastable state will last longer than t' decreases exponentially with t'



$$e^{-\frac{t'}{t_r}}$$

– Mean Time Between Failure (MTBF)

F_c : clock frequency

F_d : data transmission frequency
  
$$\frac{-t'}{t_r} e^{\frac{-t'}{t_r}} \frac{1}{T_W F_d F_c}$$



TW is a time window where the system may enter the metastable state (t_{DQ} increases)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

90

Metastability

- Phenomenon model and characteristics

Some figures

.13 micron, at 200 MHz
at 1 GHz

=> MTBF is 10^{400} seconds.
=> MTBF is 10^4 seconds (hours)

One can design a synchronizer with an MTBF longer than the life of the universe (10^{19} seconds). Is it useful ?

MTBF values depend on the applications, some hundred years is common !

Synchronizers design issues

- Trends: transistor length decreases, frequencies are increasing, synchronizers design is a key know how !
- Minimize latency and failure rate



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"



Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

91

Metastability

- Phenomenon model and characteristics

A simple synchronizer

  

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

92

Metastability

- Phenomenon model and characteristics

A mutual exclusion circuit

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

93

Controlling the MTBF

- How to improve the MTBF ?
 - Widening the data path
 - k times more wires
 - date rate divided by k
 - Limiting the critical control signal frequency
 - asynchronous FIFO
 - packet signaling => reduced frequency
 - Pipeline synchronization
 - adding synchronizer stages [Sezovic 94]
- Drawbacks :
 - Latency increased
 - Area and Power increased too

→ as a function
of MTBF



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

94

Controlling the MTBF

 - Adaptive synchronization [Ginosar 00]
 - compensate for the time-varying inter-modular clock and data phases
 - adaptation is achieved by :
 - a hardware “Adaptive Synchronizer” (A/S)
 - associated with a training session (Power-up, periodic, triggered, continuous adaptation schemes)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

95

Controlling the MTBF

- Adaptive synchronization [Ginosar 00]
 - Estimated overhead :
 - 1% area overhead for a 1 M tr. module with 10 input busses
 - 0.1 % time overhead for a typical training session
 - less than 0.001 % power overhead
 - Advantages
 - compensate skew and drift, adaptive
 - low latency (one half cycle)
 - Drawbacks
 - need of training sessions
 - adaptive synchronizer design



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

95

On-chip Communication Systems

- Multiple Clock Domains
 - Multiple Independent Clocks
=> Metastability may occur at clock domains boundaries
- Existing solutions
 - Control the Mean Time Between Failure (MTBF)
 - Non adaptive synchronization
 - Adaptive synchronization
 - Wait for metastability to resolve
 - Stretchable clocks
 - Fully asynchronous (GALA)

Probability of error is not zero

Probability of error is zero



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


97

Preventing Metastability

- Stretchable clocks [Chapiro 84...]
or Pausable/Stoppable clocks [Moore 00] [Muttersbach 00]
 - based on the use of asynchronous wrappers responsible for :
 - local clock generation
 - inter-module data communication management

Asynchronous module to
synchronous module interface.

 Two interfaces are required for
synchronous module to synchronous
module communications.



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

98

Preventing Metastability

- Stretchable clocks or Pausable/Stoppable clocks
 - Ring oscillator's frequency varies with temperature and supply voltage
→ a chip cannot work at a fixed frequency
 - if required, the real time clock must be a specific module
(or use of self calibrating clock [Moore 00])
 - Local clock buffering
 - Latency, complexity and power are all dependent on the number of channels (all processed by the same wrapper)
 - With large number of channels, conflict resolution may be long and even enter in a never-ending cyclical behavior.



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 99

Wait for Metastability to resolve

- GALA : fully asynchronous circuits
 - Modelling/Synthesis of arbitration problems [Renaudin 00]
 - from communicating processes to gates
 - requires two extra basic cells : ME and Sync
 - Safe and Fast
 - channels are independently processed
 - speed only depends of the complexity of the arbitration scheme
 - Low power
 - data driven
 - Area
 - no data buffering required
 - complexity depends on the asynchronous logic style used



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 100

Asynchronous circuit properties

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
 - Systems design requirements
 - Modularity and locality
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Noise
 - Security
 - Automatic performance regulation
 - Dynamic voltage scaling
- Design experiments
- Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 101

Asynchronous On-Chip Busses design

- Fully asynchronous circuits use DI codes which have nice properties for on-chip busses design
 - One-of-N (4-phase protocols / 2-phase protocols)
 - Low power
 - Cross-talk is reduced
 - Area is about the same
 - Speed is increased
 - Electrical buffering and pipelining at the same time
 - Safe, fast and low-power arbiters can be designed



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 102

Asynchronous On-Chip Busses design

- 1-of-4 DI code energy efficiency

	Wires/bit	Transitions/bit
single rail	1	1/2 on average
dual-rail 4-phase	2	2
dual-rail 2-phase	2	1
1-of-4 4-phase	2	1
1-of-4 2-phase	2	1/2

Same Wire/bit than dual-rail code but more energy efficient



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

103

Asynchronous On-Chip Busses design

- DI codes for cross-talk reduction

 

We know where cross-talk is likely to happen

Area overhead is small even if the number of wires is doubled

Acknowledge signals may be used as spacers



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

104

Asynchronous On-Chip Busses design

 - DI code for long wires routing
 - Repeaters perform electrical buffering and pipelining at the same time



- Safe, fast and low-power arbiters can be designed



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 105

Asynchronous circuit properties

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
 - Systems design requirements
 - Modularity and locality
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Noise and current shaping
 - Security
 - Automatic performance regulation
 - Dynamic voltage scaling
- Design experiments
- Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 106


Noise

Measurements performed with "MICA" an asynchronous QDI 8-bit microcontroller
Current profile (2000)



- **10 mA average current**
- **0.6 mA amplitude variations**

 Mean power consumption is lower
Smaller current peaks , EM emission is lower



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


107

Noise

 Measurements performed with "MICA" an asynchronous QDI 8-bit microcontroller
Current spectrum (2000)



0 to 12.5 GHz

 

0 to 0.5 GHz



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

108

Noise

 - Data Encryption Standard (DES) crypto-processors



Asynchronous DES Chip architecture




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

109

Results : DES Chip

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

110

Asynchronous circuit properties

- Asynchronous circuit design principles
 - Basic structures and asynchronous circuit classes
 - Design methodologies and tools
 - Asynchronous circuits properties and potentials
 - Systems design requirements
 - Modularity and locality
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Noise and **current shaping**
 - Security
 - Automatic performance regulation
 - Dynamic voltage scaling
- Design experiments
 - Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

111

Current shaping

 - Power aware scheduling (thèse de Dhanistha Panyasak)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

112


Power Aware Scheduling

 - By relaxing synchronization between blocks :



...use of low EMI advantage of Asynchronous Circuits !

- By scheduling events :

 

... spread spectrum of handshaking !



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

113

Power Aware Scheduling

RTL code
to
Asynchronous Circuits

Applying
scheduling
(FDS)

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

114

Asynchronous circuit properties

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
 - Systems design requirements
 - Modularity and locality
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Noise
 - **Security**
 - Automatic performance regulation
 - Dynamic voltage scaling
- Design experiments
- Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex




CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


115

Security

- Processor MICA

   

 - Number of points : 100000
- 10000 computations



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

116

Tamper-resistant hardware

 - Hardware cryptanalysis (measurements, post-processings)
- Counter measures design using ASL
 - PA
 - DFA
- Prototyping ASL
 - Asic : DES, AES
 - FPGAs
- Methodologies and CAD tools for improving PA and DFA chip resistance using ASL



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

117

Asynchronous circuit properties

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
 - Systems design requirements
 - Modularity and locality
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Noise
 - Security
 - **Automatic performance regulation**
 - Dynamic voltage scaling
- Design experiments
- Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


118

Self adapting performance

® Minimum energy computation

Processing and data have irregular natures (exploiting the dynamic)

 A breakdown with respect to the synchronous approach => algorithms must be different
(just in time processing)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex



CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

119

8-bit CISC Asynchronous Microcontroller : Vdd range

  - 1-of-4 DI codes for arith. and reg.
- 1-of-n DI codes for the control
- Complexity
 - 145 000 transistors, 0.25 µm STM
 - 1 M transistors with memories
 - 13 mm² with pads (prototype)
 - PGA120 package for the prototype
- Test
 - BIST (approx. 300 instr)
 - functional al 1^{er} silicium between 3v et 0.65 v
- 24 Mips / 28 mW @ 2.5V
- 4,3 Mips / 0.8 mW @ 1V



Supply(V)	Mips	Core Current (mA)	Power(mW)	Mips/Watt
1	4,3	0,8	0,8	5503,6
1,5	11,9	3,1	4,7	2560,2
2	18,6	6,7	13,3	1398,0
2,5	23,8	11,2	28,0	850,3
3	27,8	16,3	48,9	568,1
3,5	31,3	22,0	77,0	405,8




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

120

DES chip (HCMOS8) : Vdd range

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex




CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

121


Asynchronous AES crypto-processor

	CMOS 0.13 µm (HCMOS9) from STMicroelectronics 6-LM, Power Supply 1.2 volt					
Key length	Area (core)	Area with pads	Ciphering Time (ns)	Energy (nJ)	Throughput	
128-bit	0.49 (mm ²)	1.69 (mm ²)	910	10	141 Mbits/s	
192-bit			1.100	12	116 Mbits/s	
256-bit			1.440	14.2	89 Mbits/s	

   

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

 CIS group
"Concurrent Integrated Systems"




Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

122


Asynchronous AES crypto-processor

- Current profiles

Powered at 1.2 volt

 

Powered at 0.4 volt

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


123

Limited power budget

- Power supply controlled systems
- Processing power is limited by the power budget available

→ Maximum performance delivered with the available power received

 Applications :
remotely powered systems (RFIDs)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

124

Contactless Smart-Card Chip

- "SoC" for Contactless Smart-Card

 - Power reception system
(on-chip coil)
- ISO 14443-B std compliant
- 8-bit CISC Asynchronous
Microcontroller designed with
standard cells (Mica)
- Rom
- Rams



Collaboration with France Telecom/R&D
Cmos 0.25 µm STMicroelectronics
[IEEE-JSSC July 2001]



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

125

Asynchronous circuit properties

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
 - Systems design requirements
 - Modularity and locality
 - On-chip communication systems
 - Asynchronous on-chip busses design
 - Current consumption profile
 - Dynamic voltage scaling
- Design experiments
- Conclusion et prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


126

Voltage Scaling : sync. vs async. !

Synchronous

 

Clock-less

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin


127

Voltage Scaling Overheads !

Synchronous

 

Clock-less

 


TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

128

Voltage Scaling Overheads !

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

129

Asynchronous vs Synchronous : synchronous processor performance

- | StrongARM-1100
 - | 59MHz - 0.79V et 251MHz - 1.65V
 - | Un changement de fréquence prend 140µs
 - | Un changement de tension prend 40µs
 - | Mise en veille : 90µs - Réveil : 160 ms
- | lpARM (ARM8 Berkeley)
 - | 6Mips, 5MHz - 1.2V et 85Mips, 80MHz - 3.8V
 - | Un changement de fréquence de 5MHz à 80MHz prend environ 70µs
 - | Veille (idle) : 0.8mW
- | Transmeta Crusoe
 - | 300MHz - 1.2V à 600 MHZ - 1.6V
 - | Un changement de fréquence de f_{min} à f_{max} prend 300 µs
 - | pas de 33 MHz, 25 mV







TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

130

    Asynchronous vs Synchronous : standby mode







TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

131

    Asynchronous vs Synchronous : speed adaptation



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

132

Dynamic Voltage Scaling/Scheduling

- Benefits of an asynchronous processor :
 - No software to manage the processor or the peripherals activity (run, idle, sleep)
 - Consumption in sleep mode = consumption in idle mode (ratio higher than 100 for the synchronous processors)
 - Wake up/stop at very high frequency for the processor and the peripherals (thousands of cycles for a synchronous processor)
 - Speed and energy controlled by the voltage only (switching time much smaller : factor of 2 to 5)
 - Large voltage range (more and more critical with the supply voltage decreasing)

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

133

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
- Design experiments
 - Contact-less Smart Card
 - ASPRO RISC microprocessor
 - Towards fully asynchronous systems
- Conclusion and prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

134

Contactless Smart-Card Chip

- "SoC" for Contactless Smart-Card

 - Power reception system
(on-chip coil)
- ISO 14443-B std compliant
- 8-bit CISC Asynchronous Microcontroller designed with standard cells (Mica)
- Rom
- Rams



Collaboration with France Telecom/R&D
Cmos 0.25 µm STMicroelectronics
[IEEE-JSSC July 2001]



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

135

Mica : an 8-bit CISC QDI Asynchronous µC

 - 1-of-4 DI codes for arith. and reg.
- 1-of-n DI codes for the control
- Complexity
 - 145 000 transistors (0.25 µm)
 - 1 M transistors with memories
 - 13 mm² with pads (prototype)
 - PGA120 package for the prototype
- Test
 - BIST (approx. 300 instr)
 - functional at 1^{er} silicon between 3v et 0.65 v
- 24 Mips / 28 mW @ 2.5V
- 4,3 Mips / 800 µW @ 1V



Supply(V)	Mips	Core Current (mA)	Power(mW)	Mips/Watt
1	4,3	0,8	0,8	5503,6
1,5	11,9	3,1	4,7	2560,2
2	18,6	6,7	13,3	1398,0
2,5	23,8	11,2	28,0	850,3
3	27,8	16,3	48,9	568,1
3,5	31,3	22,0	77,0	405,8




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

136

MICA : Architecture

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

137

MICA : Instruction Set

Arithmetic/logic	Register Add, Addc, Sub, Subb, Inc, Dec, Neg And, Or, Xor, Not, Cbn (clear bit n), Sbn (set bit n), Tbn (test bit n) Rol, Ror, Rcl, Rcr (rotate without and with carry) Shl, Shr, Shrs (shift left, shift right unsigned and signed)
Index	Addx, Subx
Load/Store	Register Ld, Ldp, Stp (load, store peripheral), St Cp (copy from memory to memory is available) Pl (push & load) Psh, Pshsr (push, push status register) , Pop Index Pshx, Popx
Control flow	Rti, Rts, Jmp, Jsr Bcc, Bsrec (cc = a,eq,ne,cc,cs,l,le,lt,lte,g,ge,gt,gte,vc,vs)
Misc	Nop, Wfi, Eint, Dint (enable and disable interrupt)



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex


CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

138

Contactless Smart-Card Chip

 - Asynchronous Logic relaxed Design constraints
 - Not sensitive to supply voltage variations
→ Power reception system (capacitances area, voltage regulation)
 - Lower current peaks
→ The Micro-controller can be running during the communications without disturbing the load modulation.
 - Maximum processing power delivered according to the power received



Collaboration with France Telecom/R&D



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

139

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
- Design experiments
 - Contact-less Smart Card
 - ASPRO RISC microprocessor
 - Towards fully asynchronous systems
- Conclusion and prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

140

ASPRO : a RISC Microprocessor

- A QDI Asynchronous 16 Bit RISC Microprocessor

 => Performance
=> Standard-Cells
=> Ease of design (4 m.y)
 - Architecture
 (out of order completion)
 - System Board




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 141

ASPRO

 - QDI asynchronous logic
- Standard Cells
- 500 KTr for the core
- 6.3 MTr with memories
- Total area is 42 mm²
- CMOS 0.25µm 6 metal layers
STMicroelectronics
- Use of standard tools except
 - CHP2VHDL translator
 - Synthesis





TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 142

ASPRO

  - Functional at first silicon : 0.65V and 3.0V
- 140 MIPS (max)
- ASPRO includes DSP capabilities (MACC unit, brv...), RIF routine runs at 115 MIPS, 500 mW (including memories)
- Serial links (2 phase) : 50Mbit/s



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

143

ASPRO

Processor's main features

Memories

- program : 16 kwords on chip
48 kwords off chip
- data : 64 kbytes on chip

16 general purpose registers

On chip peripherals


- 2 parallel ports
- 4 bidirectional serial links (2F)

Custom units

- added to the peripheral area
- embedded in the data path

Three supply voltages

Interrupt mechanism

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

144

ASPRO

- **ASPRO's instruction set**

Alu instructions : std arithmetic, logic and shift/rotate

- min/max, bit reverse, slt/sltu (no status register)

Load/Store instructions : byte/word load and store

- basic addressing mode is indirect with displacement
- immediate load is provided (16 bit values)
- load relative address (relocatable code)
- program memory load/store through a dedicated register (boot)

Program flow instructions

- conditional relative branch (eq,ne,lt,ltu) => delayed or not
- djmp, dbsr, djsr => delayed

Custom instructions : 64 slots

- mpy, macc (integer, fixed point, rounding and saturation modes)
 $(16 \times 16) + 40 \Rightarrow 40$ bit



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"


Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 145

ASPRO : a RISC Microprocessor

- ASPRO
 - Flash memories
 - Reset/Interrut logic
 - Peripherals : 2φ Serial Links & Parallel Ports
- => A multi-processor system

Daughter board

Switches
&
LEDs

 

Mother board



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
- **Design experiments**
 - Contact-less Smart Card
 - ASPRO RISC microprocessor
 - Towards fully asynchronous systems
- Conclusion and prospects




TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 147

Towards Fully Asynchronous Smart Devices

 - Camera
 - Image processing
 - RF communication
- Integration on a single chip
 - Modular
 - Event driven
 - Low power
 - Low noise



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 148

Asynchronous Circuits Design

- Asynchronous circuit design principles
- Basic structures and asynchronous circuit classes
- Design methodologies and tools
- Asynchronous circuits properties and potentials
- Design experiments
- Conclusion and prospects



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 149

Conclusions et prospects

Delay insensitivity

- ? circuits are insensitive to IR drop phenomenon
- ? circuits are insensitive to PVT variations
- ? characterization efforts can strongly be reduced

This is a serious solution to « easily » and « rapidly » design IPs using advanced CMOS processes, 65nm, 42 nm ...



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 150

Asynchronous circuits in SoCs

Asynchronous communication systems

- flexible (clock, power)
- performance/cons.
- transport/synchronization

Logic functions embedded in analog blocks


- low noise/power.
- no clock

Power Management

- Voltage scaling (Vdd, Vt)

Soft asynchronous blocks

- power
- security
- noise

 

TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

151

Conclusion and Prospects

- High quality/complexity demonstrators exist
- Commercial products available
- Some new are coming (smart card)
- Companies (Handshake solutions, Theseus Logic, Fulcrum, Silistix, Achronix)

→ Strong need of efficient CAD Tools !

→ Asynchronous circuits testing is still a major issue !



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin

152

Links

- TIMA CIS group
<http://tima.imag.fr/cis/>
- Asynchronous bibliography :
<http://www.win.tue.nl/cs/pa/wsinap/async.html>
<http://www.cs.man.ac.uk/amulet>
- Tools :
<http://www.lsi.upc.es/~jordic/petrify>
http://www.cs.columbia.edu/async/minimalist/minimalist_homepage.html
<http://www.cs.man.ac.uk/amulet/projects/balsa>
<http://www.async.elen.utah.edu/>



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 153

Links

- Commercial circuits :
<http://www.sharpsdi.com>
<http://www-us.semiconductors.com/pip/PCA5007H>
<http://www-us.semiconductors.com/pip/PCA5010H>
- European "Asynchronous Circuit Design" Working Group :
<http://www.scism.sbu.ac.uk/ccsv/ACID-WG>



TIMA -CNRS-INPG-UJF
46 Av. Félix Viallet
38031 Grenoble Cedex

CIS group
"Concurrent Integrated Systems"

Ecole IN2P3 d'Electronique
28 Juin 2006, Roscoff
Marc Renaudin 154