

Embedded System Design

Dr. Hamid Vakilzadian

Guest Professor

Department of Informatics

University of Hamburg

Course Outline

- Review of FSM Design
- Review of ROM/PAL implementation
- Datapath Design
- Controller Design
- VHDL Description
- Design Using Altera FPGA (UP1 System)
- Codesign and virtual design
- Hardware/Software Partitioning

Review of FSM Design Process

Combinational Logic CKTs

Output(s) of these circuits that is a function of the present inputs.

Sequential CKTs

Output(s) of these circuits is a function of the current inputs and their past history. Memory elements are needed to store the past history. These circuits have feedbacks.

Basic Design Approach of Sequential CKTs (FSM)

Six Step Process

1. Understand the statement of the Specification
2. Obtain an abstract representation of the FSM
 - Using State Diagram or
 - Using ASM Chart
and **develop a Transition Table**
3. Perform a state minimization
4. Make state assignment
5. Choose FF types to implement FSM state register
6. Implement the FSM

Basic Design Approach

Example: Vending Machine FSM

General Machine Concept:


- Deliver a package of gum after 15 cents deposited
- Single coin slot for dimes, nickels
- No change

Step 1. Understand the problem:

Specification may not be complete:

Ex: What happens if penny is inserted or what happens after gum is delivered? Make reasonable assumptions!

Draw a picture!

 

Block Diagram

Vending Machine Example

Step 2. Map into more suitable abstract representation


Tabulate typical input sequences:

- three nickels
- nickel, dime
- dime, nickel
- two dimes
- two nickels, dime

Draw state diagram:


Inputs: N, D, reset

Output: open

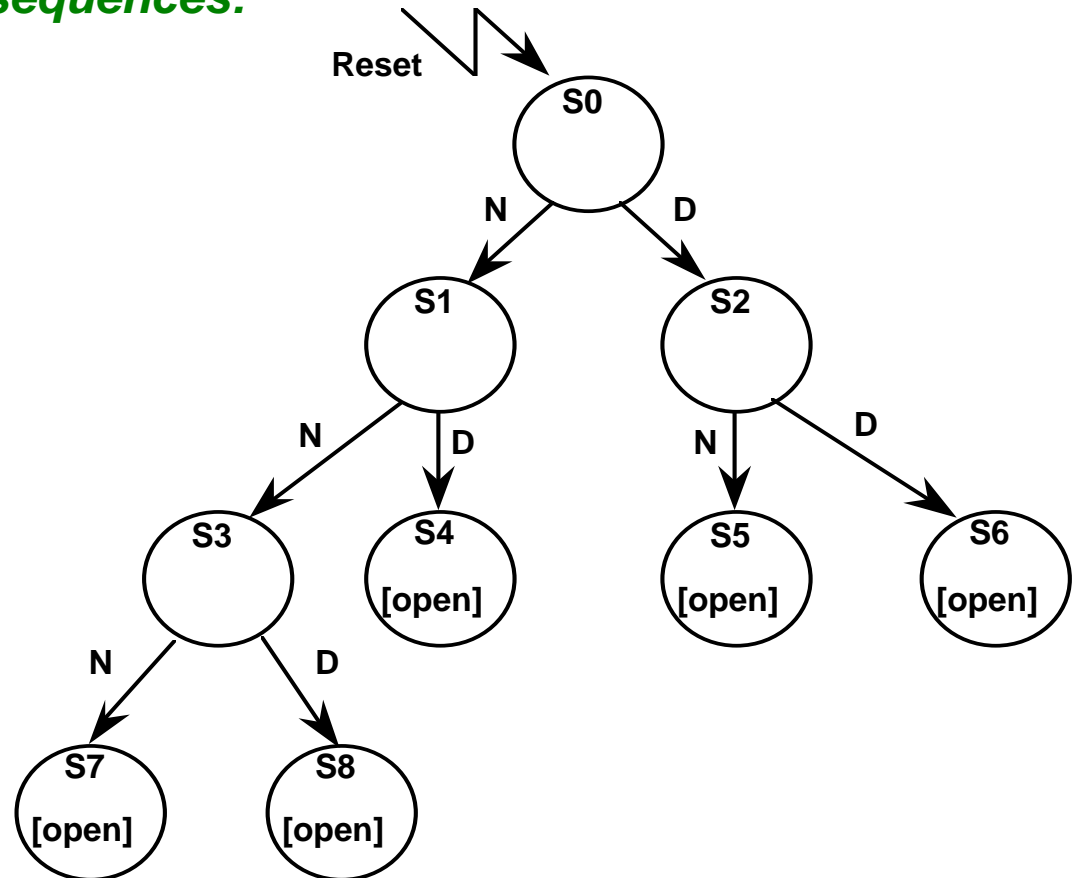


State Diagram Representation

Present State	DN				Output
	00	01	10	11	
S0	S0	S1	S2	X	0
S1	S1	S3	S4	X	0
S2	S2	S5	S6	X	0
S3	S3	S7	S8	X	0
S4	S4	X	X	X	1
S5	S5	X	X	X	1
S6	S6	X	X	X	1
S7	S7	X	X	X	1
S8	S8	X	X	X	1

 

State Transition Table

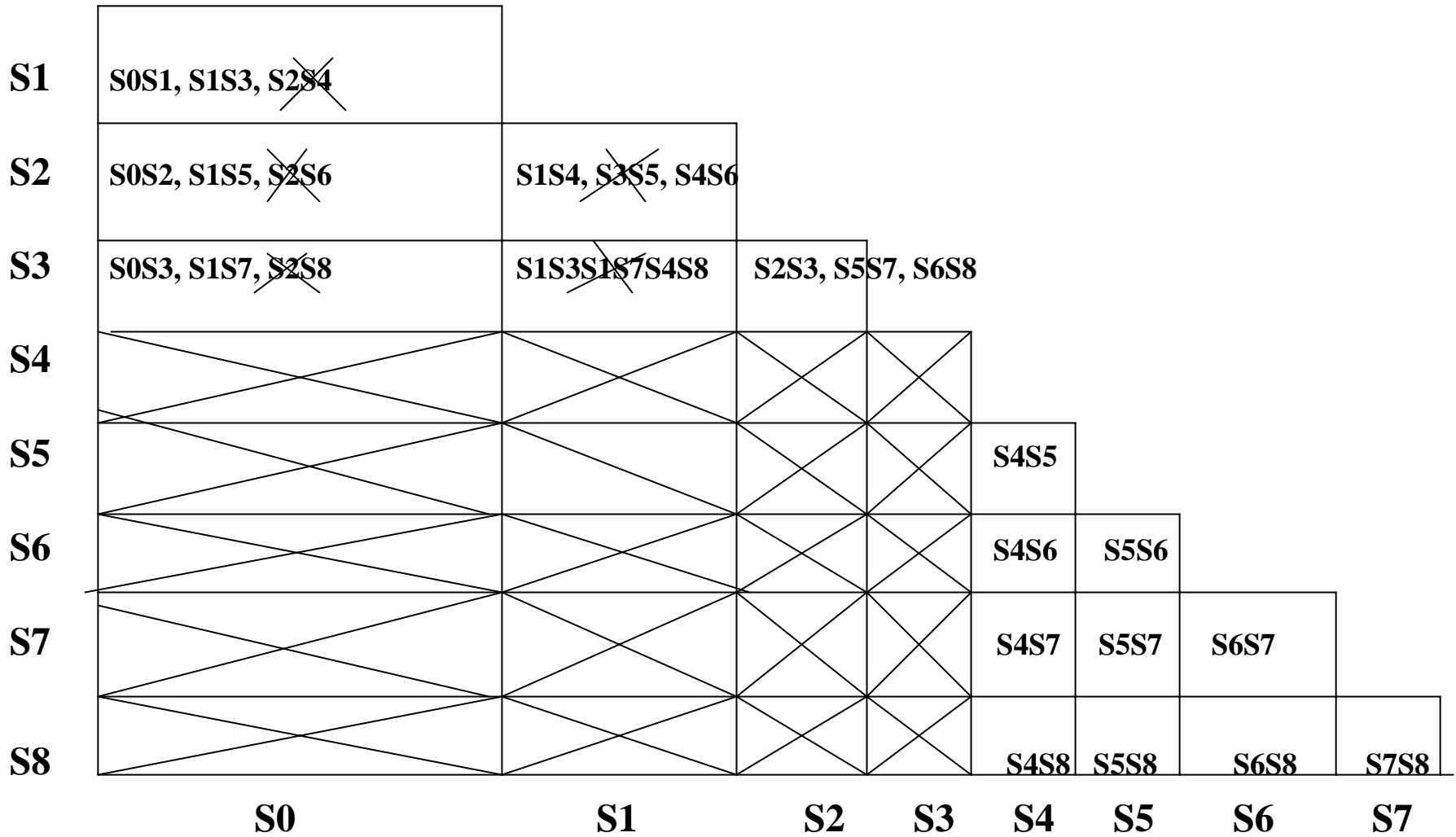

State Minimization

s0 s1 s2 s3 s4 s5 s6 s7 s8

s0 s1 s2 s3 s4 s5 s6 s7 s8

s1 s2 s3 s4 s5 s6 s7 s8


s2 s3 s3s4 s5 s6 s7 s8

s3 s4s5 s6 s7 s8

States needed: A=s0, B=s1, C=s2s3, D=s4s5s6s7s8

Vending Machine Example

Step 3: State Minimization

 

State Assignment

- **Rule 0** (Fundamental Mode CKTs Only!)
 - States which are connected on the flow graph must be adjacent or at least effectively adjacent.
- **Rule 1**
 - Under a given input condition, states which go to the same next state should be adjacent. Priority should be given to states having common next states for more number of inputs.

State Assignment

- **Rule 2**

- For each state, those states which are the “next state” entries for adjacent inputs should be adjacent

- **Rule 3**

- States with the same output class should be adjacent

State	00	01	11	10	Rule II
q0	q0	q5	x	q10	q0q5, q0q10
q5	q5	q10	x	q15	q5q10, q5q15
q10	q10	q15	x	q15	q10q15, q10q15
q15	q15	x	x	x	

Rule I					q5q10
--------	--	--	--	--	-------


	q0	0	1
q1			
0	q0	q5	
1	q10	q15	

State Encoding	
q1q0	
00	0 Cent
01	5 Cents
10	10 Cents
11	15 Cents

Vending Machine Example

Step 4: State Encoding

Present State		Inputs		Next State		Output
Q_1	Q_0	D	N	D_1	D_0	Open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	X	X	X
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	X	X	X
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	X	X	X
1	1	0	0	1	1	1
		0	1	1	1	1
		1	0	1	1	1
		1	1	X	X	X

 




Vending Machine Example

Step 5. Choosing FF for Implementation

D, J-K FF, T ?

Present State		Inputs		Next State		J ₁	K ₁	J ₀	K ₀
Q ₁	Q ₀	D	N	D ₁	D ₀				
0	0	0	0	0	0	0	X	0	X
		0	1	0	1	0	X	1	X
		1	0	1	0	1	X	0	X
		1	1	X	X	X	X	X	X
0	1	0	0	0	1	0	X	X	0
		0	1	1	0	1	X	X	1
		1	0	1	1	1	X	X	0
		1	1	X	X	X	X	X	X
1	0	0	0	1	0	X	0	0	X
		0	1	1	1	X	0	1	X
		1	0	1	1	X	0	1	X
		1	1	X	X	X	X	X	X
1	1	0	0	1	1	X	0	X	0
		0	1	1	1	X	0	X	0
		1	0	1	1	X	0	X	0
		1	1	X	X	X	X	X	X


Remapped encoded state transition table

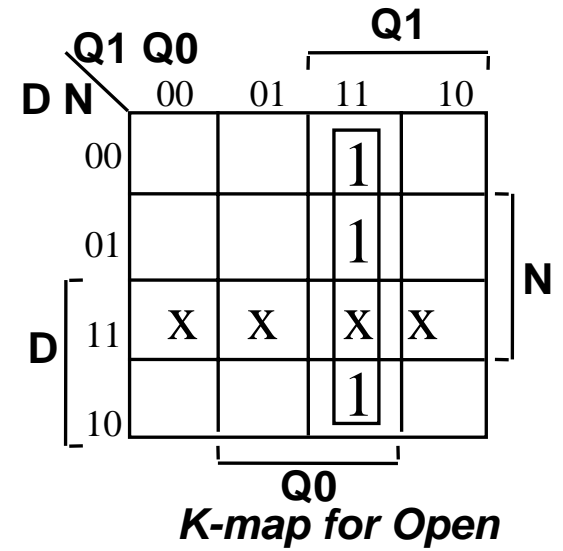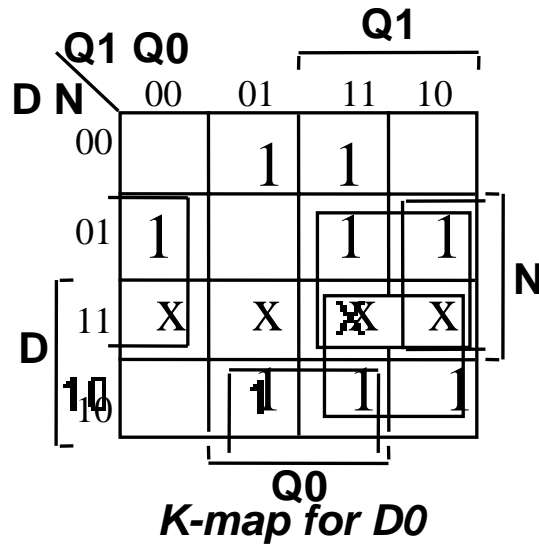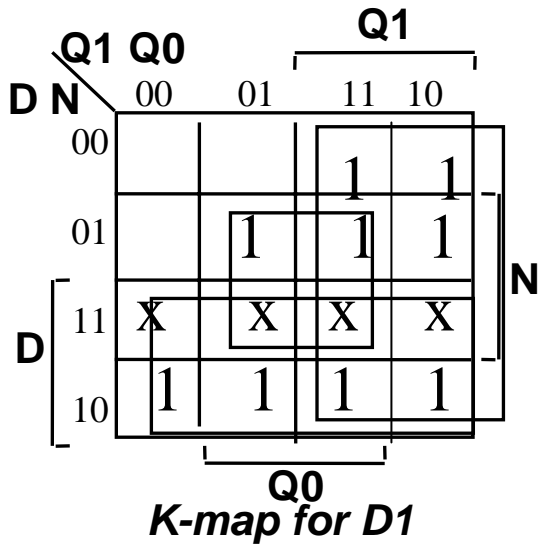


$$D1 = Q1 + D + Q0 N$$


$$D0 = N Q0 + Q0 N + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$

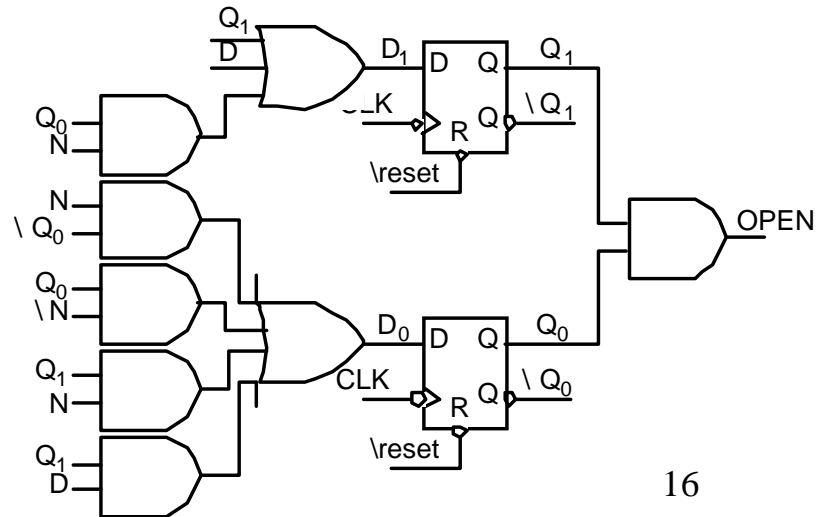


 


K-map for J1

 

K-map for K1

 

K-map for J0

 


K-map for K0

$$J1 = D + Q0 N$$


$$K1 = 0$$

$$J0 = Q0 N + Q1 D$$


$$K0 = Q1 N$$

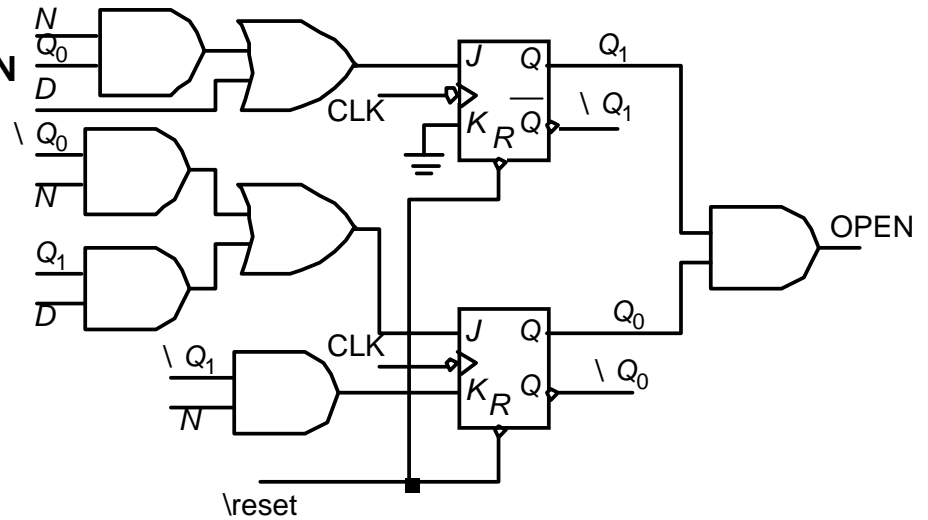

ROM Implementation

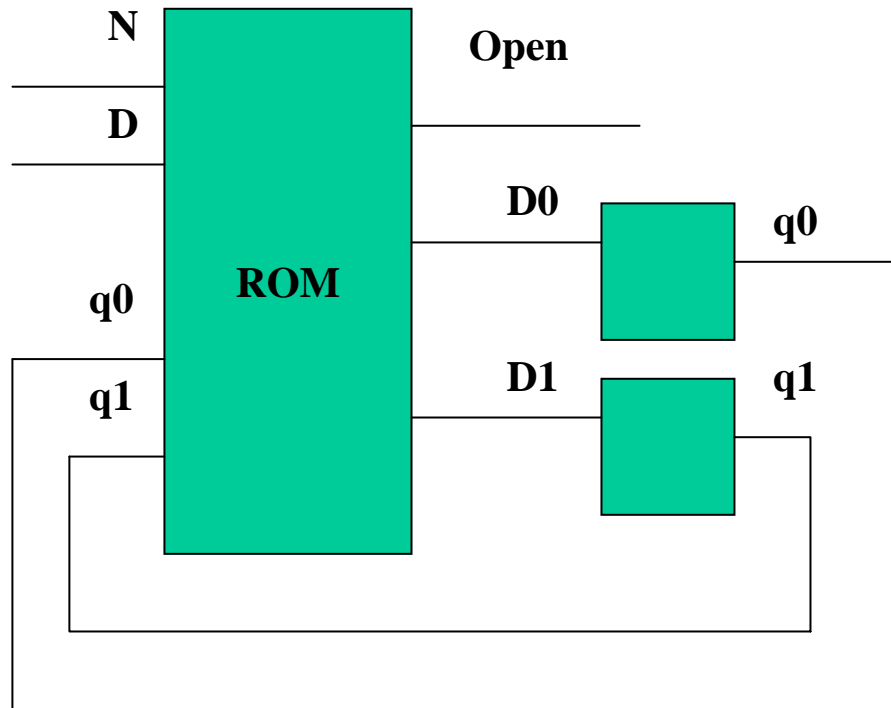

Present State		Inputs		Next State		Output
Q ₁	Q ₀	D	N	D ₁	D ₀	Open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	X	X	X
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
1	0	0	0	X	X	X
		0	1	1	0	0
		1	0	1	1	0
1	1	1	1	X	X	X
		0	0	1	1	1
		0	1	1	1	1
		1	0	1	1	1
1	1	1	1	X	X	X
		0	0	1	1	1
		0	1	1	1	1
		1	0	1	1	1
1	1	1	1	X	X	X
		0	0	1	1	1
		0	1	1	1	1
		1	0	1	1	1

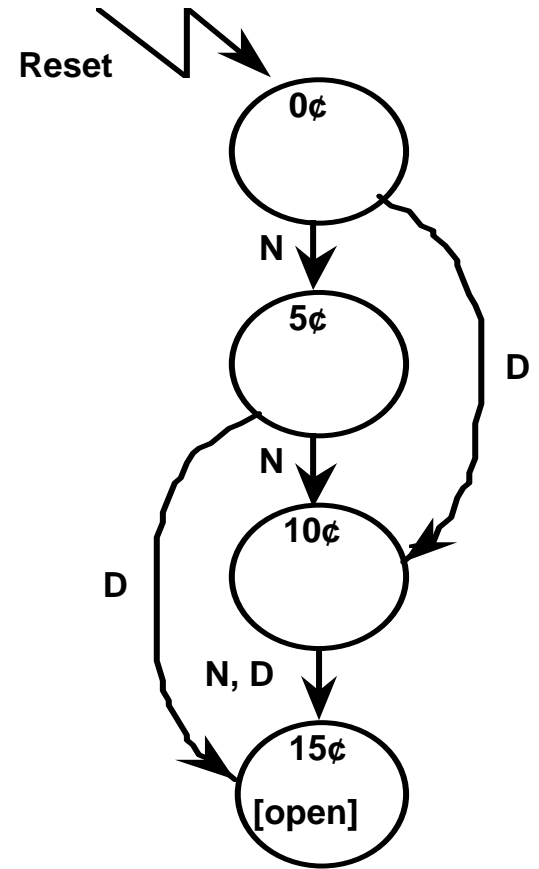

State Encoding

q1q0

00 0 Cent

01 5 Cents

10 10 Cents

11 15 Cents

Row	D ₁	D ₀	Open
0	0	0	0
1	0	1	0
2	1	0	0
3	0	0	0
4	0	1	0
5	1	0	0
6	1	1	0
7	0	0	0
8	1	0	0
9	1	1	0
10	1	1	0
11	0	0	0
12	1	1	1
13	1	1	1
14	1	1	1
15	0	0	0

ROM Contents,

ROM Size: 16 rows and 3 columns

ROM Realization doesn't need state assignment!

Module: Vending_machine;

INPUTS: D, N, Reset.

Outputs: Open

1. $\Rightarrow(D'N', D'N, DN', DN)/(1, 2, 3, 1)$ – Reset State
2. $\Rightarrow(D'N', D'N, DN', DN)/(2, 3, 4, 1)$ _ q5 State
3. $\Rightarrow(D'N', D'N, DN', DN)/(3, 4, 4, 1)$ _ q10 state
4. Open = 1 $\Rightarrow(1)$ _ q15 State

Endsequence

Controlreset(1).

End



ASM Notation

Condition Boxes:

Ordering has no effect on final outcome


Equivalent ASM charts:

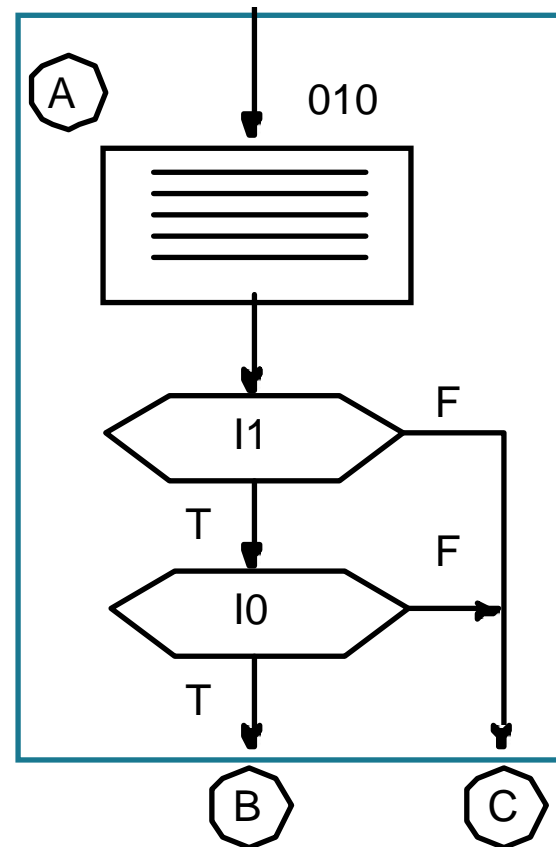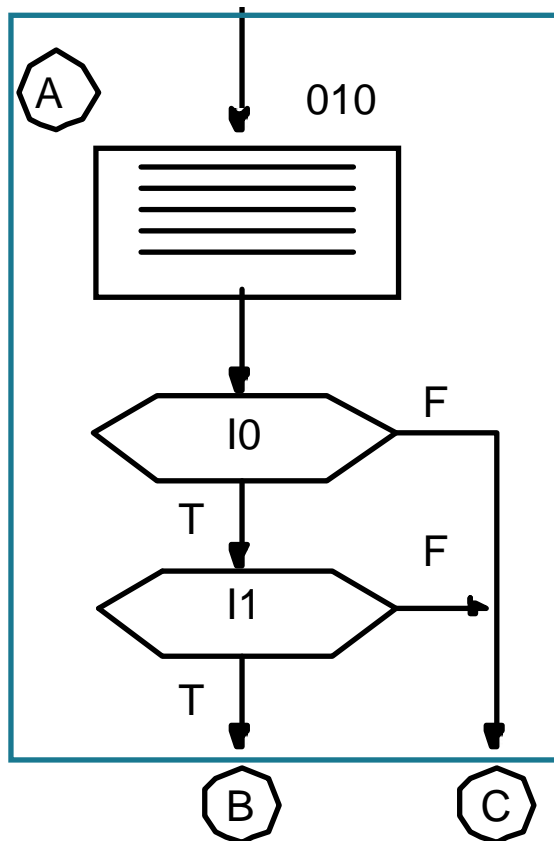A exits to B on $(I0 \bullet I1)$ else exit to C



Moore and Mealy Machines

Synchronous Mealy Machine

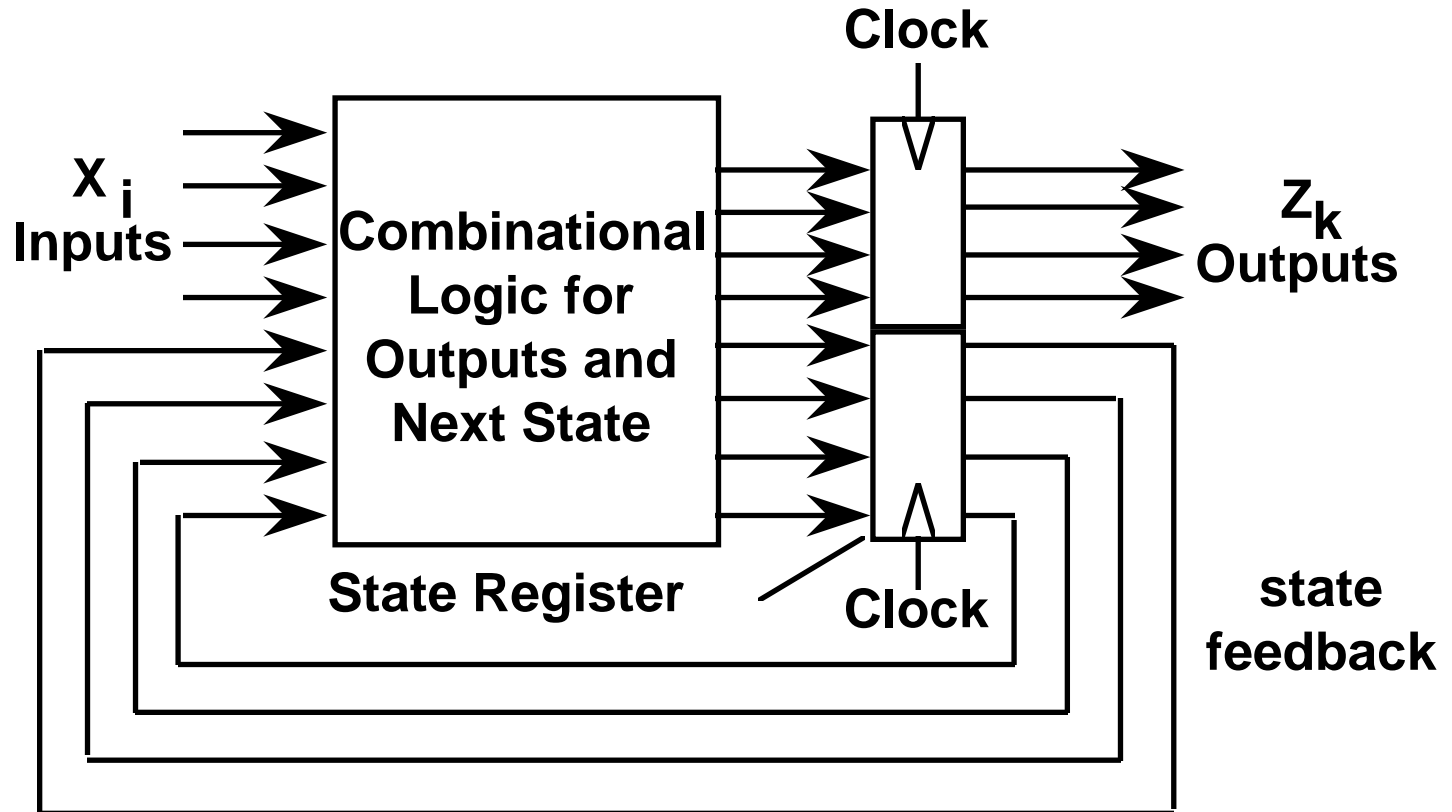

latched state AND outputs

avoids glitchy outputs!