


# **Some Fundamental Issues in Reversible Logic**

**Marek Perkowski**

**Lecture 3 continued**



# Classical vs. Quantum Circuits

Classical adder


 


# Classical vs. Quantum Circuits

Quantum adder

  

  Controlled-controlled  $\sigma_x$  is the same as Toffoli




Controlled  $\sigma_x$  is the same as Feynman

- Here we use Pauli rotations notation.
- Controlled  $\sigma_x$  is the same as controlled NOT

# Reversible Circuits
 
# Reversible Circuits


- Reversibility was studied around 1980 motivated by power minimization considerations
- Bennett, Toffoli et al. showed that any classical logic circuit  $C$  can be made reversible with modest overhead



# Reversible Circuits

- How to make a given  $f$  reversible
  - Suppose  $f: i \rightarrow f(i)$  has  $n$  inputs  $m$  outputs
  - Introduce  $n$  extra outputs and  $m$  extra inputs
  - Replace  $f$  by  $f_{\text{rev}}: i, j \rightarrow i, f(i) \oplus j$  where  $\oplus$  is XOR

- Example 1:  $f(a,b) = \text{AND}(a,b)$

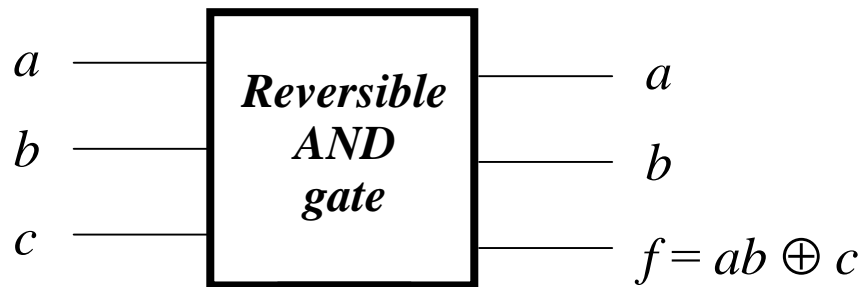


$a$	$b$	$c$	$a$	$b$	$f$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	1	1	0


- This is the well-known Toffoli gate, which realizes AND when  $c = 0$ , and NAND when  $c = 1$ .

# Reversible Circuits


- Reversible gate family [Toffoli 1980]

 

NOT

 


XOR/FAN-OUT

 

AND/NAND

(Toffoli gate)

 


generalized AND/NAND

- Every Boolean function has a reversible implementation using Toffoli gates.
- There is no universal reversible gate with fewer than three inputs
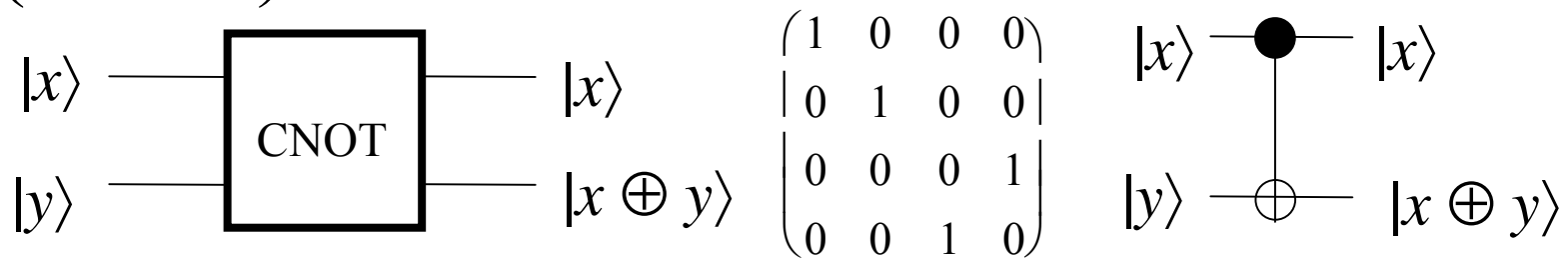
# Permutation Quantum Gates are reversible

- **Two-Input Gate: Controlled NOT (CNOT)**




- CNOT maps  $|x\rangle|0\rangle \rightarrow |x\rangle|x\rangle$  and  $|x\rangle|1\rangle \rightarrow |x\rangle|\text{NOT } x\rangle$


 
# Quantum Gates

- **3-Input gate: Controlled CNOT** (C<sup>2</sup>NOT or Toffoli gate)


$$\begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \end{pmatrix}$$


 
# Example

We calculate the Unitary Matrix  $U_2$  of the second block from left.

$$\begin{aligned}
 U_2 &= \text{CNOT}(x_1, x_2) \otimes I_1 \\
 &= \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix} \otimes \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{pmatrix}
 \end{aligned}$$



Unitary matrix of CNOT or Feynman gate with EXOR down


As we can check in the schematics, the Unitary Matrices  $U_2$  and  $U_4$  are the same

# Reversible Circuits


- **Implementing a Half Adder**

- *Problem:* Implement the classical functions  $sum = x_1 \oplus x_0$  and  $carry = x_1 x_0$


- **Generic design:**

 


# Reversible Circuits

 

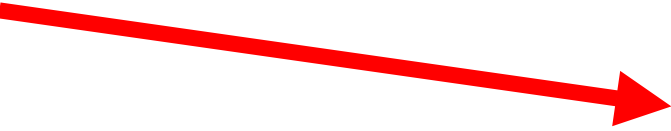- From equations we can find the following truth table




0000	0000
0001	0001
0010	0010
0011	0011
0100	0101
0101	0100
0110	0111
0111	0110
1000	1001
1001	1000
1010	1011
1011	1010
1100	1110
1101	1111
1110	1100
1111	1101

- This truth table can be rewritten to the following unitary matrix (remember that rows and columns of unitary matrix are enumerated starting from 0 on top and on left).
- NEXT SLIDE**
- 


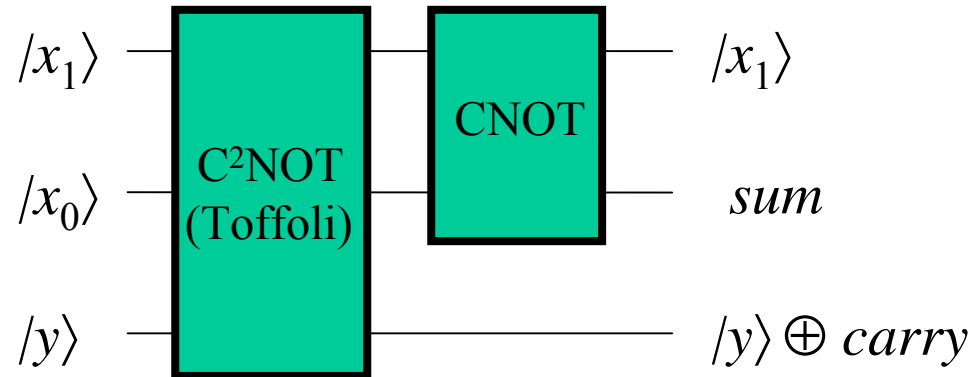
# Reversible Circuits

- **Half Adder.** Specific (reduced) design




# Agenda

- Introduction and history
- Reversible Logic and Reversible Gates
- Genetic algorithms
- The Model
- Simulation
- Conclusion

# Reversible gates...


Feynman, Toffoli, Fredkin, ...

 

Mapping of I/O allows  
unique  $(P, Q) \Rightarrow (A, B)$




 
## and Reversible Circuits

- To reduce the RL synthesis limitations one can insert constants in order to modify the functionality






# Generalized Reversible Gates

    

# Perkowski gates family

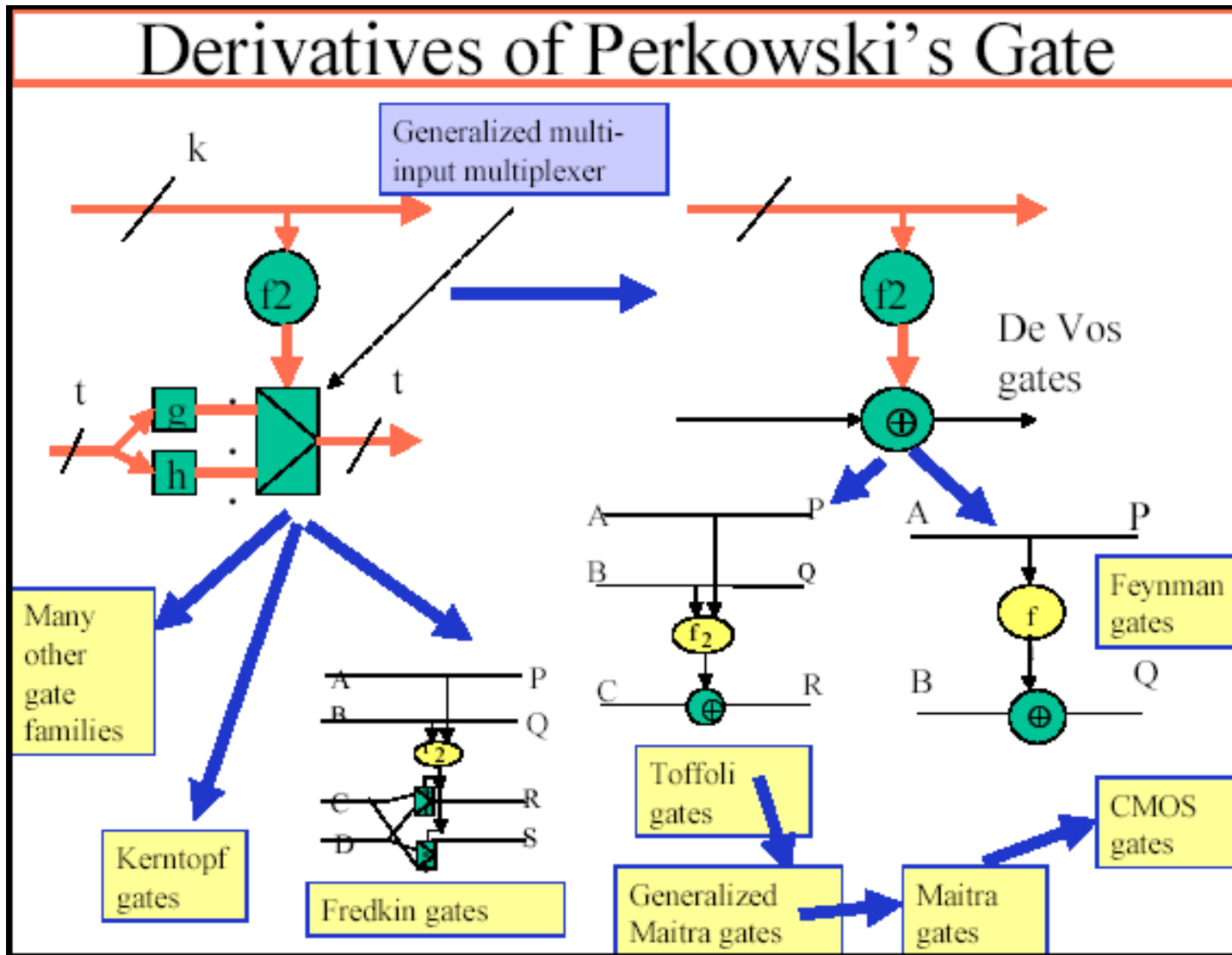

# Cascades

- *Mixed data/control inputs (generalized complex control gates)*
- *All :*
  - ESOP
  - Factorized-ESOP
  - MV Complex Terms
  - XOR family

**Last slide of lecture 3**

■ Example:

