 
 

Lecture 18

BUS and MEMORY

Slides of Adam Postula used



SIGNAL PROPAGATION

FROM ONE SOURCE TO MANY SINKS




SIGNAL PROPAGATION

FROM ONE SOURCE TO MANY SINKS

  


SIGNAL PROPAGATION

FROM MANY SOURCES TO ONE SINK

 


SIGNAL PROPAGATION

FROM MANY SOURCES TO ONE SINK

 


FROM MANY SOURCES TO MANY SINKS

 


TriState Buffer Concept

Switch model of a multiplexer

 


TriState Buffer Concept

Switch model of a multiplexer

 


 TRISTATE buffer signal drivers - a DISTRIBUTED MULTIPLEXER




TriState Buffer

SYMBOLS

 

SWITCH MODEL

 


OE	in	out
0	0	Z
0	1	Z
1	0	0
1	1	1


Z = High Impedance
output not
connected to
input

TriState Buffer

SYMBOLS

 


SWITCH MODEL

 


TriState Buffer


SYMBOLS

 

SWITCH MODEL

 


CMOS IMPLEMENTATION

 


UNIDIRECTIONAL BUS LINE

 Propagation from many sources to many sinks




UNIDIRECTIONAL BUS LINE

 
Propagation from many sources to many sinks




UNIDIRECTIONAL BUS LINE

 


BIDIRECTIONAL BUS LINE

 

BIDIRECTIONAL BUS LINE

 



WIRED LOGIC

 


TRANSISTORS WORK AS INVERTERS

OPEN COLLECTORS NEED PULL_UP RESISTORS

WIRED LOGIC

  


WIRED LOGIC BUS

 


sel1	sig1	F1
0	0	1
0	1	1
1	0	1
1	1	0


REGISTER FILE

 

REGISTER FILE

 


REGISTER FILE

 


REGISTER FILE

word select

 


MEMORY ELEMENTS

 


THE BASIC ELEMENT IS A STATIC LATCH THAT HOLDS THE STORED VALUE AS LONG THE POWER IS ON.

MEMORY ELEMENTS

 

MEMORY ARRAY

 

RAM - Random Access Memory

- ◆ Each word in the RAM memory can be read by giving its address and observing the data lines after some time.
- ◆ Each word can be re-written by giving its address, presenting the new data and keeping it stable for some time.
- ◆ Addressing can be random (there are no requirements for any sequence in addresses) - hence Random Access Memory.
- ◆ Storage matrix is usually very large and organized as a square matrix of word cells.

What have we learnt?

- ◆ TriState buffers allow to connect many signal sources to the same signal line. Wired logic can provide the same functionality although is less popular.
- ◆ Flip-flops can be organized in registers, registers in register files.
- ◆ RAM - Random Access Memory allows to read/write data at a randomly chosen address.