

Lattice Diagrams using Reed-Muller Logic

2002.10.15

Shim, Hee Jun

Introduction


- To realize arbitrary Boolean functions in a regular and planar layout
 - Universal Akers Array (UAA)
- This paper presents an extension of UAAs, called “Lattice Diagrams” and the efficient method of mapping arbitrary multi-output functions.

- Lattice Diagram

- Data structures that describe both regular geometry of connections and a logic of a circuit.

- Expansion type

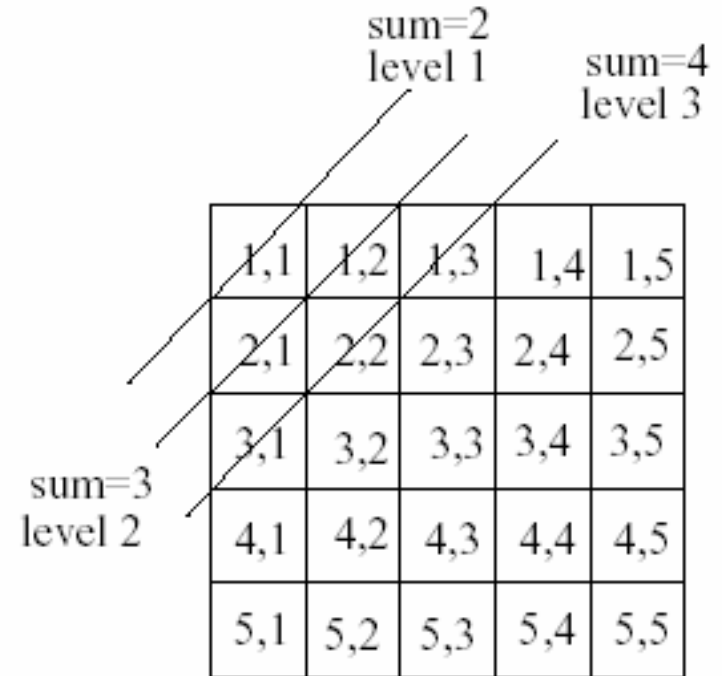- Shannon : $F = a \cdot F_a @ a' \cdot F_{a'}$
 - Positive Davio (pD)
 - : $F = a(F_a @ F_{a'}) @ 1 \cdot F_{a'}$
 - Negative Davio (nD)
 - : $F = 1 \cdot F_a @ a'(F_a @ F_{a'})$



- Array to explain Lattice concepts
- Each block means a function.






Classification of Lattice Diagram

- Order
 - Ordered \sim : one variable on a diagonal (=level)
 - Ordered \sim with Repeated Variables : one variable in a level, but the same variable may appear on various levels.
 - Free \sim : different orders of variables in the paths leading from leafs to the root
 - Folded \sim : Free \sim , but the order of variables in levels must be the same, with some variables possibly missing.
- Expansion
 - All expansions are of the same type.
 - Shannon \sim : Shannon
 - Functional \sim : pD.
 - Negative Functional \sim : nD.
 - All expansions in every level are of the same type.
 - Reed-Muller \sim : pD, nD.
 - Kronecker \sim : Shannon, pD, nD.
 - All expansions in every level are either of some expansion types.
 - Pseudo Reed-Muller \sim : pD, nD
 - Pseudo S/pD \sim : Shannon, pD
 - Pseudo S/nD \sim : Shannon, nD
 - Pseudo Kronecker \sim : Shannon, pD, nD


Joining Rule

- $R = 1 \cdot x @ b (by @ b'z)$
 $= 1 \cdot x @ by$

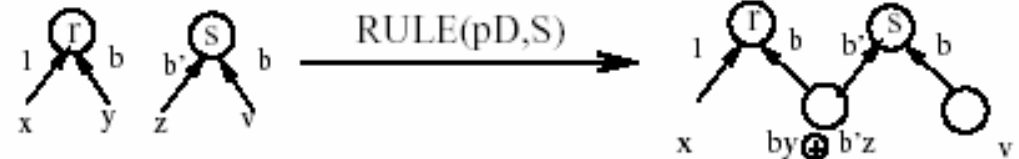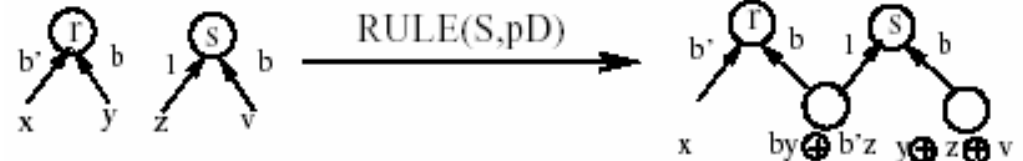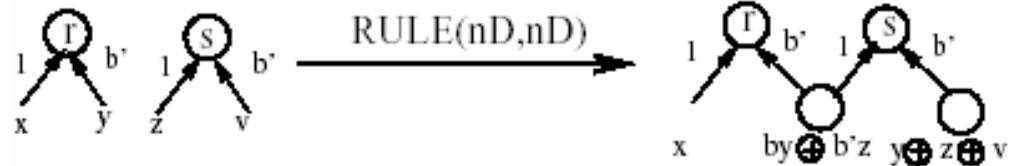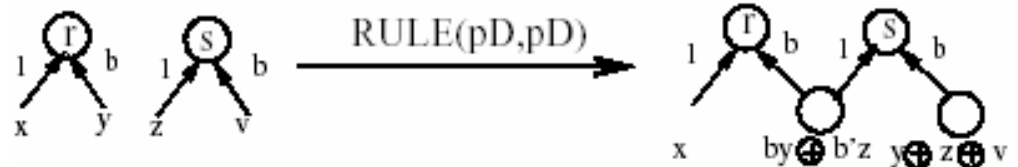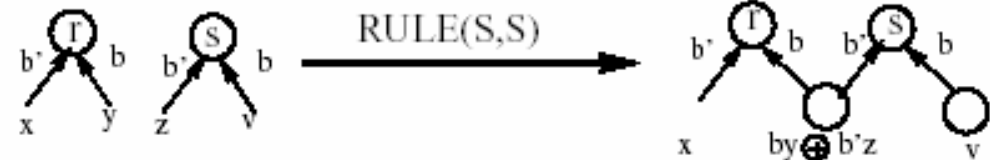- $S = 1 \cdot (by @ b'z) @$
 $b \cdot (y @ z @ v)$
 $= (by @ by) @$
 $z (b' @ b) @$
 bv
 $= 0 @ (z \cdot 1) @ bv$
 $= 1 \cdot z @ bv$





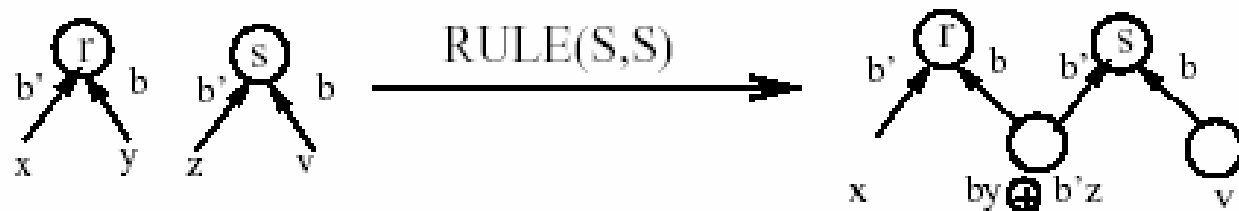- Ordered Shannon Lattice Diagram (OSLD)
 - It is expanded level-by-level, starting from the root level, and from left to right in every level.
 - In contrast to standard BDDs, the joining operation combines also non-isomorphic nodes of trees.
 - Shannon Expansion: $F = a \cdot F_a @ a' \cdot F_{a'}$
 - Joining Rule




Example 1 Single-output OSLD

Level

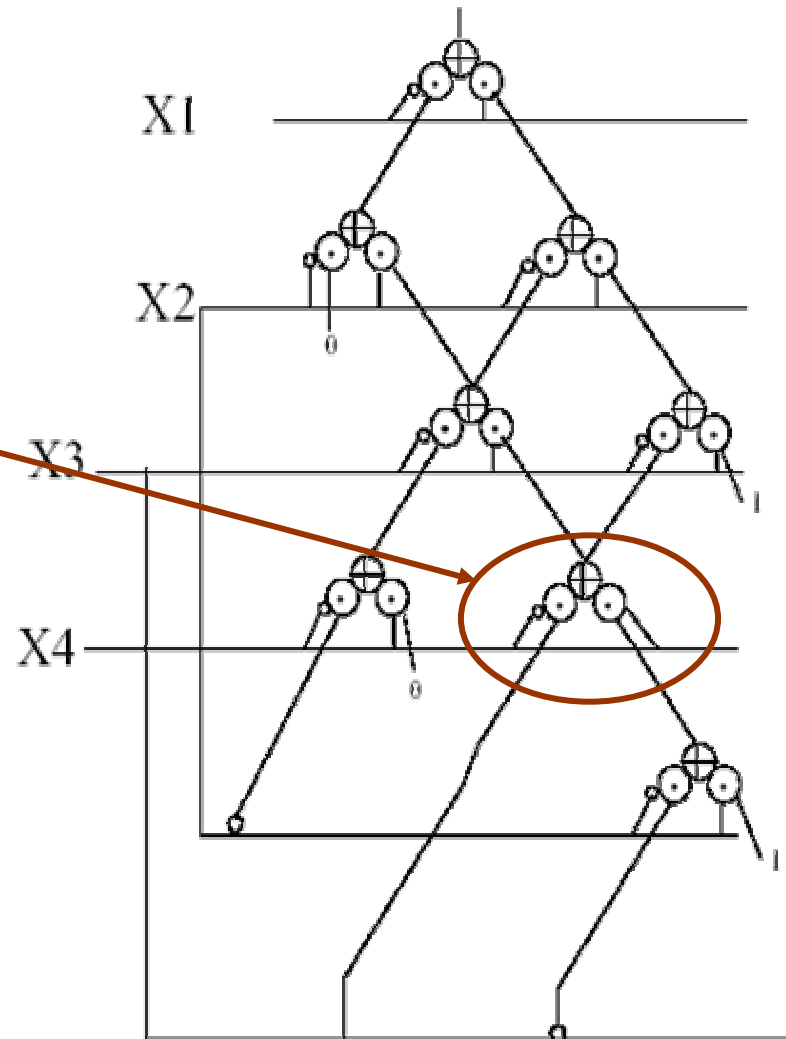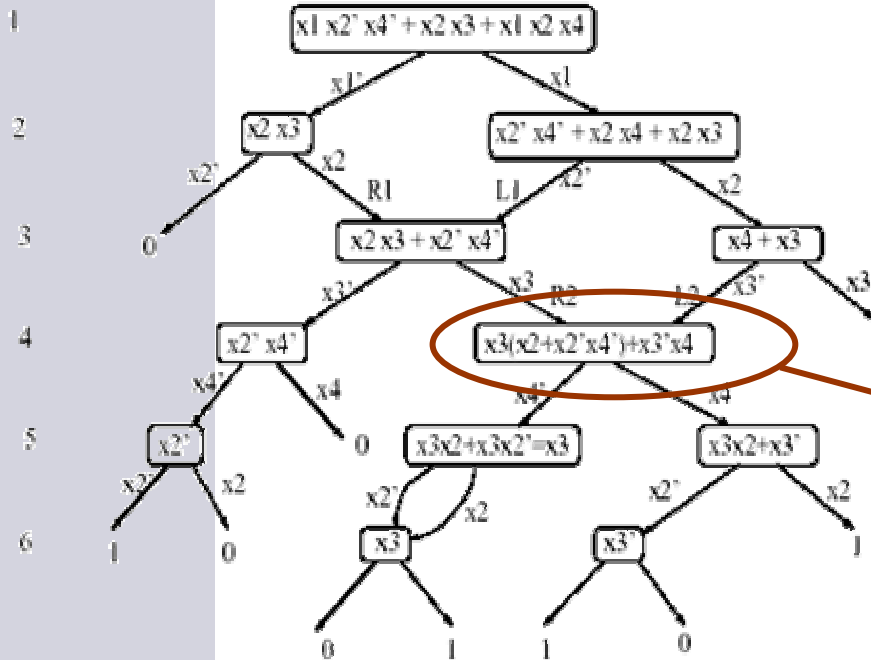


Method of Creating Lattice Diagram

Example 2 Multi-output OSLD


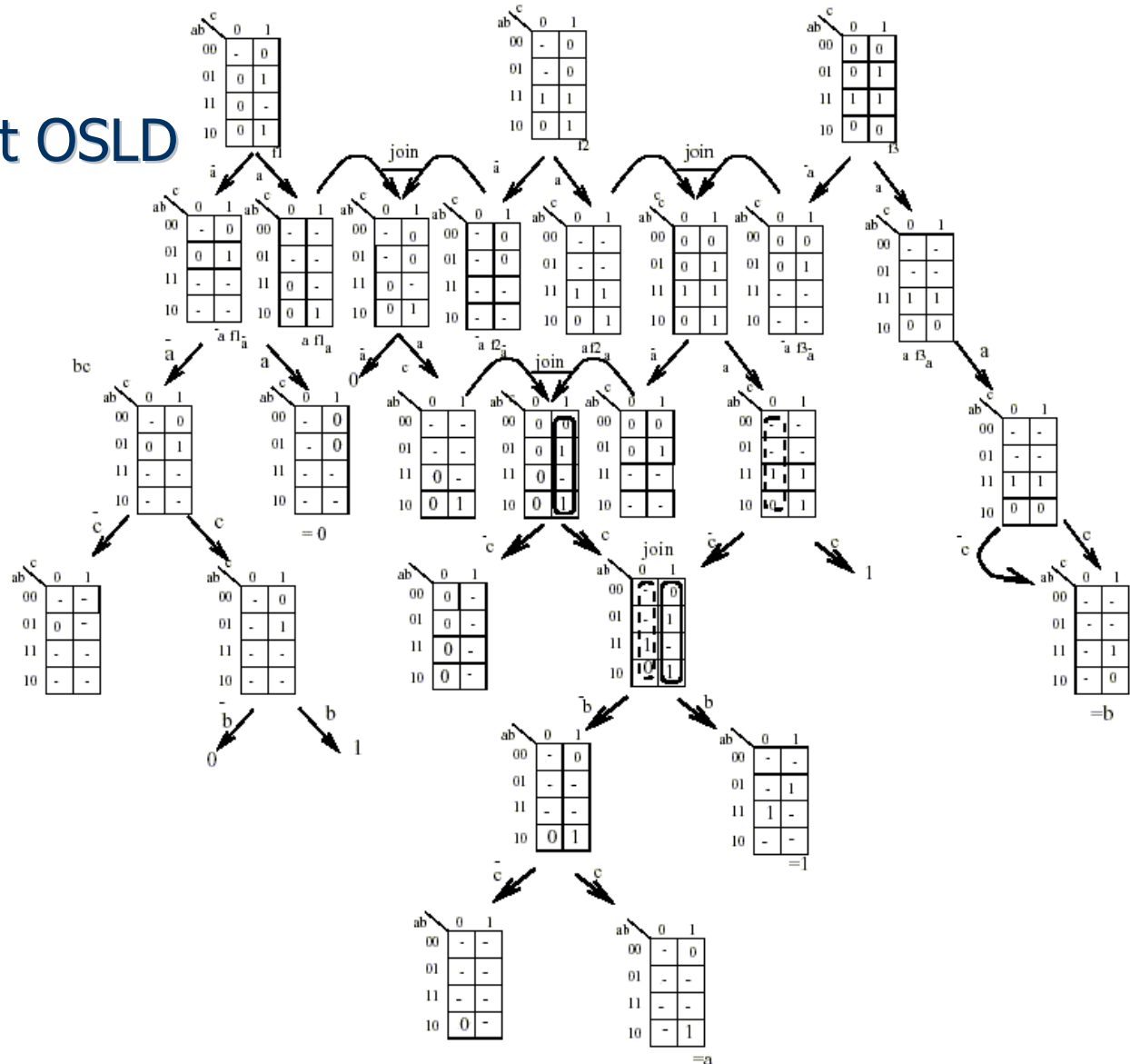


Method of Creating Lattice Diagram

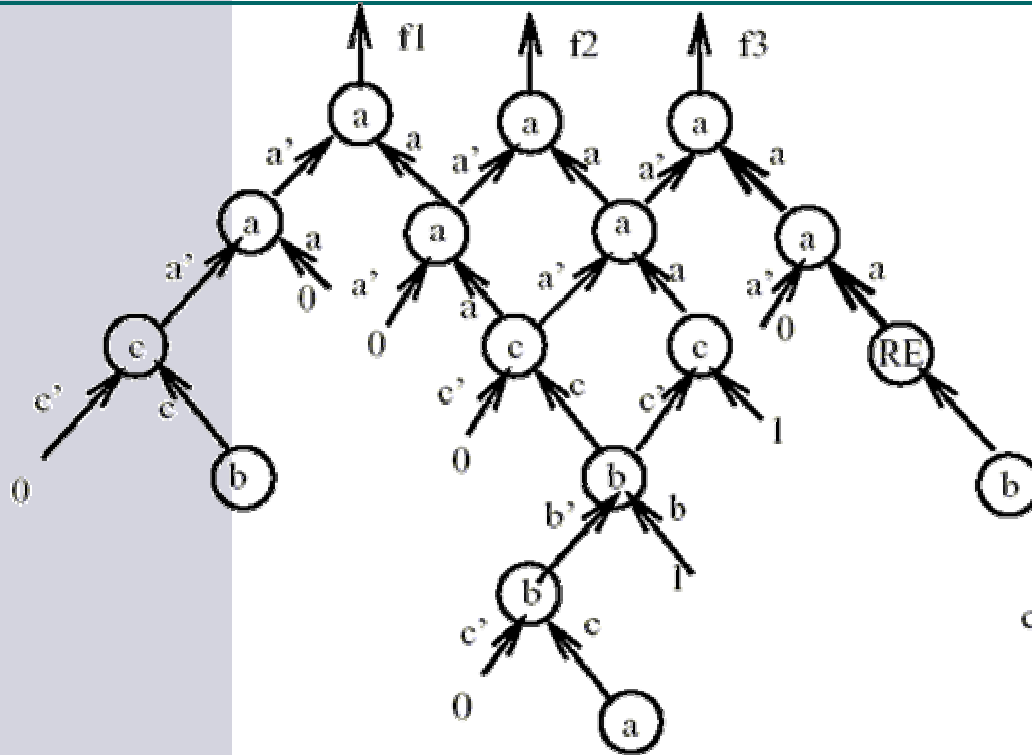

Multi-output OSLD

Folded SLD

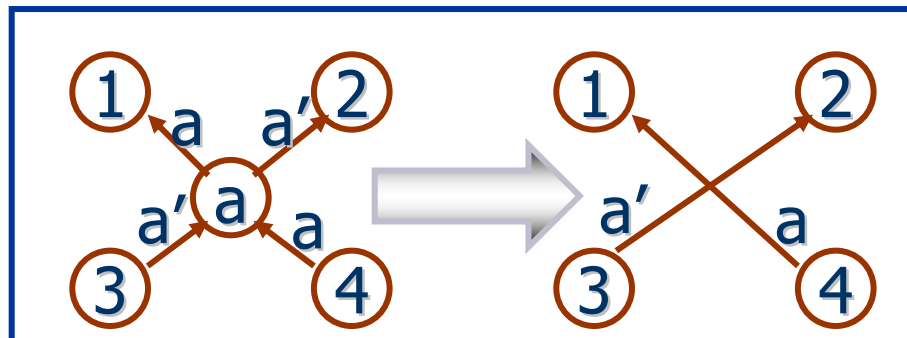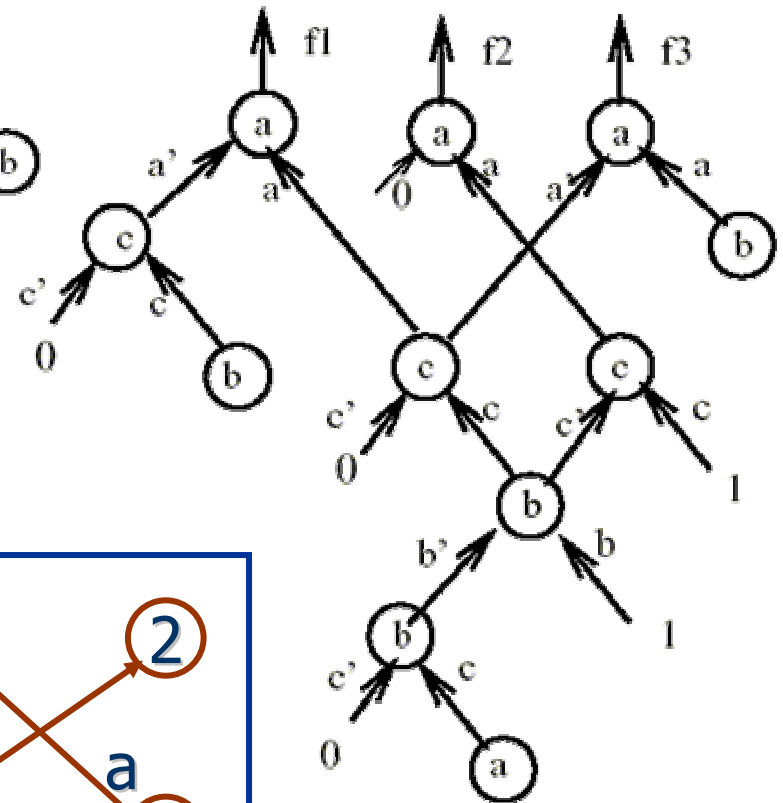


Method of Creating Lattice Diagram

- Functional Lattice Diagram

- It is like for OSLD.
- Positive Davio expansions are used instead of Shannon and the (pD,pD) joining rules instead of the (S,S) joining rules.

- Positive Davio (pD) : $F = 1 \cdot F_a' @ a(F_a' @ F_a)$

- Joining Rule (pD, pD) :

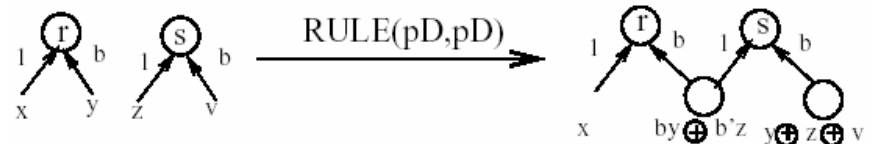

1@ad@bd@abd



1

(1)@(1@a@b@ab) = a@b@ab

a@b

a@b@d@bd



(a@b)@(a@1) = b@1

$d(a@b@ab) @ d'(a@b) =$
 $a(d@d')@b(d@d')@abd = a@b@abd$

$a@b@ab @ a@b @ b@1$
 $= ab@b@1$


Method of Creating Lattice Diagram

- Ordered Kronecker Lattice Diagrams (OKLD)

- It uses the joining rules, (S,S), (pD,pD), (nD, nD) because all expansions in every level are of the same type.

- Folded Kronecker Lattice Diagram

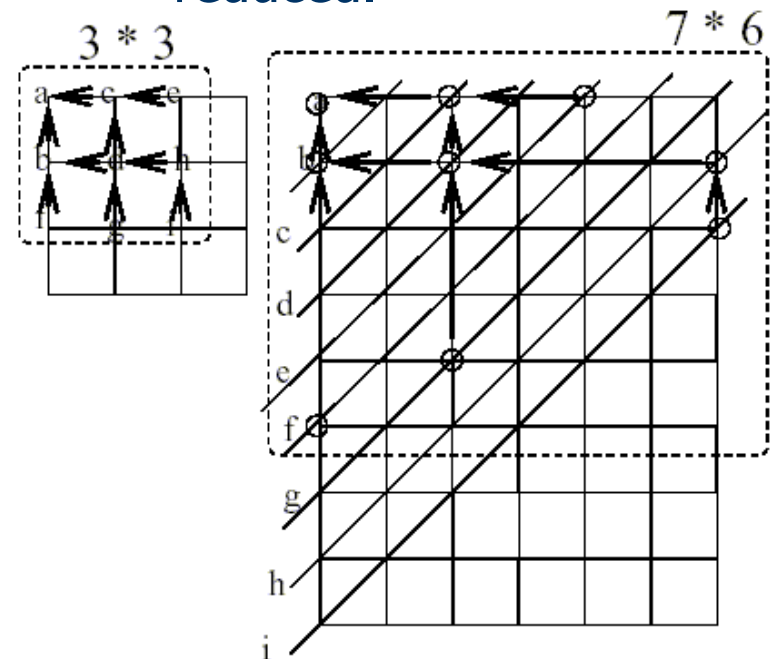- The rectangular envelope area has been reduced.



- Pseudo-Kronecker Lattice Diagram
 - Pseudo S/pD Kronecker Lattice Diagram can be solved. (only mixture of S and pD nodes in a level)
 - But, Joining rules cannot be created for combinations of expansion nodes (pD,nD) and (nD,S)
 - Open problem whether creating of Pseudo-Kronecker Lattice Diagrams for (S,pD,nD) can be solved analogously to the previous method.

Conclusion

- Introduce method of creating various type of lattice diagram by combining together non-isomorphic nodes at the same level.
- There is no constraint on repeating variables consecutively.
- Use any subset of S , pD , and nD expansions.
- Support arbitrary multi-output functions.