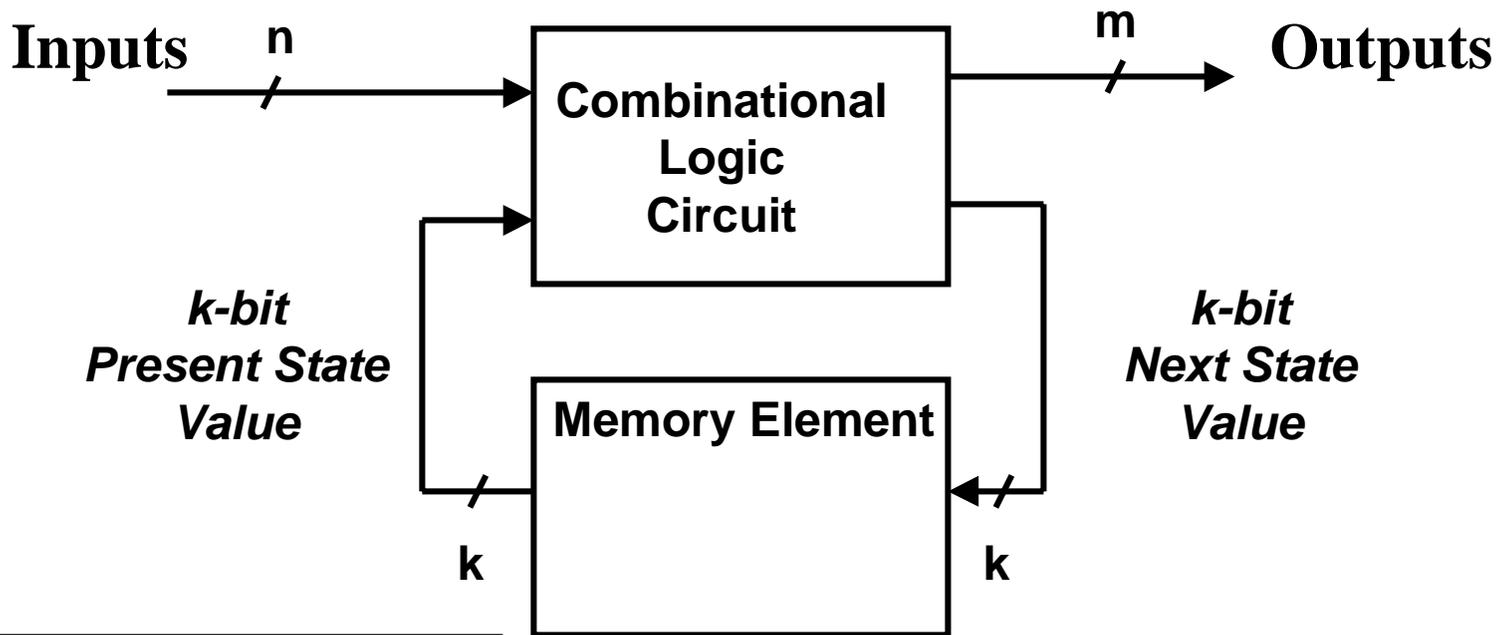


# General Sequential Design



So far we have, we have looked at basic latches, FFs and common sequential building blocks.

**All of these** can be represented by a general block diagram:



Slides from Bob  
Reese

Combinational Logic

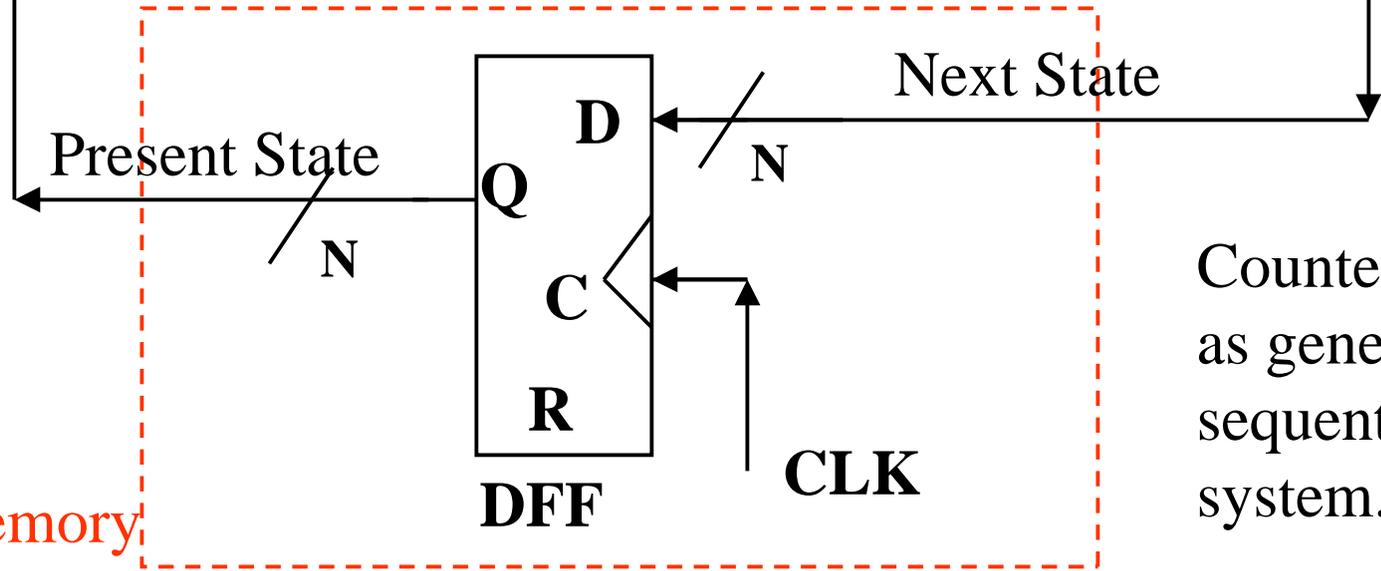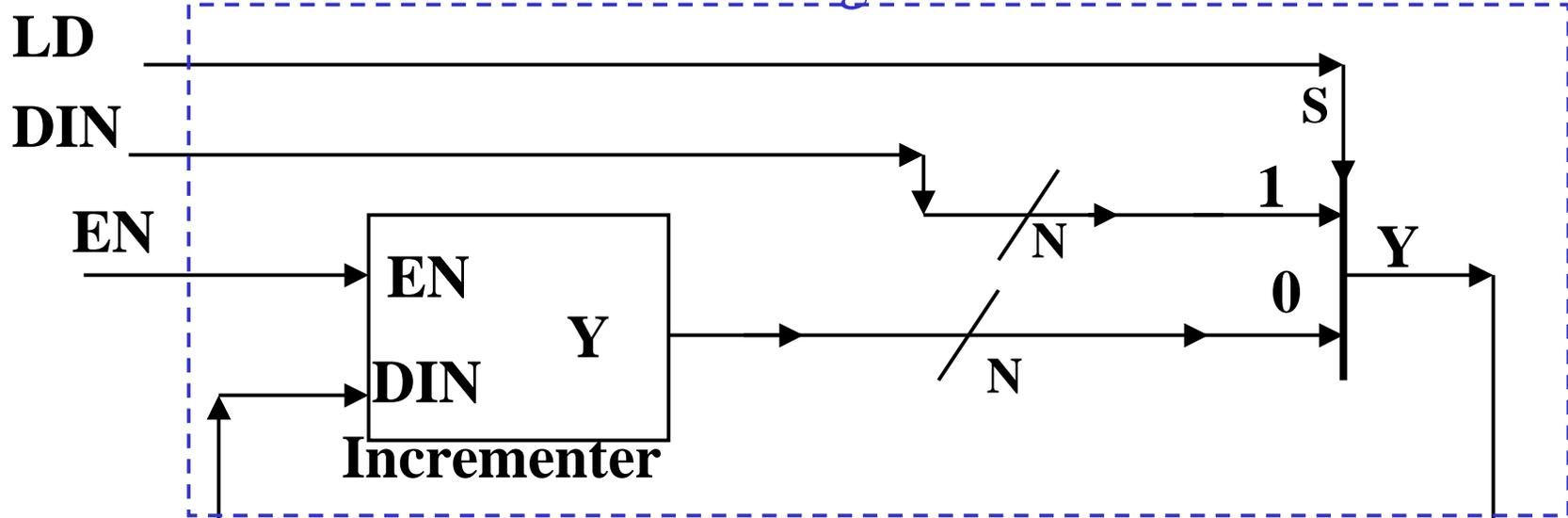

Counter drawn as general sequential system.

Memory


# Describing Sequential Systems

- So far we have used Truth Tables to describe sequential systems
- Can also use Bubble Diagrams and Algorithmic State Machine Charts (ASM) to describe a sequential system.
- Another name for a sequential system is a *Finite State Machine* (FSM).
- A sequential system with N flip-Flop has  $2^N$  possible states, so the number of possible states is FINITE.
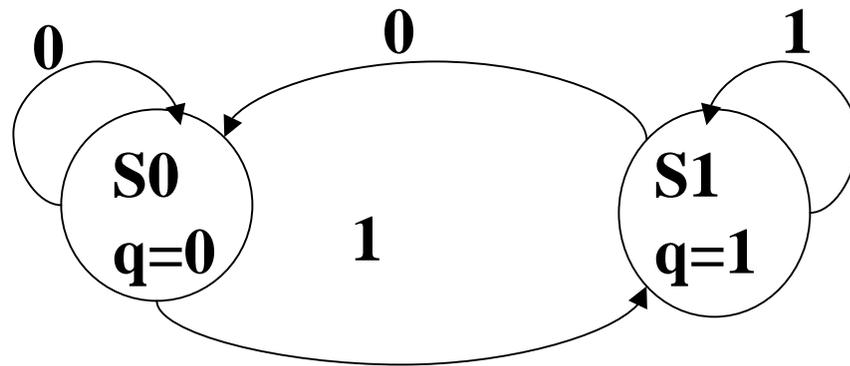
# DFF as a Finite State Machine


A DFF is a finite state machine with two possible states. Lets call these states **S0** and **S1**. (*state enumeration*).

Furthermore, lets say when the **Q** output = '0', then we are in State **S0**, and that when **Q** output = '1', we are in State **S1**. This is called the *State Encoding*.



**Bubble Diagram:** States represented by bubbles. State transitions represented by arrows. Labeling on arrows represent input values (in this case, the **D**-input!). Labeling inside bubbles represent output values.
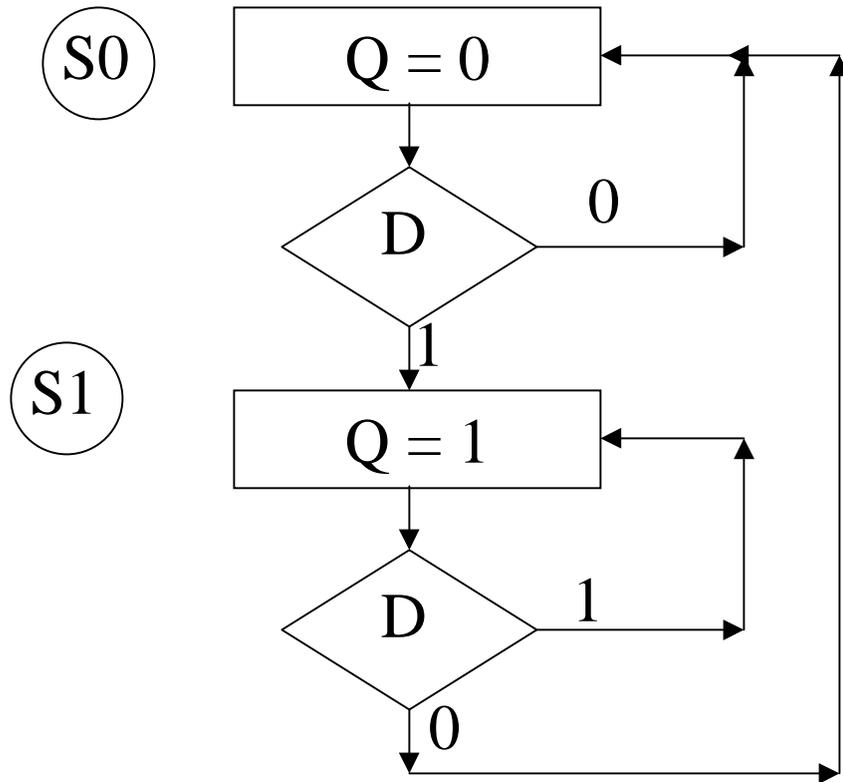
# Algorithmic State Machine Chart for DFF



A Finite State Machine (FSM) can be described via either a Bubble diagram or an ASM chart.

ASM charts are better for complex FSMs. We will use ASM charts in this class.

State S0 is usually the asynchronous Reset state.

# Algorithmic State Chart (ASM)


- An ASM chart can be used to describe FSM behavior

Only three action signals can appear within an ASM chart:




*State* box. Each box represents a state.

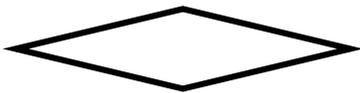Outputs within a state box is an UNCONDITIONAL output (always asserted in this state).




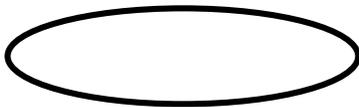*Decision* box. A condition in this box will decide next state condition.



*Conditional output* box. If present, will always follow a decision box; output within it is conditional.
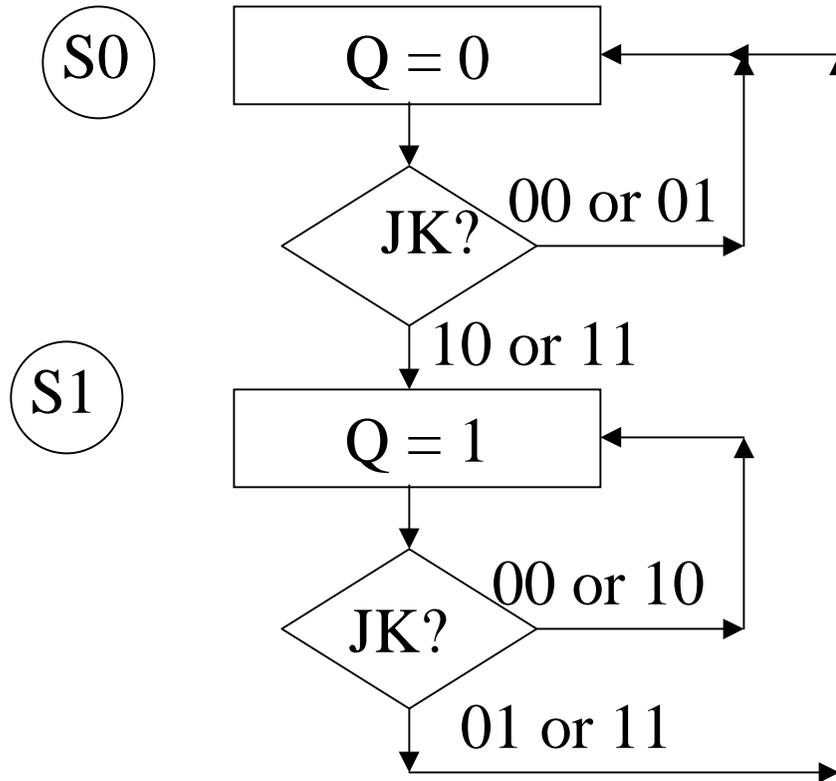
# Algorithmic State Machine Chart for JKFF



# Finite State Machine Implementation

Given an Algorithmic State Machine chart that describes a Finite State Machine, how do we implement it?????

Step #1: Decide on the State Encoding (how many Flip Flips do I use and how what should the FF outputs be for EACH state). The problem definition *may* decide the state encoding for you.

Step #2: Decide what kind of FFs to use! (We will always use DFFs in this class, but you could use JKFFs or TFFs if you wanted to).

Step #3: Write the State Transition Table.

Step #4: Write the FF input equations, and general output equations from the state transission table.


# Problem Definition

Design a *Modulo three* counter. The count sequence is:


“00” → “01” → “10” → “00” → “01” → “10”, etc.

There is an “en” input that should control counting (count when en=1, hold value when en=0). Assume ACLR line used to reset counter to “00”.

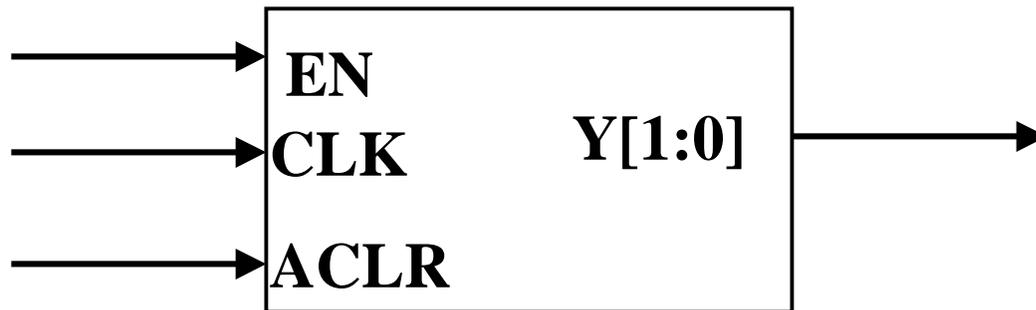How many states do we need? Well, we have three unique output values, so lets go with three states.



# ASM Chart for Modulo Three Counter

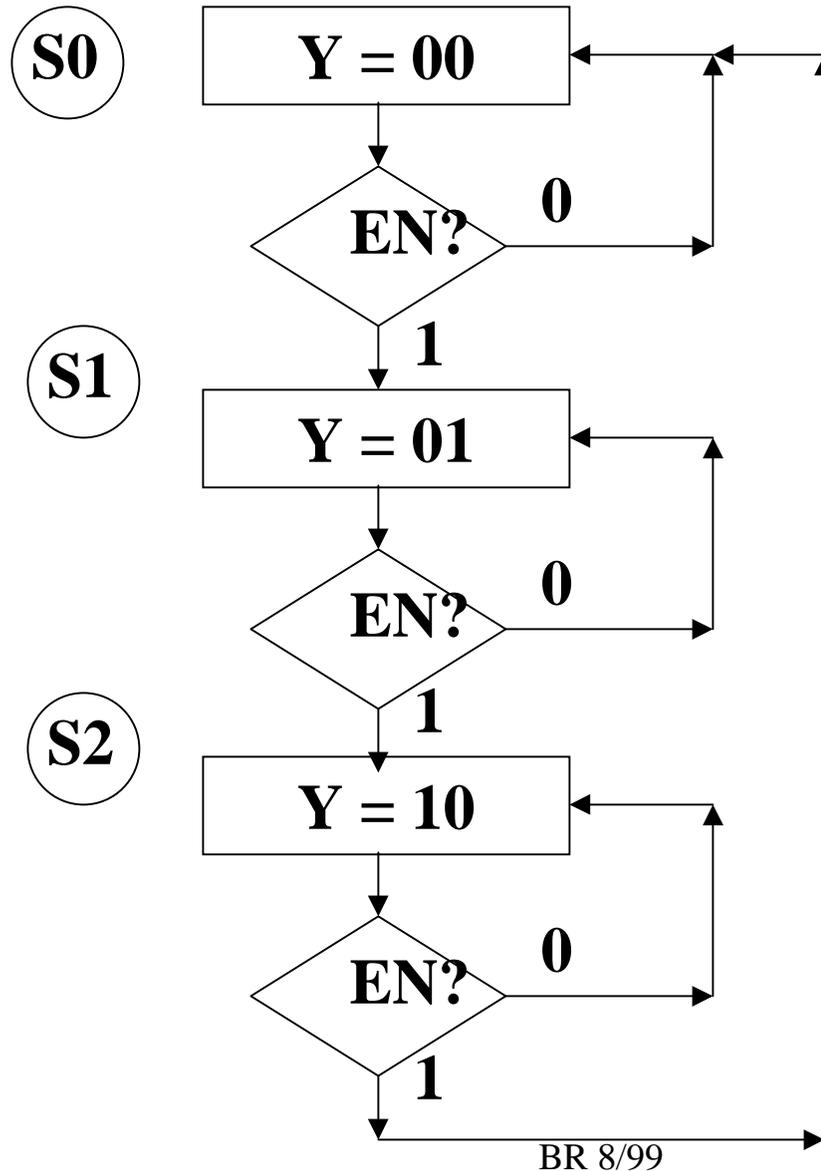

# State Transition Table

**State transition table shows next state, output values for present state, input values.**

<b>Inputs(EN)</b>	<b>Present State</b>	<b>Next State</b>	<b>Y</b>
<b>0</b>	<b>S0</b>	<b>S0</b>	<b>00</b>
<b>0</b>	<b>S1</b>	<b>S1</b>	<b>01</b>
<b>0</b>	<b>S2</b>	<b>S2</b>	<b>10</b>
<b>1</b>	<b>S0</b>	<b>S1</b>	<b>00</b>
<b>1</b>	<b>S1</b>	<b>S2</b>	<b>01</b>
<b>1</b>	<b>S2</b>	<b>S0</b>	<b>10</b>

# Decisions

- **State encoding** - will be based on number of FFs we use.
  - Three states means the minimum number of FFs we can use two FFs ( $\log_2(3) = 2$ ).
- If we use two FFs, then could pick a state encodings like:
  - S0: 00, S1: 01, S2: 10 (binary counting order)
  - S0: 01, S1: 01, S2: 11 (gray code - may result in less combinational logic)
- Could also use 1 FF per state (3 FFs) and use one hot encoding
  - S0: 001, S1: 010, S2: 100 (may result in less combinational logic)

## Decisions (cont.)

- **What type of FF to use?**
- **DFF - most common type, always available in programmable logic**
- **JKFF - sometimes available, will usually result in less combinational logic (more complex FF means less combinational logic external to FF)**

Lets use **two FFs** with state encoding **S0=00, S1=01, S2=10.**

Lets use **DFFs.**

# New State Transition Table

**Modify State Transition table to show what FF inputs need to be in order to get to that state. Also, use actual state encodings**

<b>Inputs(EN)</b>	<b>Present State (Q1Q0)</b>	<b>Next State (Q1Q)*</b>	<b>D1D0</b>	<b>Y</b>
<b>0</b>	<b>00</b>	<b>00</b>	<b>00</b>	<b>00</b>
<b>0</b>	<b>01</b>	<b>01</b>	<b>01</b>	<b>01</b>
<b>0</b>	<b>10</b>	<b>10</b>	<b>10</b>	<b>10</b>
<b>1</b>	<b>00</b>	<b>01</b>	<b>01</b>	<b>00</b>
<b>1</b>	<b>01</b>	<b>10</b>	<b>10</b>	<b>01</b>
<b>1</b>	<b>10</b>	<b>00</b>	<b>00</b>	<b>10</b>

**For DFFs, D inputs are simply equal to next state!!!!**

# D-input Equations, Y equations

**Unoptimized equations:**

$$\mathbf{D0 = EN' Q1'Q0 + EN Q1'Q0'}$$


$$\mathbf{D1 = EN' Q1 Q0' + EN Q1' Q0}$$

$$\mathbf{Y0 = Q0}$$

$$\mathbf{Y1 = Q1}$$

**The output Y is simply the DFF outputs! Here is one case where state encoding is affected by problem definition (does not make much sense to use a different state encoding, even though we could do it).**

# DFF Implementation

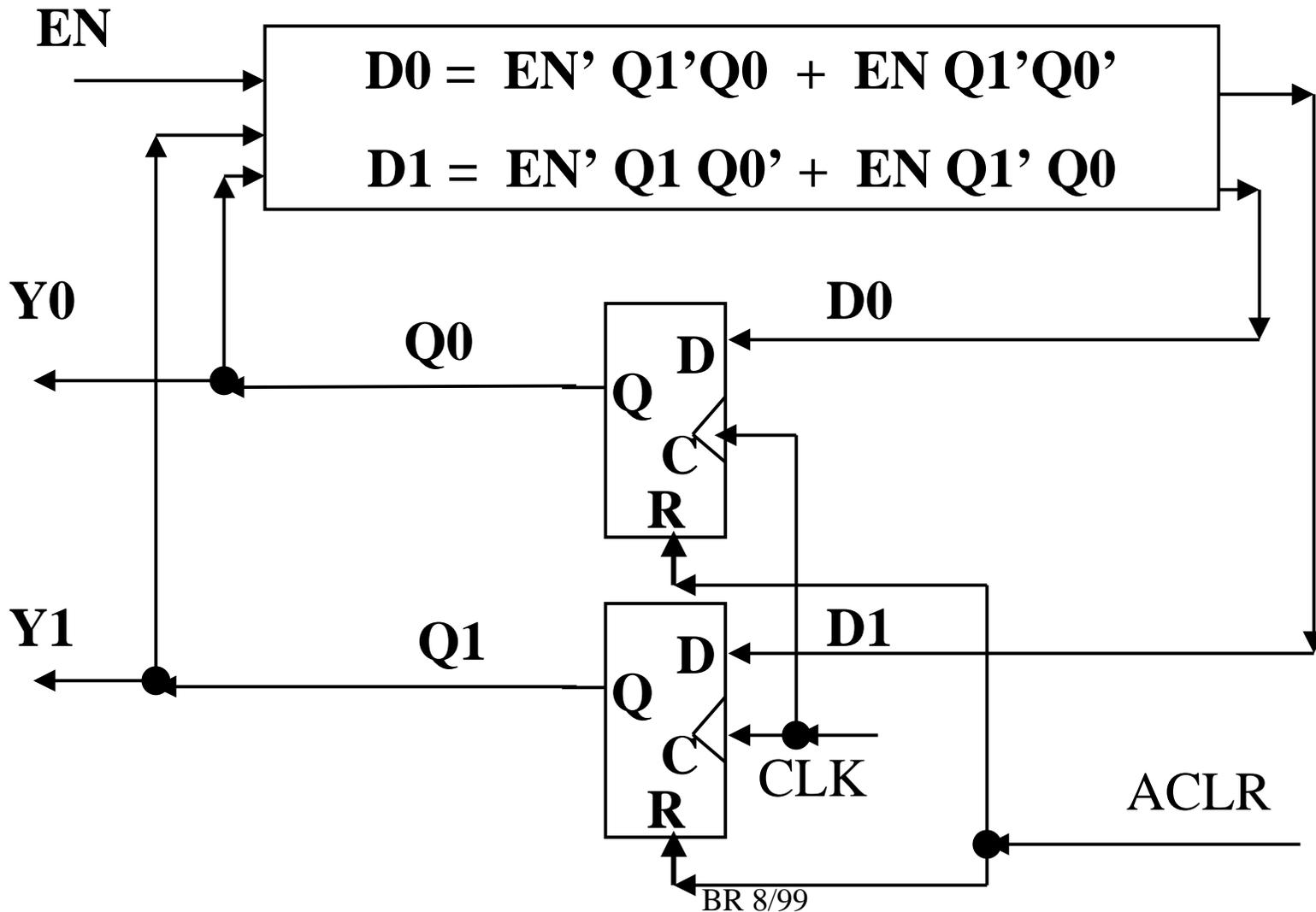

# What if we used JKFFs?

Need to change State Transition table to reflect JK input values.

Inputs EN	Present State (Q1Q0)	Next State (Q1Q0)*	J1 K1	J0 K0	Y
0	00	00	0 X	0 X	00
0	01	01	0 X	X 0	01
0	10	10	X 0	0 X	10
1	00	01	0 X	1 X	00
1	01	10	1 X	X 1	01
1	10	00	X 1	0 X	10

**JK FF Q transitions:  $0 \rightarrow 0$  (J=0, K=X);  $0 \rightarrow 1$  (J=1, K=X);  
 $1 \rightarrow 1$  (J=X, K=0);  $1 \rightarrow 0$  (J=X, K=1);**

# JK Input Equations, Output Equations

## Unoptimized equations

$$J_0 = \overline{EN} Q_1' Q_0'$$

$$K_0 = \overline{EN} Q_1' Q_0$$

$$J_1 = \overline{EN} Q_1' Q_0$$


$$K_1 = \overline{EN} Q_1 Q_0'$$

$$Y_0 = Q_0$$

$$Y_1 = Q_1$$

**Using JK FFs will mean simpler external optimized combinational logic because FFs are more complex (provide more functionality).**

# JK FF Implementation

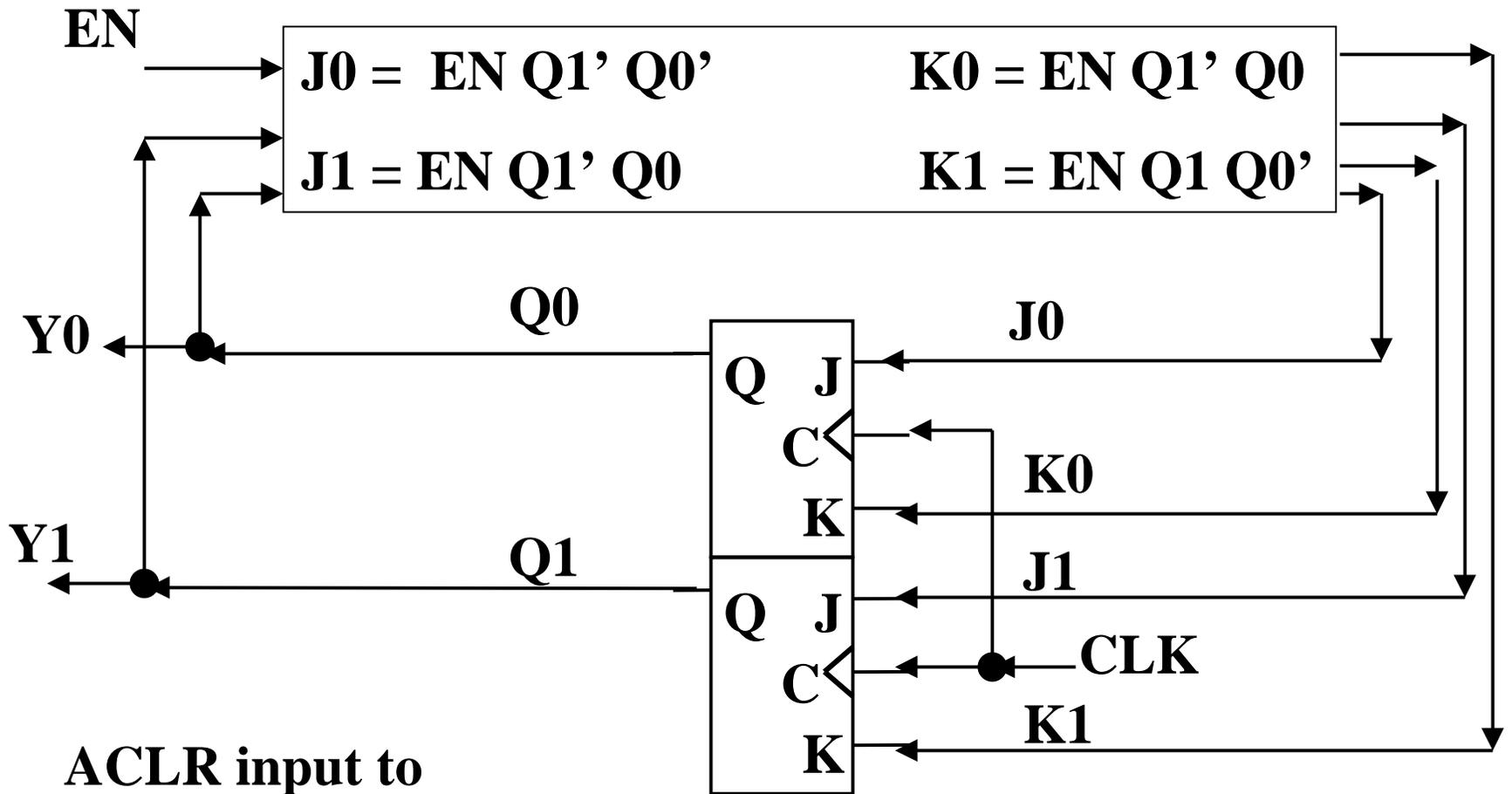

**ACLR input to JKFFs not shown.**

# 3 DFFs and One Hot Encoding

State encoding:  $S0 = 001$ ,  $S1 = 010$ ,  $S2 = 100$

Inputs EN	Present State (Q2Q1Q0)	Next State (Q2Q1Q0)*	D2D1D0	Y
0	001	001	001	00
0	010	010	010	01
0	100	100	100	10
1	001	010	010	00
1	010	100	100	01
1	100	001	001	10

# DFF input equations, Output Equations

$$D0 = EN'Q0 + ENQ2$$

$$D1 = EN'Q1 + ENQ0$$

$$D2 = EN'Q2 + ENQ1$$

$$Y0 = EN'Q1 + EN Q1 = Q1$$

$$Y1 = EN'Q2 + EN Q2 = Q2$$

In equations, because a FF Q will only be '1' in a **single state**, do not have to include all FFs to define state!!

(  $Q2'Q1'Q0 = Q0!!$ ,  $Q2'Q1Q0' = Q1!!$ ,  $Q2Q1'Q0' = Q2!!$  )

**This is one of the advantages of one-hot encoding!**

# Generic Next State Equations

Generic next state equations can be written directly from the ASM chart as an alternative to the Transition table

$$S^* = (\text{conditions to remain in this state}) + (\text{conditions to enter state})$$

From ASM chart of modulo three counter:

$$S0^* = EN' S0 + EN S2$$

$$S1^* = EN' S1 + EN S0$$

$$S2^* = EN' S2 + EN S1$$

If **One hot encoding and DFFs** are used, then Generic Next State equations ARE the specific next State Equations!!

$$D0 = EN' Q0 + EN Q2$$

$$D1 = EN' Q1 + EN Q0$$

$$D2 = EN' Q2 + EN Q1$$