

# **Using BDDs to Design ULMs for FPGAs**


**Zeljko Zilic and Zvonko Vranesic  
Department of Electrical and  
Computer Engineering  
University of Toronto**

# Overview

- Motivation
- Universal Logic Modules (ULMs)
- ULMs for FPGAs
- New Design Method for ULMs useful in FPGAs
- Design Examples: 3- input and 4- input blocks
- Applications

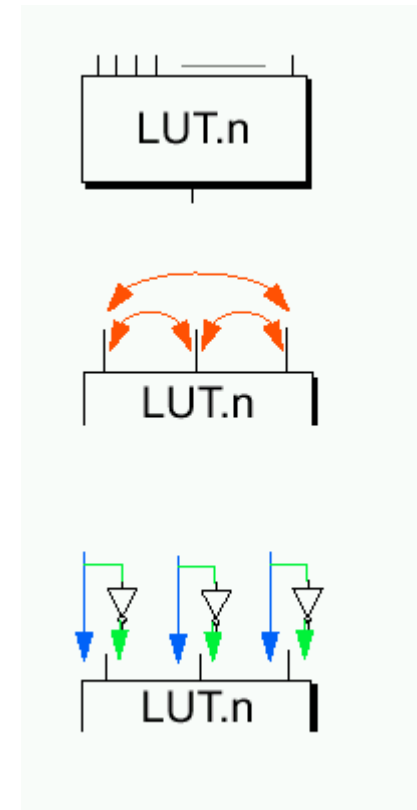
# More Efficient FPGAs?

- Given LUT architecture:
- **Input Permutations:**
  - Provided by routing resources
- **Input Inversions:**
  - Provided by previous blocks
- LUT replacements that exploit permutations and inversions?



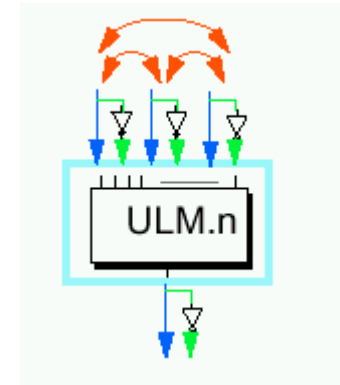
# ULMs

- Logic Blocks that realize any function of  $n$  variables
- Assumed that input permutations and inversions are free




- Example: ULM. 2 - used in Actel

 


# Standard ULMs

- Many pins needed:

 

$$m = \Theta\left(\frac{2^n}{\log(n)}\right)$$

 - Attempts to use in FPGAs: incomplete functionality
  - ULM.3: [Lin, Sadowska, Gatlin 94]




10/14 functions

- ULM.4: [Thakur, Wong 95] -  $n=4, m=8, 201/208$  functions

# Need Different ULMs


- No additional inputs
- Just like LUTs:

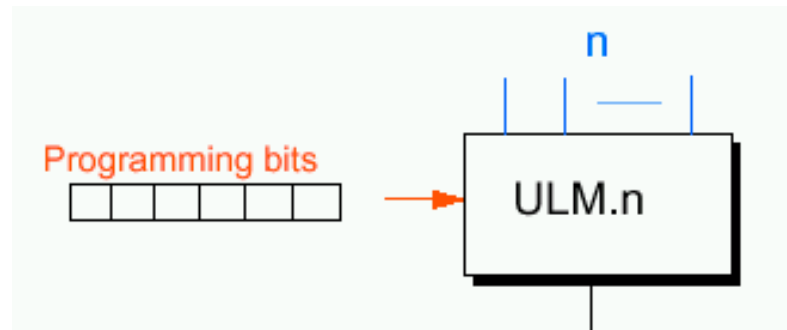


- Design procedure for these ULMs?
 
# Design of ULMs - Idea

- Equivalence classes:  $n\bar{p}n$ ,  $np$



 - Sufficient to realize only class representatives in ULM




- Programming bits encode only class

n	3	4	5
$n\bar{p}n$ Classes	14	222	616126
Bits - $n\bar{p}n$	4	8	20
Bits - $np$	5	9	21
Bits- LUT	8	16	32
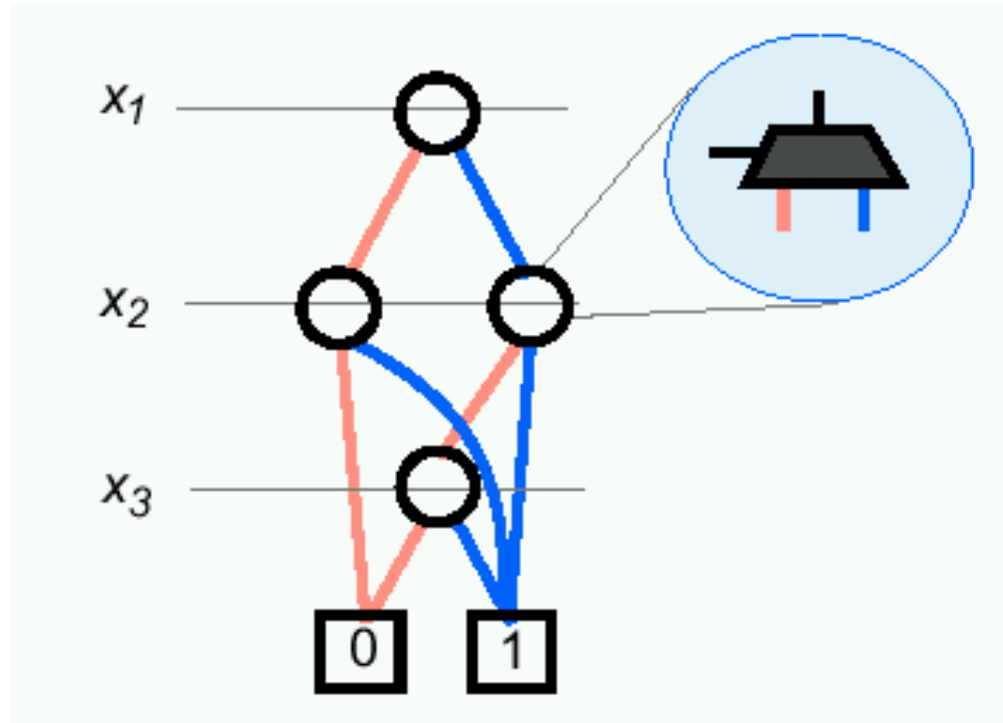
# ULM Design - Using BDDs



- Want to both classify and physically realize
- Use BDDs



- Unique representation
- Realization: each node is a MUX:




# BDDs for all classes: n=3

  

# Super BDD: n=3

- SBDD.3: can realize all 10 BDDs

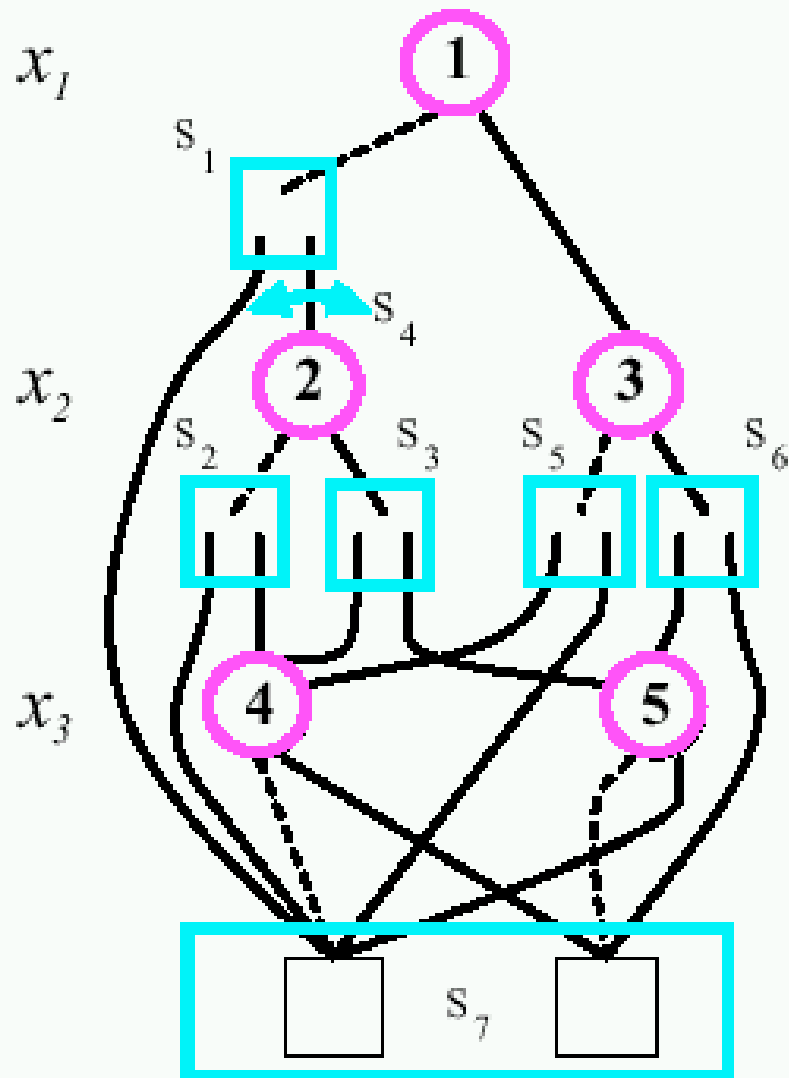


Edges optimized by  
inversions, permutations

5 nodes

7 switches - 1 bit saved

# Complete ULM


- Encode all possible input combinations

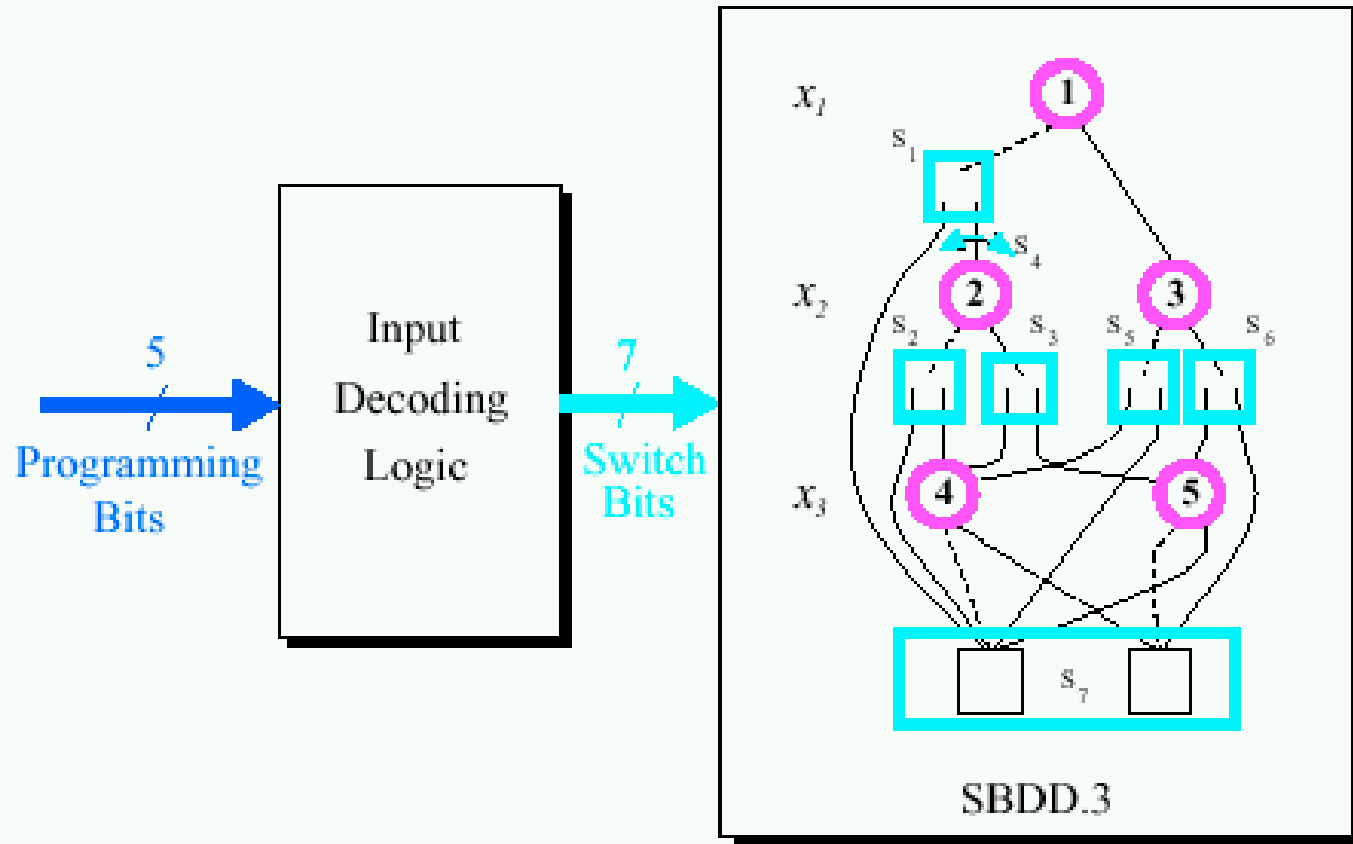

- Input Encoding - No influence on speed
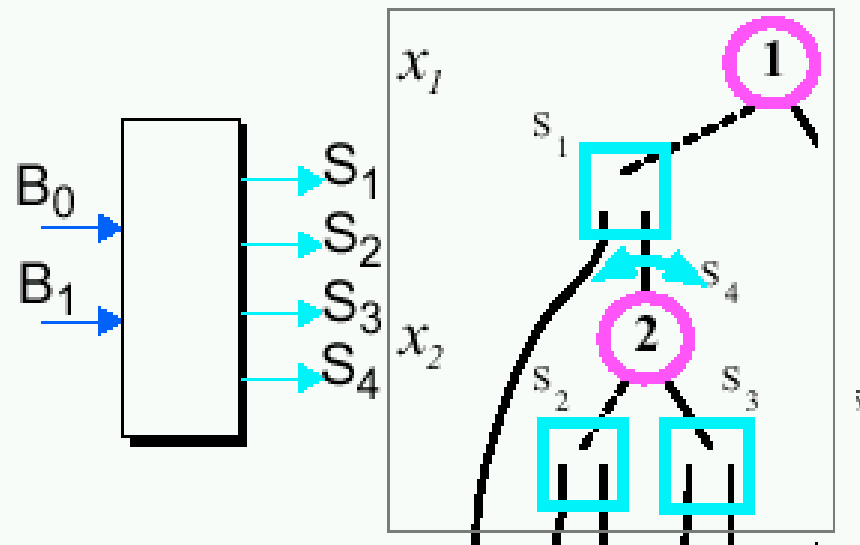
# Input Encoding

- First four switches: only 4 combinations → 2 bits



$S_1$	$S_2$	$S_3$	$S_4$	$B_0$	$B_1$
0	x	x	x	0	0
1	0	0	1	0	1
1	0	0	0	1	0
1	1	1	1	1	1


- Simple decoding logic:

$$S_1 = B_0 + B_1$$

$$S_2 = S_3 = B_0 \cdot B_1$$

$$S_4 = B_1$$

# Implementation Comparison

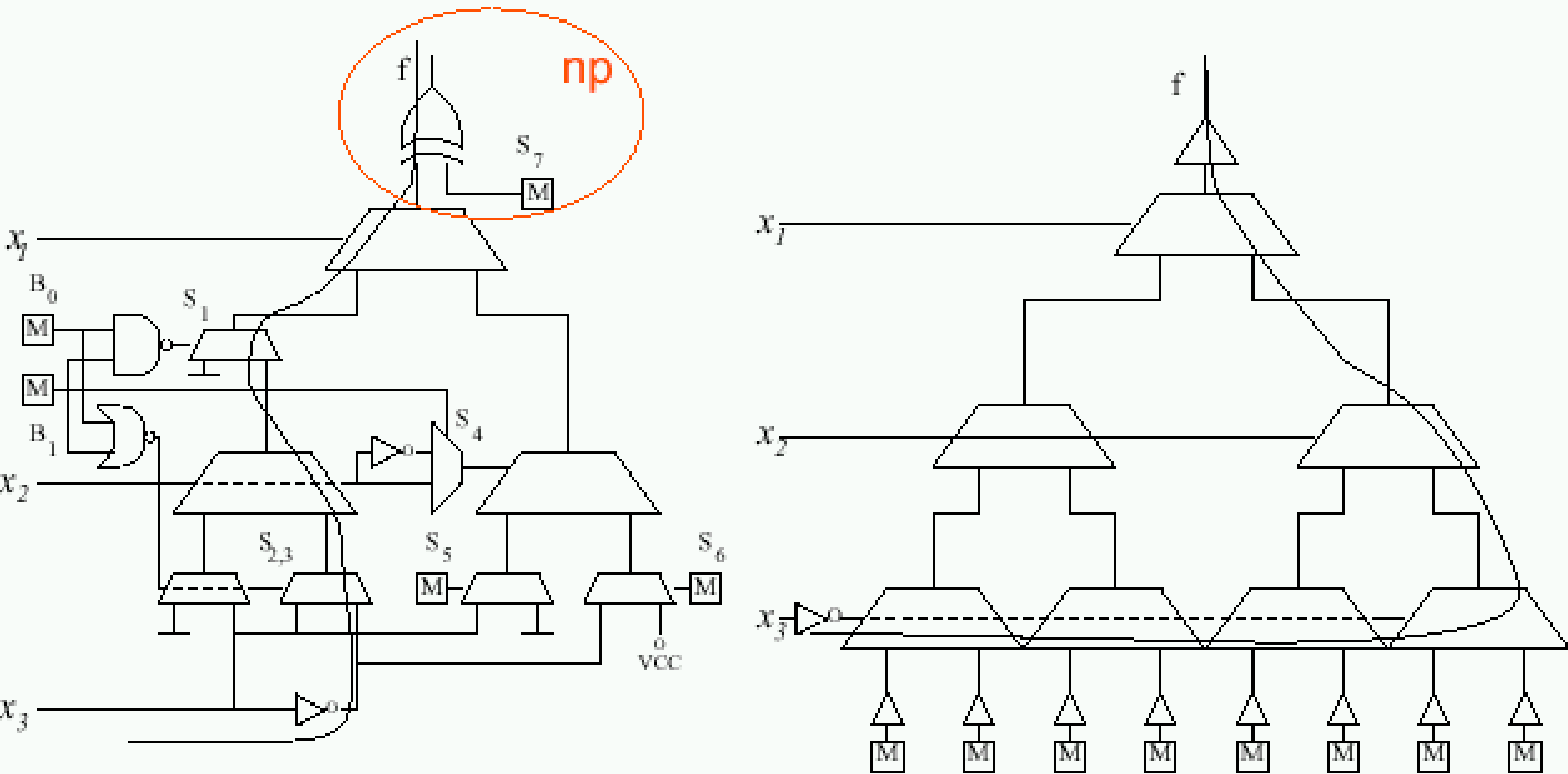


	ULM.3	LUT.3
Memory	5 bits	8 bits
Transistors	70	78
Delay	1.31ns	1.38 ns

# Larger Case: $n=4$

- Enumeration of classes
- Representative Realization: 208 BDDs
- Super BDD - optimize interconnection
- Minimize # switches in SBDD
- Optimize circuits by input encoding
- Several alternative encodings

# ULM. 4 - LUT. 4 Replacement

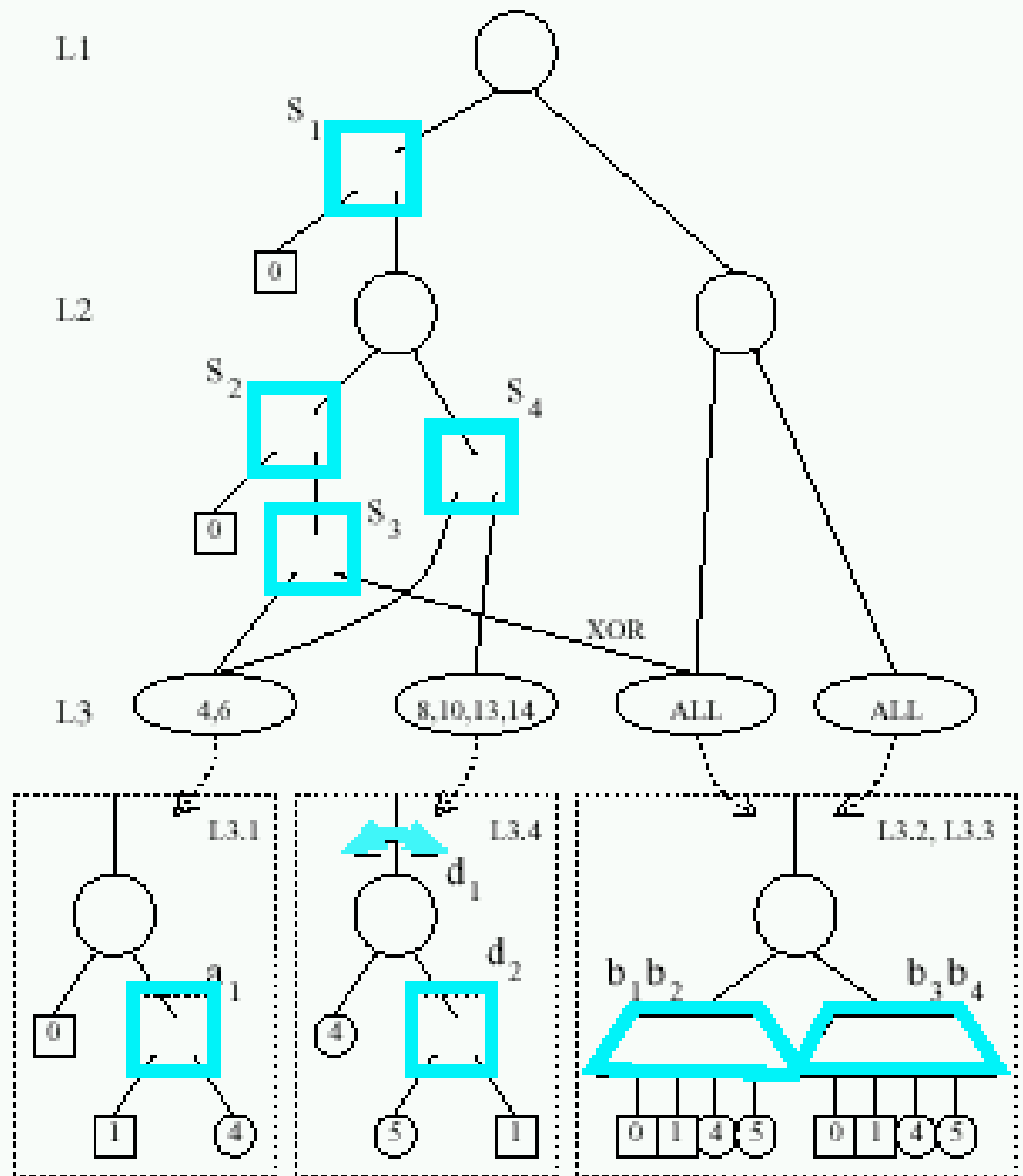

- Super BDD -  
SBDD. 4

# Input Encodings

- **Optimal number of bits - logic too complex**
- **Tradeoff: area versus number of bits**
- **Combine input encoding programs and decompositions**

Encoding	Pre-encoding	Logic	Bits
None	none	none	16
4 Switches	2 gates	none	15
Bit Sharing	3-input decoder	10 gates	13
Dense Groups	groups decoder	126 literals	11
Group Compact	folding circuits	683 literals	9
Flat	none	719 literals	9



# Technology Mapping and Applications

- **Technology Mapping**
  - Assume: np- equivalent ULM
  - Polarity disagreement - blocks need opposing polarities
  - [Lin, Sadowska 94] - 6.6% extra blocks needed for ULM. 3
- **Functionally incomplete blocks**
  - Not interesting for  $n=3$
  - Many possibilities - 201/ 208 functions with 13 bits and logic overhead of 2 gates
  - ULMs can help evaluate tradeoffs
- **Realistic architectures that can use ULMs**
  - • Reconfigurable computing [Jones, Lewis]
  - • Hard- wired blocks [Chung, Rose]

# Conclusions

- Exploited permutation and inversion availability in FPGAs
- New kind of ULMs
- Applicable in FPGAs
- LUT replacements that save programming bits
- Comparable to LUTs (area, speed)
- Require optimal or suboptimal number of programming bits
- Possible basis for new architectures