

Self-Repairing and Self-Replicating Hardware: The Embryonics Approach

D. Mange, M. Sipper, A. Stauffer, and G. Tempesti



**2nd NASA/DoD Workshop on Evolvable Hardware
Palo Alto, July 13-15, 2000**



Caenorhabditis Elegans



We understand completely
the chromosome and role of
the genes in the organism of
the Elegans!


Model for studies in genetics

11 December 1998

Multicellular Organization

FIGURE 16

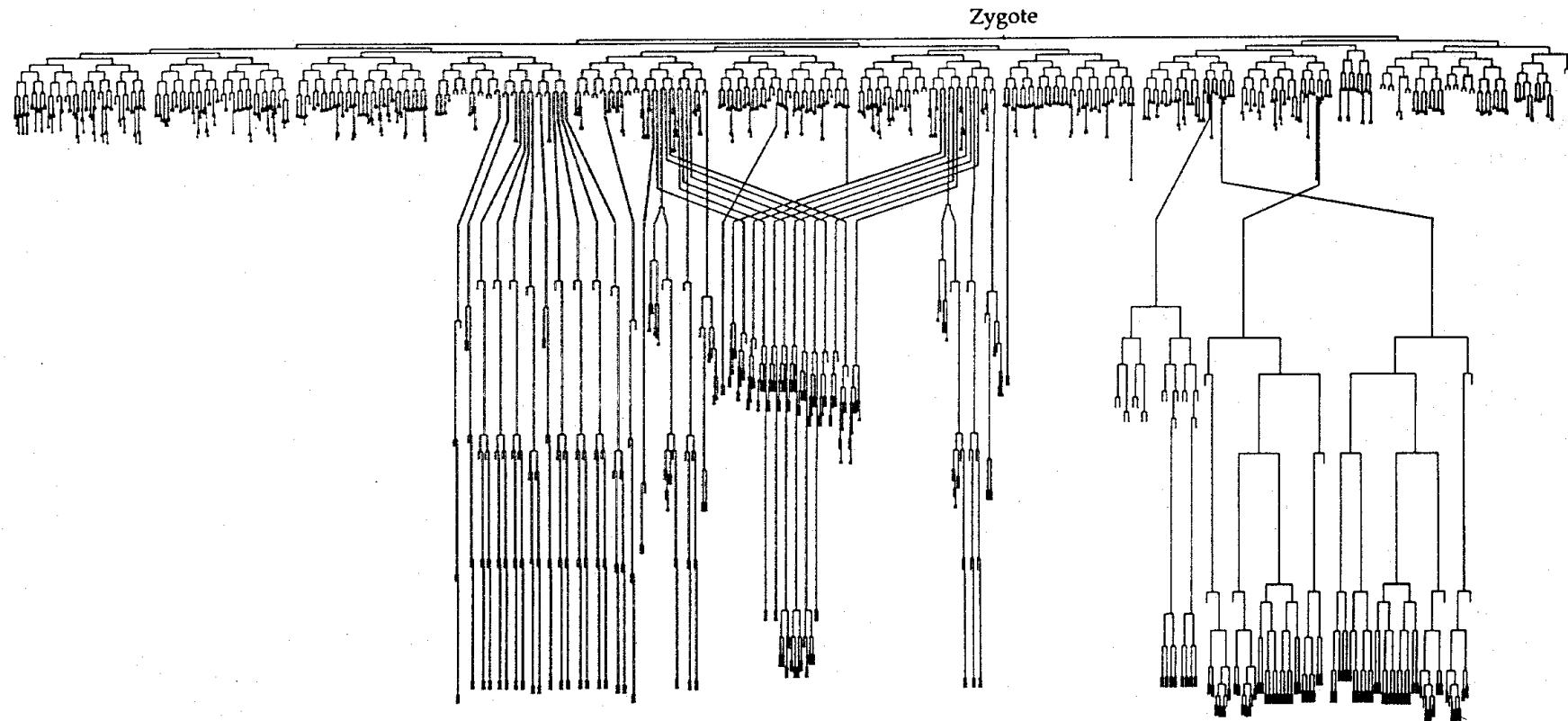Entire cell lineage chart for *C. elegans*. Each vertical line represents a cell; each horizontal line represents a cell division. (From Sulston et al., 1983.)



959 somatic cells

Embryonics: Why?

Design of robust integrated circuits
able to:

- self-repair (healing)
- self-replicate (cloning)

Embryonics: Why?

Today:

- space exploration
- nuclear plants
- avionics

Tomorrow:


- molecular electronics

Embryonics: How?

Iterative electronic circuit based on
3 features:

- multicellular organization
- cellular division
- cellular differentiation


Cellular Division

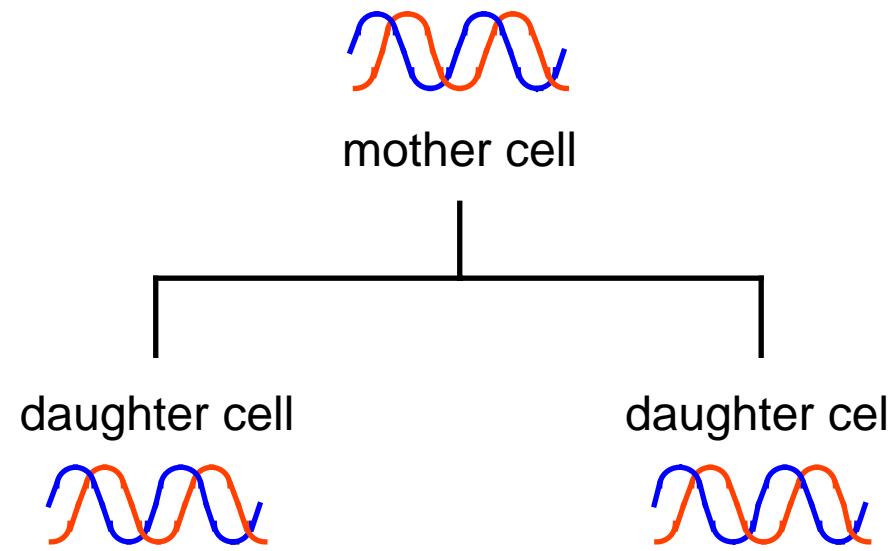

Cellular Differentiation

FIGURE 16

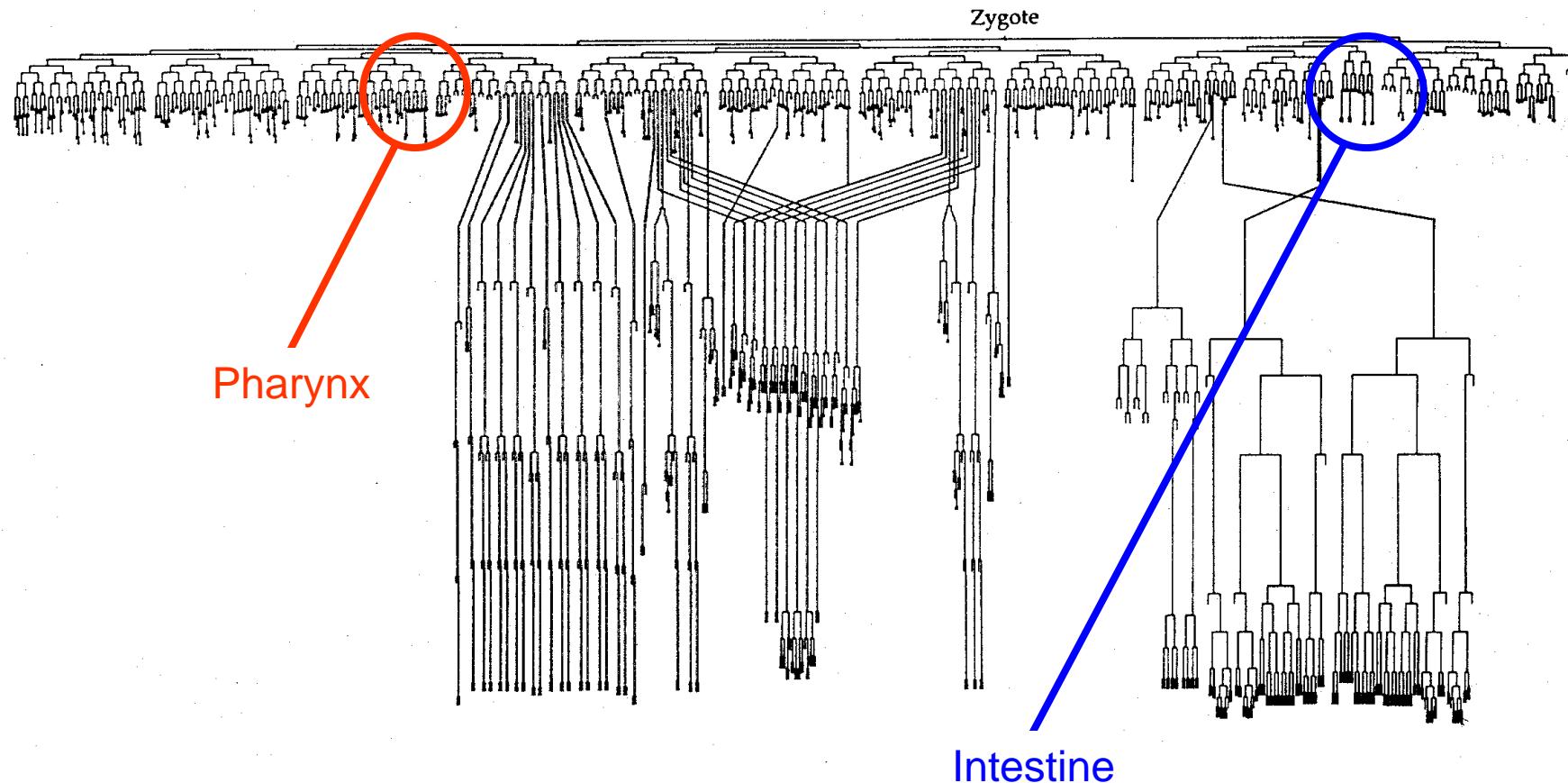
Entire cell lineage chart for *C. elegans*. Each vertical line represents a cell; each horizontal line represents a cell division. (From Sulston et al., 1983.)



BioWatch



The Future of Embryonics


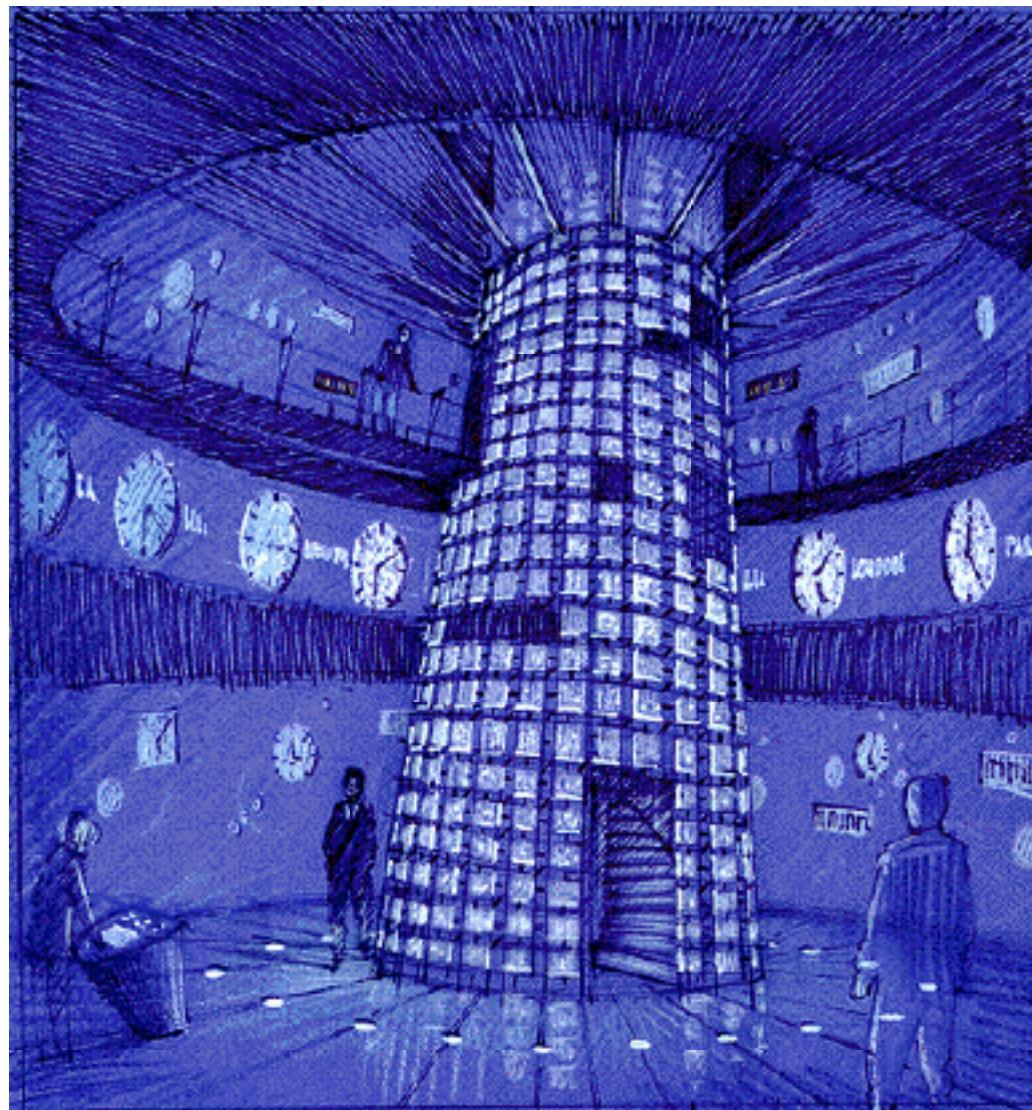


Two kinds of Programmable Arrays

Based on logic functions in cells

Based on switchboxes


Mixed

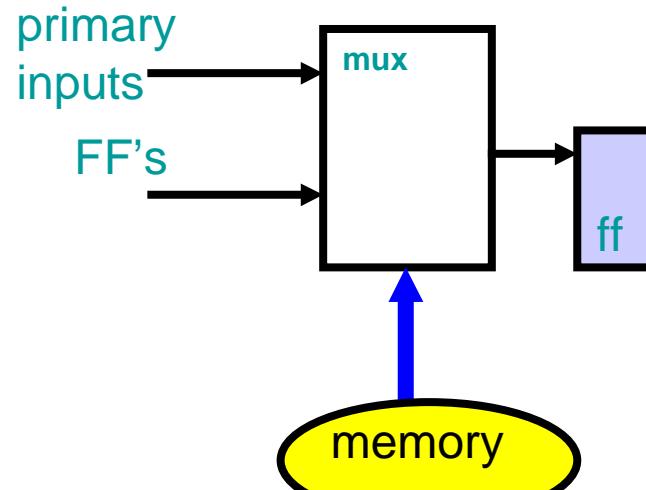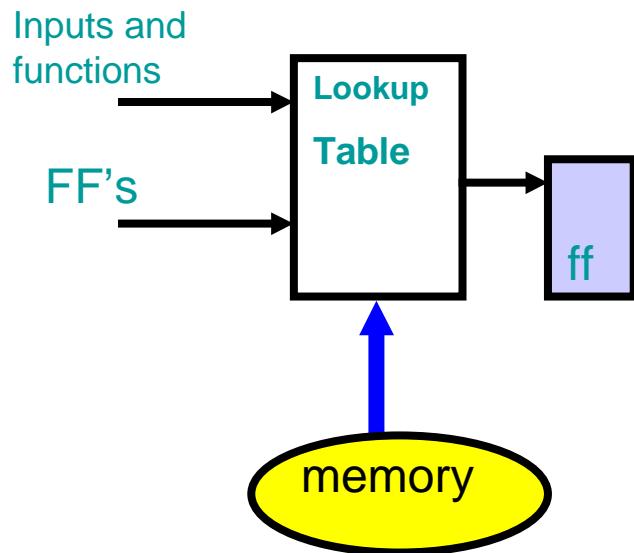


Based on logic functions

Based on switchboxes


Based on switching

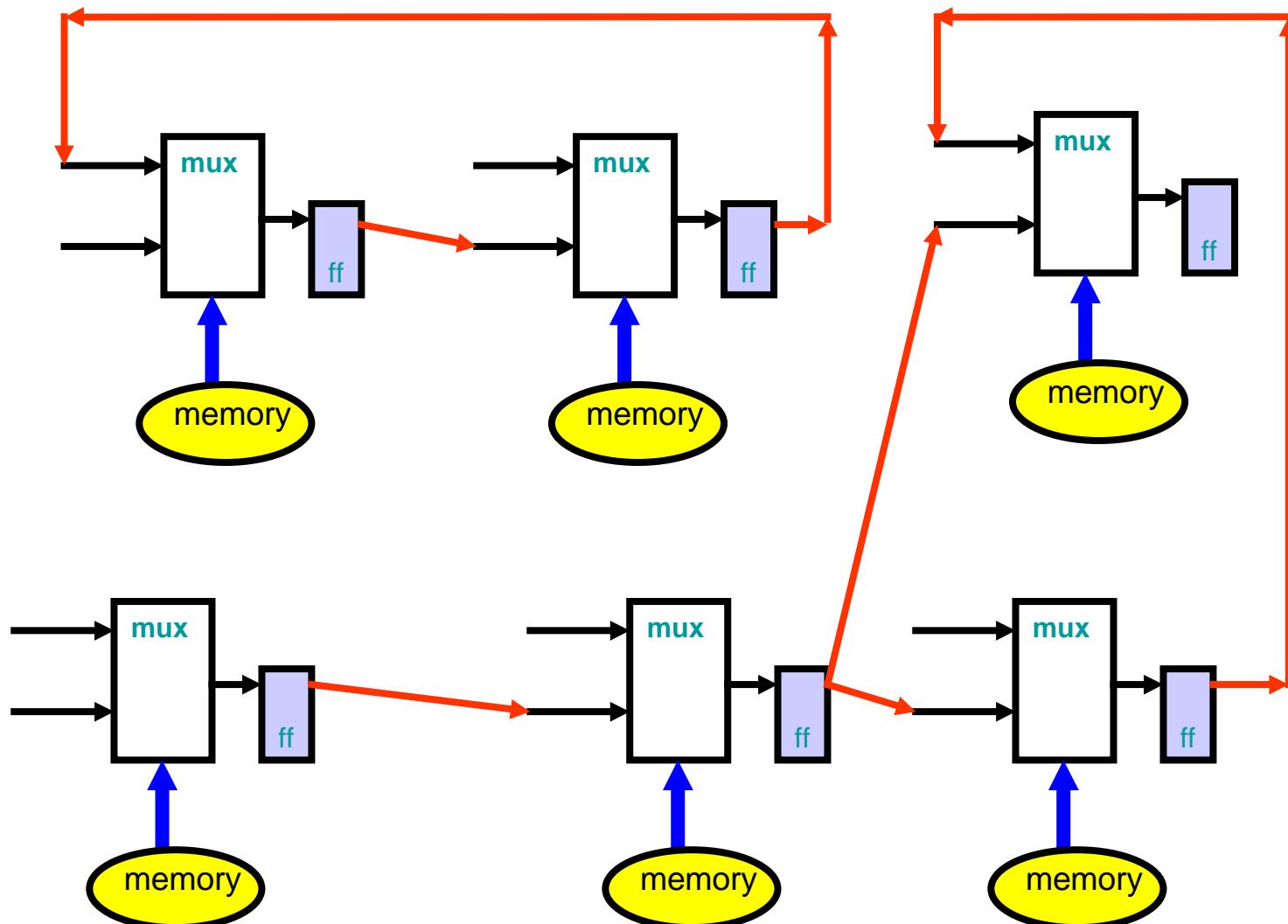

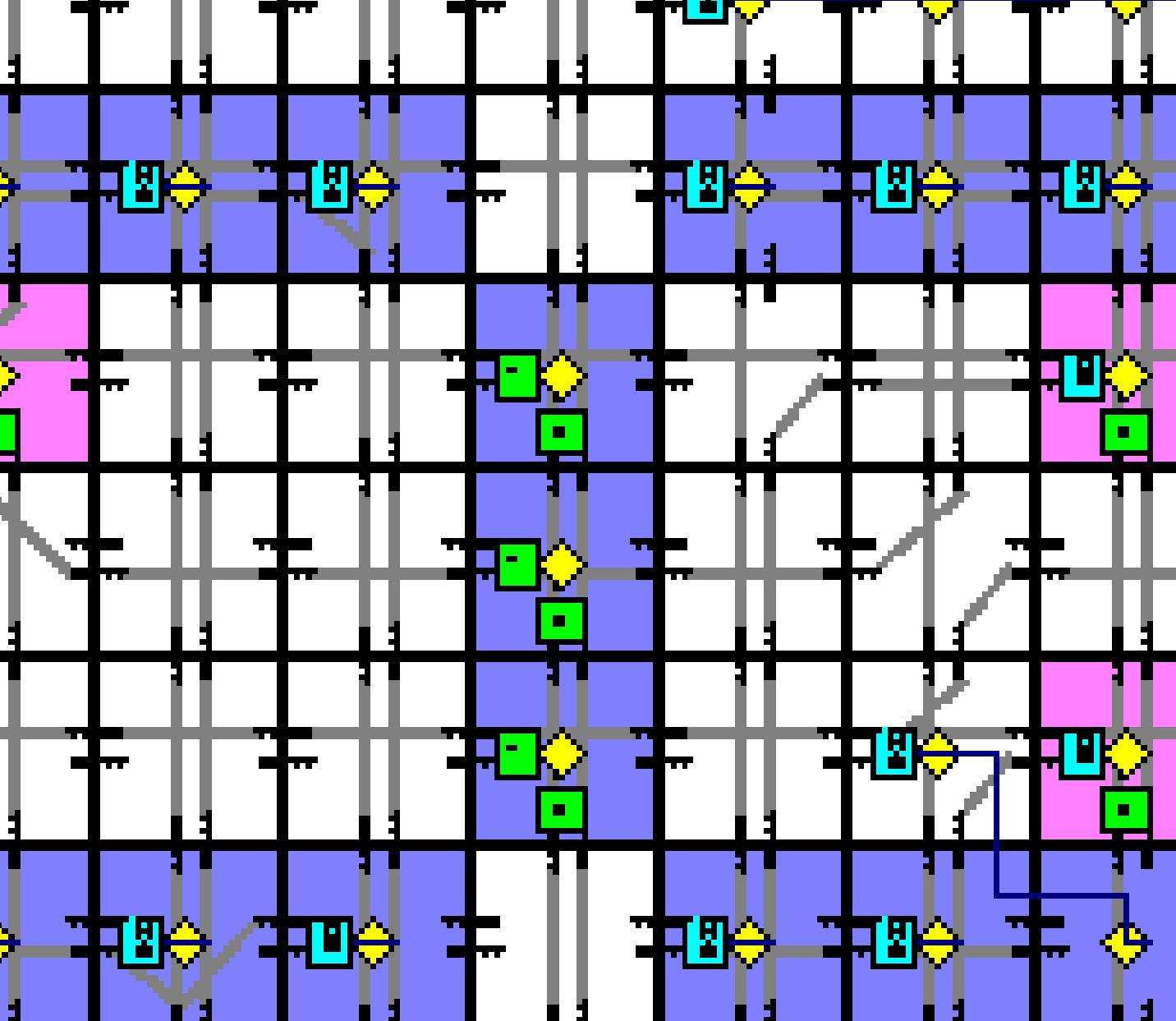

Multicellular Organization

Organism is composed of bio-cells

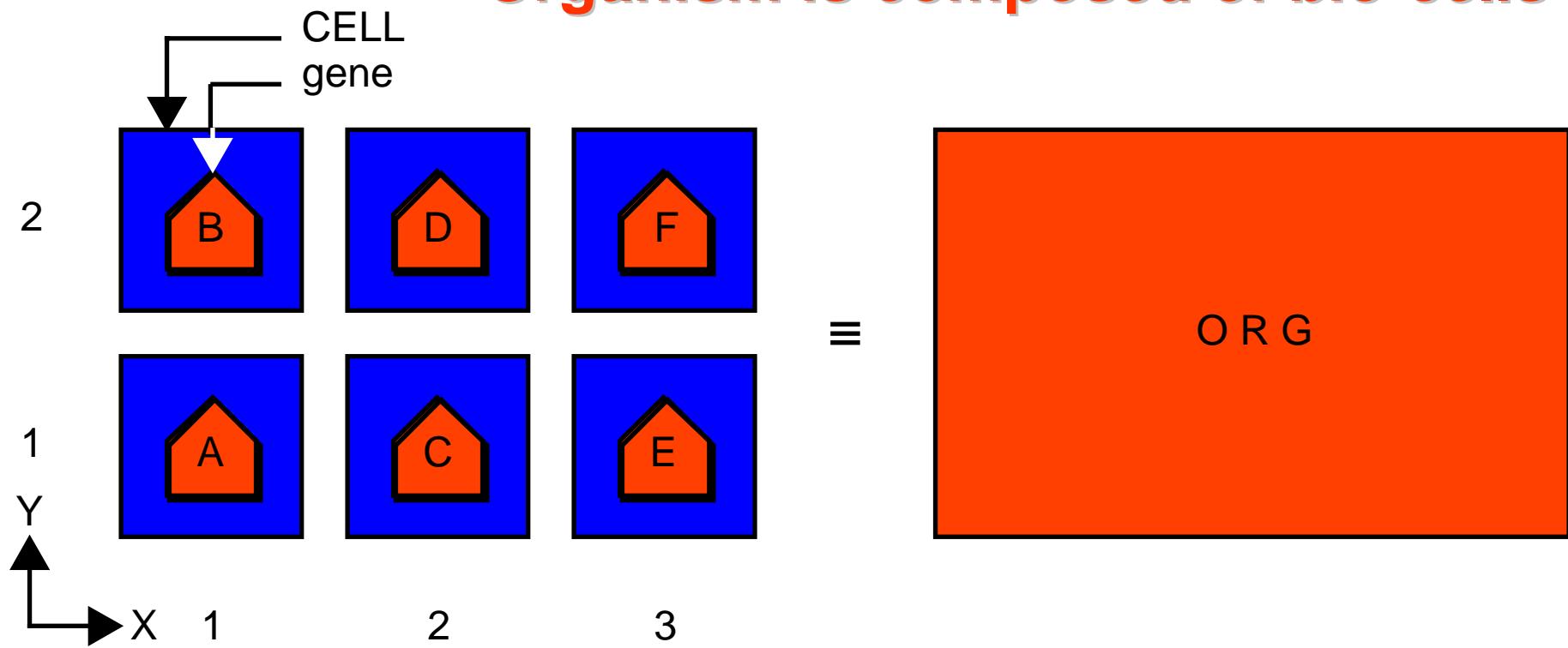


bio-cell = phenotype from genotype

bio-cell = logic circuit (virtual)

Chromosome = memory contents

MUXTREE Molecule

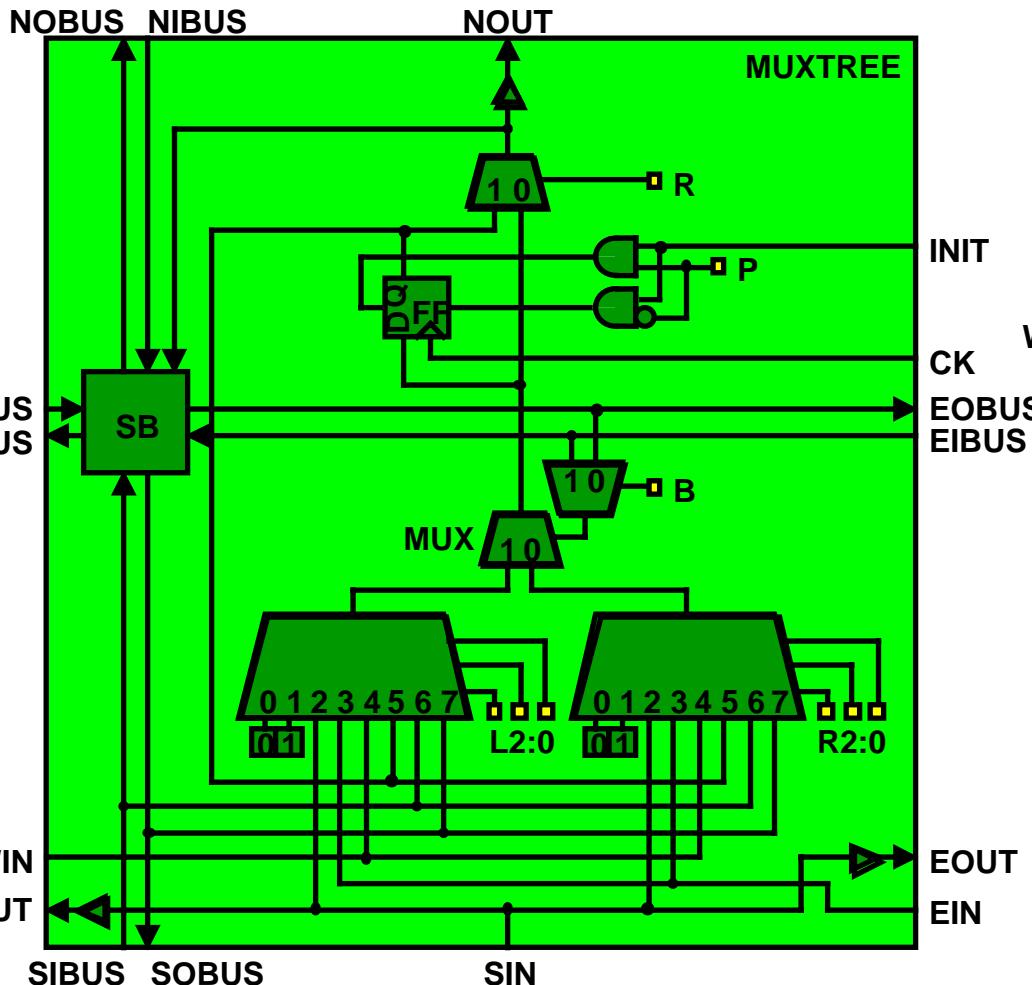
Bio-cell has several molecule cells like this




9 memory cells

9+8+3=20 memory cells

8 memory cells

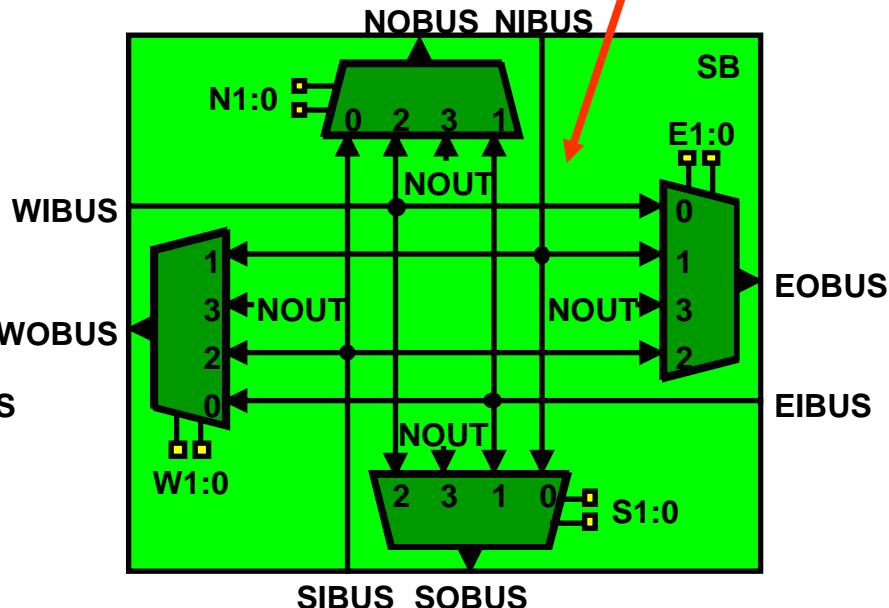


Block SB

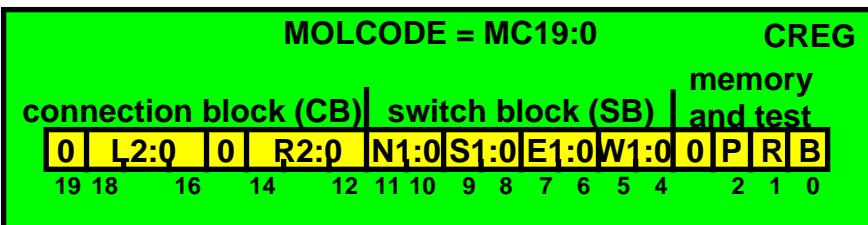

20 programming bits in memory of the molecule cell

Embryonics Landscape

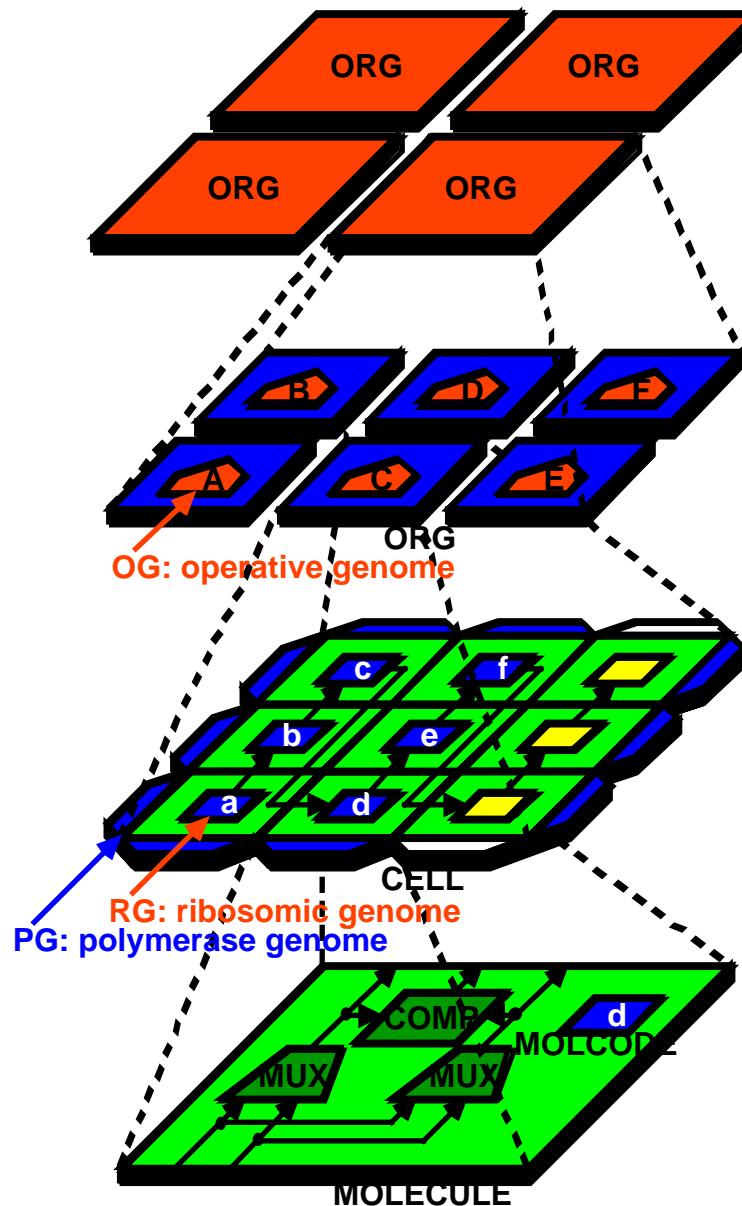

Population level
(population = Σ organisms)

Organismic level
(organism = Σ cells)

Cellular level
(cell = Σ molecules)

Molecular level
(basic FPGA's element)


Operative genome
is the same as
chromosome in
previous lectures

**Bio-cell is one or
more FPGA cells**

StopWatch

START
STOP


RESET

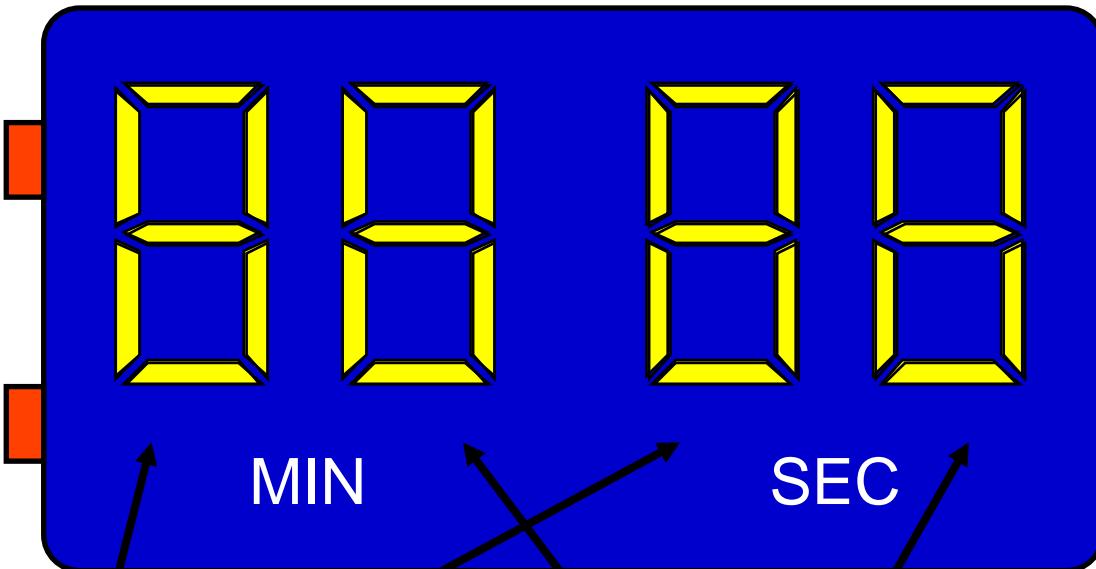


Max = 5

Max = 9

StopWatch

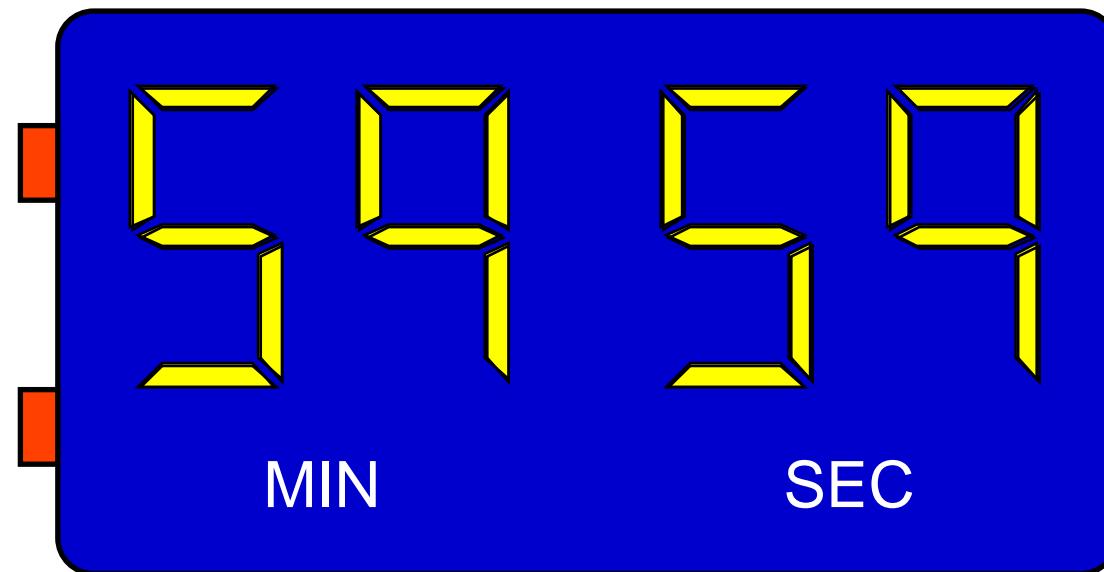

StopWatch

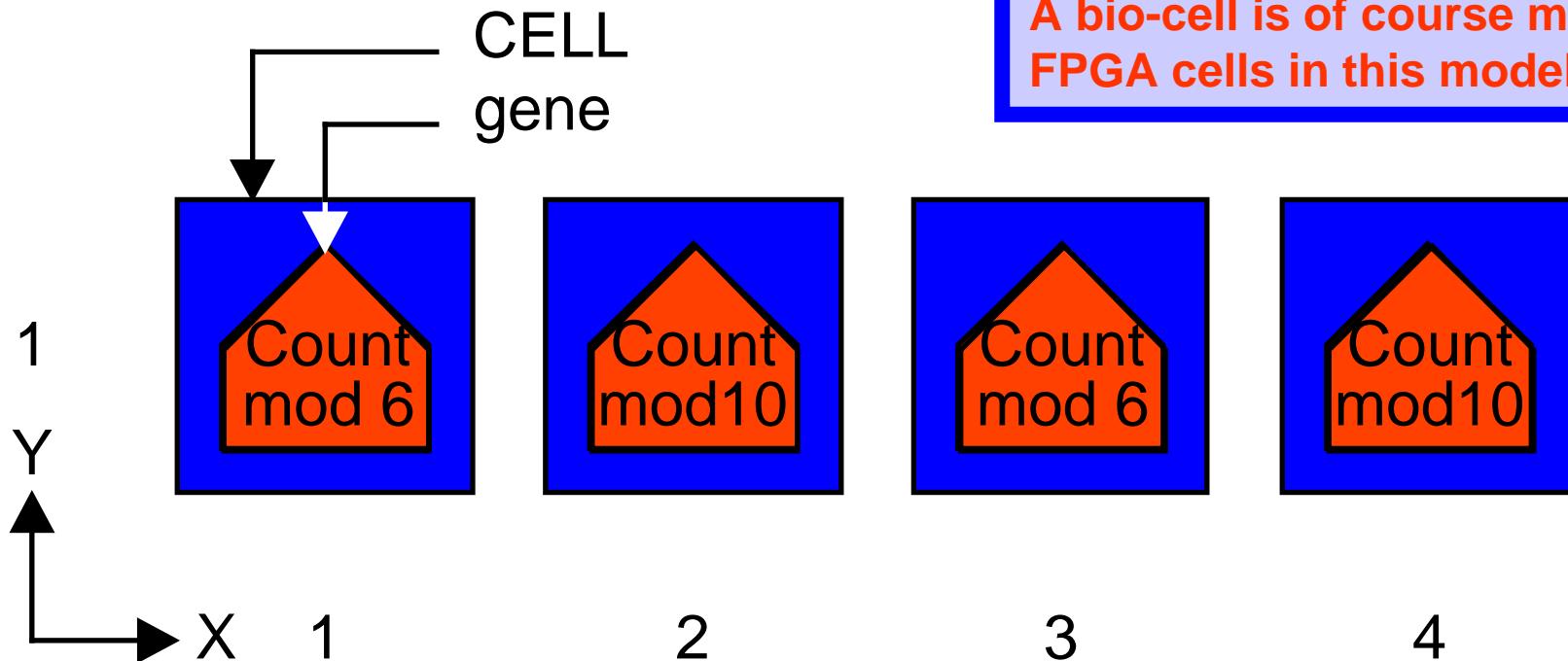

- The organism is one-dimensional
- It has four bio-cells


The whole counter is an organism

The component module 6 or module 10 counter is a bio-cell

A bio-cell is of course many FPGA cells in this model

- There are two types of bio-cells:
 - Count mod 6
 - Count mod 10

StopWatch

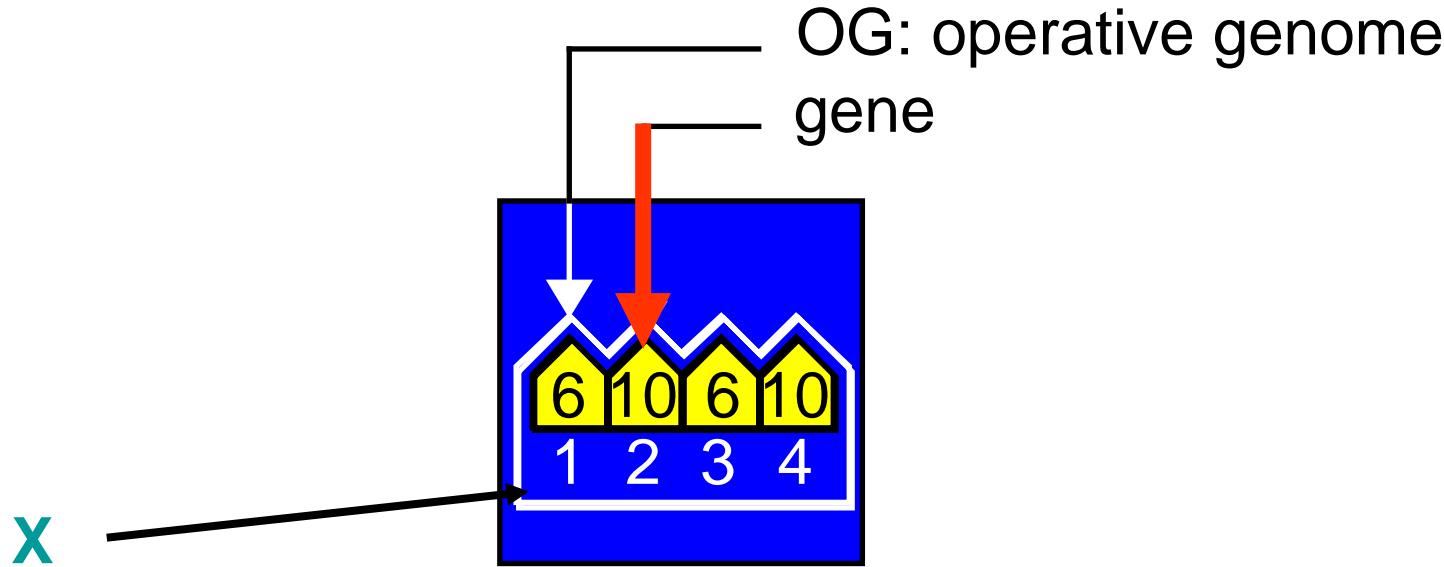

4 genes

**genes responsible for
two types of bio-cells in
the phenotype**

Operative genome => for organism
gene => for bio-cell of the organism


StopWatch

OG: operative genome


case of X:

X = 1: Countmod 6 (10 minutes)
X = 2: Countmod 10 (minutes)
X = 3: Countmod 6 (10 seconds)
X = 4: Countmod 10 (seconds)

StopWatch

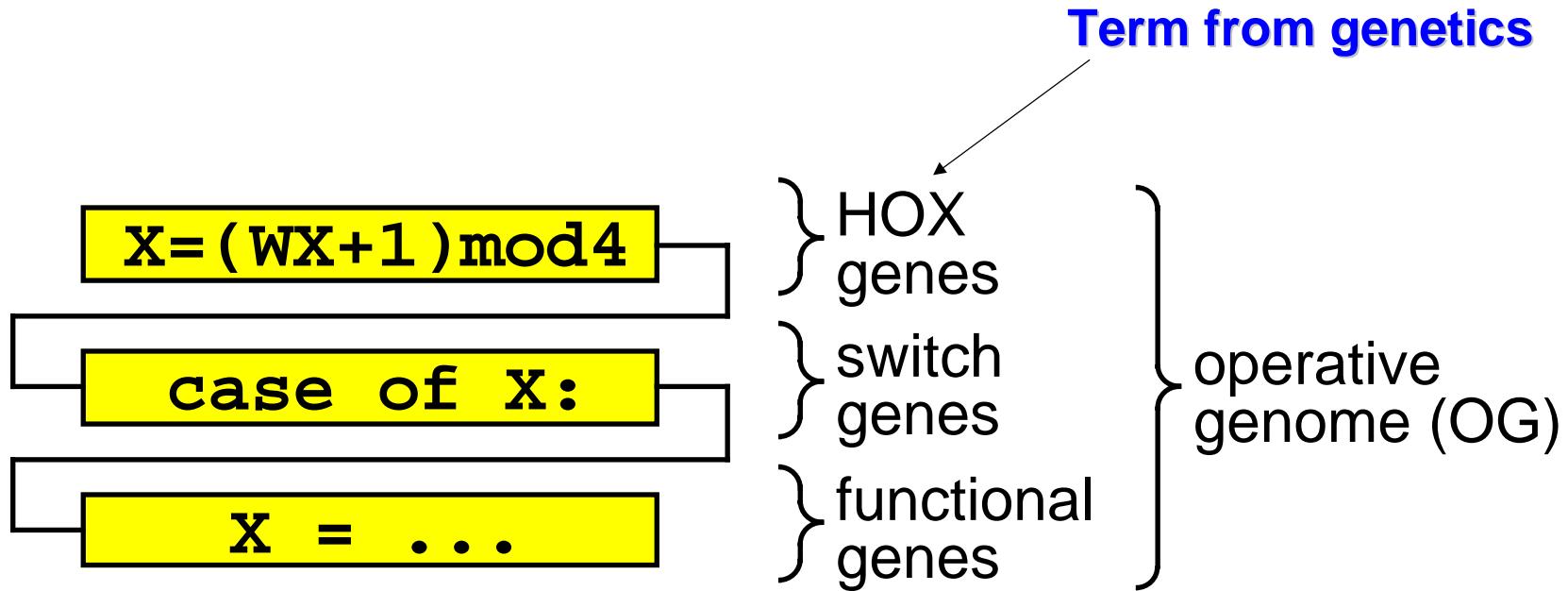

Cellular Differentiation

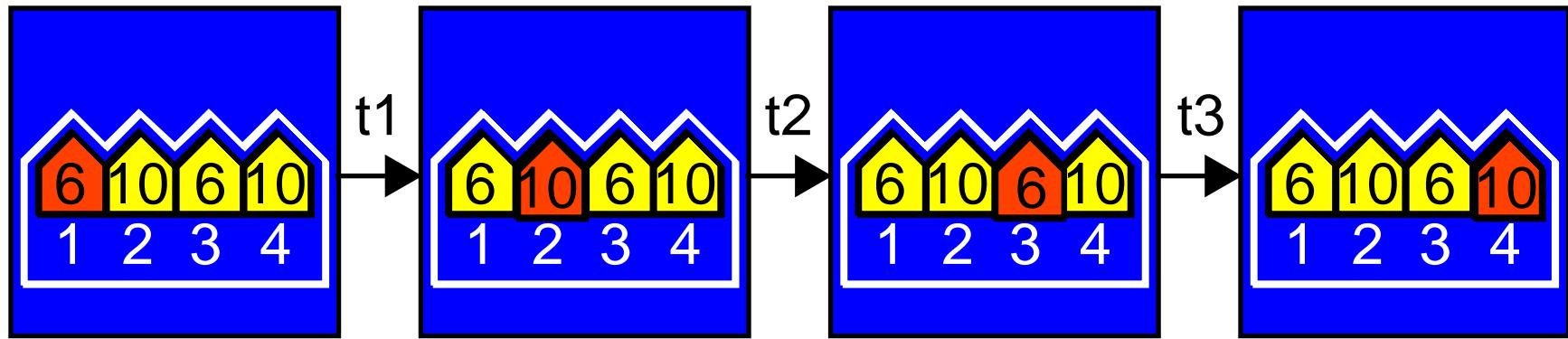


X = 1

2

3


4

Self-Replication

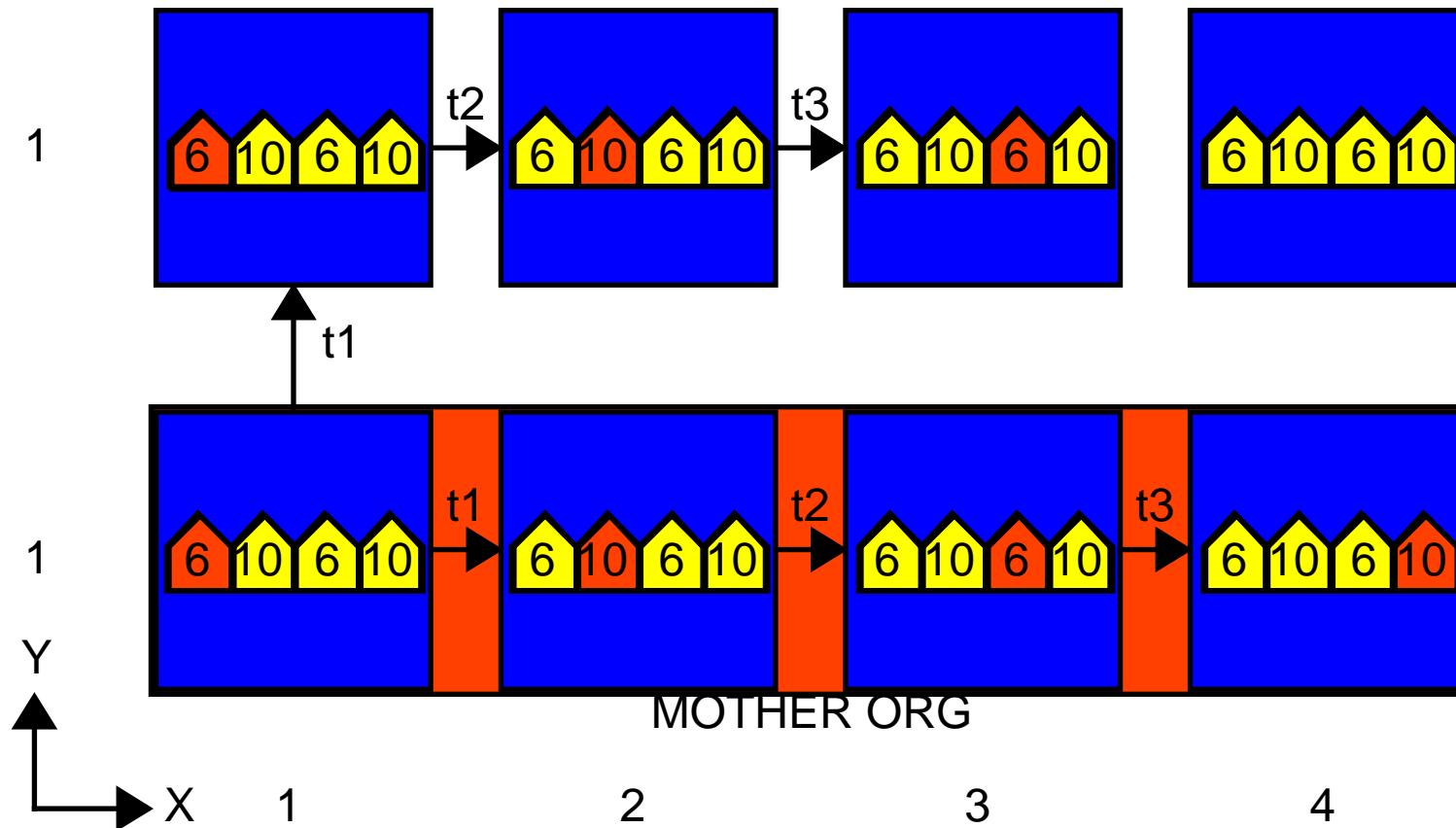


Self-Replication


Directions of self-replication

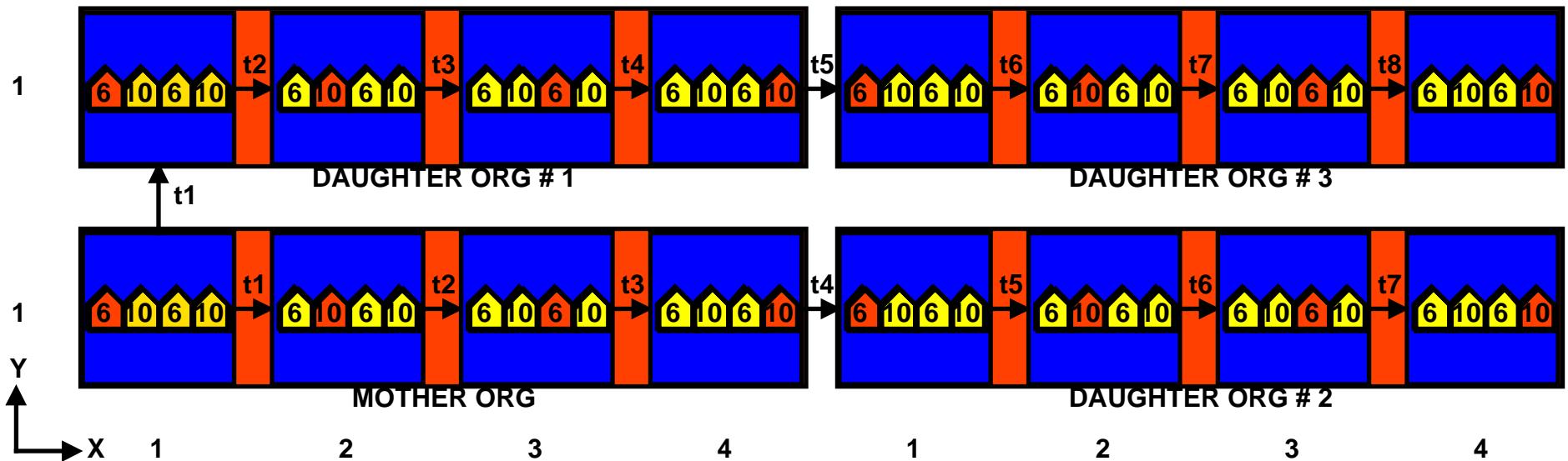




Self-Repair

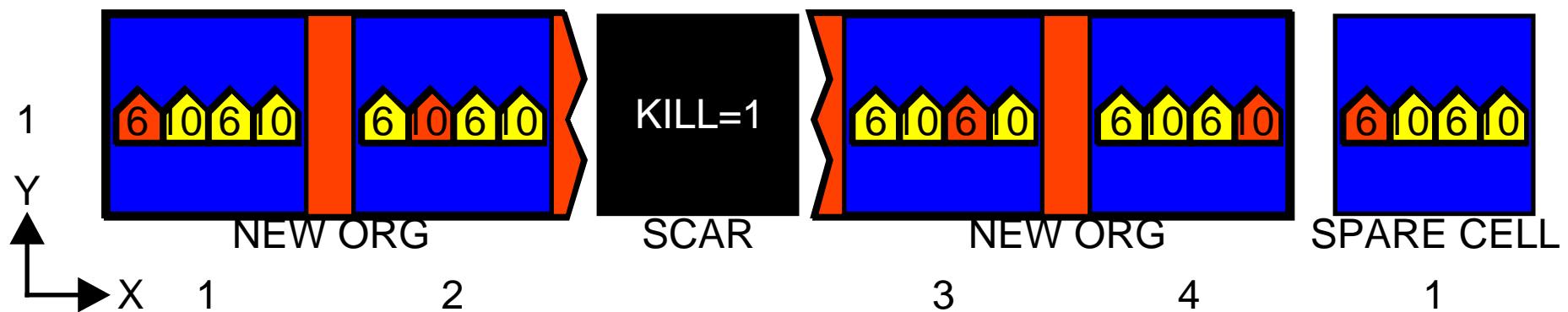



Embryonics Landscape

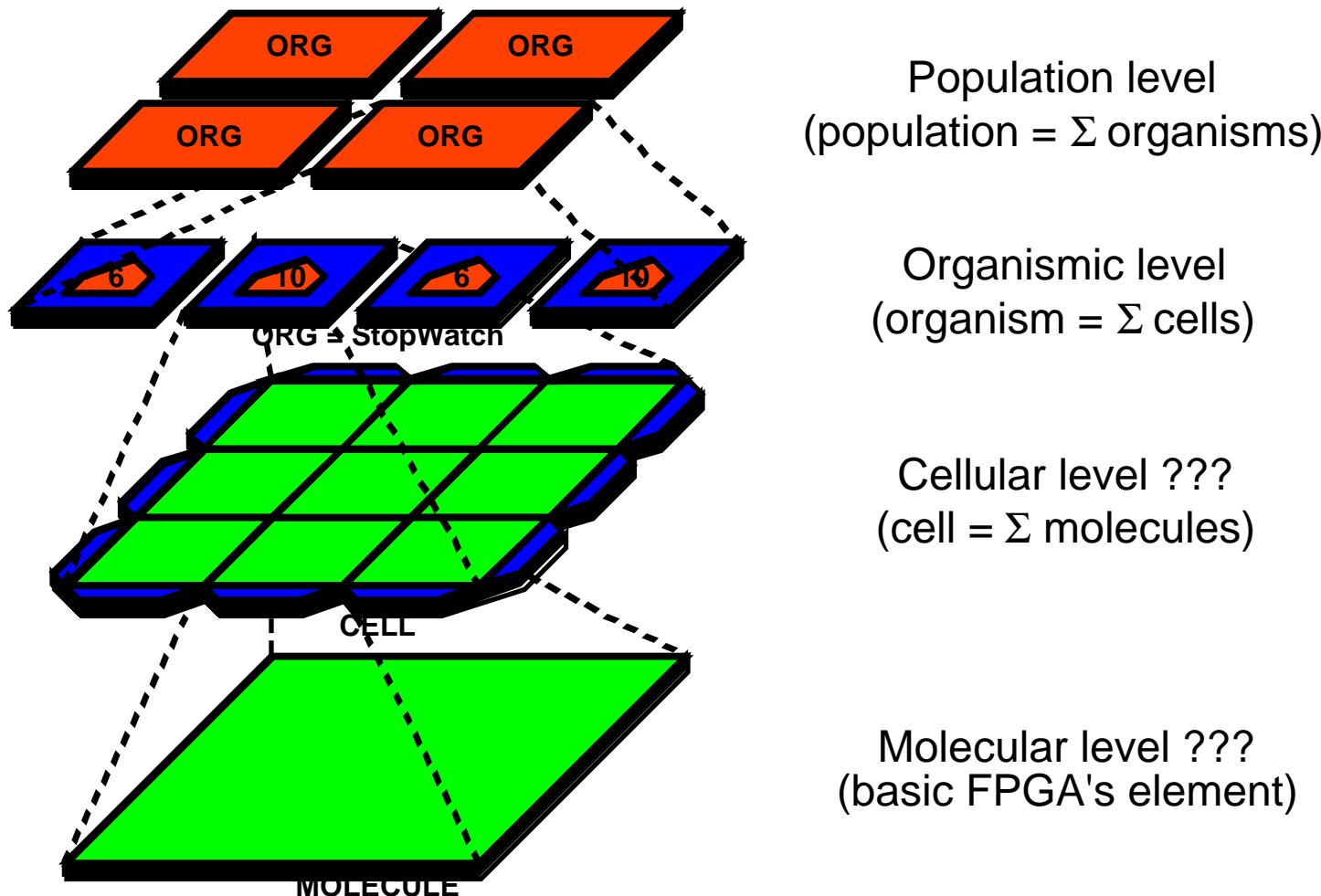



MUXTREE Molecule

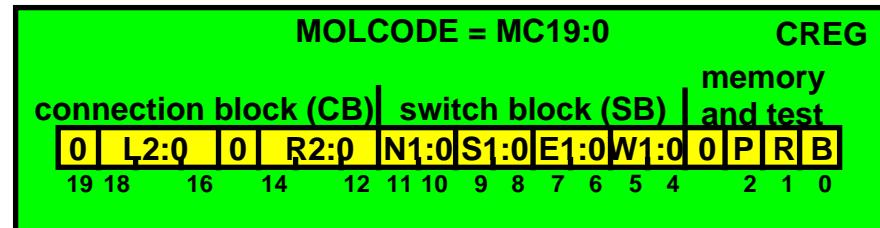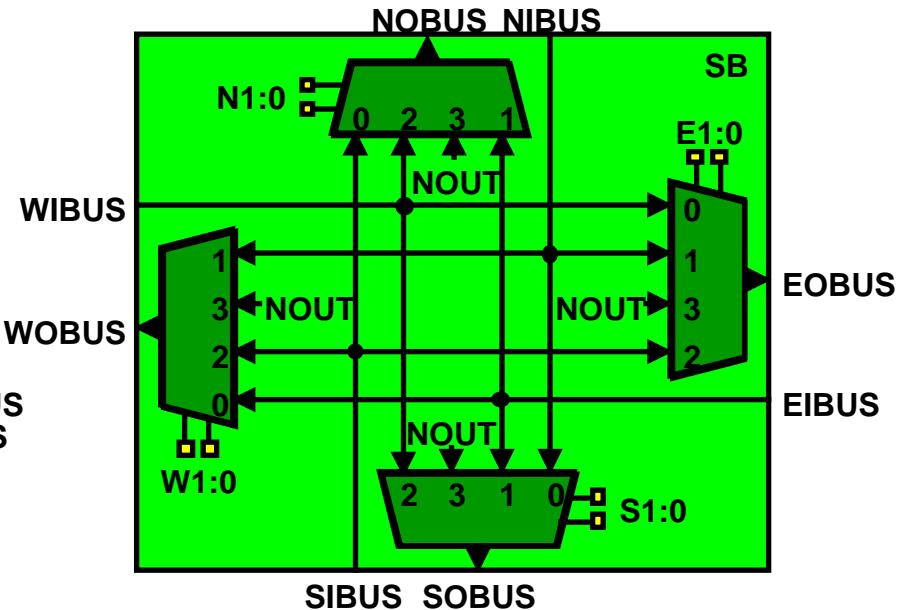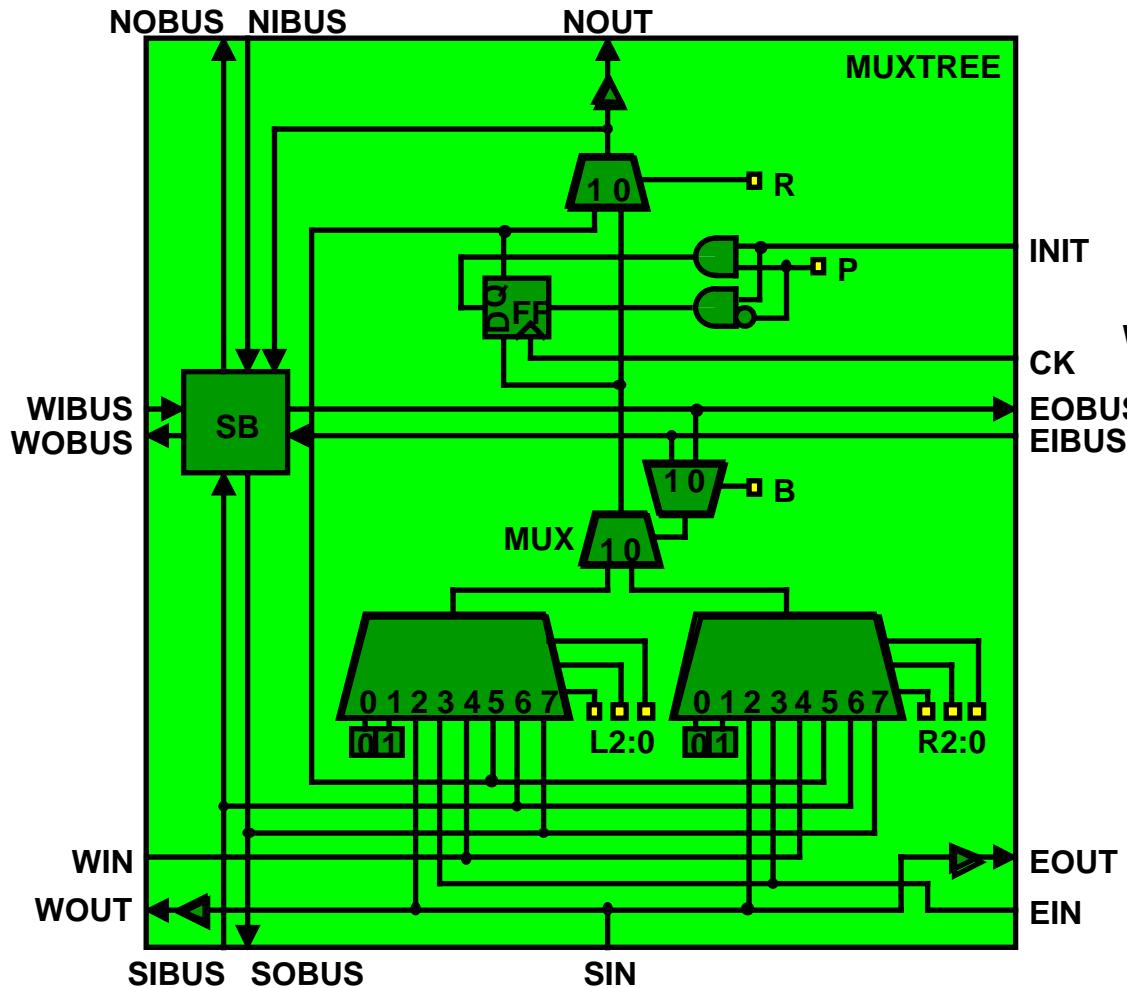

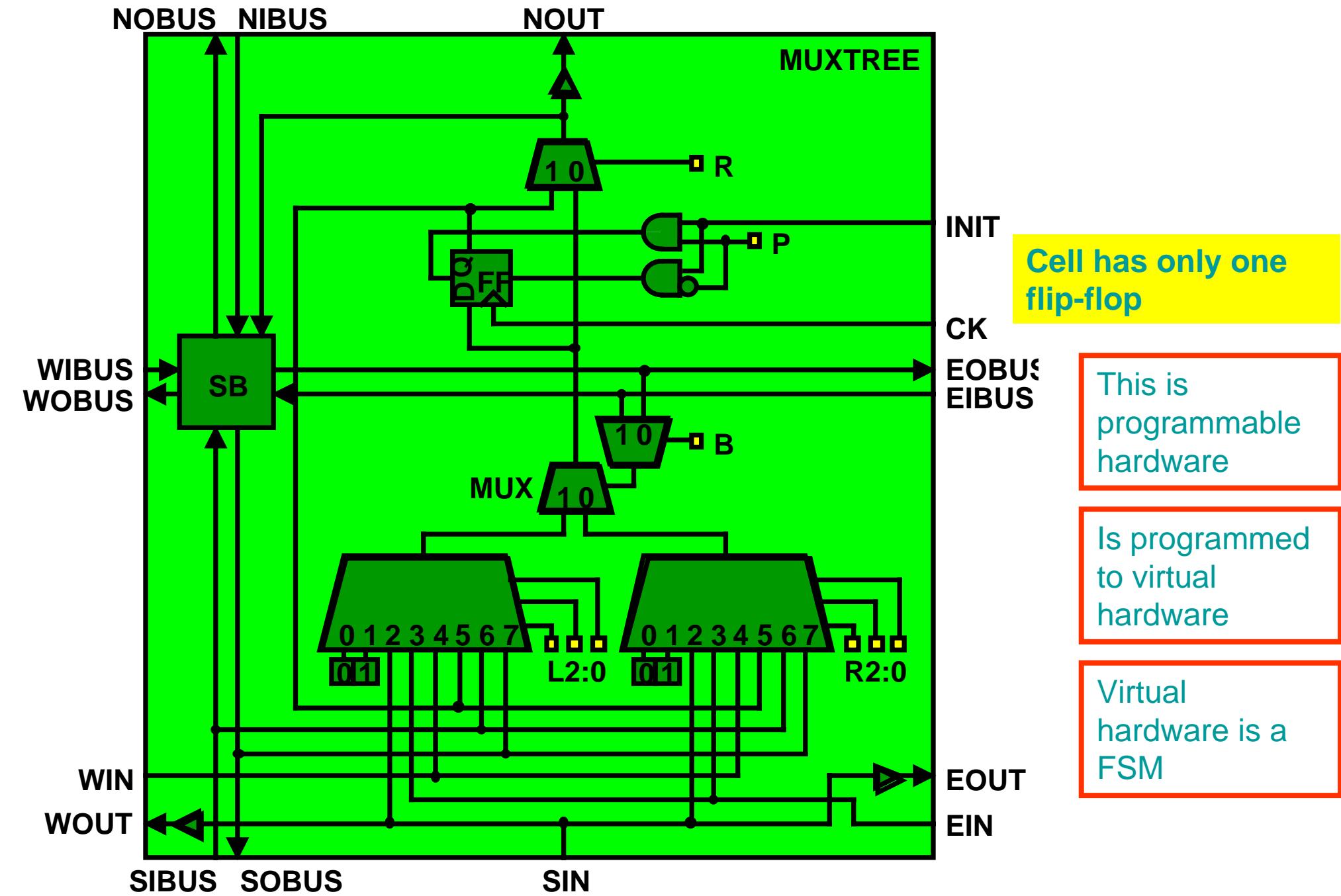

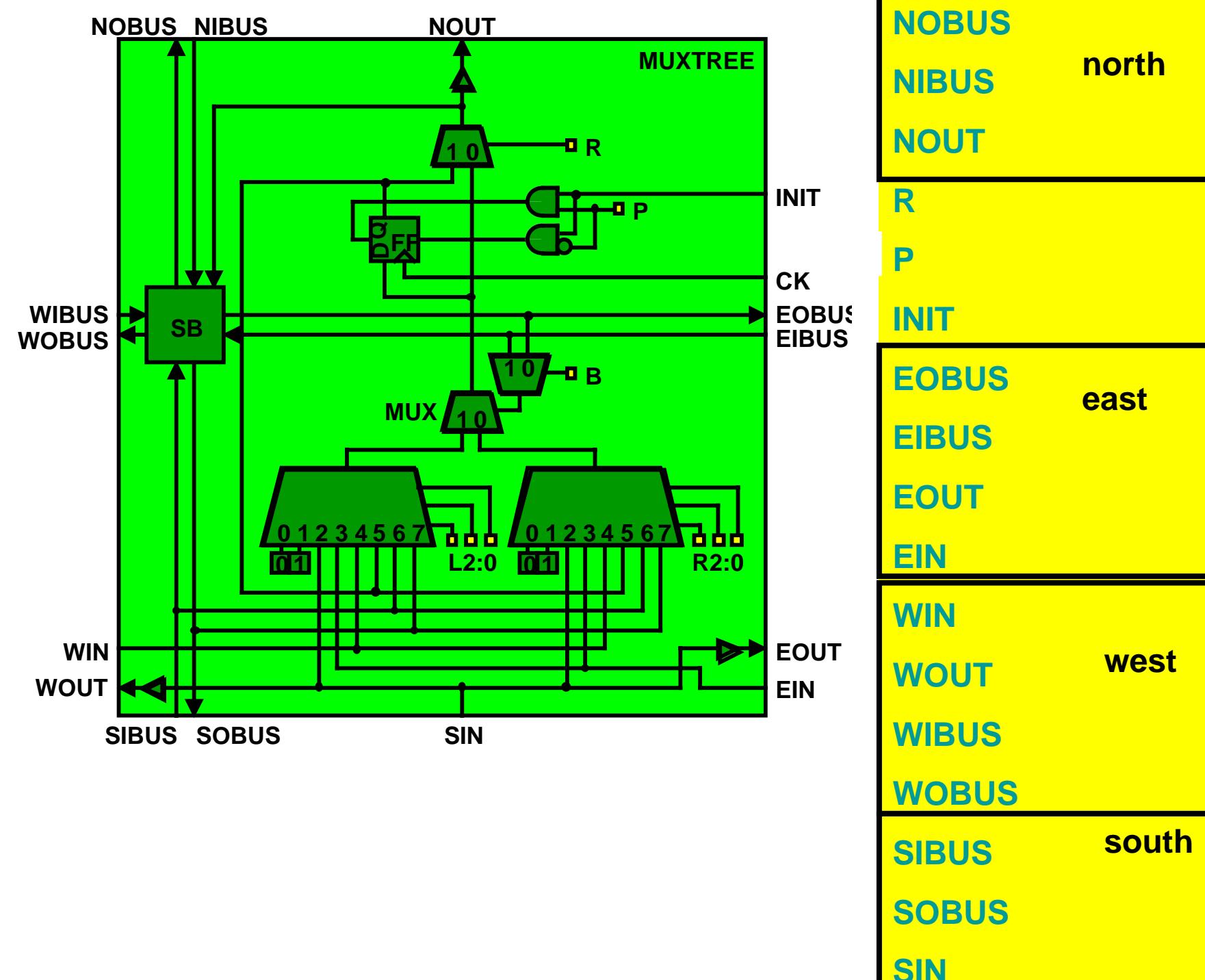


Space Divider

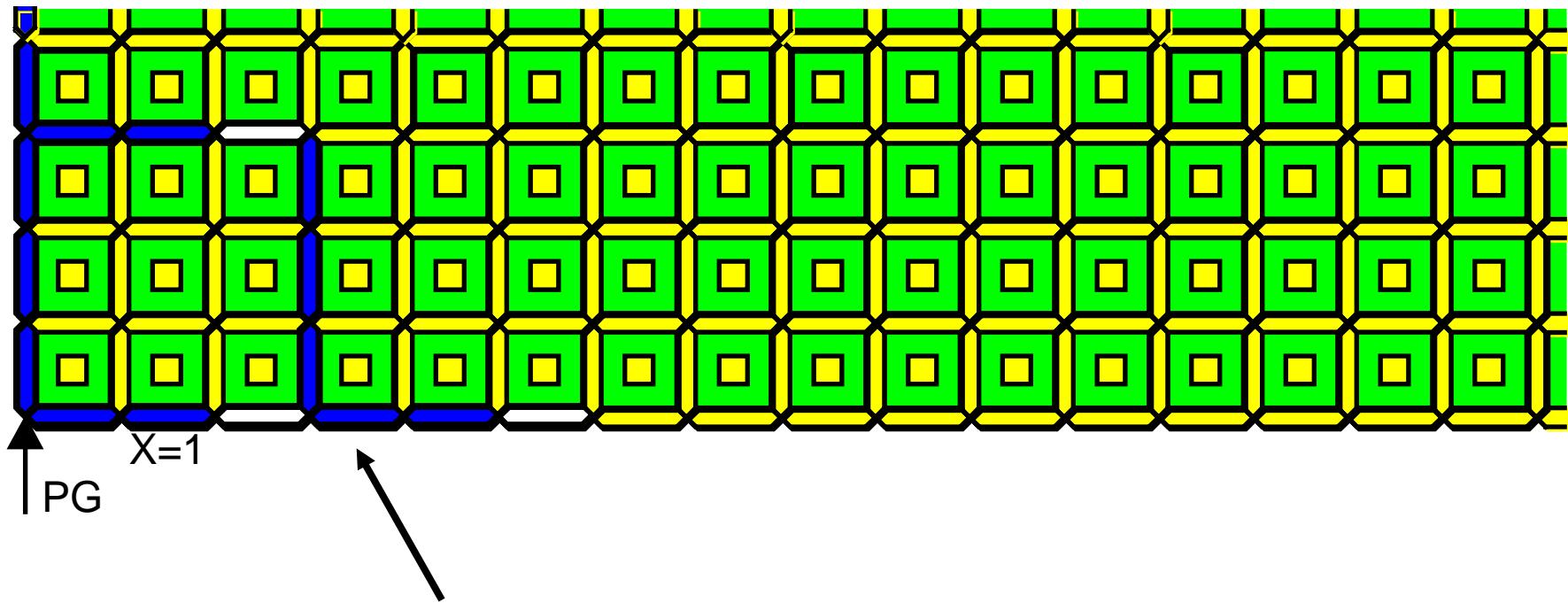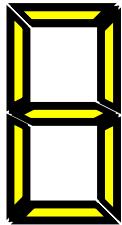


Separation concerns only some signals


Space Divider

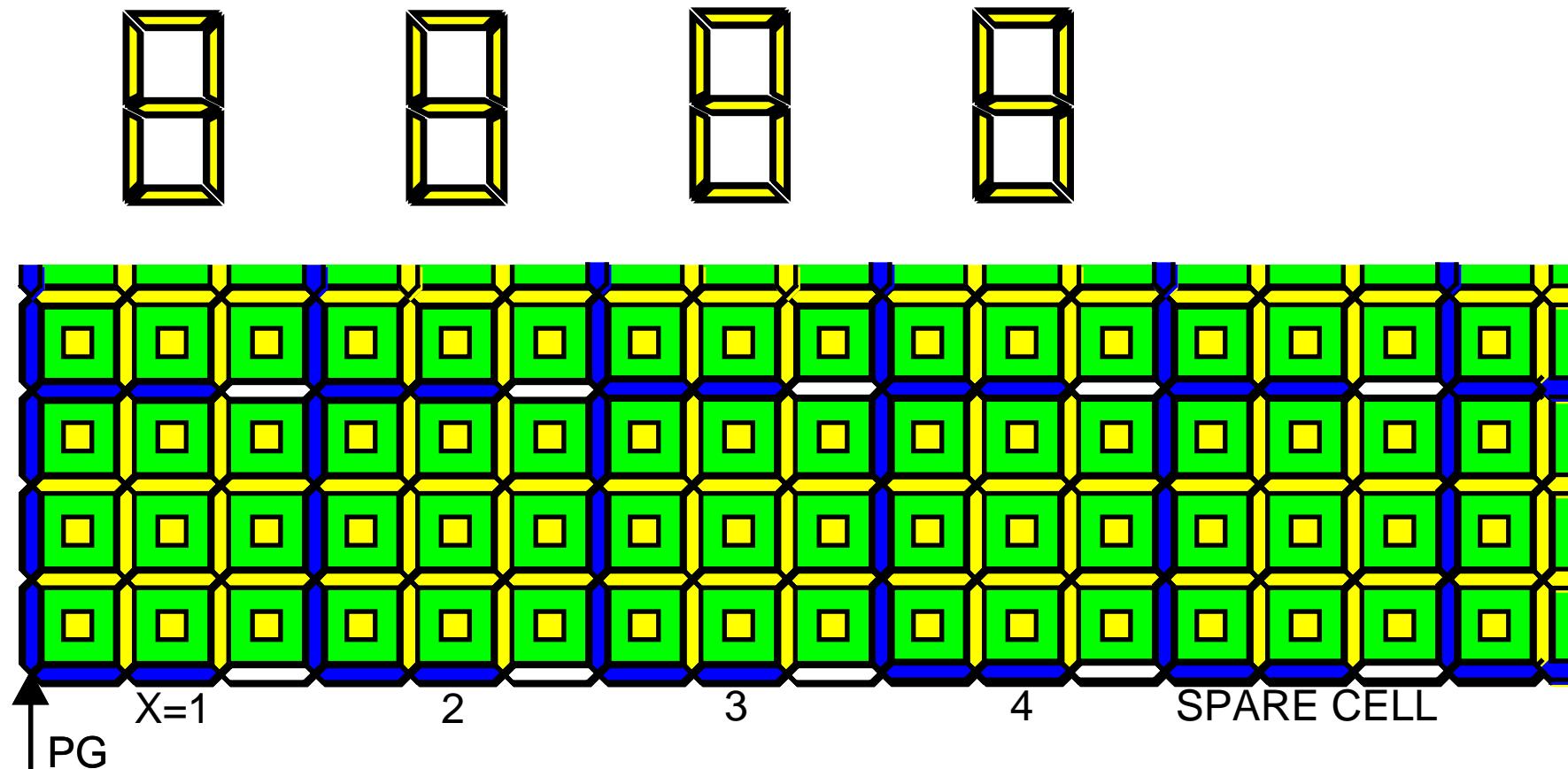


Cellular Self-Replication

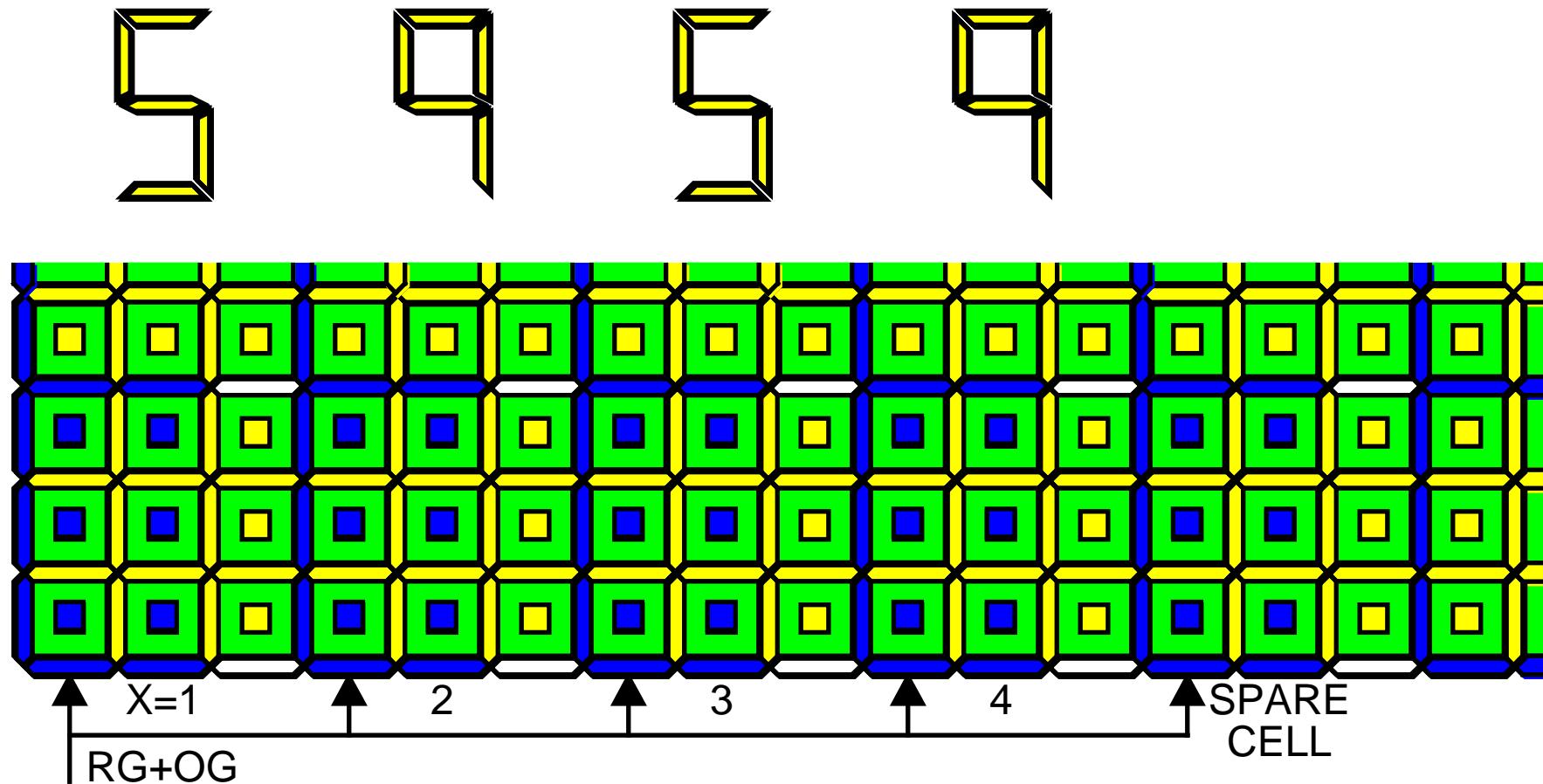

Cellular Self-Repair

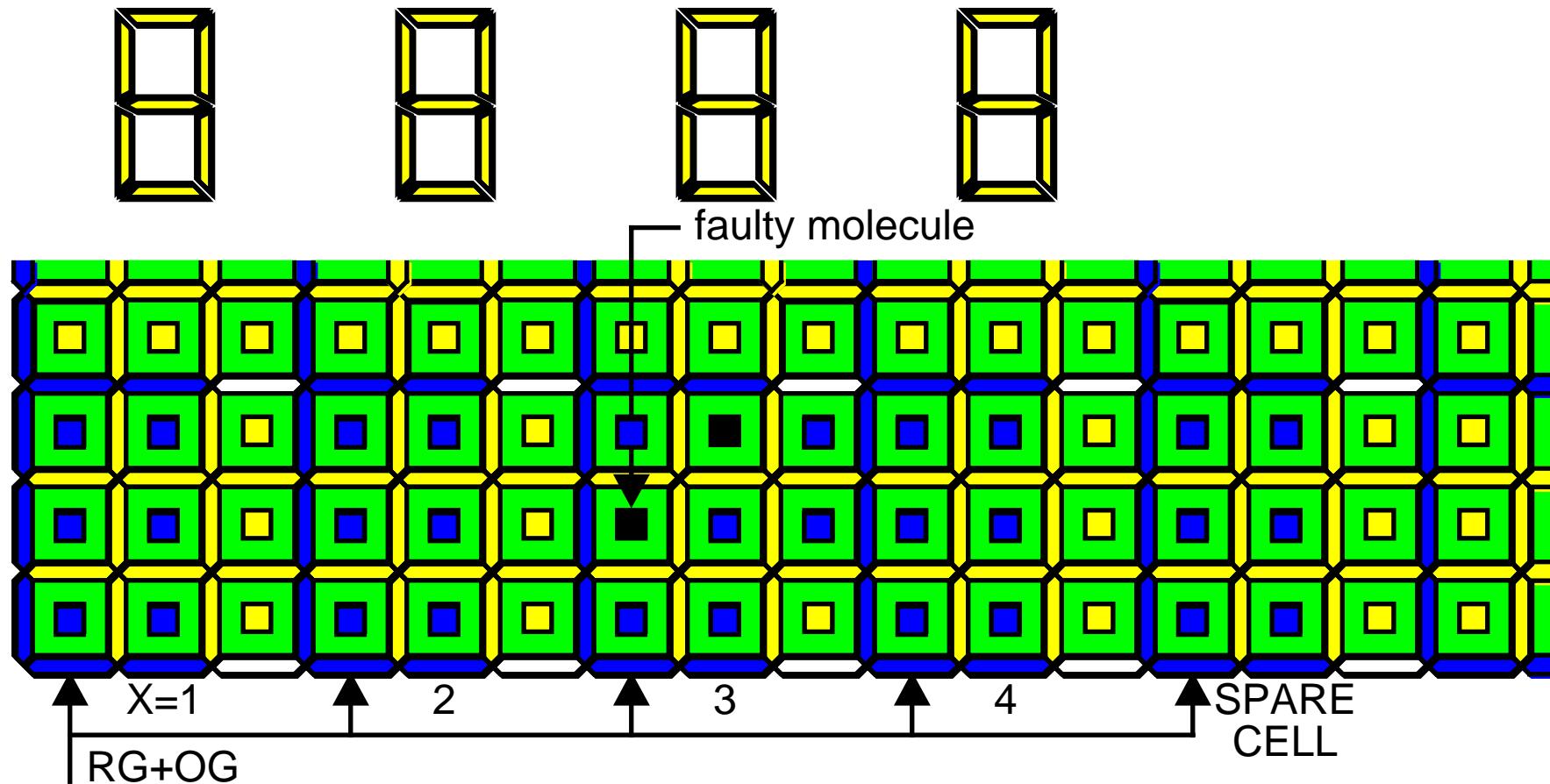



Cellular Self-Repair

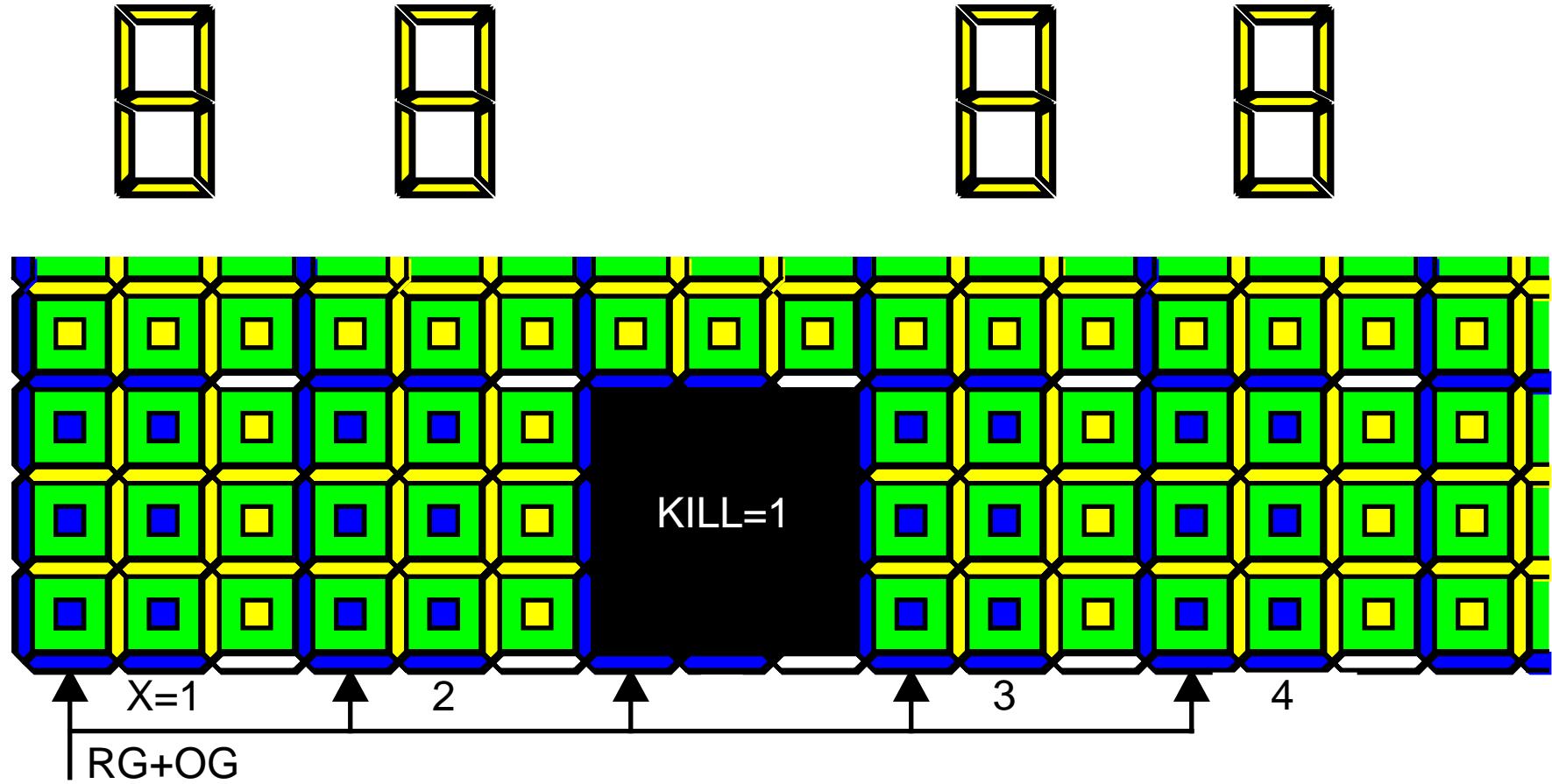


Stuck-at-one, stuck-at-zero fault
models


Molecular Implementation

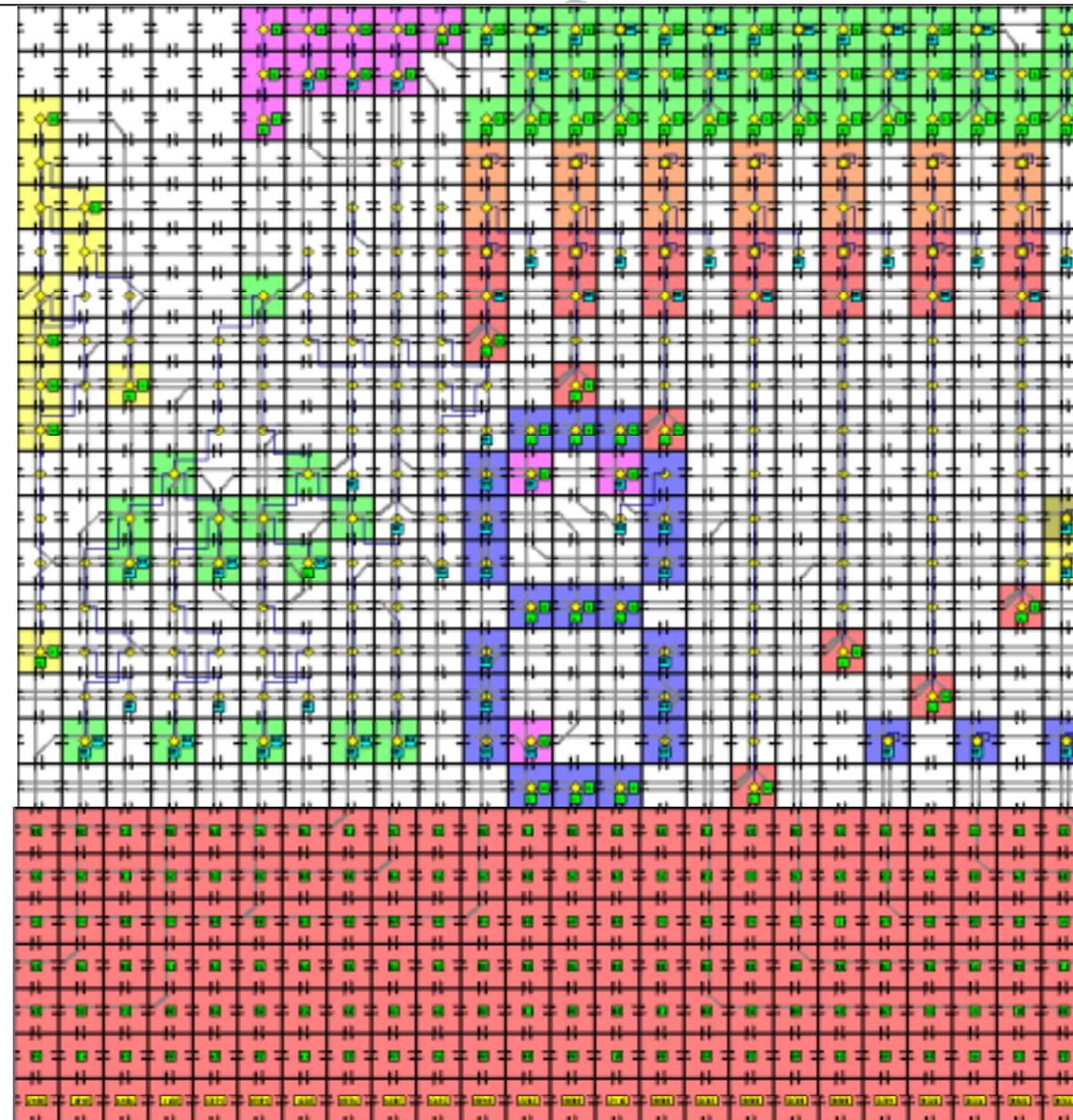

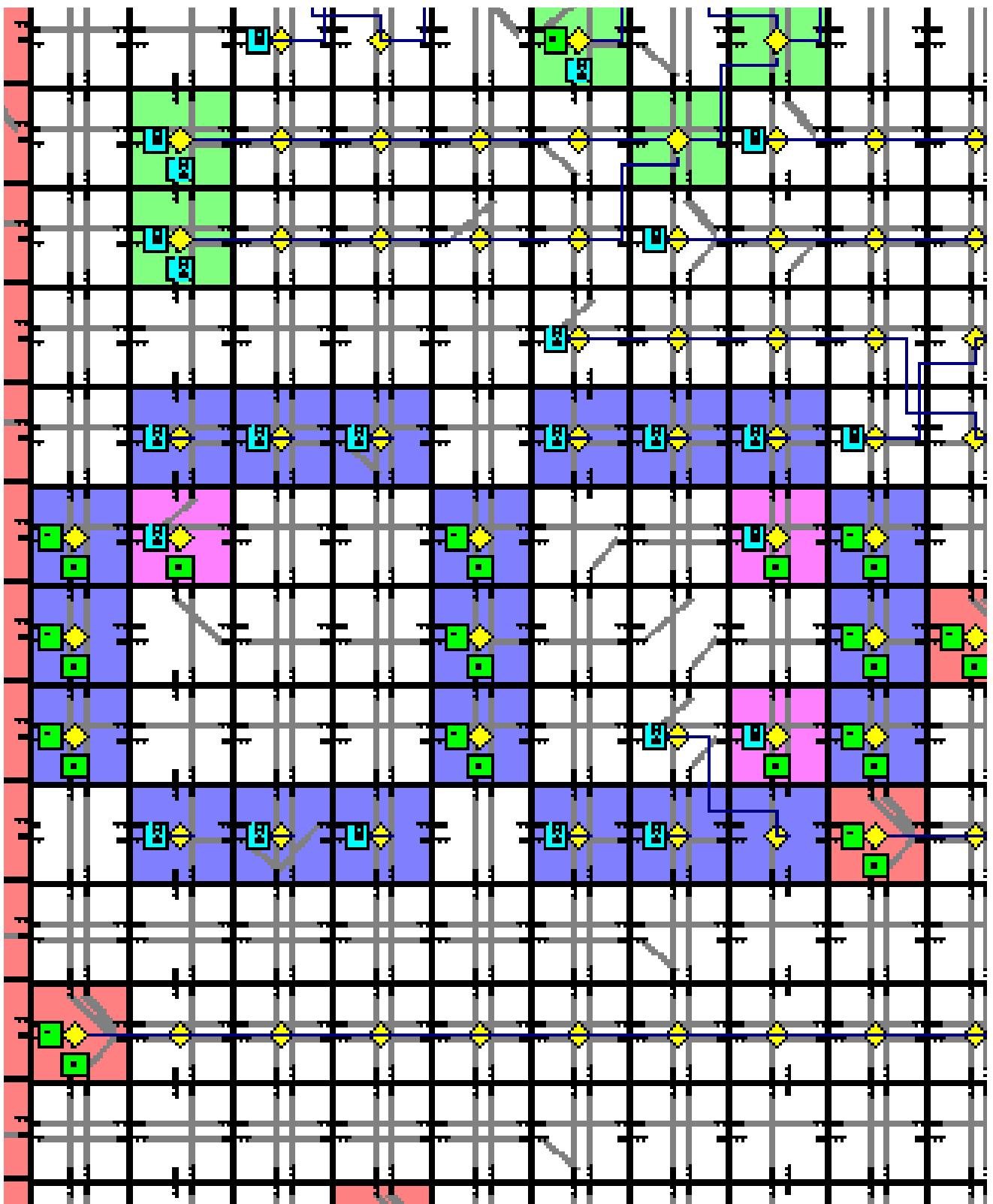


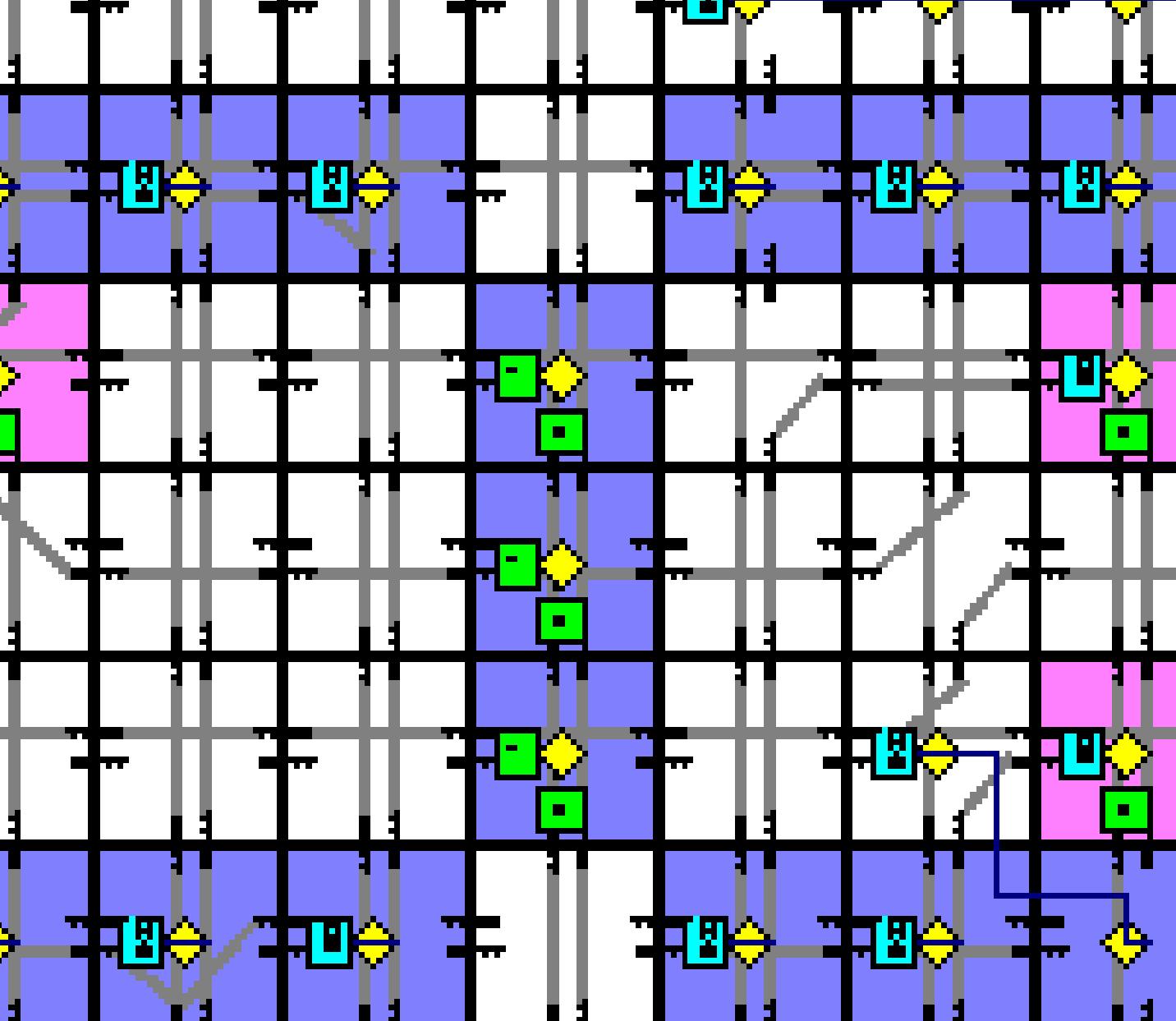

Embryonics Landscape

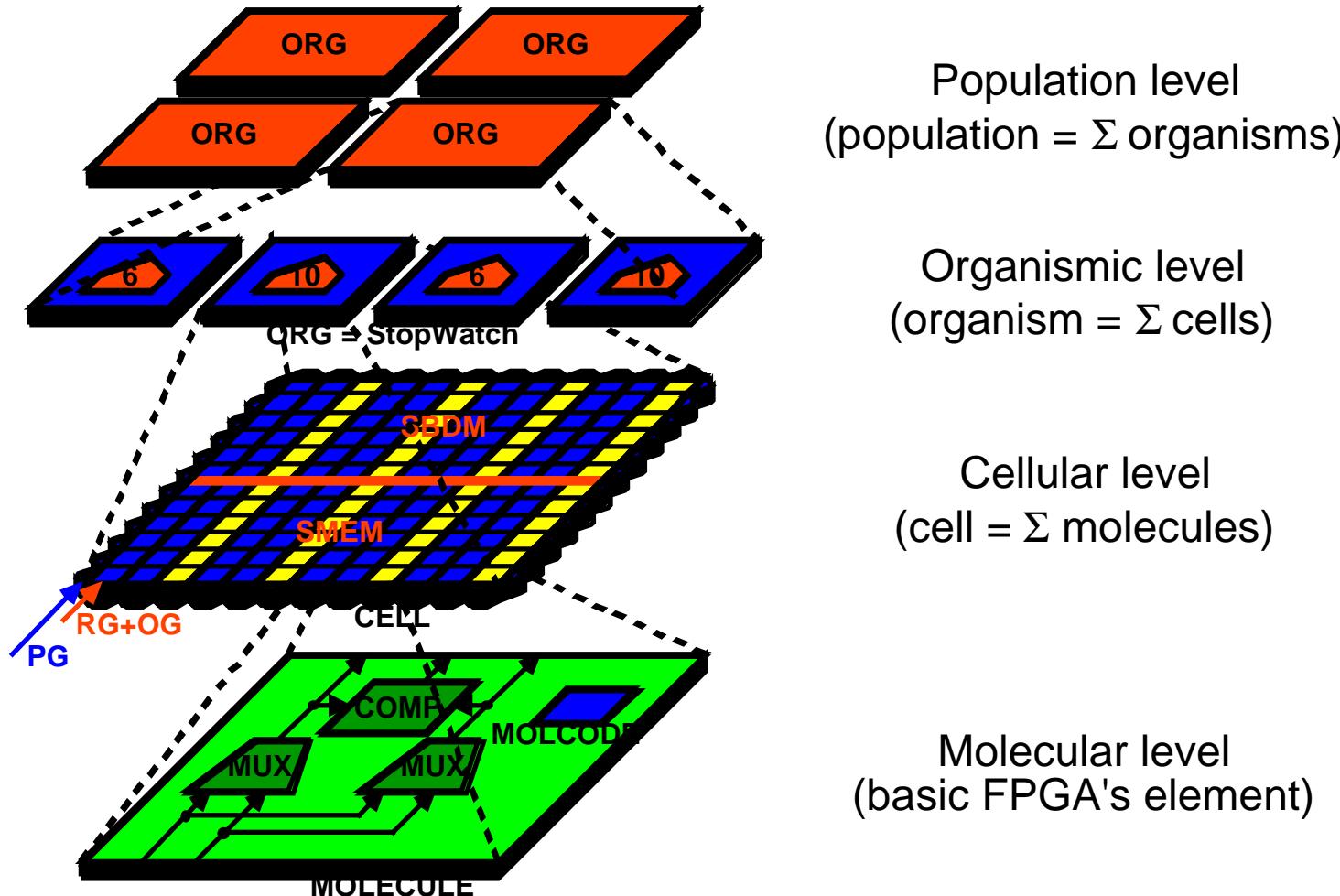

Artificial Genome

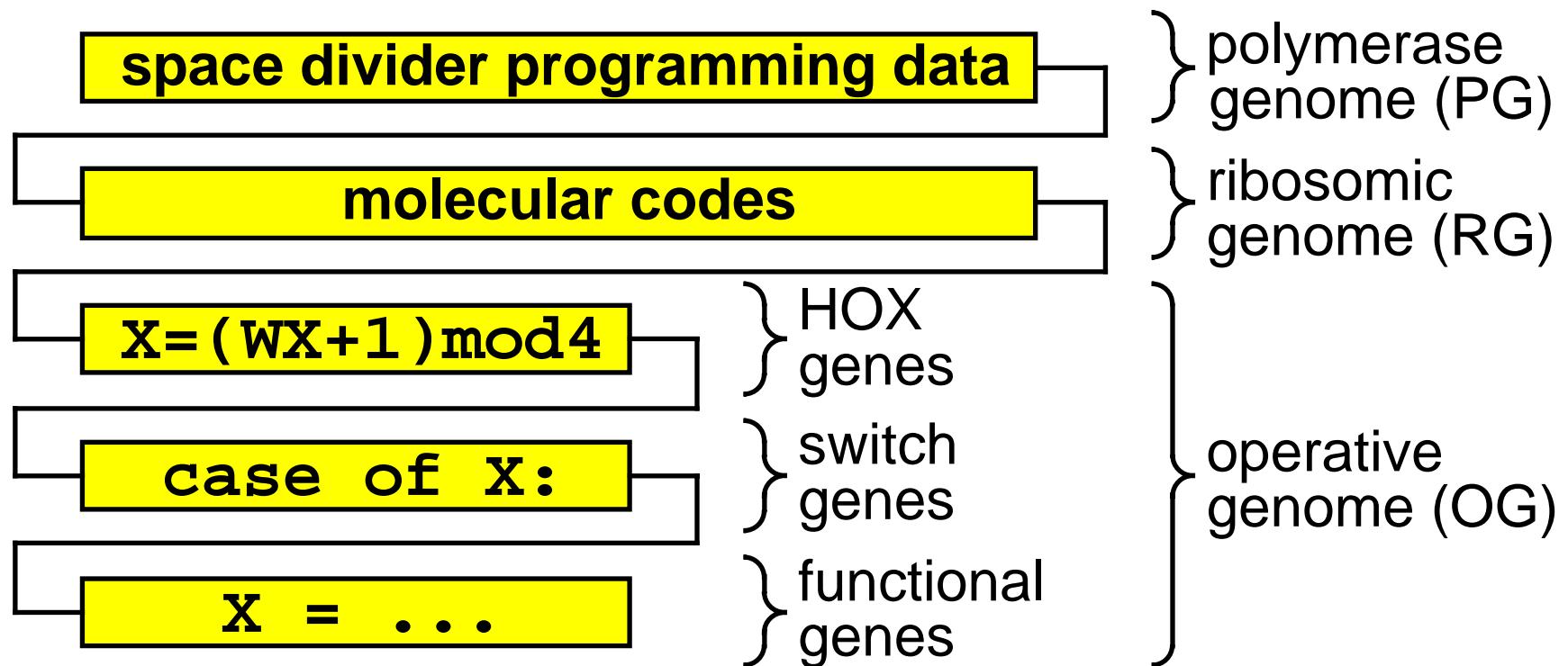

Problems to solve

- Draw a modulo 6 counter using only flip-flops and multiplexed constants
- Do the same for module 10 counter.
- Design a complete watch, as in this lecture from such elements.
- Explain a methodology of realizing arbitrary autonomous machines in the switch/constant cellular model
- Explain how to realize arbitrary state machine with single input in this model