

Multiple-Valued Quantum Logic Synthesis

2002 International Symposium on New Paradigm VLSI Computing

December 12, 2002, Sendai, Japan,

- **Marek A. Perkowski***, **Anas Al-Rabadi[^]** and **Pawel Kerntopf⁺**

- *Department of Electrical Engineering and Computer Science, Korea Advanced Institute of Science and Technology (**KAIST**), 373-1 Gusong-dong, Yusong-gu, Daejeon 305-701, KOREA, *mperkows@ee.kaist.ac.kr*
- [^] Department of Electrical and Computer Engineering, Portland State University, Portland, Oregon, 97207-0751, 1900 S.W. Fourth Ave. *alrabadi@ee.pdx.edu*
- ⁺Institute of Computer Science, Warsaw University of Technology, Nowowiejska 15/19, 00-665 Warsaw, POLAND, *pke@ii.pw.edu.pl*

What size of
(binary)
Quantum
Computers can
be build in
year 2002?


- *7 bits*



Is logic synthesis
for quantum
computers a
practical research
subject?

*Yes, it is a useful technique for
physicists who are mapping logic
operations to NMR computers.*


CAD for physicists.

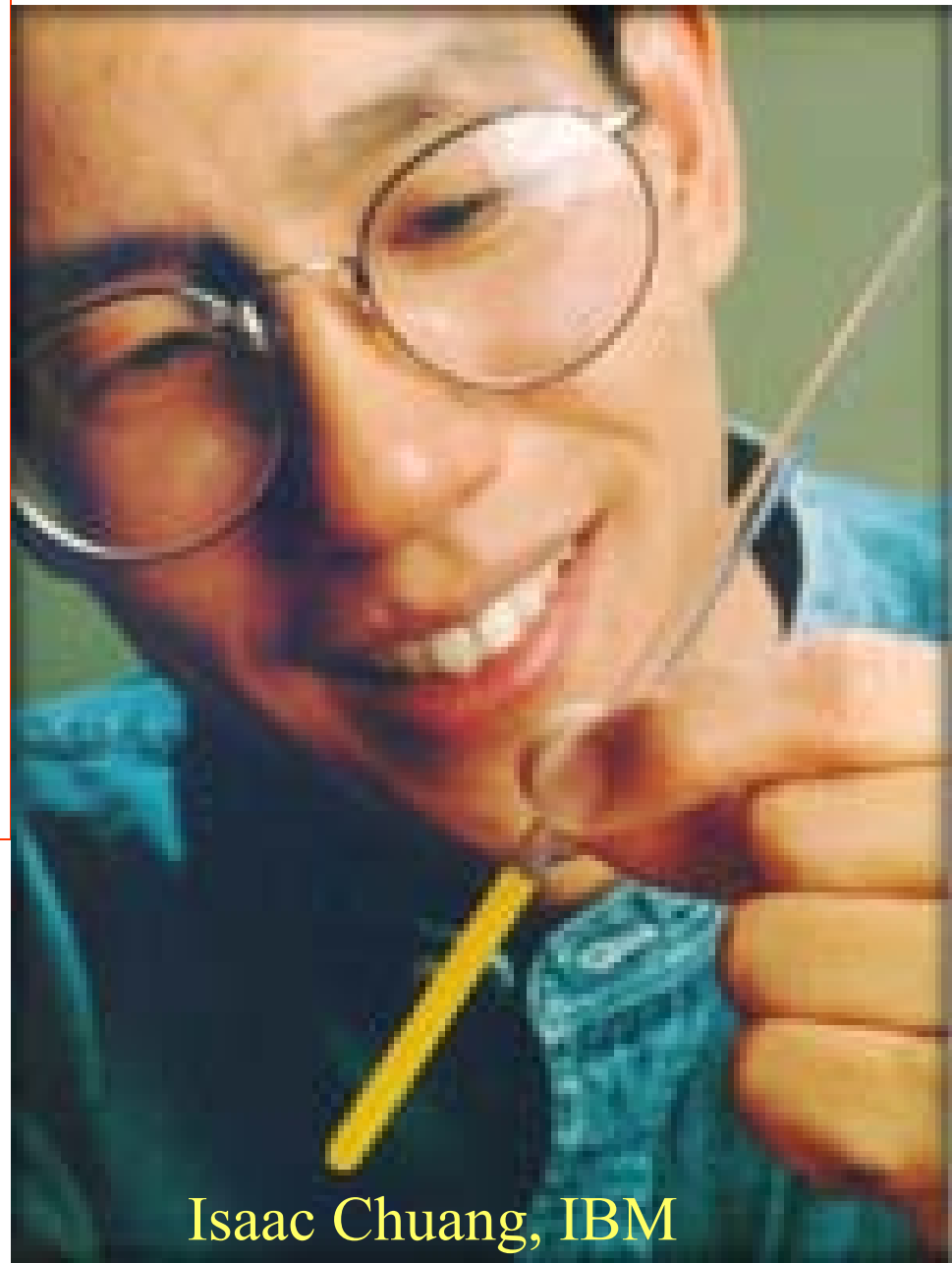


Isaac Chuang, IBM

5 qubit 215 Hz Q. Processor

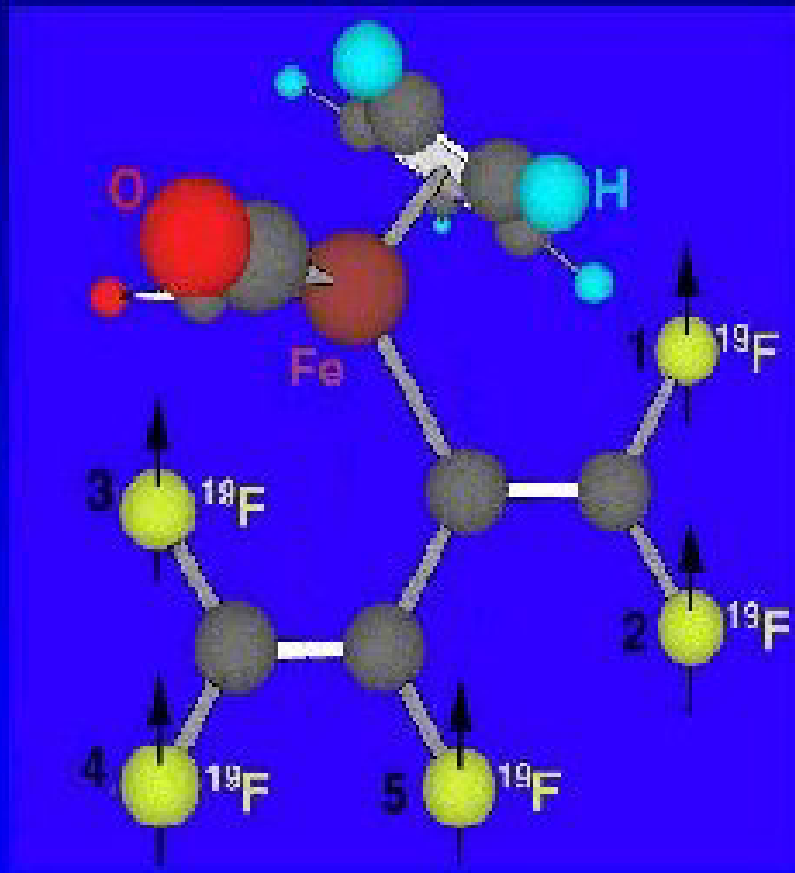(Vandersypen, Steffen, Breyta Yannoni, Cleve, and Chuang, 2000)




• The Molecule

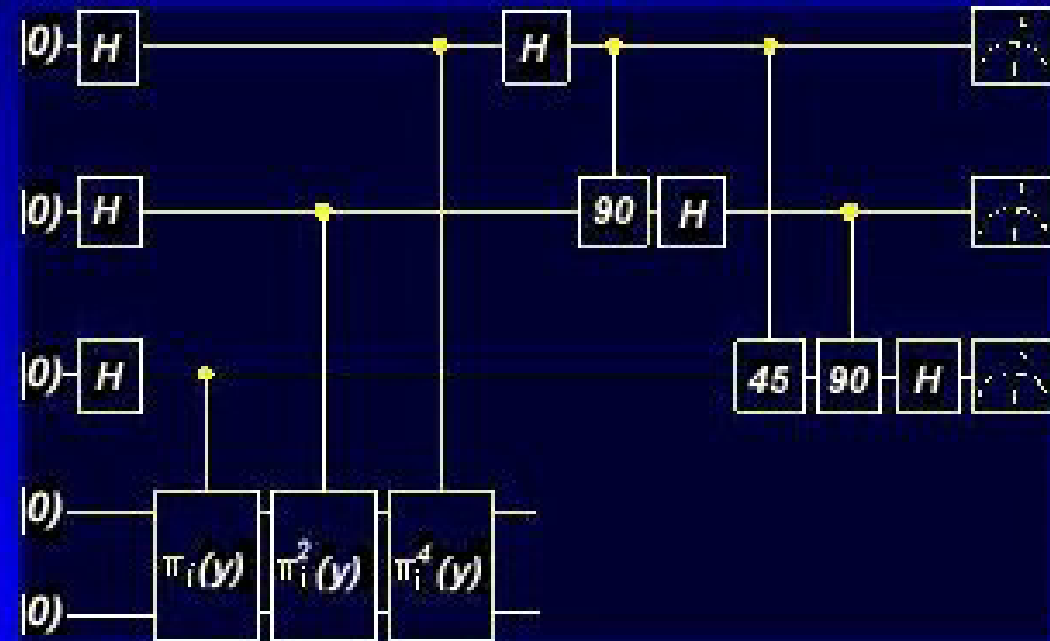


• Quantum Circuit

$T_2 > 0.3$ sec ; ~ 200 gates


The molecule

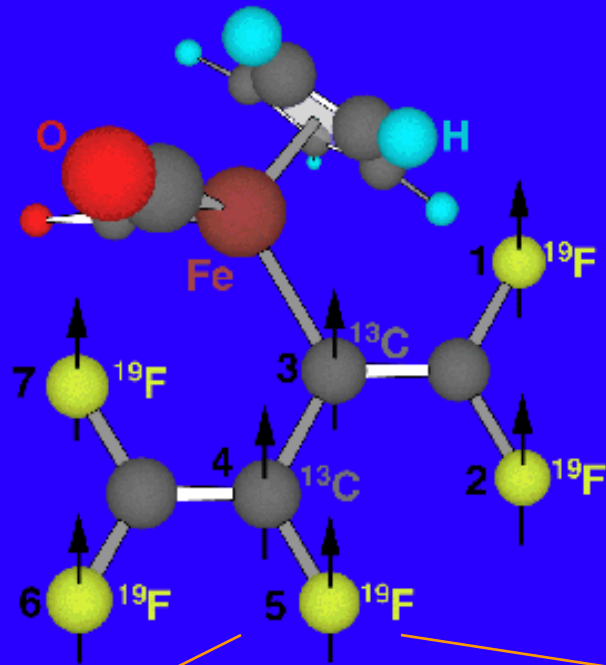

i	$\omega_i/2$	$T_{1,i}$	$T_{2,i}$	J_{7i}	J_{6i}	J_{5i}	J_{4i}	J_{3i}	J_{2i}
1	-22052.0	5.0	1.3	-221.0	37.7	6.6	-114.3	14.5	25.16
2	489.5	13.7	1.8	18.6	-3.9	2.5	79.9	3.9	
3	25088.3	3.0	2.5	1.0	-13.5	41.6	12.9		
4	-4918.7	10.0	1.7	54.1	-5.7	2.1			
5	15186.6	2.8	1.8	19.4	59.5				
6	-4519.1	45.4	2.0	68.9					
7	4244.3	31.6	2.0						

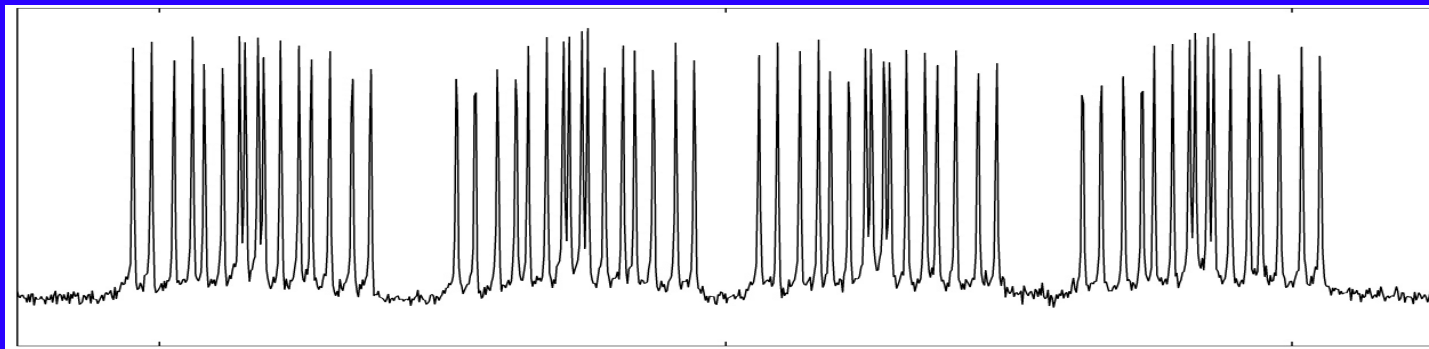


Pulse Sequence

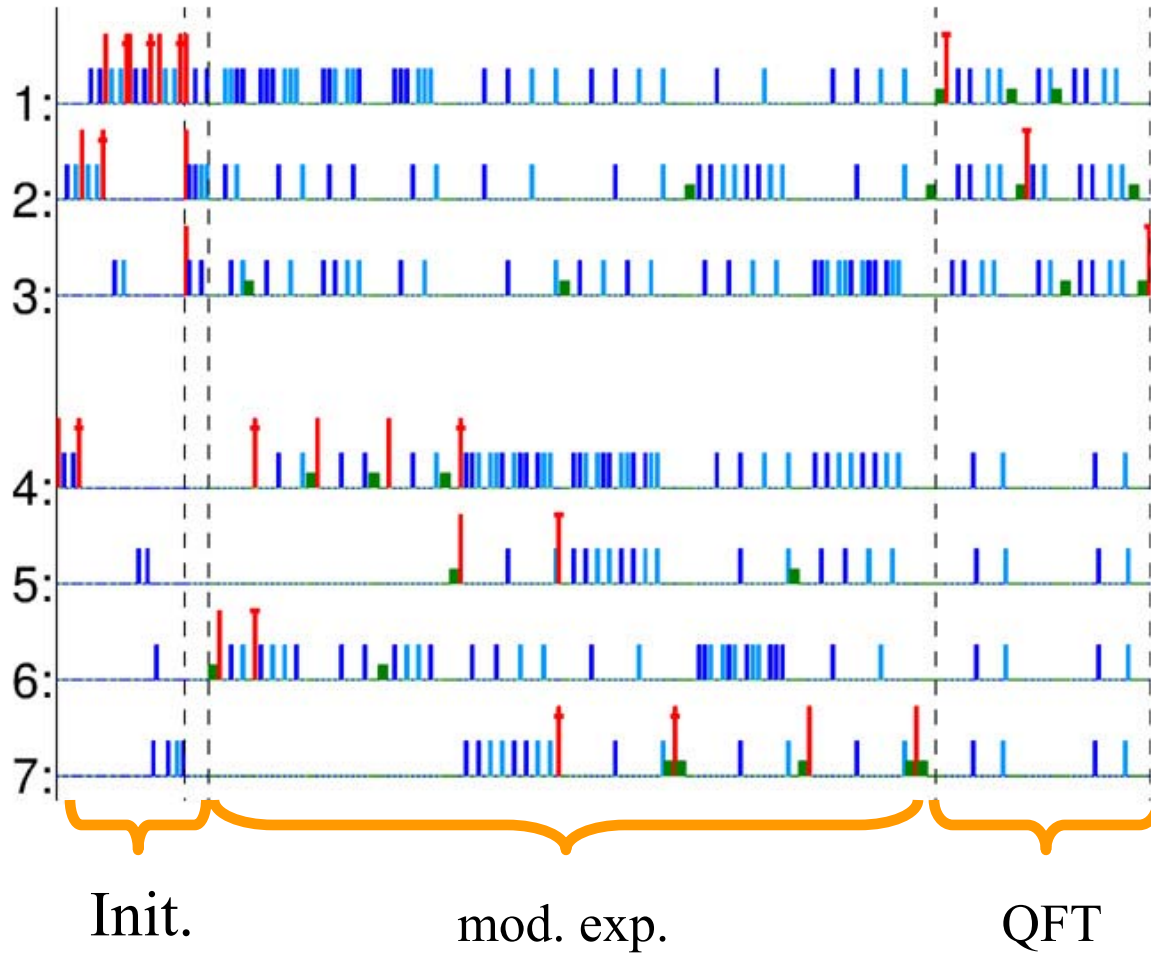

~ 300 RF pulses || ~ 750 ms duration

Results: Spectra

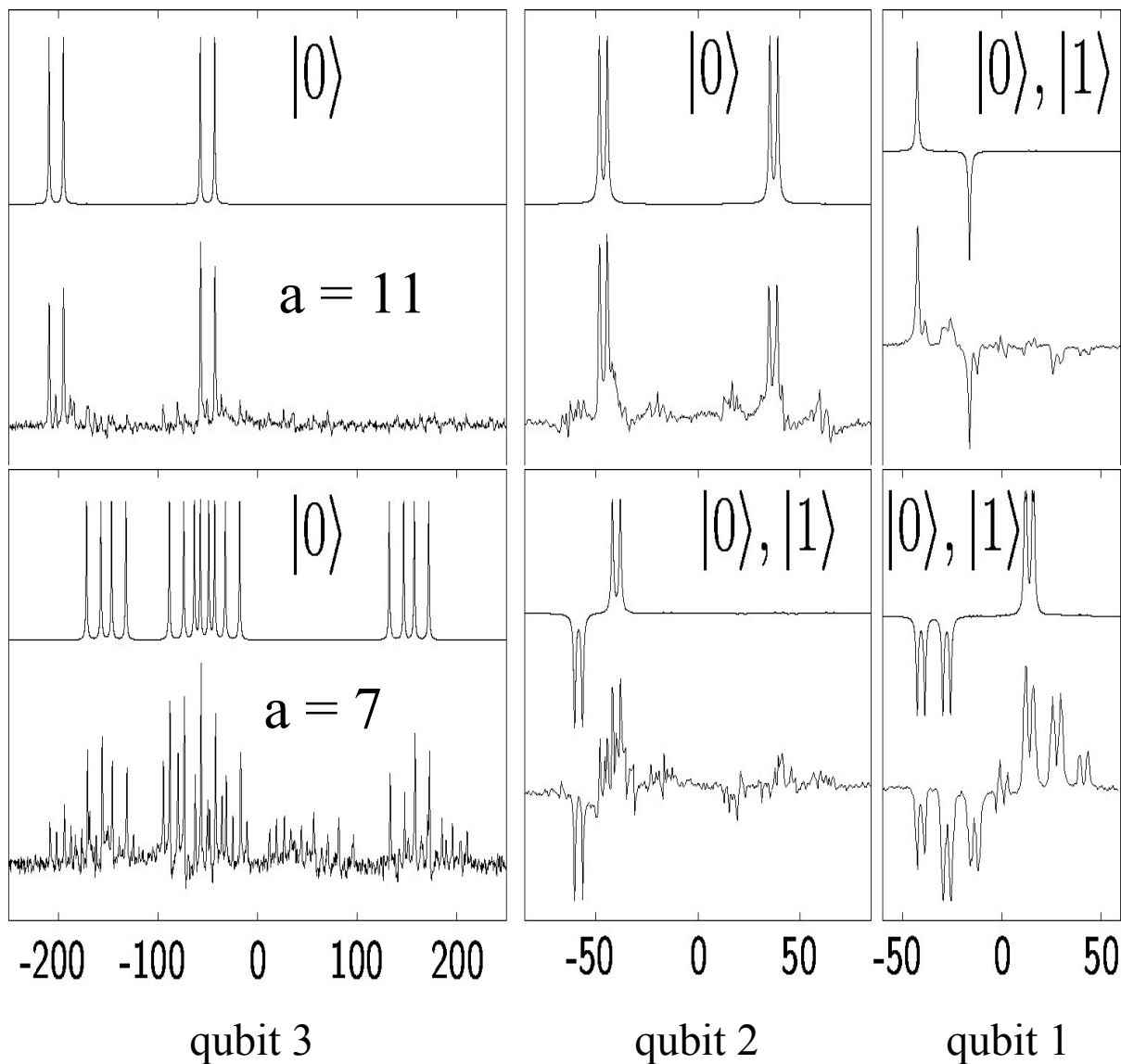

Mixture of $|0\rangle, |4\rangle$
 $2^{3/4} = r = 2$
 $\gcd(11^{2/2} \pm 1, 15) = 3, 5$




$$15 = 3 \cdot 5$$



Mixture of $|0\rangle, |2\rangle, |4\rangle, |6\rangle$
 $2^{3/2} = r = 4$
 $\gcd(7^{4/2} \pm 1, 15) = 3, 5$

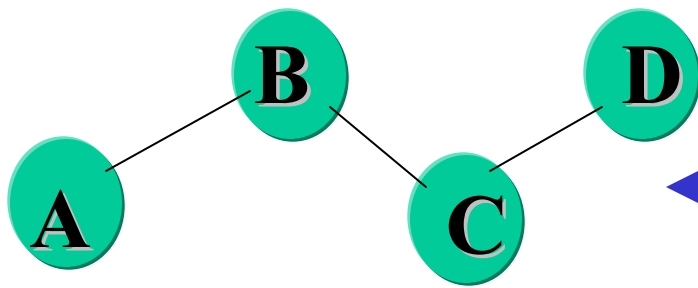
Problem

- We would like to assume that any two quantum wires can interact, but we are limited by the **realization constraints**
- Structure of atomic bonds in the molecule **determines neighborhoods** in the circuit.
- This is similar to restricted routing in FPGA layout - *link between logic and layout synthesis* known from CMOS design **now appears in quantum**.
- Below we are interested only in the so-called **“permutation circuits”** - their unitary quantum matrices are permutation matrices




Quantum wires A and C are not neighbors

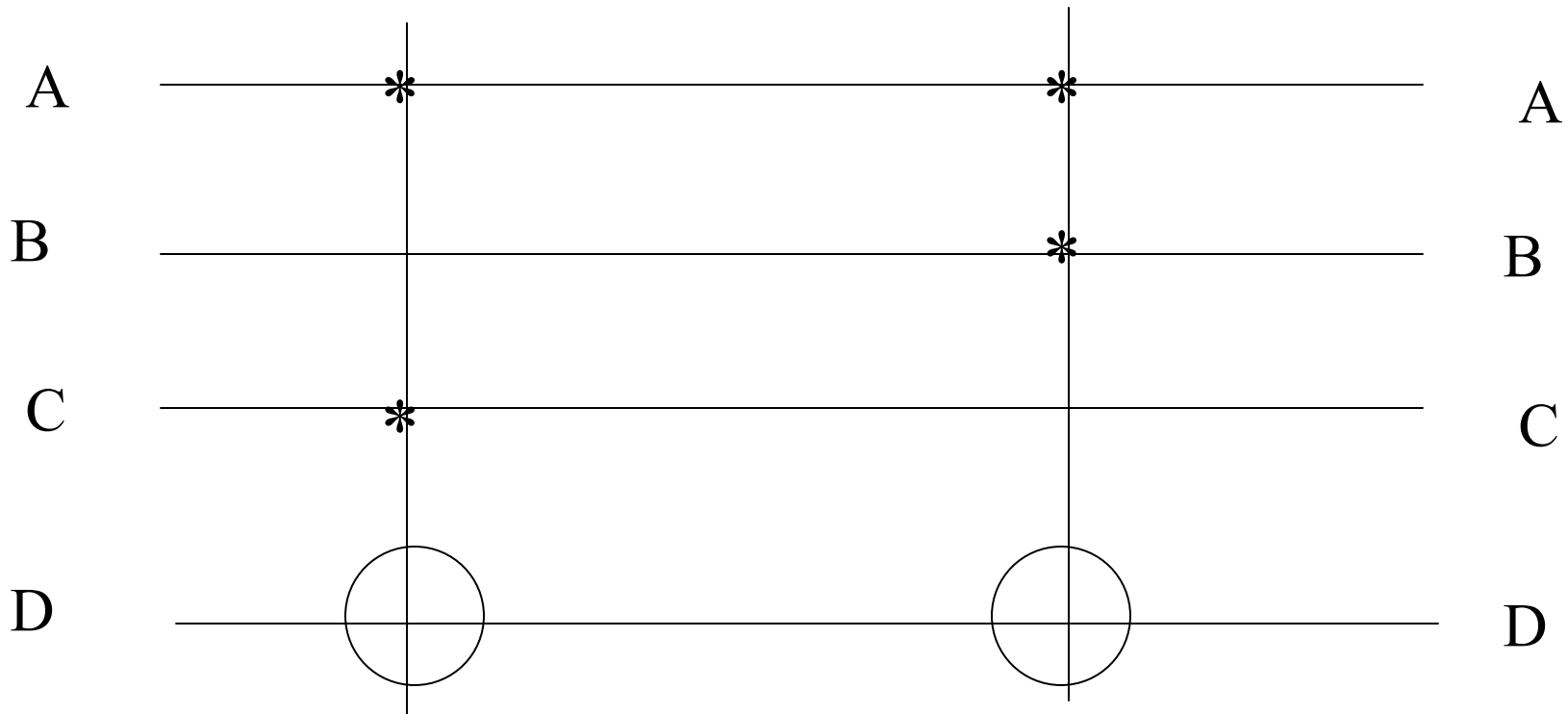A schematics with two binary Toffoli gates




This is a result of our ESOP minimizer program, but this is not realizable in NMR for the above molecule


So I modify the schematics as follows

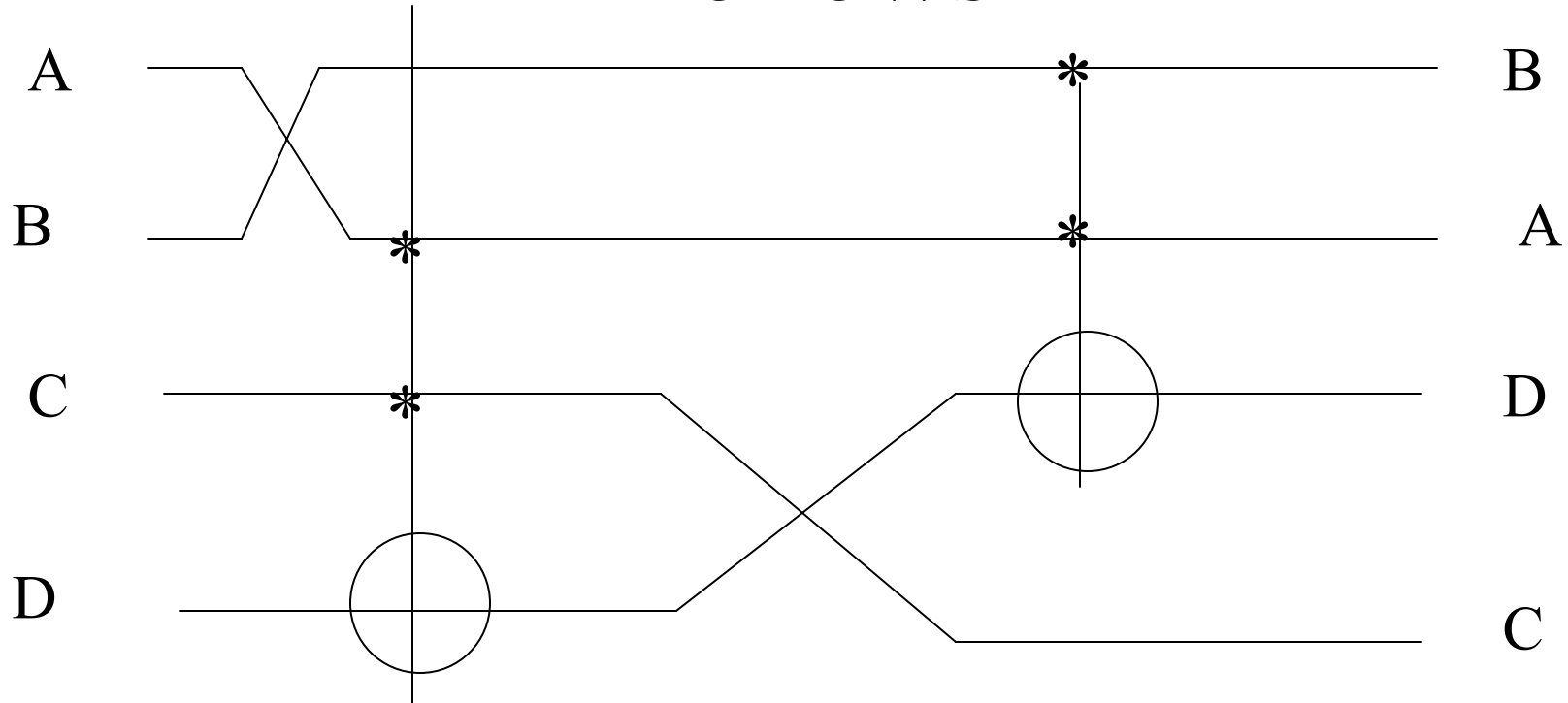

But this costs me two swap gates

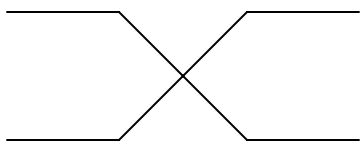

Costs 3
Feynmans

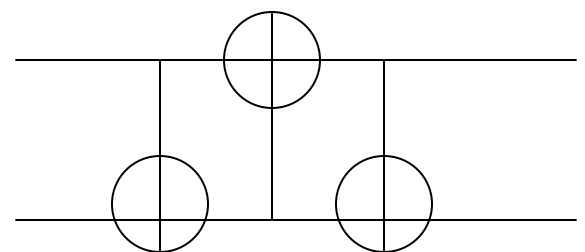

Solution

- One solution to connection problem in VLSI has been to **increase the number of values** in wires.
- Have a **“quantum wire”** have **more than two** eigenstates.
- Increase from superpositions of 2^n to **superpositions of 3^n**
- Basic gate in quantum logic is a **$2*2$** (2-qubit gate). We have to build from such gates.

Can we build multiple-valued Quantum Computers in year 2002?

- *In principle, yes*

Has one tried?


No.

Gates, yes

Qudits not qubits

- In ternary logic, the notation for the superposition is $\alpha|0\rangle + \beta|1\rangle + \gamma|2\rangle$.
- These intermediate states cannot be distinguished, rather a **measurement** will yield that the qudit is in one of the basis states, $|0\rangle$, $|1\rangle$ or $|2\rangle$.
- The **probability** that a measurement of a qudit yields state $|0\rangle$ is $|\alpha|^2$, the probability is $|\beta|^2$ for state $|1\rangle$ and $|\gamma|^2$ for state γ . The **sum of these probabilities** is one. The absolute values are required, since in general, α β and γ are

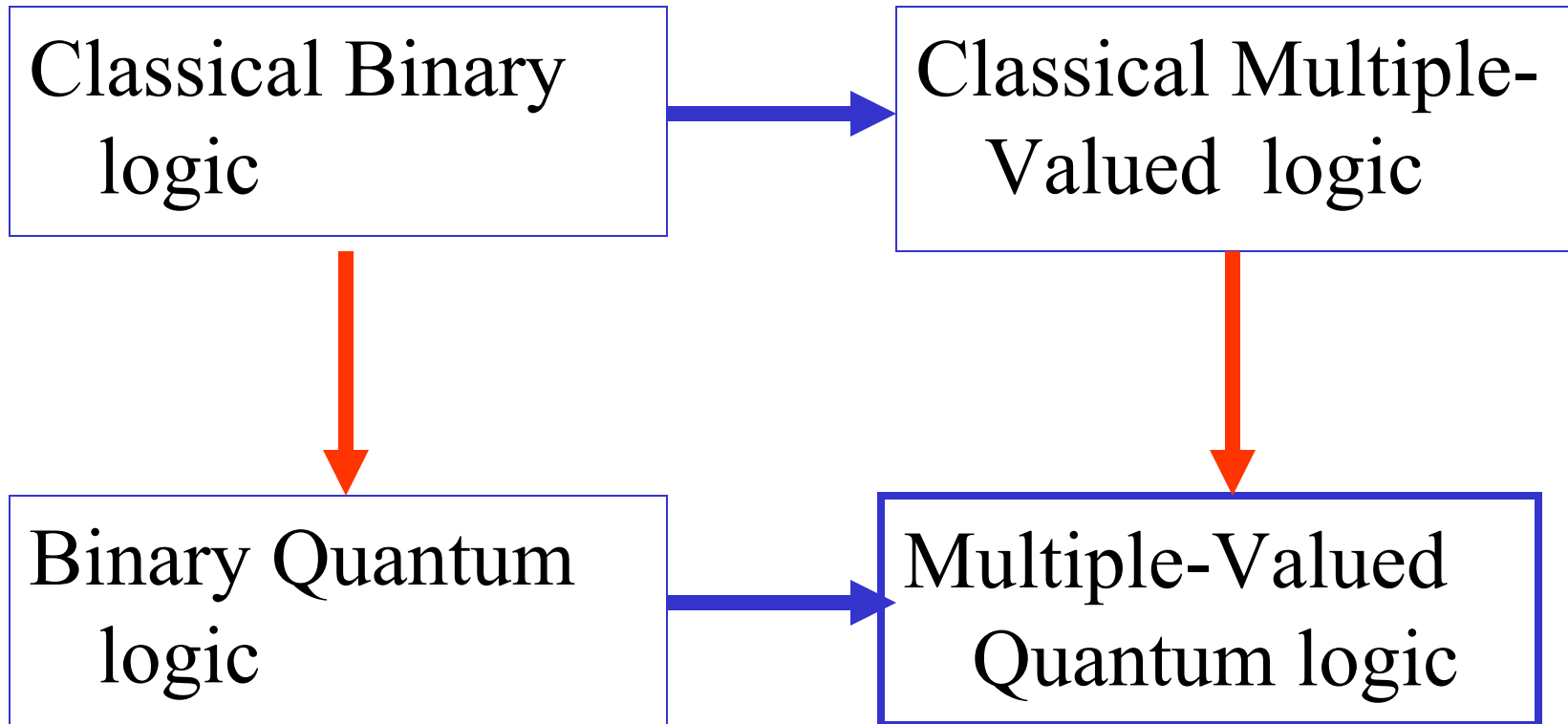The concept of Multiple-Valued Quantum Logic



What is known?

- **Mattle** 1996 - *Trit* $|0\rangle$, $|1\rangle$, $|2\rangle$
- Chau 1997 - *qudit, error correcting quantum codes*
- Ashikhmin and Knill 1999, *MV codes*.
- Gottesman, Aharonov and Ben-Or 1999 - *MV fault tolerant gates*.
- Burlakov 1999 - *correlated photon realization of ternary qubit*.
- Muthukrishnan and Stroud 2000 - *multi-valued universal quantum logic for linear ion trapped devices*.
- Picton 2000 - *Multi-valued reversible PLA*.
- Perkowski, Al-Rabadi, Kerntopf and Portland Quantum Logic Group 2001 - *Galois Field quantum logic synthesis*

What is known?

- Al-Rabadi, 2002 - *ternary EPR and Chrestenson Gate*
- De Vos 2002 - *Two ternary $1*1$ gates and two ternary $2*2$ gates for reversible logic.*
- Zilic and Radecka 2002 - *Super-Fast Fourier Transform*
- Bartlett et al, 2002 - *Quantum Encoding in Spin Systems*
- Brassard, Braunstein and Cleve, 2002 - *Teleportation*
- Rungta, Munro et al *Qudit Entanglement.*

Ternary Galois Field (GF3) operations.







+	0	1	2
0	0	1	2
1	1	2	0
2	2	0	1

(a) Addition

•	0	1	2
0	0	0	0
1	0	1	2
2	0	2	1

(b) Multiplication


Reversible ternary shift operations.

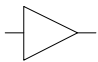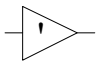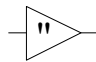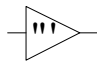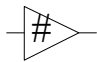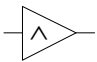Operator Name		Buffer	Single-Shift	Dual-Shift	Self-Shift	Self-Single-Shift	Self-Dual-Shift
Operator symbol & equation		A	$A' = A + 1$	$A'' = A + 2$	$A''' = A + A = 2A$	$A^\# = 2A + 1$	$A^\wedge = 2A + 2$
Gate symbol							
A	0	0	1	2	0	1	2
	1	1	2	0	2	0	1
	2	2	0	1	1	2	0


Conversion of one shift form to another shift form using ternary shift gates

Input	Output					
	A	A'	A''	A'''	$A^\#$	A^\wedge
A						
A'						
A''						
A'''						
$A^\#$						
A^\wedge						

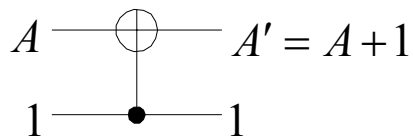
Quantum realization of ternary shift gates.




(a) Single-Shift

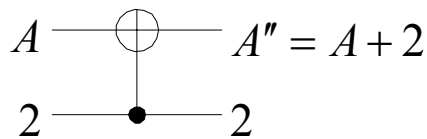


(b) Dual-Shift

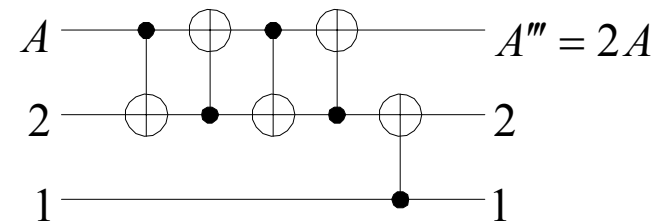

(c) Self-Shift

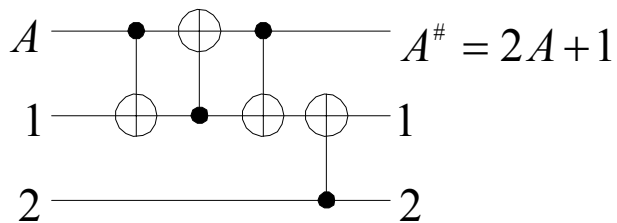


(d) Self-Single-Shift

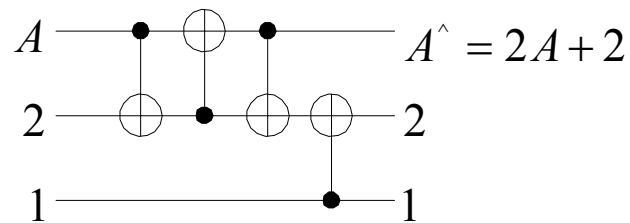



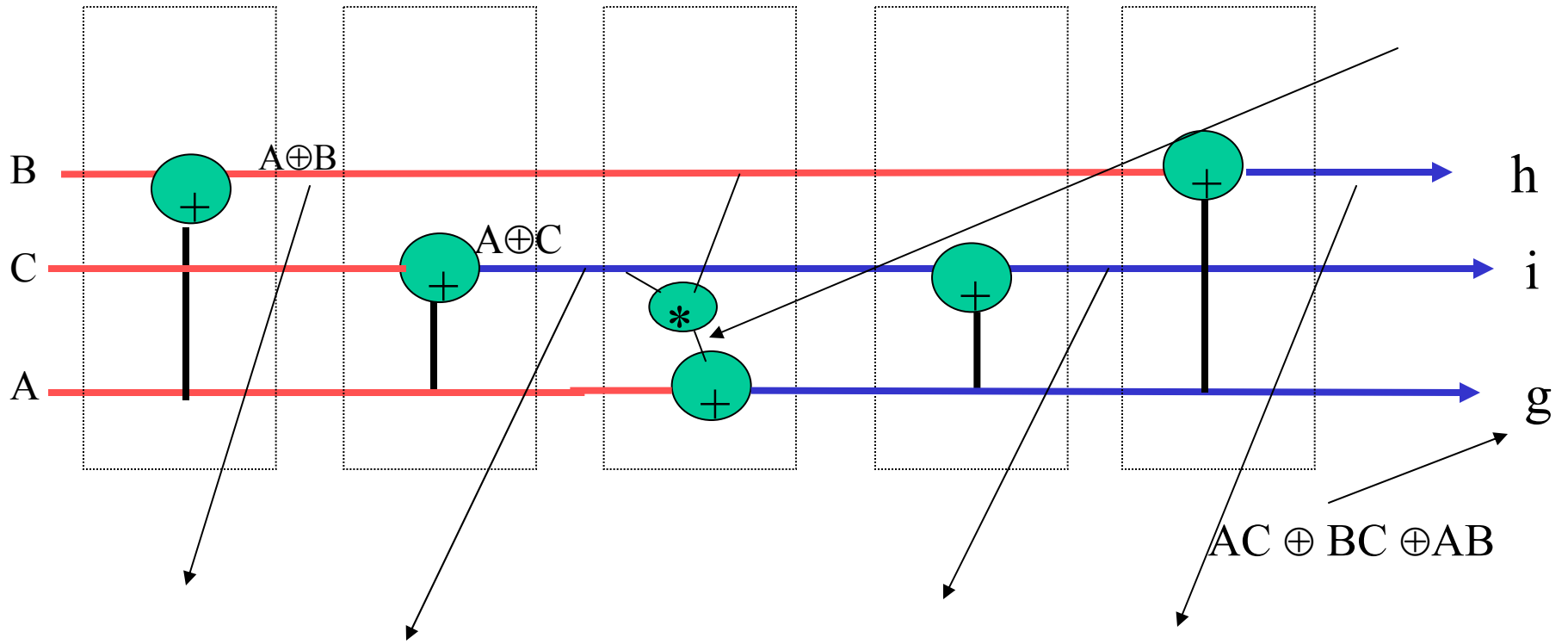
(e) Self-Dual-Shift

Optimal Solution to Ternary Miller Function




Check ternary maps

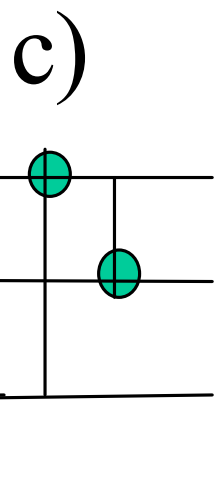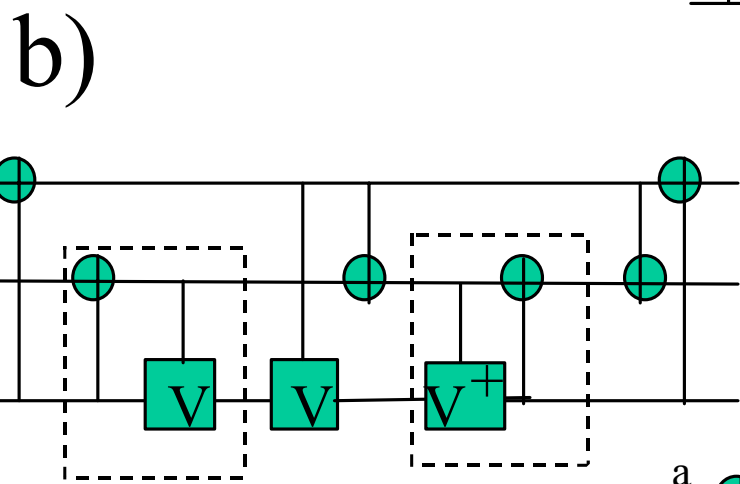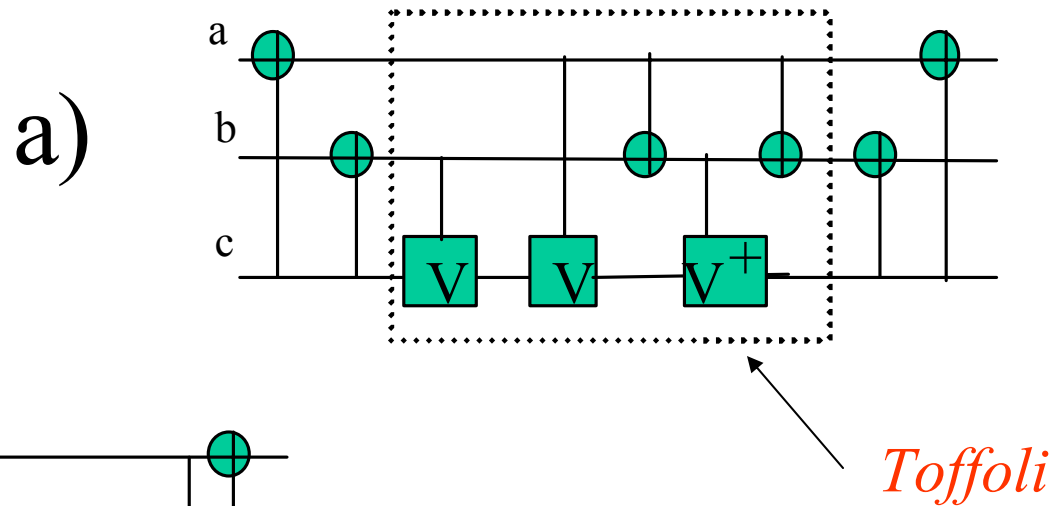2-qubit quantum realization of Miller Gate




These techniques can be also applied for Multiple-Valued Quantum Logic

a)

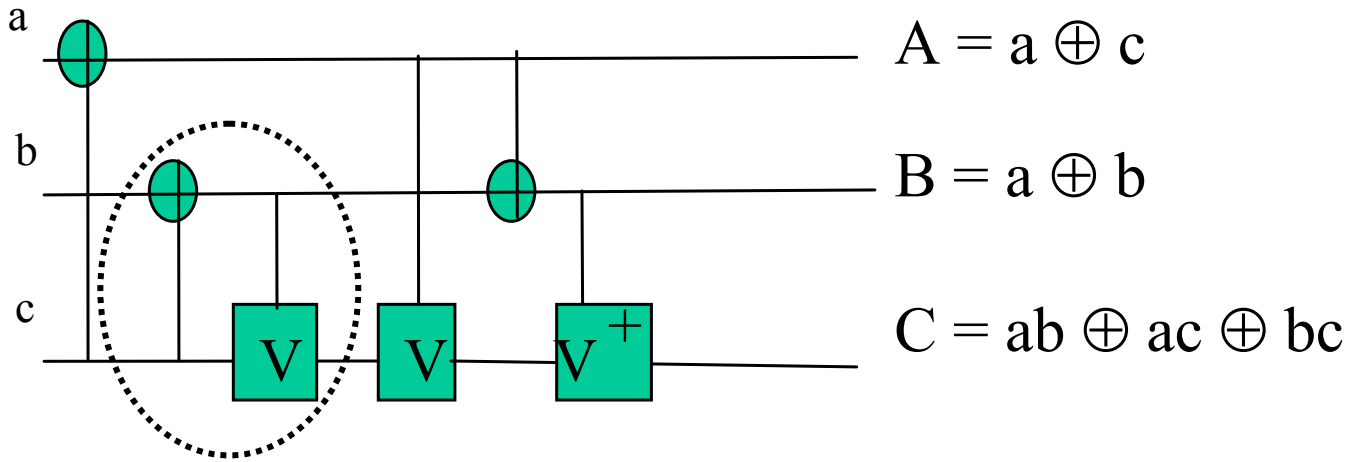


b)

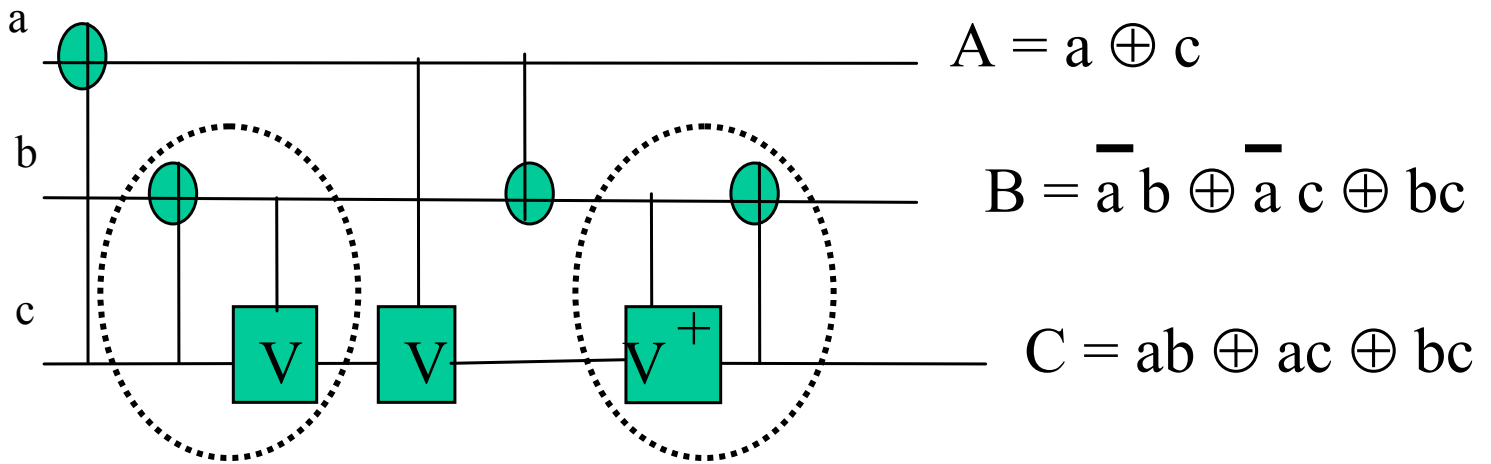


**Design a Ternary
Toffoli Gate from
2-qubit quantum
primitives**

Ternary controlled gates

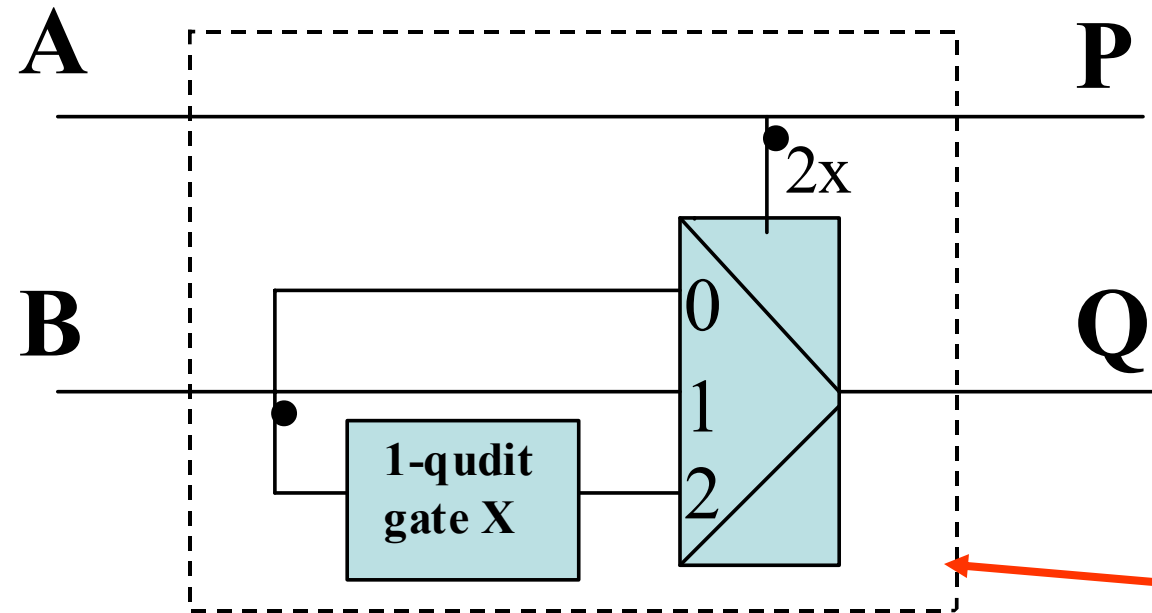First task is to demonstrate that a universal 3-qubit gate can be built from MV quantum primitives




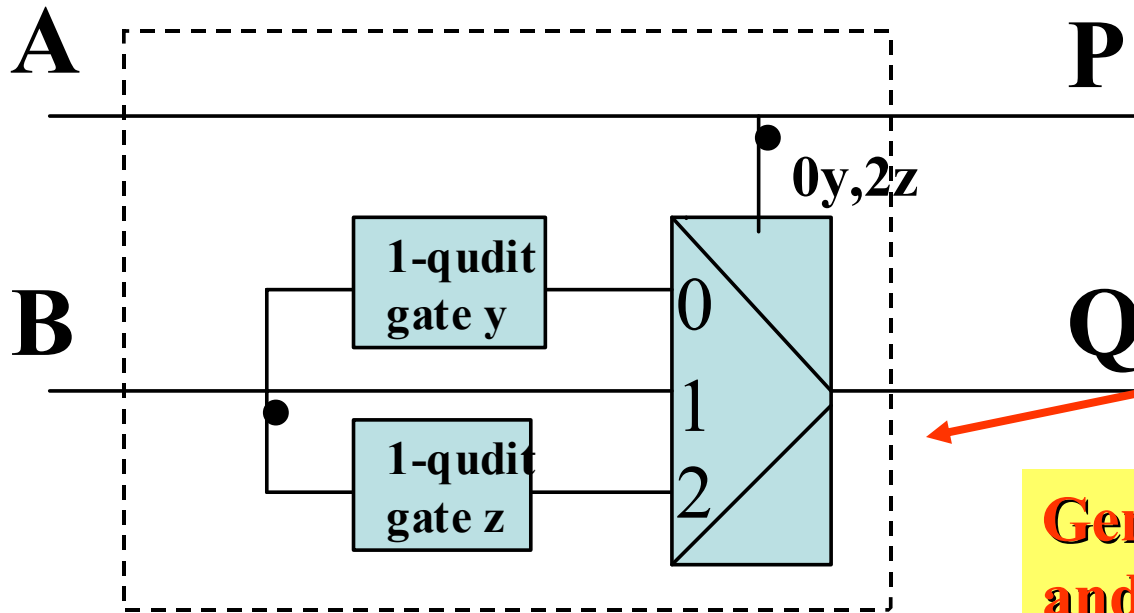2-qubit controlled gate with controlling value $d-1 = 2$




2-qubit controlled gate with controlling values 0 and 2

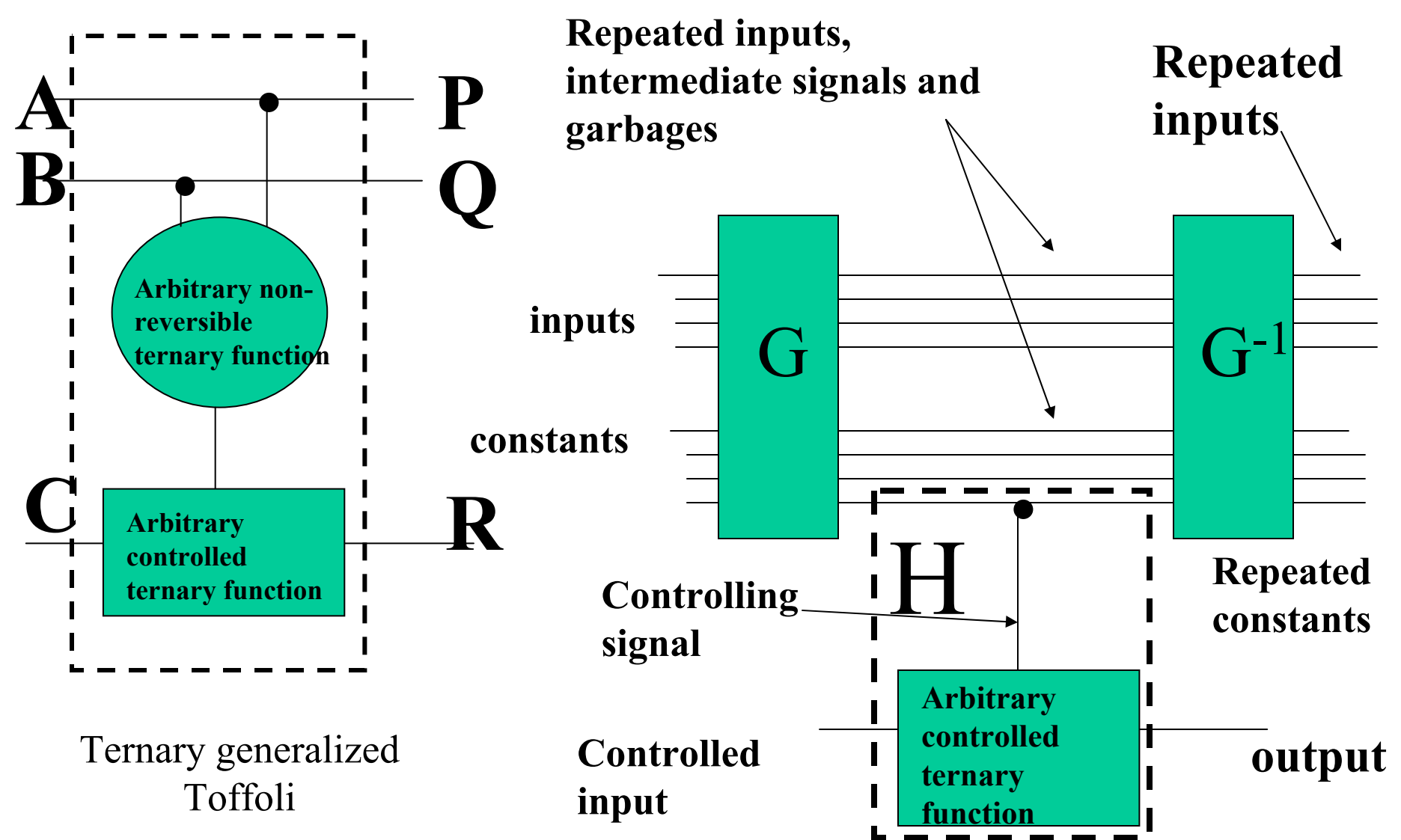Generalization of Stroud and De Vos gates




Principle of creating arbitrary reversible gates

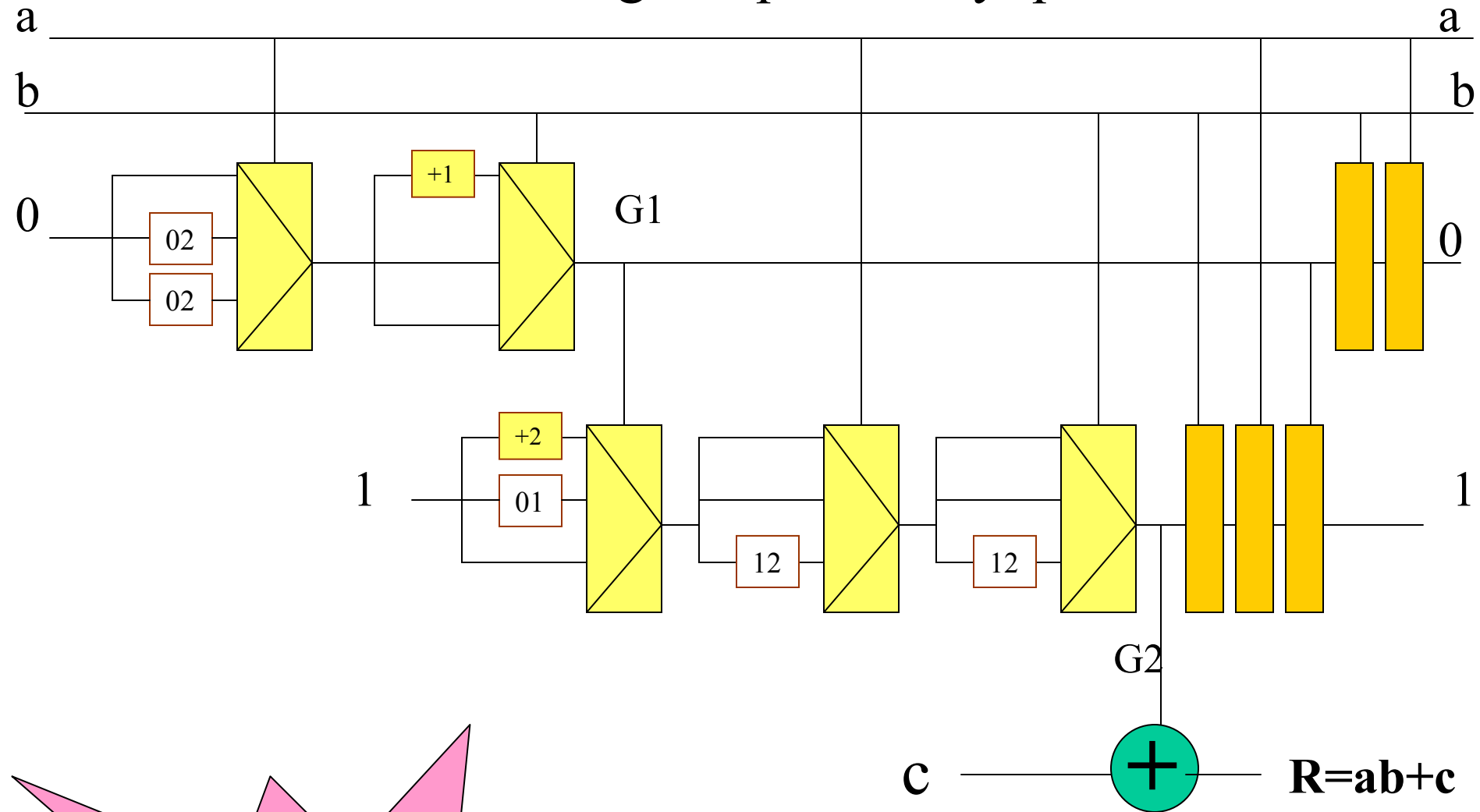Main Result - Galois Logic is practically quantum-realizable



Toffoli for Ternary

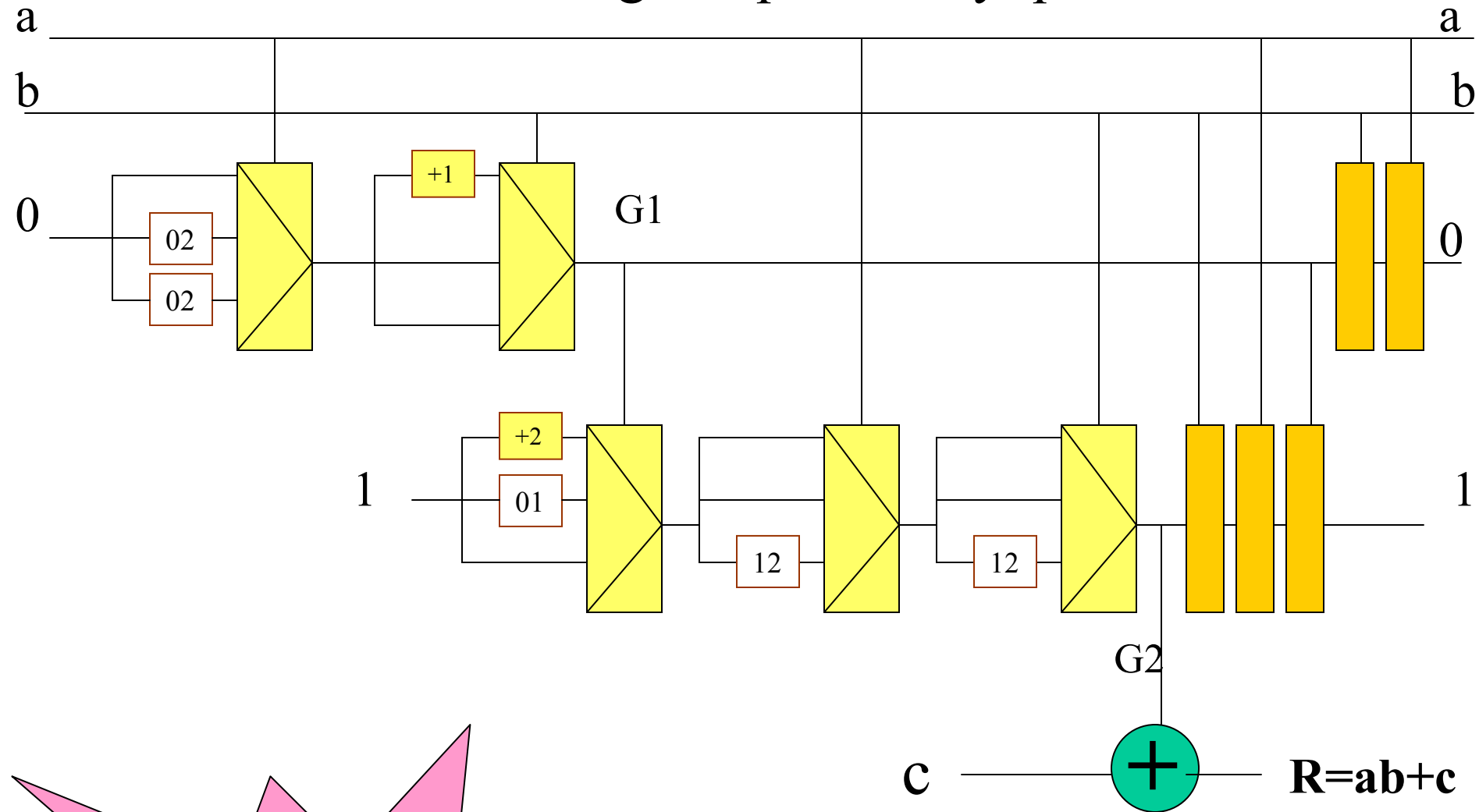Main Result - Galois Logic is practically quantum-realizable



But is it worthy?

This structure realizes also a very huge family of ternary Toffoli-like gates

Complete ternary systems

- System 1. Post literal, min, max
- System 2. Power of variable, shifts of variable (two of them for ternary – these are optional), Galois ADD, Galois MUL
- System 3. Post Literals, MIN, MODSUM.
- These three are most popular, but there are many other.

**Are they good for
quantum?**

Ternary Operator Kmaps

		B		
		0	1	2
A				
0		0	0	0
1		0	1	2
2		0	2	1

Galois Multiplication. Also has latin square for non-zero columns and rows

		B		
		0	1	2
A				
0		0	1	2
1		1	2	0
2		2	0	1

MODSUM which for primary number 3 is the same as Galois Addition. Observe latin square property, very important

Example : Ternary Kmaps of ternary adder

		B		
		0	1	2
A	0	0	0	0
	1	0	0	1
	2	0	1	1

$$C = {}^1A * {}^2B + {}^2A * {}^1B + {}^2A * {}^2B$$

Step1: write from Kmap the formula for mv minterms

		B		
		0	1	2
A	0	0	1	2
	1	1	2	0
	2	2	0	1

This is modsum3 by inspection, so $S = A +_3 B$. But you can also calculate is with much formula writing the same as I show for C

Step 2. Algebraic Simplifications using rules of ternary Galois Field Algebra

$$\begin{aligned}
 C &= {}^1A * {}^2B + {}^2A * {}^1B + {}^2A * {}^2B = (2A^2+2A) * (2B^2+B) \\
 &+ (2A^2+A) * (2B^2+2B) + (2A^2+A) * (2B^2+B) \\
 &= 2(A^2+A) * (2B^2+B) + 2*2A^2B^2 + 2*2A^2B + 2AB^2 + 2AB + \\
 &2*2A^2B^2 + 2A^2B + 2AB^2 + AB = \mathbf{2A^2B + 2AB^2 + 2AB}
 \end{aligned}$$


Example of Post literal, it has value 1 for argument value 1 and 0 otherwise

Here Post literals are next replaced by tautological polynomials in Galois Field

Complex Ternary Quantum Gates


Ternary Fredkin Gate build from Ternary Toffoli and Ternary Feynman gates
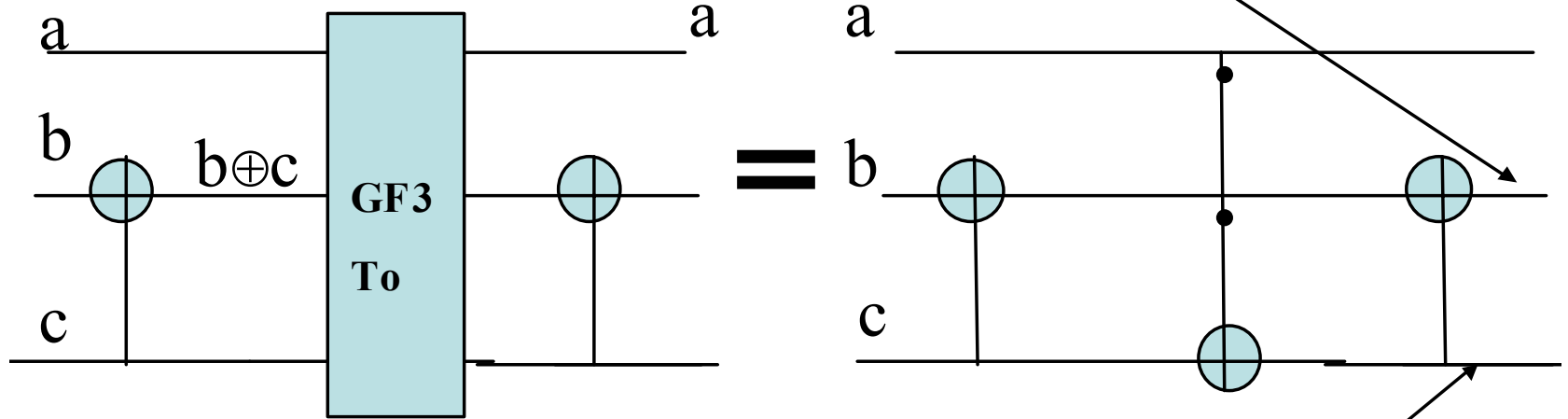
$$b \oplus c \oplus ab \oplus a'c = ac \oplus ba''$$




$$c \oplus a(b \oplus c) = c \oplus ab \oplus ac = ca' \oplus ab$$

Generalized Ternary Feynman Gate

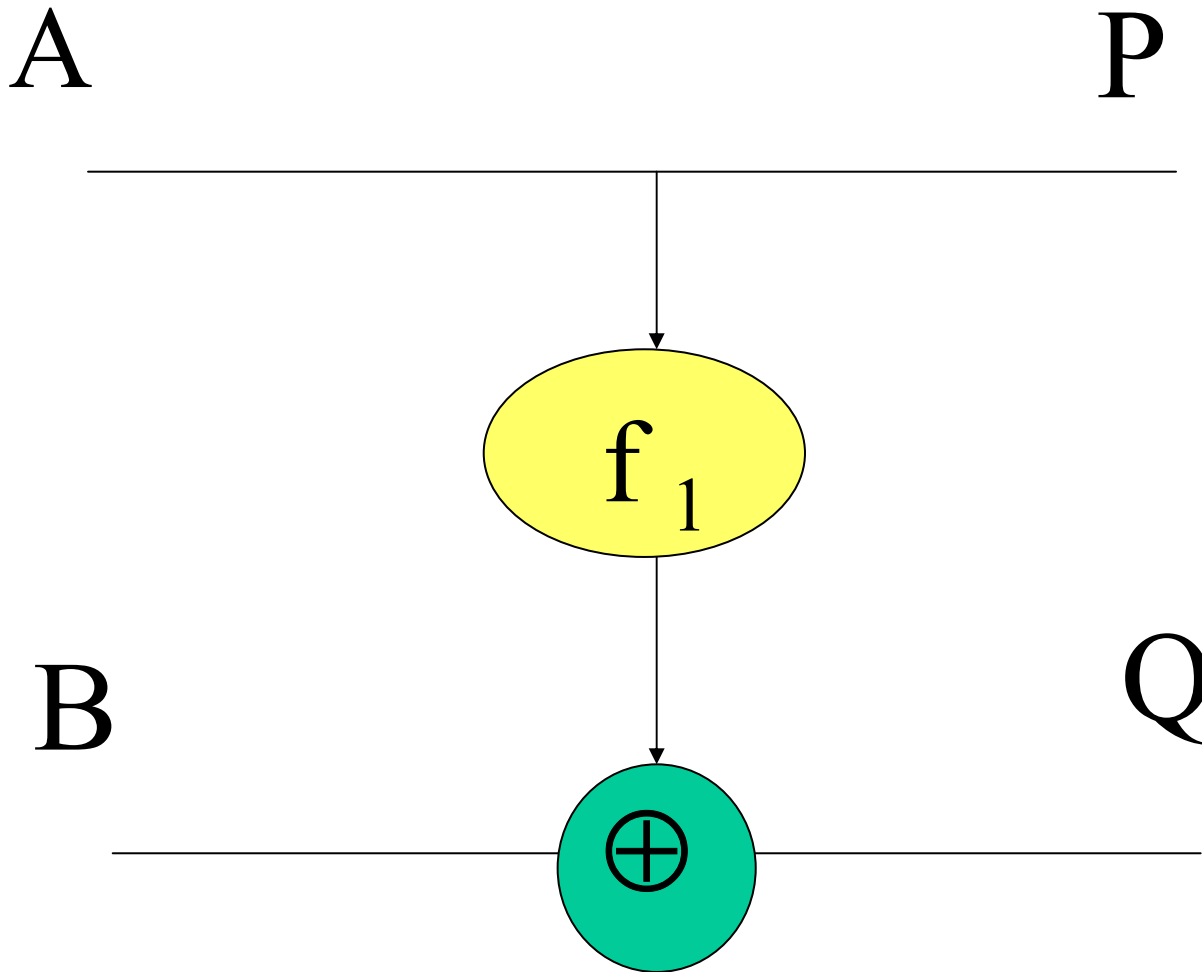


If f_1 is reversible, gate is correct, what about non-reversible f_1 , please check if the gate is still reversible

Generalized Ternary 3*3 Toffoli Gate

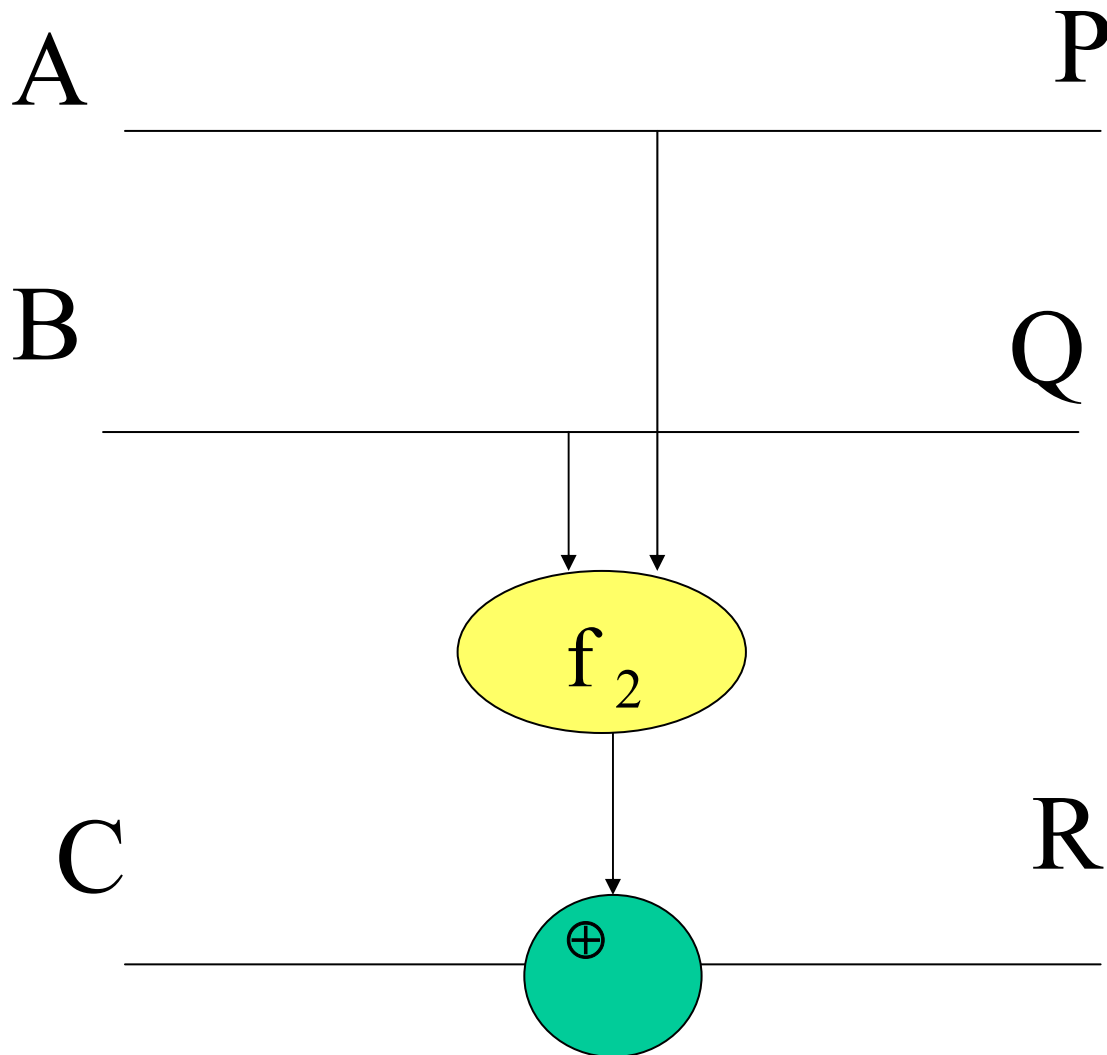


Do the same exercise as in previous slide, this will help you get intuition in MV logic.

Generalized Ternary n*n Toffoli Gate

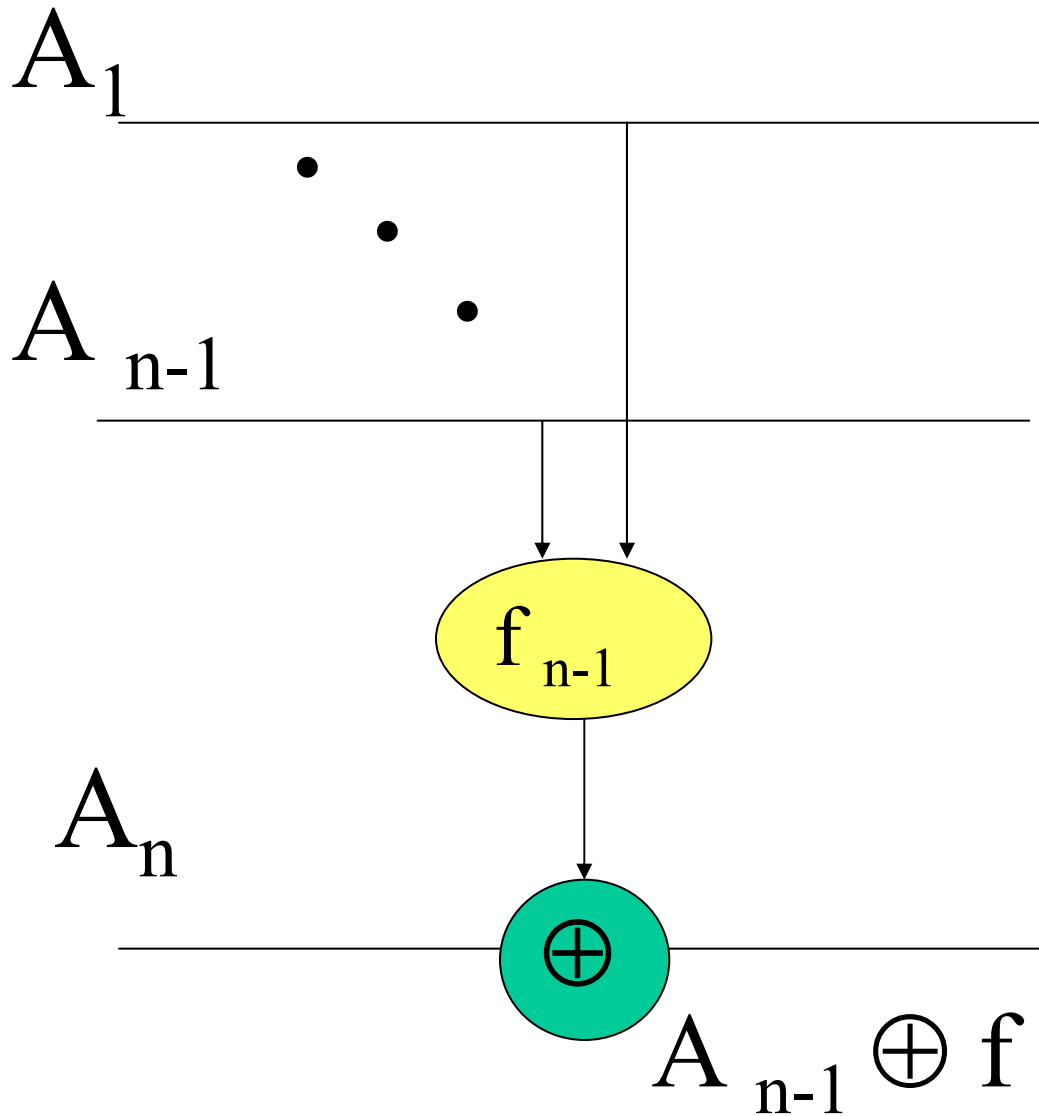


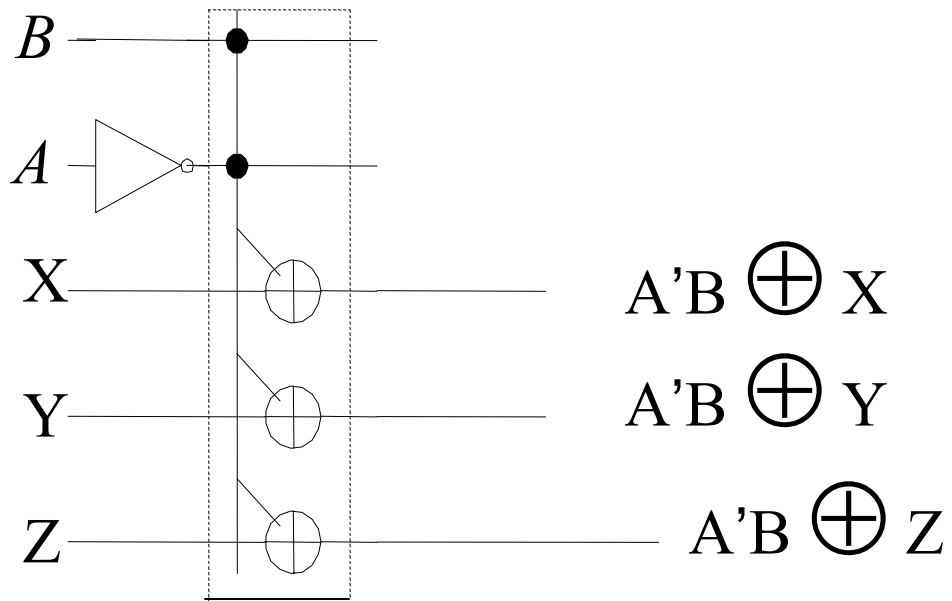Do the same exercise as in previous slide, this will help you get intuition in MV logic.




Is this a realizable quantum gate ? **-yes**

Generalized Ternary 4*4 Fredkin Gate

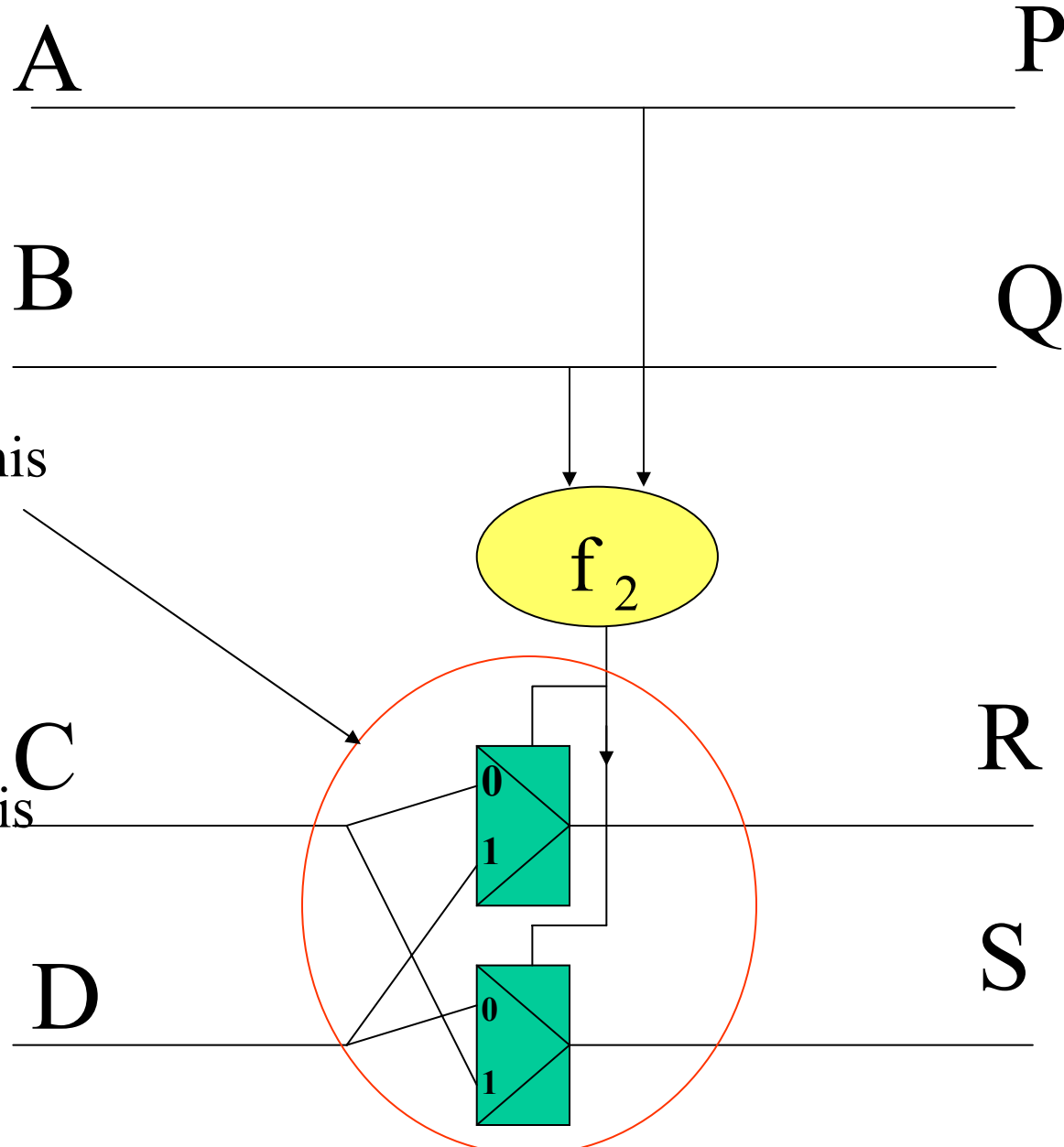


Rewrite this part to quantum ternary notation with Galois Logic


Generalized Ternary n*n Fredkin Gate

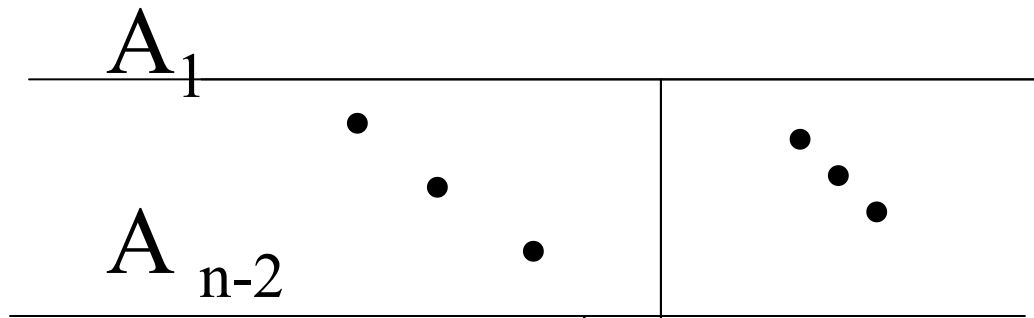

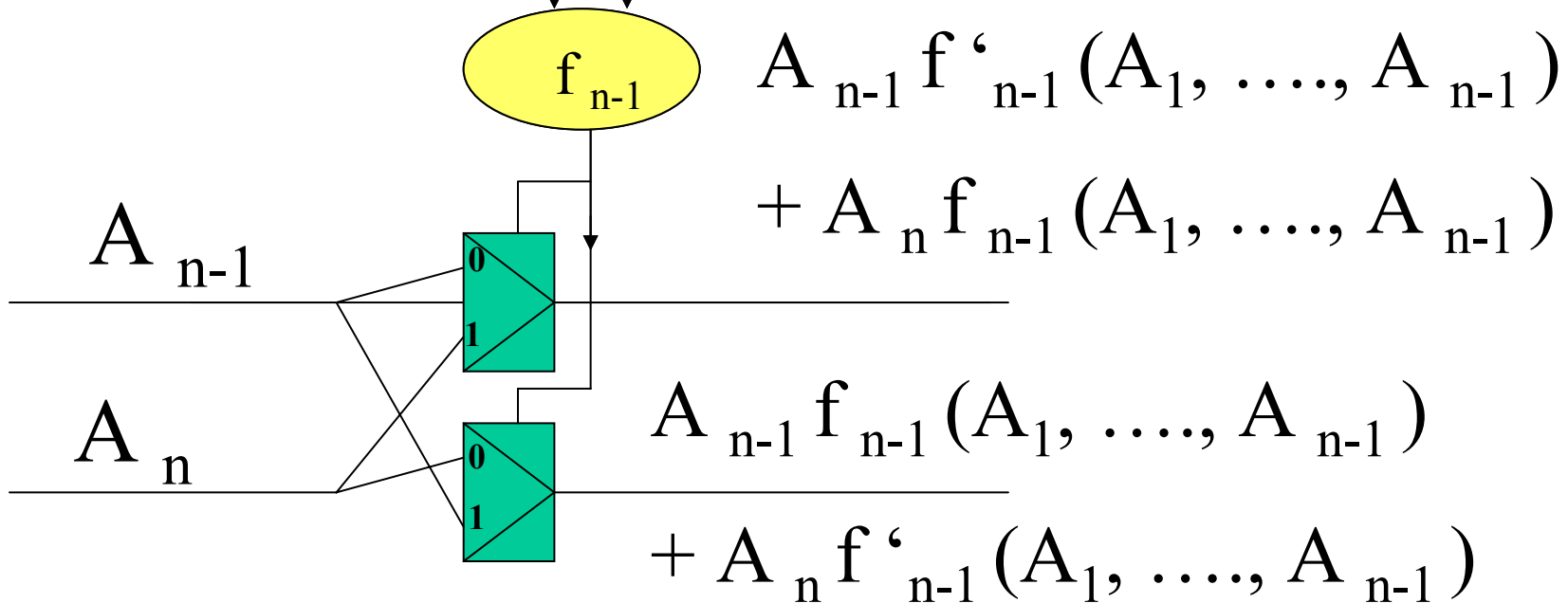Do the same exercise as in previous slide, this will help you get intuition in MV logic.




Generalized Ternary 4*4 Kerntopf Gate

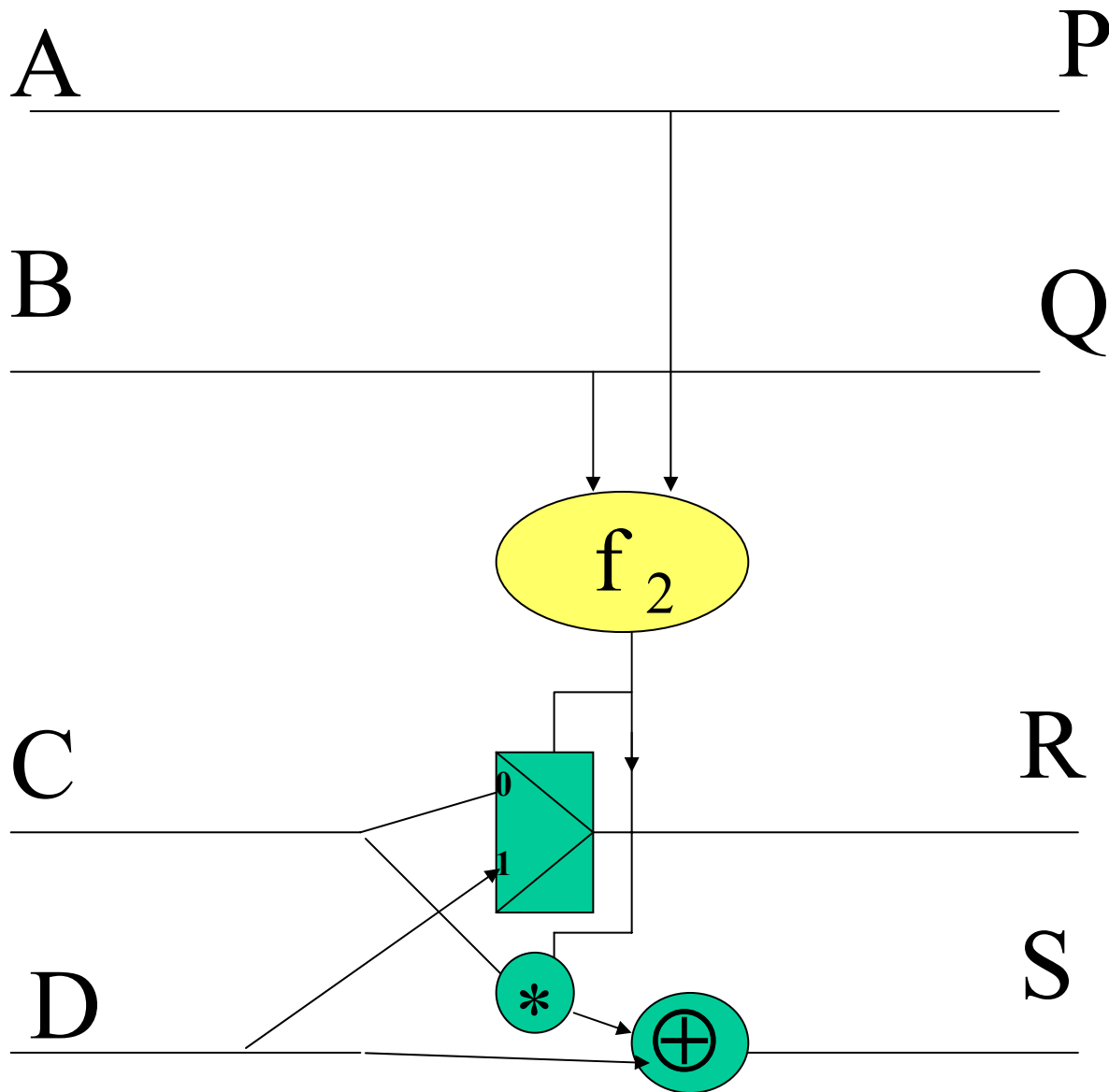

Do the same exercise as in previous slide, this will help you get intuition in MV logic.

Ternary Quantum Circuits

Ternary GFSOP Cascade (non-optimal)

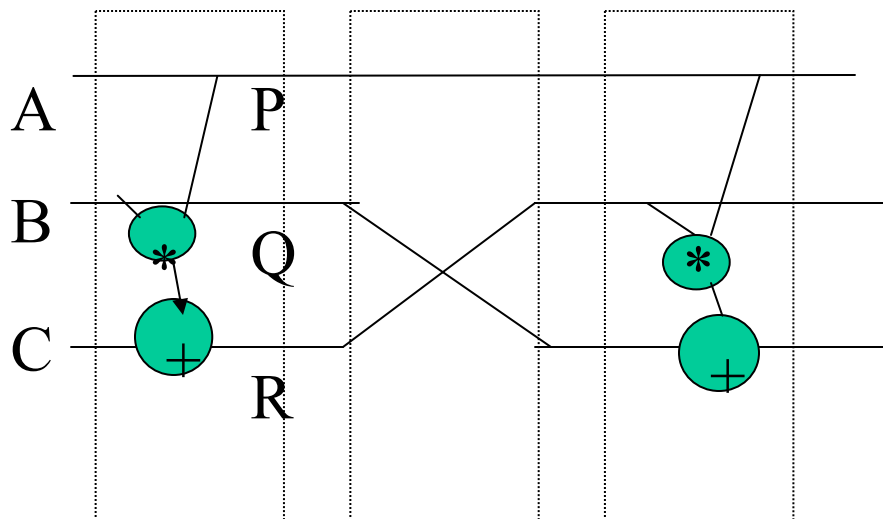

All operations are Galois

A

$$AB \oplus C$$

$$B \oplus A (AB \oplus C) = B \oplus AB \oplus$$

$$AC = A'B \oplus AC$$

Notation for EACH


gate:

Inputs: A,B,C

Outputs: P,Q,R

How to realize ternary swap gate?
In any case, this is very costly!

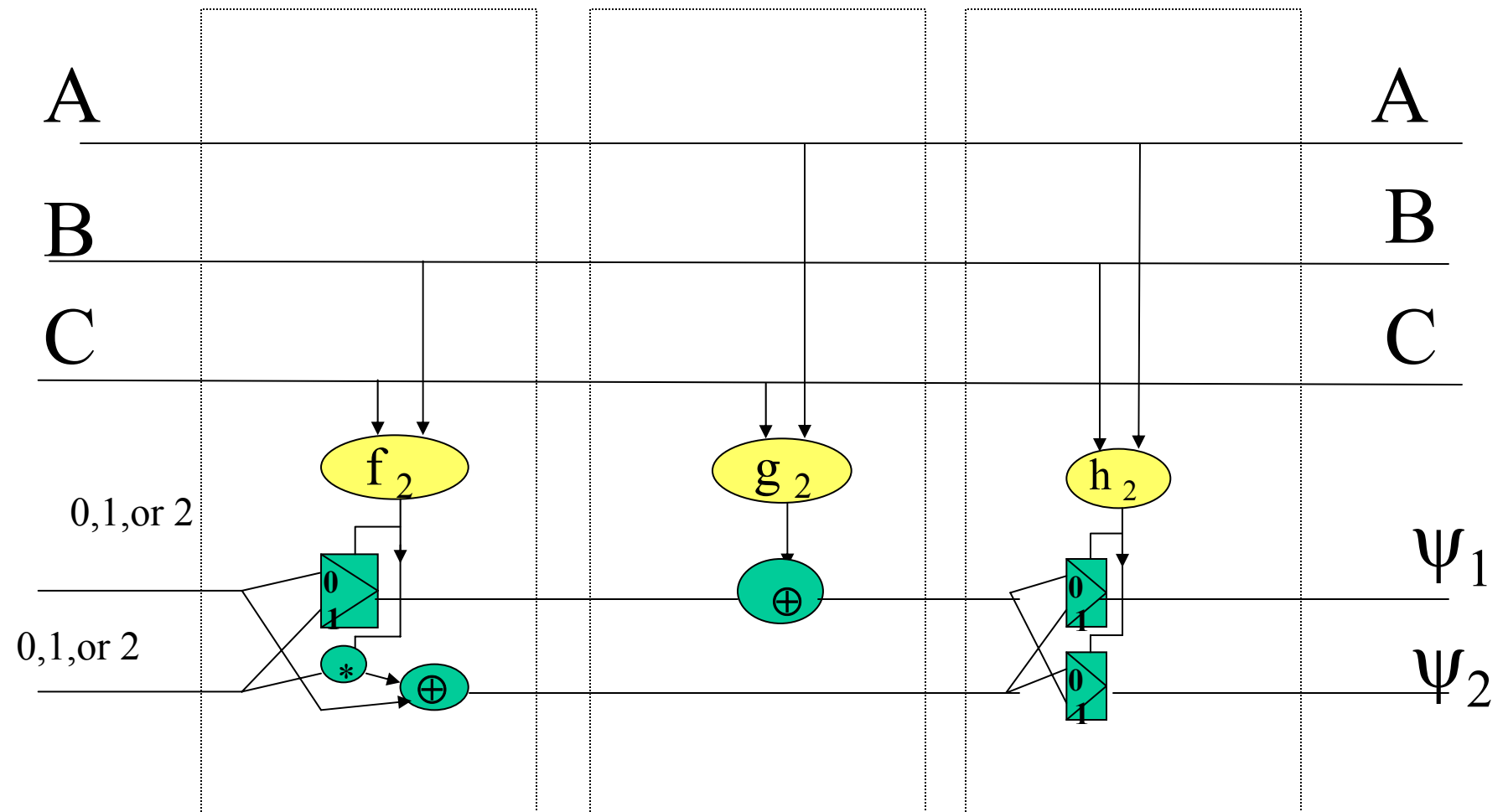
General Ternary Cascade of Kerntopf, Toffoli and Fredkin Family Gates



Example of multi-output FPRM-like GFSOP cascade of Toffoli family gates

$$\psi_1 = 1 \oplus C'' \oplus A'BC \oplus A' B$$

$$\psi_2 = 2 \oplus C'' \oplus A' B$$

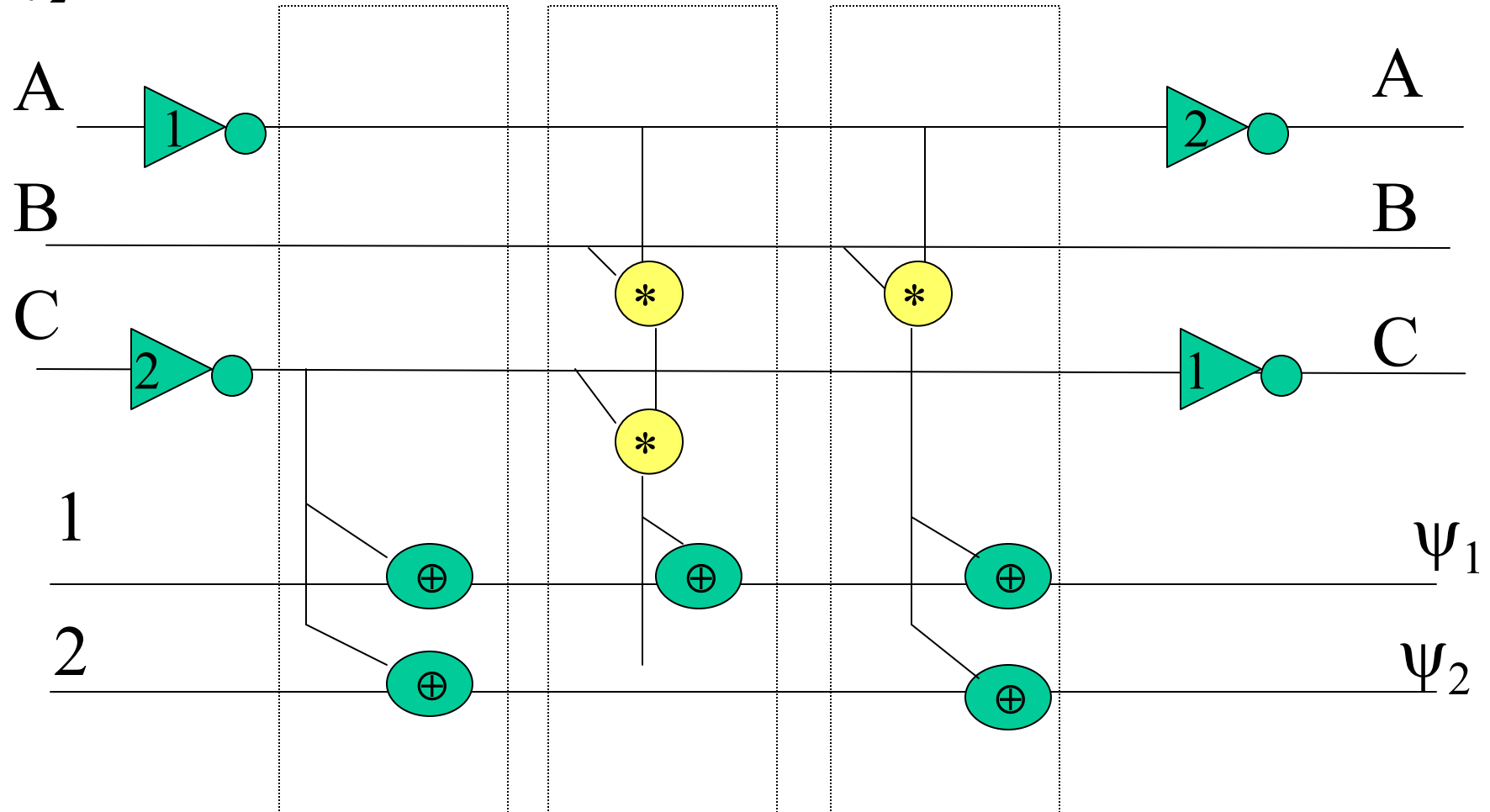


Example of ternary multi-output GFSOP cascade of Toffoli family gates

$$\psi_1 = 1 \oplus C \oplus ABC \oplus A' B$$


$$\psi_2 = 0 \oplus C \oplus A' B$$

This is notation for single shift


This is notation for dual shift

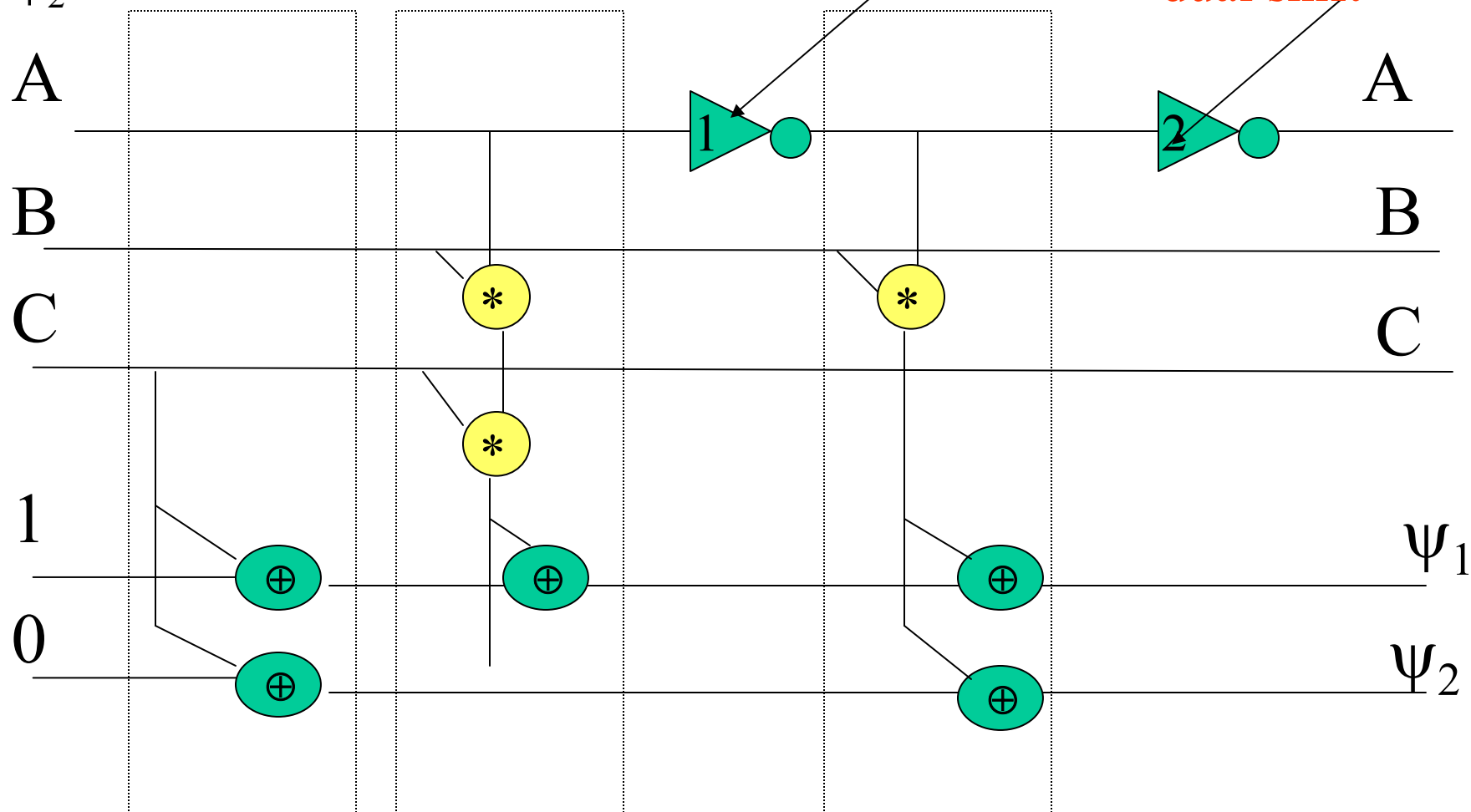

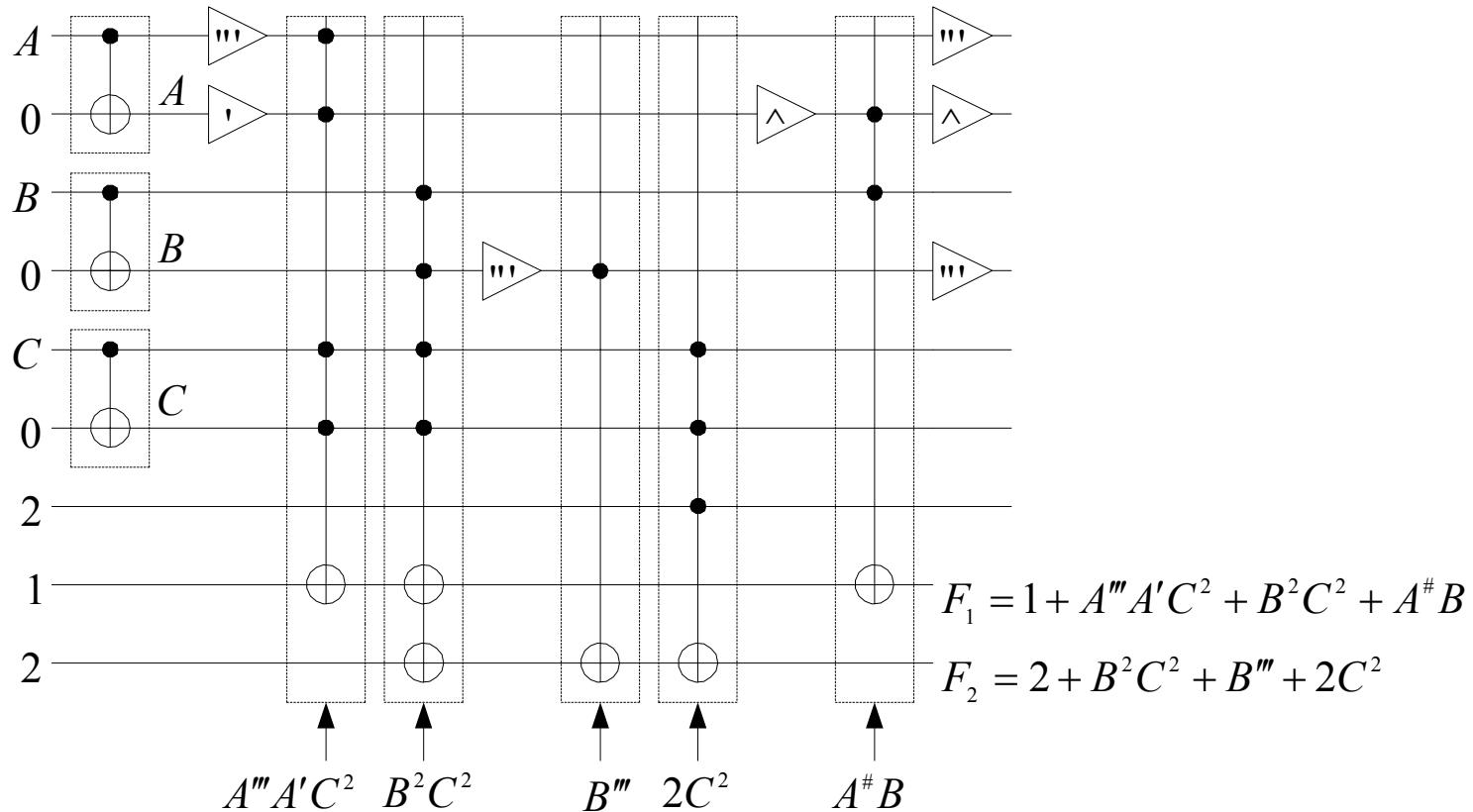The **general pattern** of a cascade to implement any ternary function using ternary Toffoli gates



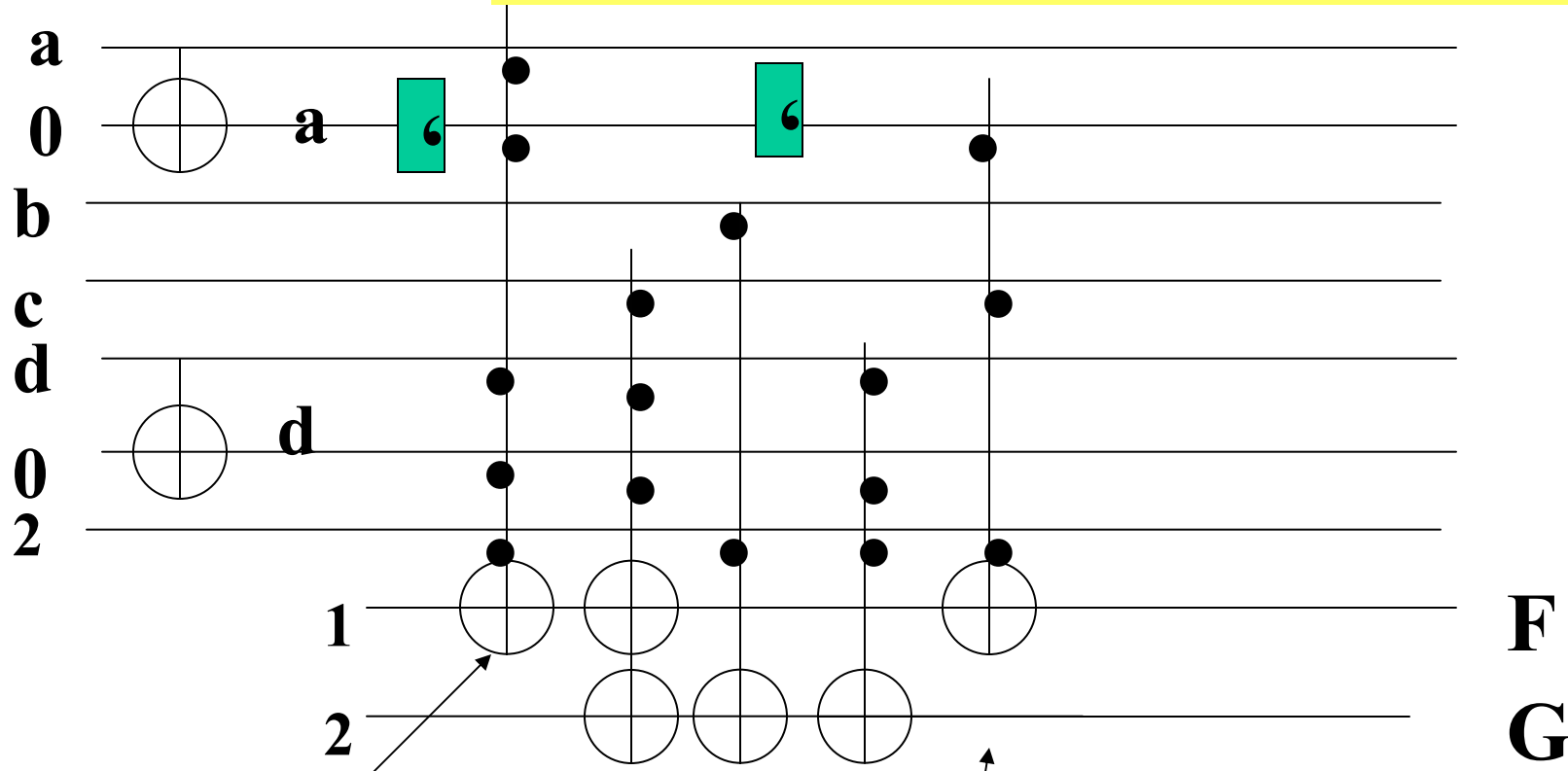Simplified GFSOP array when powers are not used for some variables. Function of four variables



$$2a a'$$

$$d^2$$

$$c d^2$$


$$2b$$

$$2 d^2$$

$$2 a'' b$$

$$F=1+2a a' d^2 + c d^2 + 2 a'' c$$

$$G=2+ c d^2 + 2b + 2d^2$$

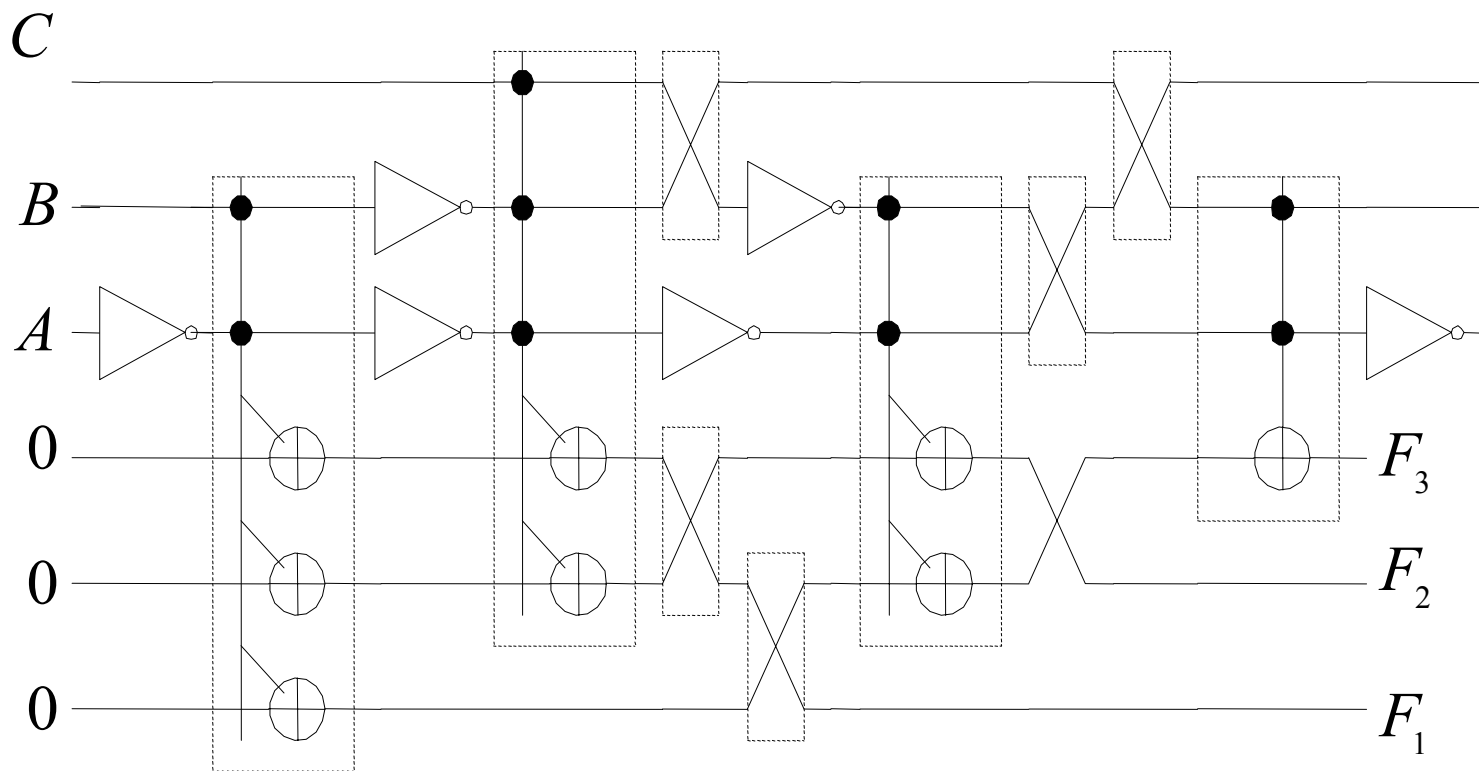


$$F_1 = A'B \oplus A B' C$$

$$F_2 = A'B \oplus A' C \oplus B' C'$$

$$F_3 = A'B \oplus B' C \oplus AC'$$

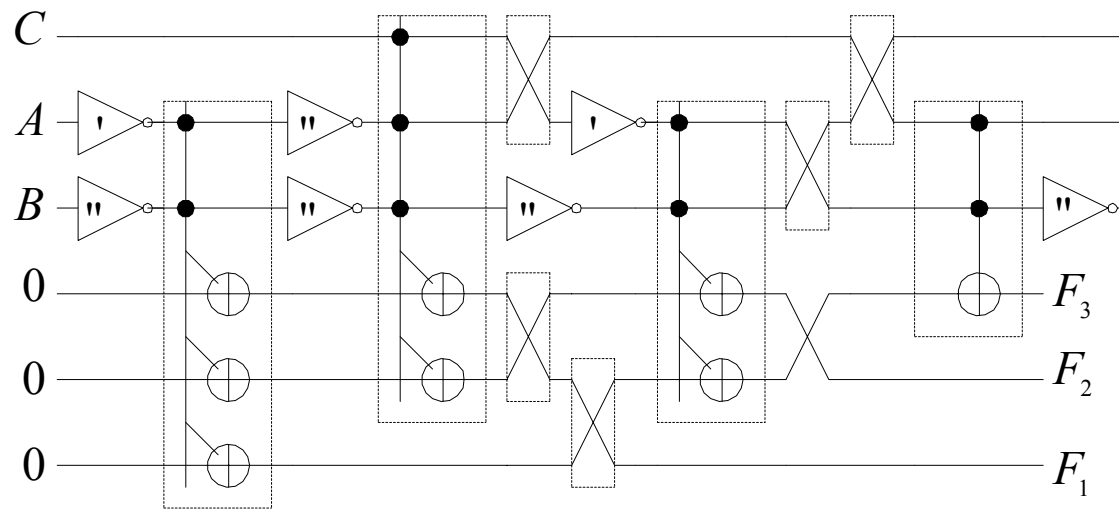(a) Realization of multi-output ESOP

Macrogeneration introduces many **Feynman gates** that originate from **swaps**




$$F_1 = A'B'' \oplus AB'C$$

$$F_2 = A'B'' \oplus AB'C \oplus BC'$$

$$F_3 = A'B'' \oplus BC' \oplus AC'$$

(a) Realization of multi-output GFSOP

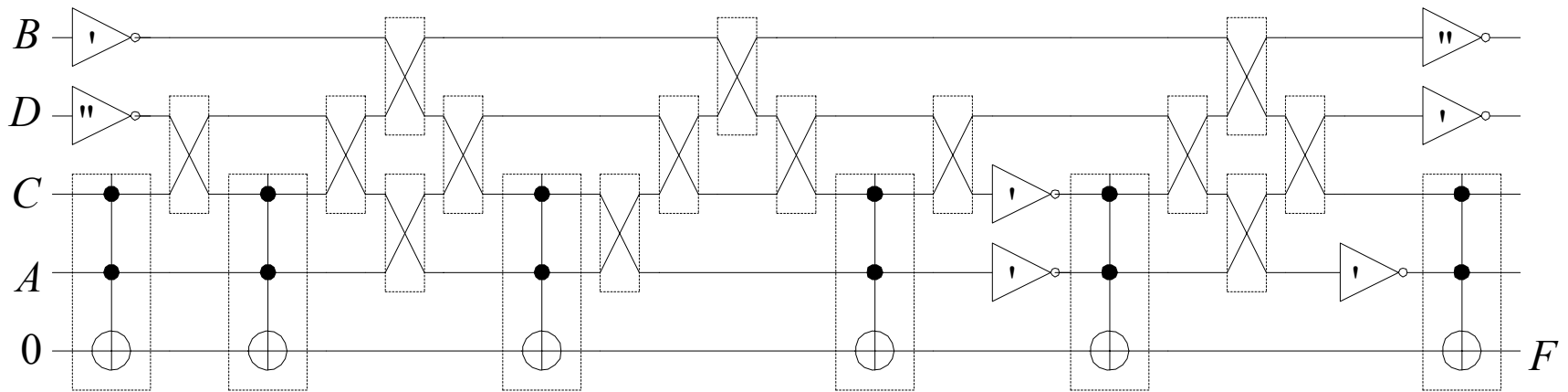

$$F = AC \oplus AD'' \oplus B'C \oplus B'D'' \oplus CD \oplus A'B''$$

(b) Realization of single-output GFSOP

MV Quantum Design Structures and Approaches

- **1.** GFSOP
- **2.** Multiple-Valued Reed-Muller
- **3.** Canonical Forms over Galois Logic
(equivalents of PPRM, FPRM, GRM, etc)
- **4.** Multiple-Valued Maitra Cascades and Wave Cascades.
- **5.** Other cascades of specific type of elements
- **6.** Cascades of general gates


Design Issues

- **1.** Local mirroring
- **2.** Variable ordering versus gate ordering
- **3.** Return to zero and folding
- **4.** Realization of complex multiple-valued reversible gates (permutation gates) using directly 1-qubit and 2-qubit quantum primitives



“Return to Zero” and Folding

Technique of local mirror can improve your ternary circuits, reduce the number of zeros in inputs. Here is the explanation for **ternary** logic

1*1 GATE THAT
MULTIPLIES BY 2

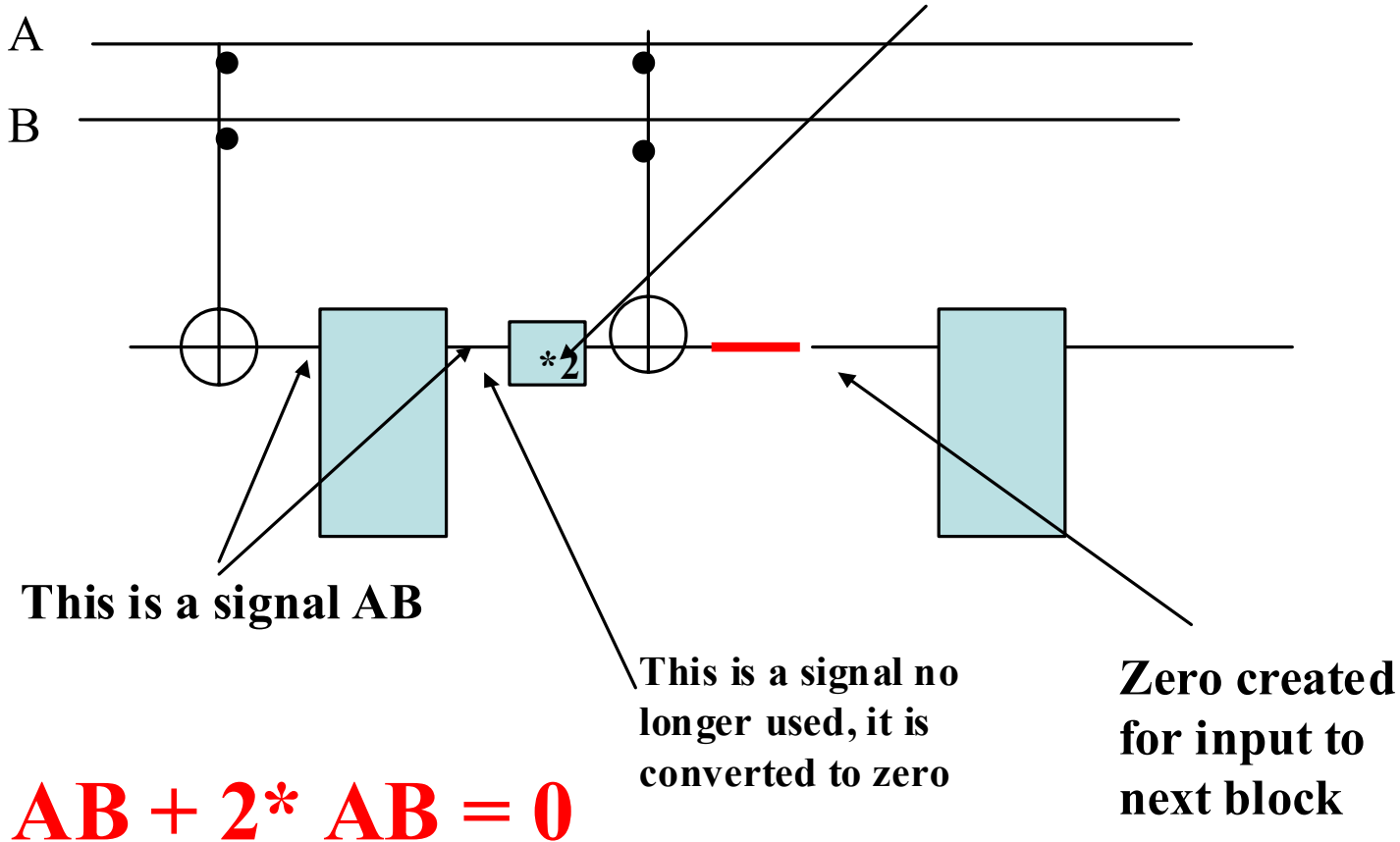


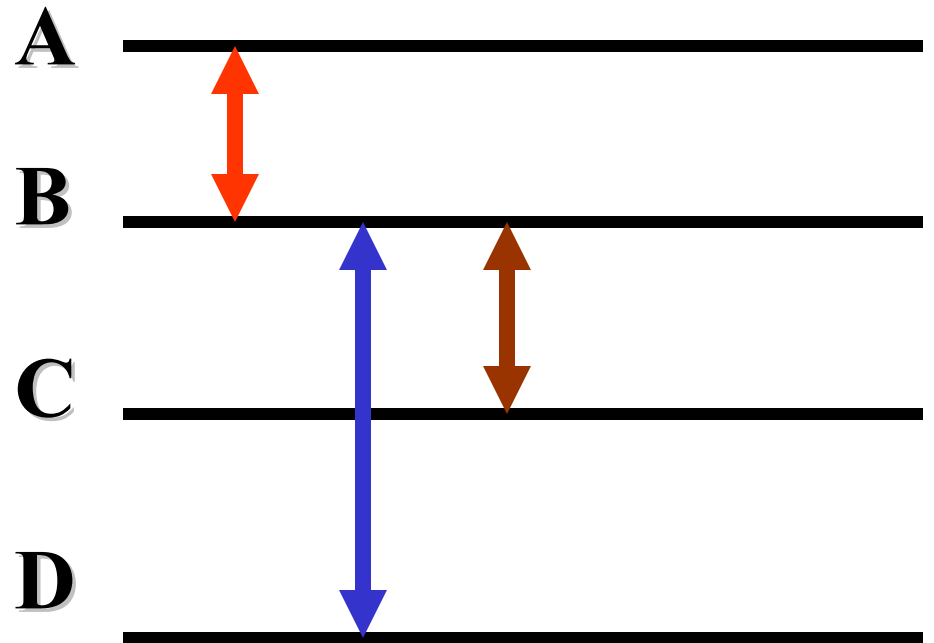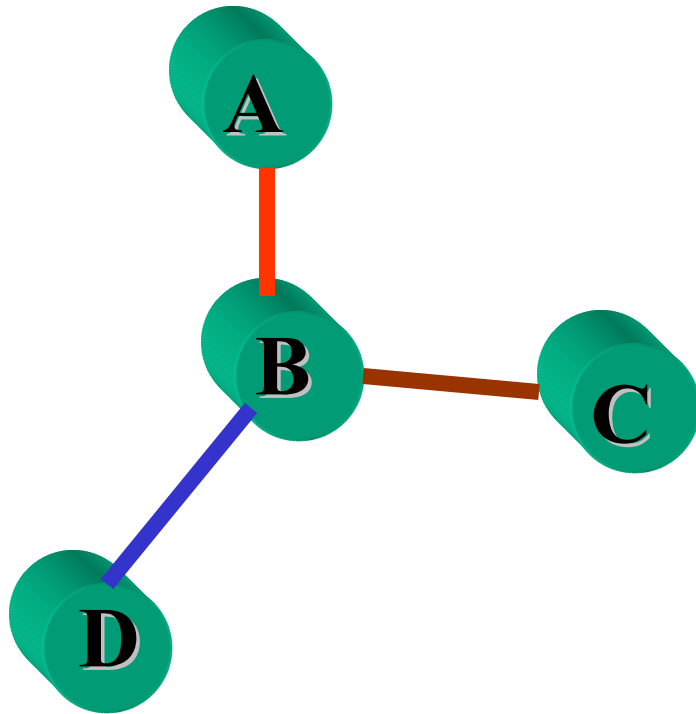
Molecule - Driven Layout and Logic Synthesis




Allowed gate neighborhood for
2 qubit gates

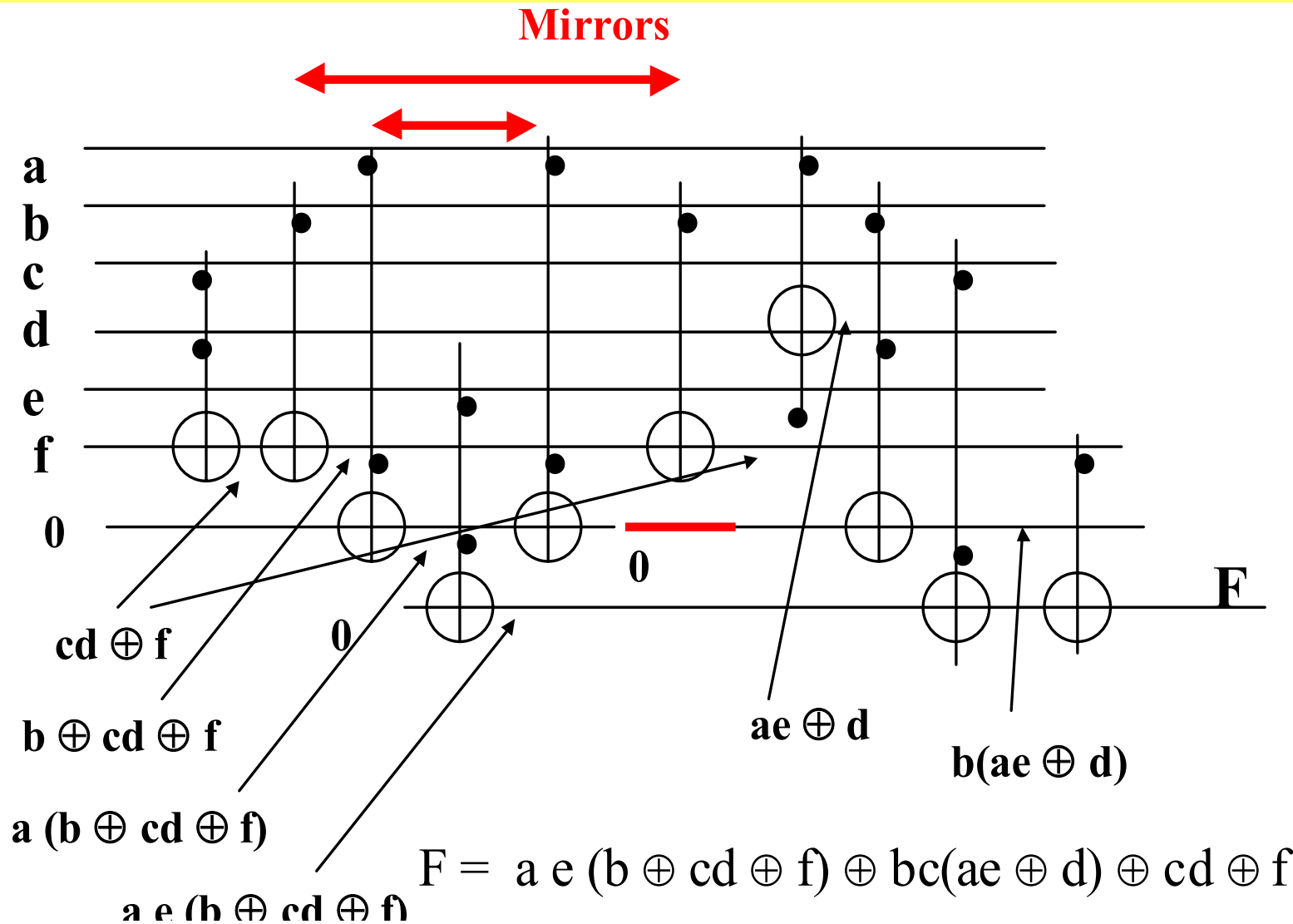Using Local Mirrors and Return-to-zero factorization




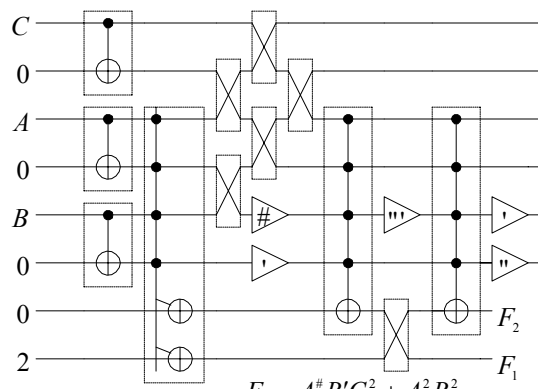

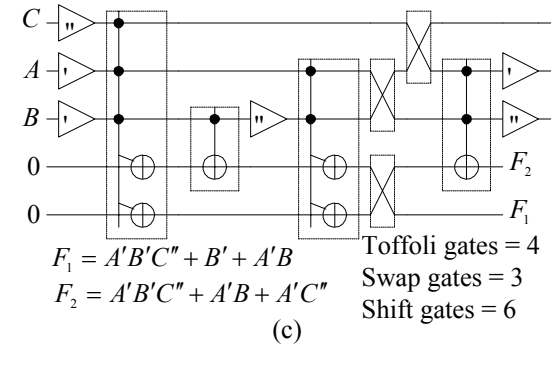
Toffoli gates = 6 $F_1 = A^{\#}B'C^2 + A^2B^2$
 Swap gates = 6 $F_2 = 2 + A''B'C^2 + A^2B^2$
 Shift gates = 5 (a)



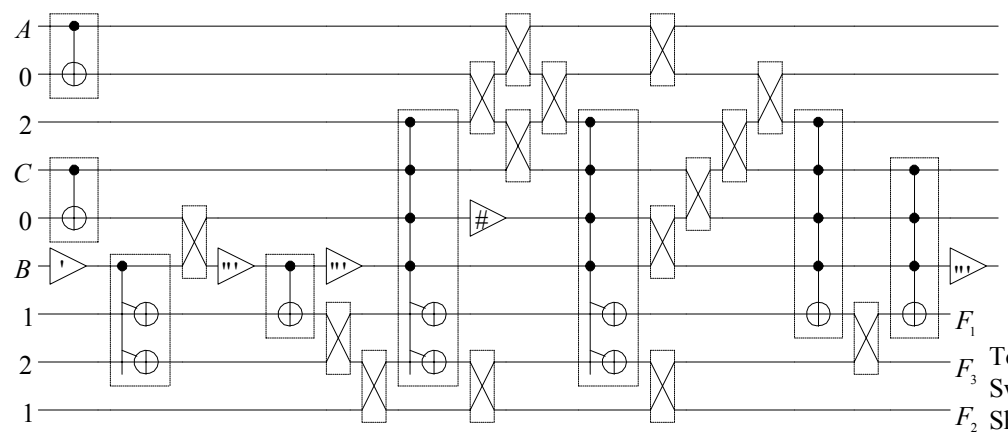$F_1 = A'B'C'' + B' + A'B$ Toffoli gates = 4
 $F_2 = A'B'C'' + A'B + A'C''$ Swap gates = 3
 Shift gates = 6 (c)




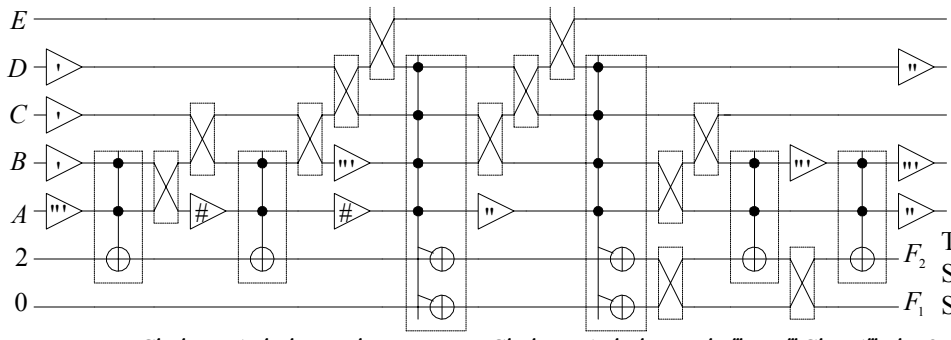$F_1 = 1 + 2B'C^2 + A^2B'''$ $F_2 = 1 + B' + A^2B'''C + C'''$ $F_3 = 2 + 2B'C^2 + 2A^2B''' + B' + A^2B'''C$
 Toffoli gates = 8
 Swap gates = 15
 Shift gates = 5 (b)



$F_1 = BC'D'E + AB'D'E + D'E$ $F_2 = BC'D'E + AB'D'E + D'E''' + B'''C' + A'''B' + 2$
 Toffoli gates = 6
 Swap gates = 12
 Shift gates = 12 (d)

System for mixed quantum logic NMR

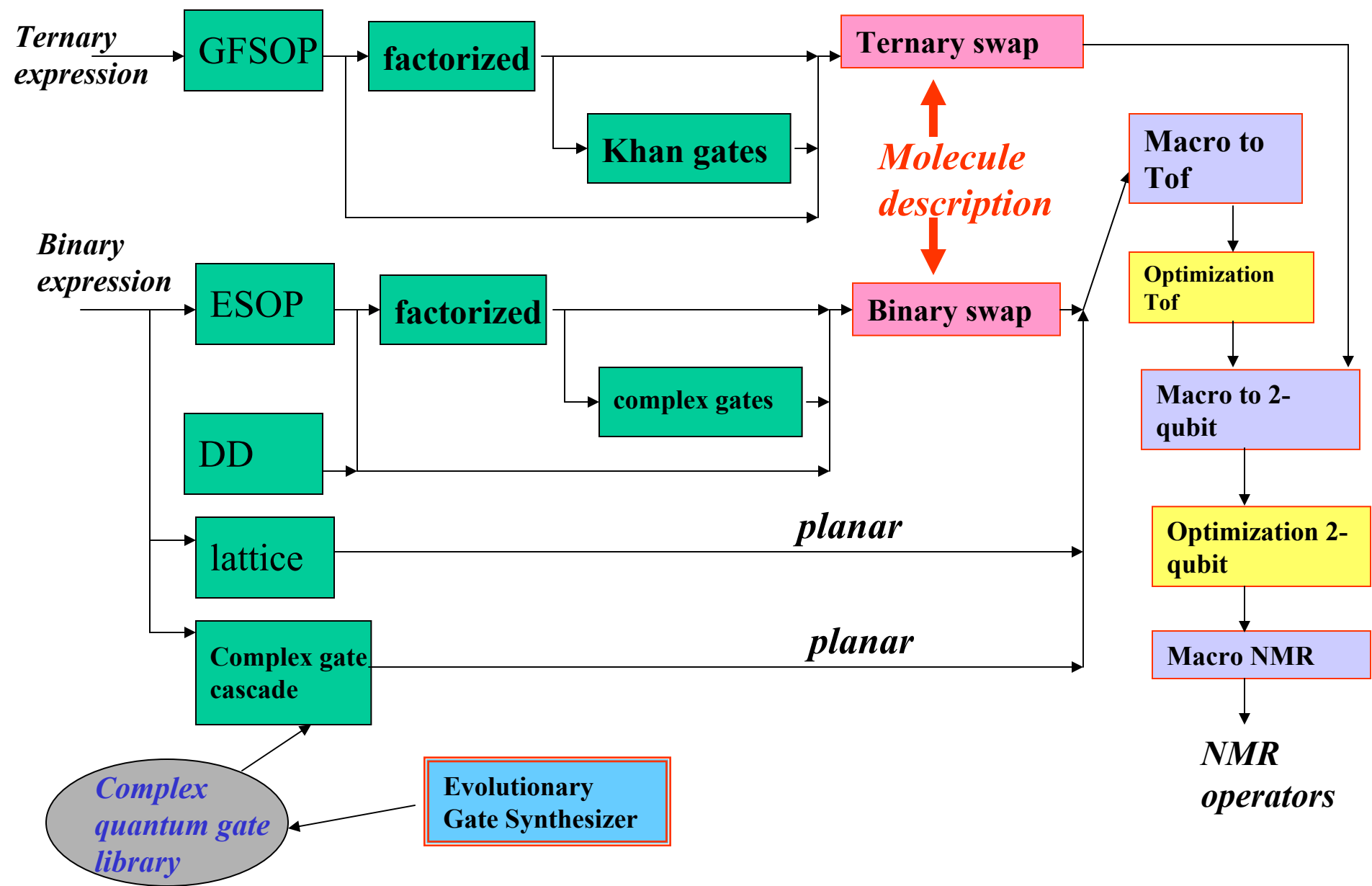

Open Problems

1. How to select the best gates for permutation circuit synthesis.
2. Simplest practical realization of a ternary Toffoli-like gate
3. Best realization, in quantum circuit sense (simplicity and ease of realization), of other Galois gates and non-Galois standard MV operators such as minimum, maximum, truncated sum and others.
4. Synthesis algorithms for MV reversible circuit families:
 - GFSOP ,
 - nets,
 - lattices,
 - PLAs
 - MV counterparts of Maitra cascades and wave cascades
 - other reversible cascades

Conclusion

- Practical algorithms for MV quantum circuits. **Quantum permutation circuits design (for NMR) is not the same as standard reversible logic.**
- **CAD Tools** for quantum physicists: *link levels of design*.
- Evolutionary Approaches versus GFSOP-like approaches
- MV Quantum Simulation
- MV Quantum Circuits Verification
- Designing MV counterparts of Deutch, Shorr, Grover and other original MV quantum algorithms
- Generalization to MV Of efficient Garbage-less quantum gates by Barenco, DiVincenzo, etc.
- NMR realization of ternary logic.
- MV Quantum Computational Intelligence