



ECE317 : Feedback and Control

Lecture: Modeling of electrical & mechanical systems

Dr. Richard Tymerski
Dept. of Electrical and Computer Engineering
Portland State University

Course roadmap



Modeling

✓ Laplace transform

Transfer function

Block Diagram

Linearization

▶ Models for systems

- electrical
- mechanical
- example system

Analysis

Stability

- Pole locations
- Routh-Hurwitz

Time response

- Transient
- Steady state (error)

Frequency response

- Bode plot

Design

Design specs

Frequency domain


Bode plot

Compensation

Design examples

Matlab & PECS simulations & laboratories

Controller design process (review)

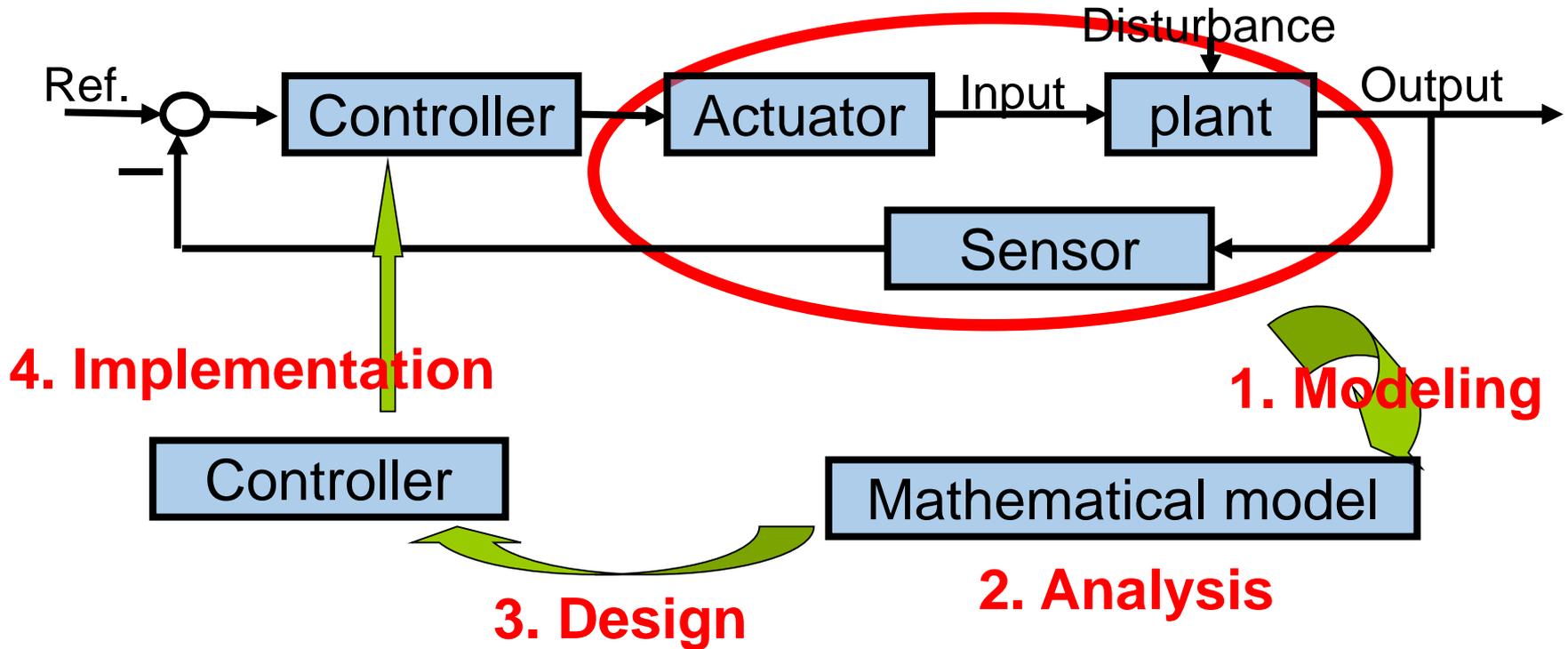


- What is the “mathematical model”?
- Transfer function
- Modeling of electrical & mechanical systems

Mathematical model



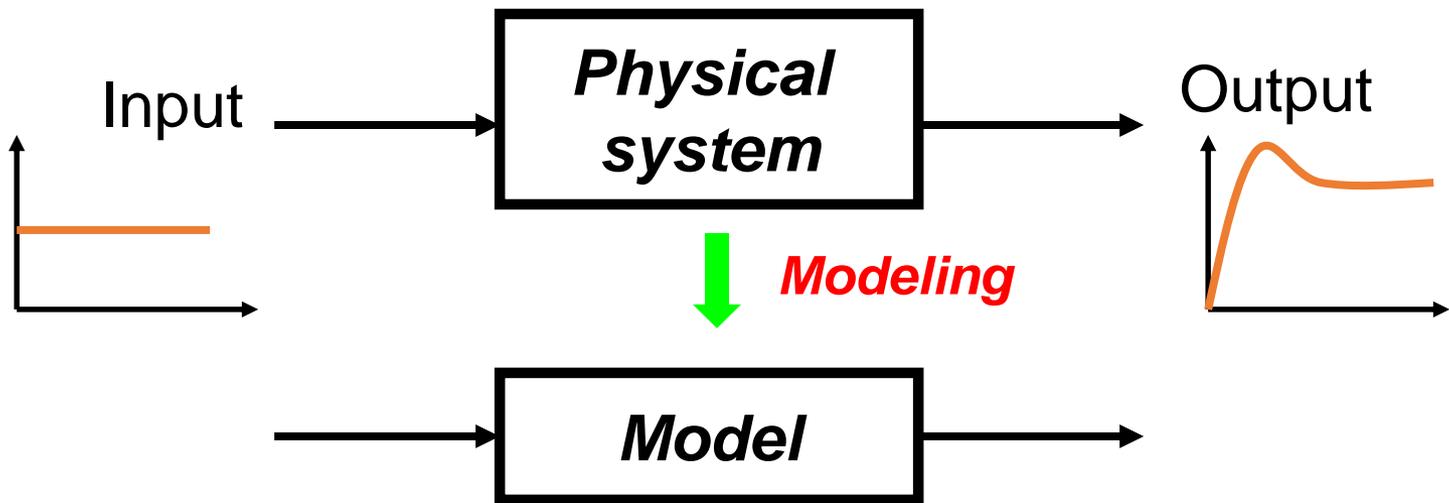- Representation of the input-output (signal) relation of a physical system



- A model is used for the **analysis** and **design** of control systems.

Important remarks on models



- Modeling is the **most important and difficult task** in control system design.
- No mathematical model exactly represents a physical system.

Math model \neq Physical system

Math model \approx Physical system

- Do not confuse **models** with **physical systems**!
- In this course, we may use the term “**system**” to mean a mathematical model.

Course roadmap



Modeling

- ✓ Laplace transform
- ➔ Transfer function
- Block Diagram
- Linearization
- ✓ Models for systems
 - electrical
 - mechanical
 - example system

Analysis

- Stability
 - Pole locations
 - Routh-Hurwitz
- Time response
 - Transient
 - Steady state (error)
- Frequency response
 - Bode plot

Design

- Design specs
- Frequency domain
- Bode plot
- Compensation
- Design examples

Matlab & PECS simulations & laboratories


Transfer function



- A **transfer function** is defined by

$$G(s) := \frac{Y(s)}{R(s)}$$

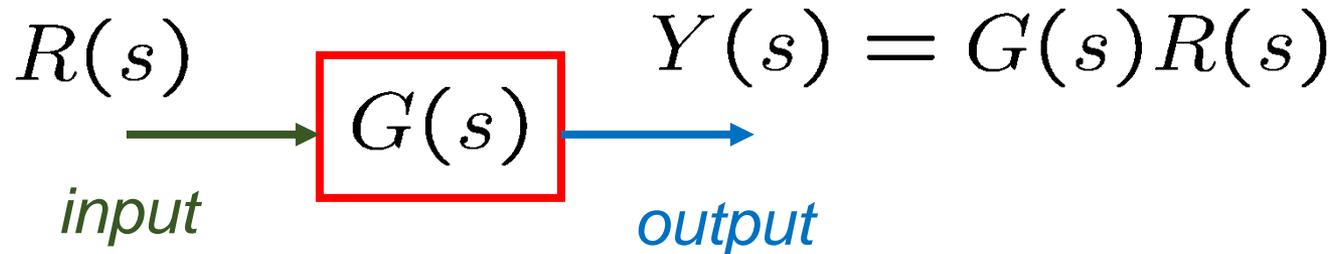$Y(s)$ ← Laplace transform of system output
 $R(s)$ ← Laplace transform of system input




- A system is assumed to be at rest. (zero initial condition)
- Transfer function is a generalization of “gain” concept.

Impulse response



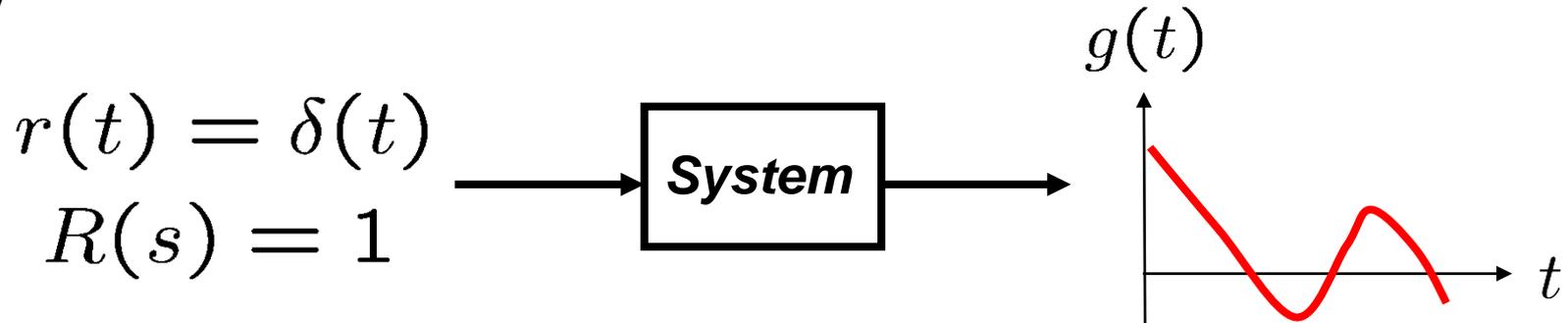- Suppose that $r(t)$ is the unit impulse function and system is at rest.



- The output $g(t)$ for the unit impulse input is called *unit impulse response*.
- Since $R(s)=1$, the transfer function can also be defined as the **Laplace transform of impulse response**:

$$G(s) := \mathcal{L} \{g(t)\}$$

Course roadmap



Modeling

- ✓ Laplace transform
- ✓ Transfer function
- Block Diagram
- Linearization
- ✓ Models for systems
 - electrical
 - mechanical
 - example system

Analysis

- Stability
 - Pole locations
 - Routh-Hurwitz
- Time response
 - Transient
 - Steady state (error)
- Frequency response
 - Bode plot

Design


- Design specs
- Frequency domain
- Bode plot
- Compensation
- Design examples

Matlab & PECS simulations & laboratories

Models of electrical elements



Resistance

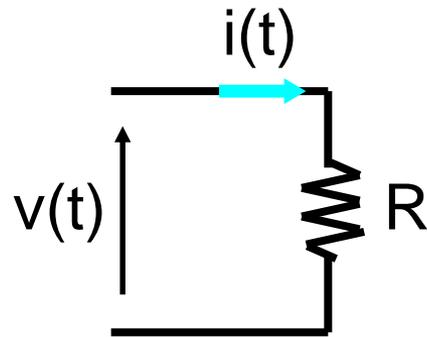


$$v(t) = Ri(t)$$

↓ Laplace transform

$$\frac{V(s)}{I(s)} = \underline{R}$$

Inductance

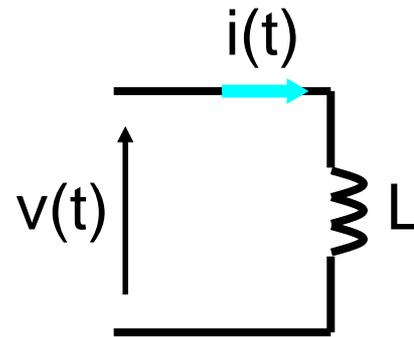


$$v(t) = L \frac{di(t)}{dt}$$

↓ ($i(0) = 0$)

$$\frac{V(s)}{I(s)} = \underline{sL}$$

Impedance

Capacitance

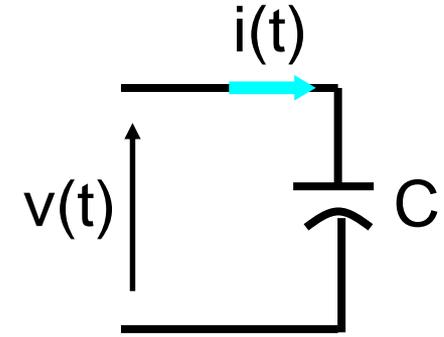


$$i(t) = C \frac{dv(t)}{dt}$$

↓ ($v(0) = 0$)

$$\frac{V(s)}{I(s)} = \underline{\frac{1}{sC}}$$

Modeling example

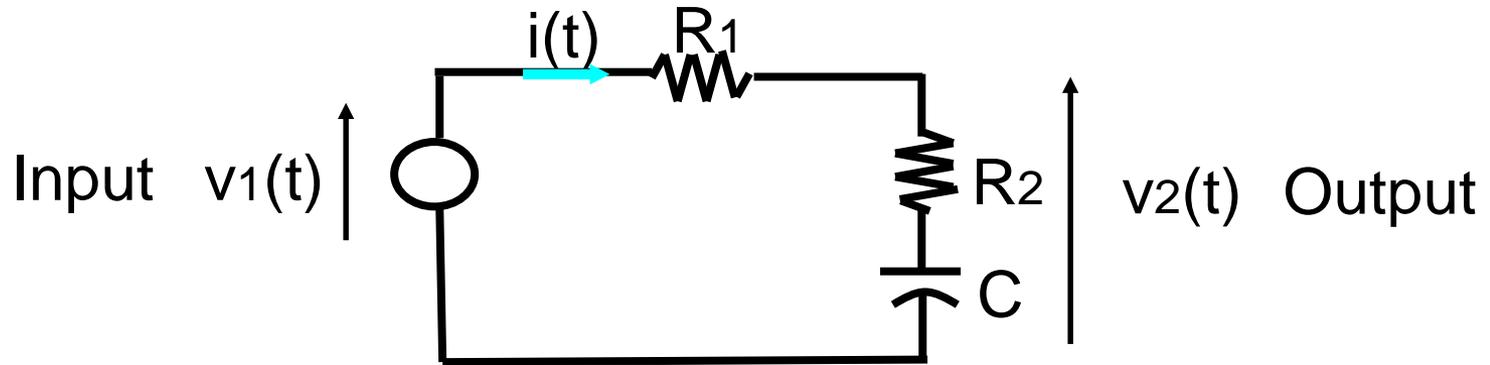


- **Kirchhoff voltage law** (with zero initial conditions)

$$\begin{aligned}v_1(t) &= (R_1 + R_2)i(t) + \frac{1}{C} \int_0^t i(\tau) d\tau \\v_2(t) &= R_2 i(t) + \frac{1}{C} \int_0^t i(\tau) d\tau\end{aligned}$$

- By **Laplace transform**,

$$\begin{aligned}V_1(s) &= (R_1 + R_2)I(s) + \frac{1}{sC}I(s) \\V_2(s) &= R_2 I(s) + \frac{1}{sC}I(s)\end{aligned}$$

Modeling example (cont'd)

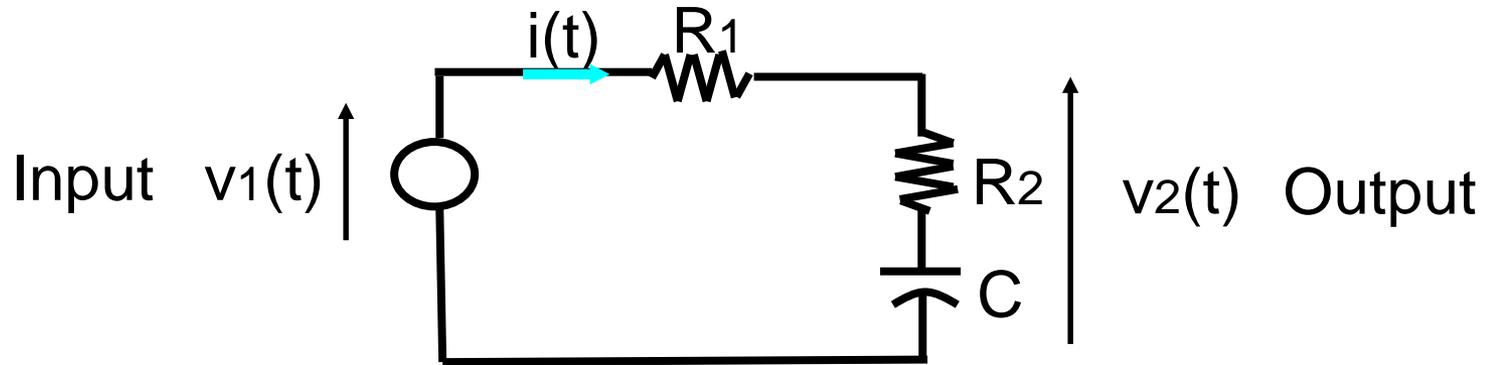

- Transfer function


$$\begin{aligned} G(s) = \frac{V_2(s)}{V_1(s)} &= \frac{R_2 + \frac{1}{sC}}{(R_1 + R_2) + \frac{1}{sC}} \\ &= \frac{R_2Cs + 1}{(R_1 + R_2)Cs + 1} \quad (\text{first-order system}) \end{aligned}$$

- If output is $i(t)$, then

Modeling example (cont'd)



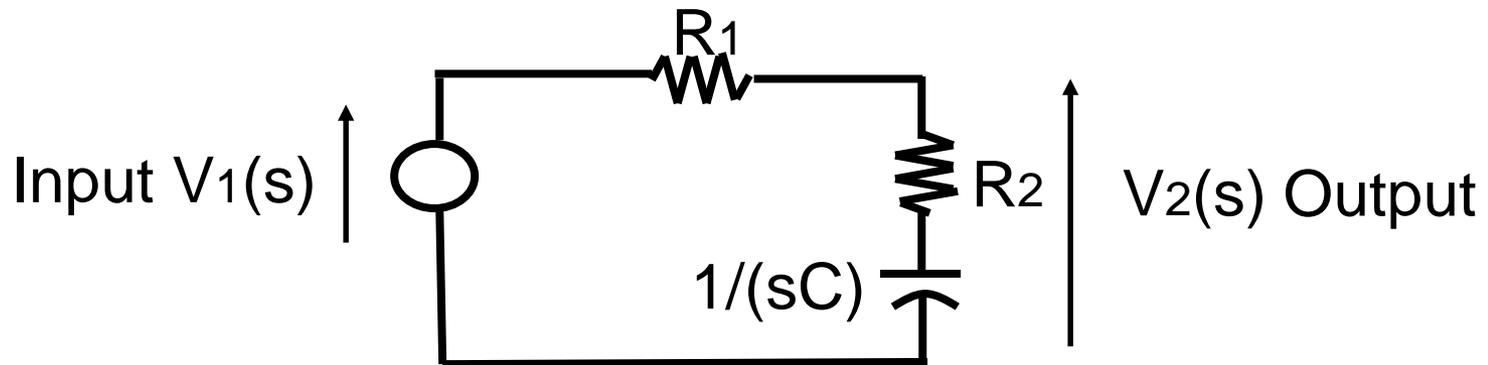- Impedance method
 - Replace electrical elements with impedances.
 - Deal with impedances as if they were resistances.




$$G(s) = \frac{V_2(s)}{V_1(s)} = \frac{\text{(Impedance for output)}}{\text{(Total impedance)}} = \frac{R_2 + \frac{1}{sC}}{R_1 + R_2 + \frac{1}{sC}}$$

Impedance computation



- Series connection


$$Z(s) = Z_1(s) + Z_2(s)$$

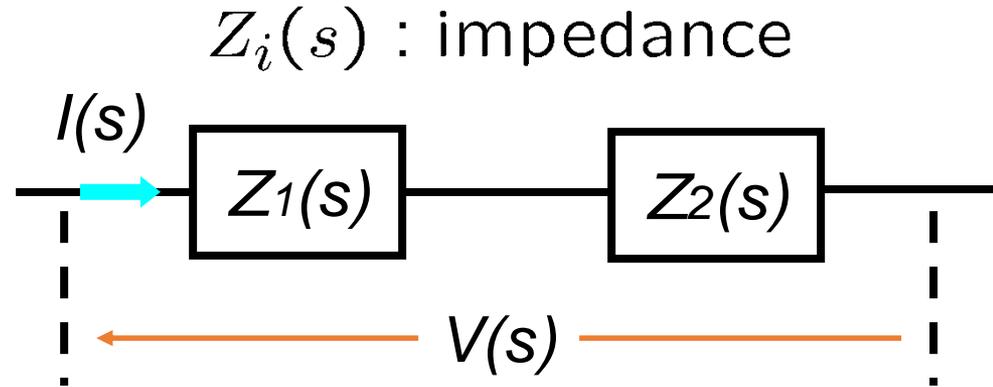

- Parallel connection

$$Z(s) = \frac{Z_1(s)Z_2(s)}{Z_1(s) + Z_2(s)}$$

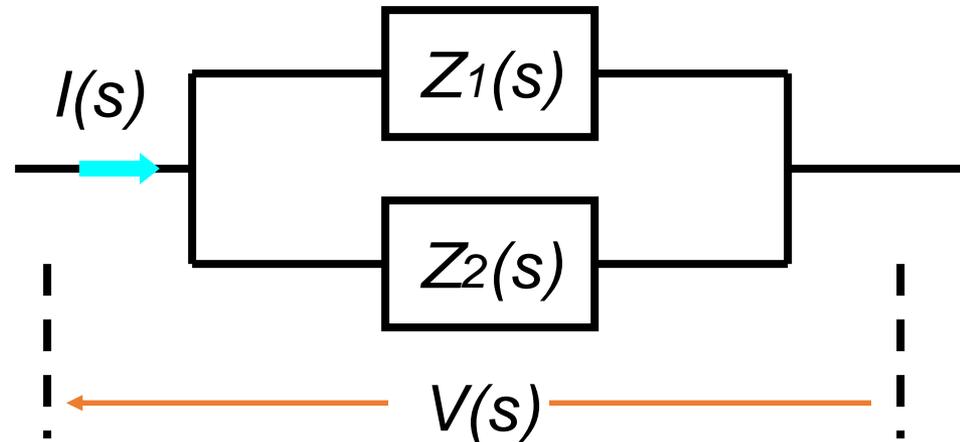
$$\frac{1}{Z(s)} = \frac{1}{Z_1(s)} + \frac{1}{Z_2(s)}$$




Operational amplifier (op-amp)



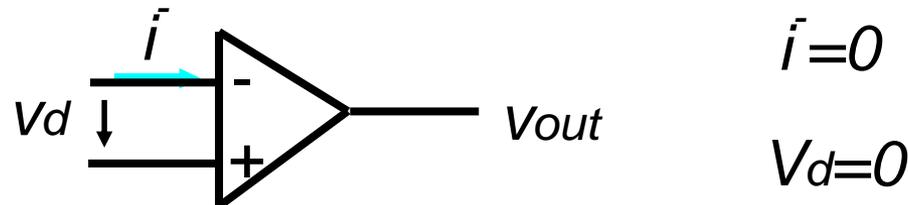- Electronic voltage amplifier
- Basic building block of analog circuits, such as
 - Voltage summation (math operation)
 - Voltage integration
 - Various transfer functions (Signal conditioning, filtering)
- Ideal op-amp (does not exist, but is a good approximation of reality)




Modeling of op-amp

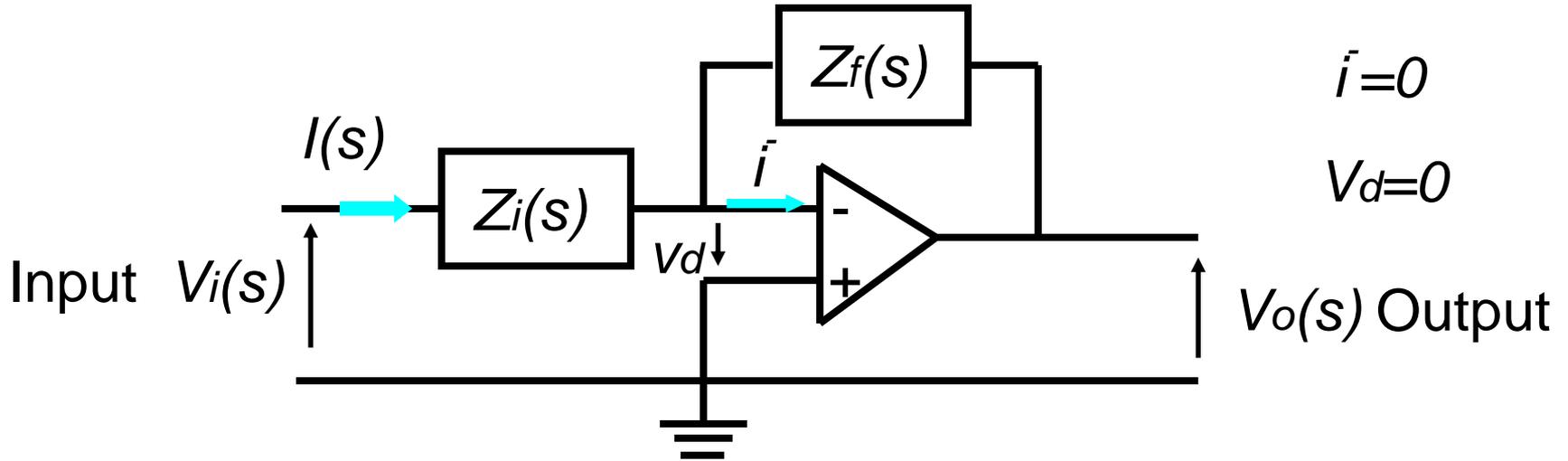

- **Impedance** $Z(s)$: $V(s)=Z(s)I(s)$
- **Transfer function** of the above op amp:

$$G(s) = \frac{V_o(s)}{V_i(s)} = \frac{-Z_f(s)I(s)}{Z_i(s)I(s)} = -\frac{Z_f(s)}{Z_i(s)}$$

Modeling example: op-amp

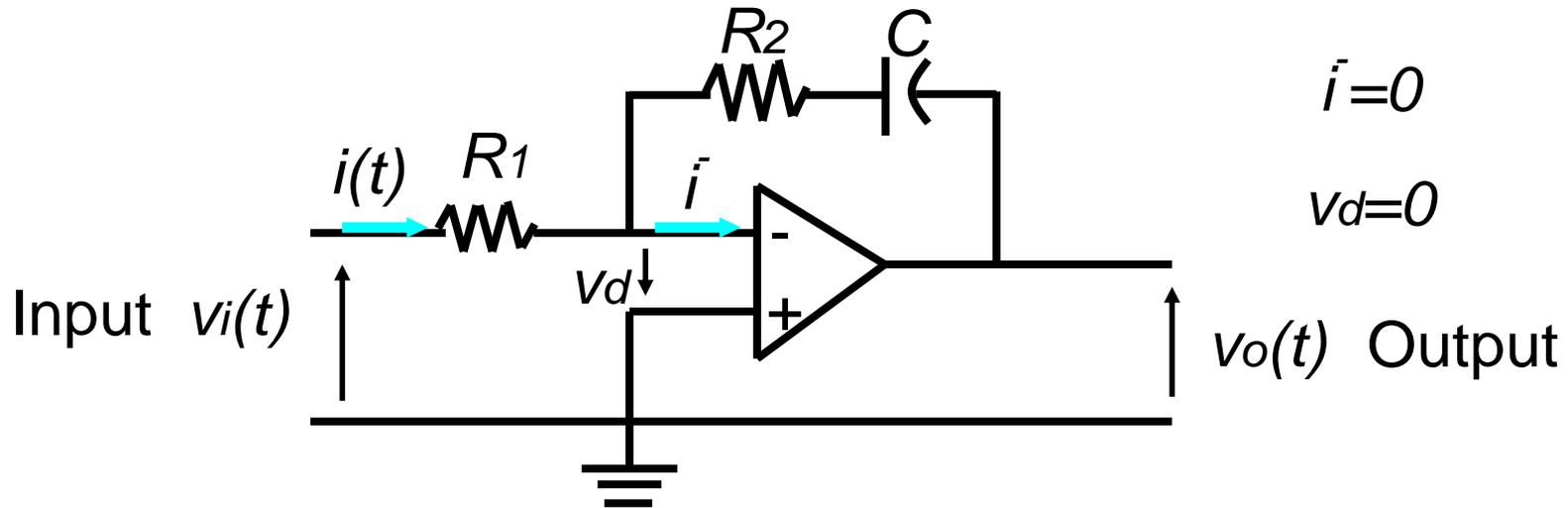

- By the formula in previous two slides,

$$G(s) = \frac{V_o(s)}{V_i(s)} = \frac{-(R_2 + \frac{1}{sC})}{R_1} = -\frac{R_2Cs + 1}{R_1Cs}$$

(first-order system)

Course roadmap



Modeling

- ✓ Laplace transform
- ✓ Transfer function
- Block Diagram
- Linearization
- ✓ Models for systems
- electrical
- mechanical
- example system

Analysis

- Stability
 - Pole locations
 - Routh-Hurwitz
- Time response
 - Transient
 - Steady state (error)
- Frequency response
 - Bode plot


Design

- Design specs
- Frequency domain
- Bode plot
- Compensation
- Design examples

Matlab & PECS simulations & laboratories

Translational mechanical elements

Mass

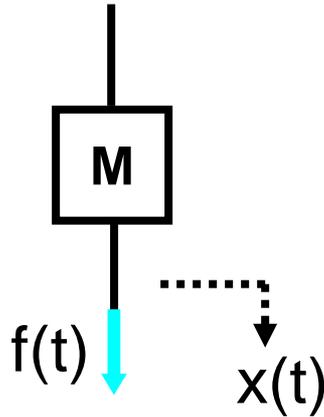


$$f(t) = Mx''(t)$$


 $\left(\begin{array}{l} x(0) = 0 \\ \dot{x}(0) = 0 \end{array} \right)$

$$F(s) = Ms^2X(s)$$

Spring

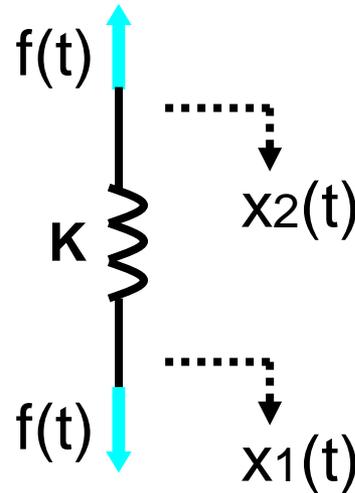


$$f(t) = K(x_1(t) - x_2(t))$$



$$F(s) = K(X_1(s) - X_2(s))$$

Damper

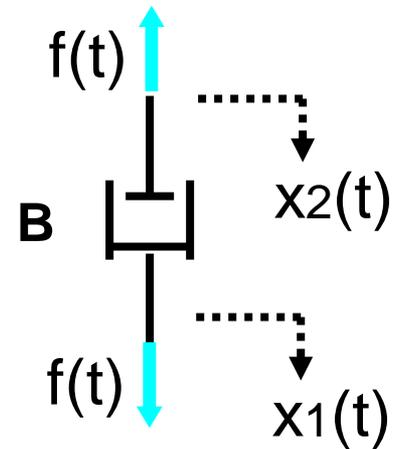

$$f(t) = B(x_1'(t) - x_2'(t))$$


 $\left(\begin{array}{l} x_1(0) = 0 \\ x_2(0) = 0 \end{array} \right)$

$$F(s) = Bs(X_1(s) - X_2(s))$$

Summary



- Modeling
 - Modeling is an important task!
 - Mathematical model
 - Transfer function
 - Modeling of electrical & mechanical systems
- Next lecture, block diagram reduction